

MORE FUN WITH TESLA COILS

48784

Popular Electronics[®]

NOVEMBER 1992

BAD VIDEOTAPES

They carry the VHS logo and call themselves "*high grade*," but the performance that these videotapes deliver is low grade, and some might even damage your VCR!

CHOOSING AND USING VIDEO AND AUDIO TAPES

How to choose the best tape for any recording job, and ensure that the life of your recording does not end prematurely

BUILD THE VOICE-MAIL ALERT

There's no need to pick up your telephone to see if you have voice-mail messages waiting with our easy-to-build project

BUILD A 49-MHz FM TRANSMITTER

Use it with cordless telephones, FM walkie-talkies, baby monitors, and many other devices



A
GERNSBACK
PUBLICATION



\$3.50 U.S.
\$3.95 CANADA

3 NEW
FactCards
IN THIS ISSUE



Countersurveillance

Never before has so much professional information on the art of detecting and eliminating electronic snooping devices—and how to defend against experienced information thieves—been placed in one VHS video. If you are a Fortune 500 CEO, an executive in any hi-tech industry, or a novice seeking entry into an honorable, rewarding field of work in countersurveillance, you must view this video presentation again and again.

Wake up! You may be the victim of stolen words—precious ideas that would have made you very wealthy! Yes, professionals, even rank amateurs, may be listening to your most private conversations.

Wake up! If you are not the victim, then you are surrounded by countless victims who need your help if you know how to discover telephone taps, locate bugs, or “sweep” a room clean.

There is a thriving professional service steeped in high-tech techniques that you can become a part of! But first, you must know and understand Countersurveillance Technology. Your very first insight into this highly rewarding field is made possible by a video VHS presentation that you cannot view on broadcast television, satellite, or cable. It presents an informative program prepared by professionals in the field who know their industry, its techniques, kinks and loopholes. Men who can tell you more in 45 minutes in a straightforward, exclusive talk than was ever attempted before.

Foiling Information Thieves

Discover the targets professional snoopers seek out! The prey are stock brokers, arbitrage firms, manufacturers, high-tech companies, any competitive industry, or even small businesses in the same community. The valuable information they filch may be marketing strategies, customer lists, product formulas, manufacturing techniques, even advertising plans. Information thieves eavesdrop on court decisions, bidding information, financial data. The list is unlimited in the mind of man—especially if he is a thief!

You know that the Russians secretly installed countless microphones in the concrete work of the American Embassy building in Moscow. They converted



1-516-293-3751

**HAVE YOUR
VISA or MC CARD
AVAILABLE**

what was to be an embassy and private residence into the most sophisticated recording studio the world had ever known. The building had to be torn down in order to remove all the bugs.

Stolen Information

The open taps from where the information pours out may be from FAX's, computer communications, telephone calls, and everyday business meetings and lunchtime encounters. Businessmen need counselling on how to eliminate this information drain. Basic telephone use coupled with the user's understanding that someone may be listening or recording vital data and information greatly reduces the opportunity for others to purloin meaningful information.

The professional discussions seen on the TV screen in your home reveals how to detect and disable wiretaps, midget radio-frequency transmitters, and other bugs, plus when to use disinformation to confuse the unwanted listener, and the technique of voice scrambling telephone communications. In fact, do you know how to look for a bug, where to look for a bug, and what to do when you find it?

Bugs of a very small size are easy to build and they can be placed quickly in a matter of seconds, in any object or room. Today you may have used a telephone handset that was bugged. It probably contained three bugs. One was a phony bug to fool you into believing you found a bug and secured the telephone. The second bug placates the investigator when he finds the real thing! And the third bug is found only by the professional, who continued to search just in case there were more bugs.

The professional is not without his tools. Special equipment has been designed so that the professional can sweep a room so that he can detect voice-activated (VOX) and remote-activated bugs. Some of this equipment can be operated by novices, others require a trained countersurveillance professional.

The professionals viewed on your television screen reveal information on the latest technological advances like laser-beam snoopers that are installed hundreds of feet away from the room they snoop on. The professionals disclose that computers yield information too easily.

This advertisement was not written by a countersurveillance professional, but by a beginner whose only experience came from viewing the video tape in the privacy of his home. After you review the video carefully and understand its contents, you have taken the first important step in either acquiring professional help with your surveillance problems, or you may very well consider a career as a countersurveillance professional.

The Dollars You Save

To obtain the information contained in the video VHS cassette, you would attend a professional seminar costing \$350-750 and possibly pay hundreds of dollars more if you had to travel to a distant city to attend. Now, for only \$49.95 (plus \$4.00 P&H) you can view *Countersurveillance Techniques* at home and take refresher views often. To obtain your copy, complete the coupon or call.

CLAGGK INC. PE
P.O. Box 4099 • Farmingdale, NY 11735

Please rush my copy of the Countersurveillance Techniques Video VHS Cassette for a total cost of \$53.95 each (which includes \$4.00 postage and handling).

No. of Cassettes ordered _____

Amount of payment \$ _____

Sales tax (N.Y.S. only) _____

Total enclosed _____

Bill me ☐ VISA ☐ MasterCard

Card No. _____

Expire Date _____ / _____

Signature _____

Name _____

Address _____

City _____ State _____ ZIP _____

All payments in U.S.A. funds. Canadians add \$4.00 per VHS cassette. No foreign orders.

Popular Electronics®

THE MAGAZINE FOR THE ELECTRONICS ACTIVIST!

CONSTRUCTION ARTICLES

BUILD A 49-MHz FM TRANSMITTER	Dan Becker	39
<i>Use it with FM walkie-talkies, wireless microphones, baby monitors, and more</i>		
BUILD AN AUTOMATIC POWER SWITCH FOR YOUR TV	Terrence Vaughn	43
<i>It automatically turns on your TV, monitor, or other A/V component when your VCR is turned on</i>		
BUILD A ONE-AMP CURRENT INJECTOR	David A. Johnson	46
<i>Measure very small resistances with this handy multimeter accessory</i>		
BUILD A VOICE-MAIL ALERT	Steven M. O'Kelley	53
<i>With this circuit there's no need to pick up your phone to see if you have any messages</i>		

FEATURE ARTICLES

BAD VIDEOTAPES	Len Feldman	31
<i>"Bargain-priced" videotapes you should avoid at any cost</i>		
CHOOSING AND USING VIDEO AND AUDIO TAPE	Marc Spiwak	35
<i>Pick the best tape for any audio or video recording task</i>		
INSTALLING AND MAINTAINING TELEPHONE SYSTEMS	Robert A. Young	55
<i>It's an easy job—if you follow these simple hints and procedures</i>		
DAVID HUGHES: ELECTROMAGNETIC PIONEER	James P. Rybak	60
<i>Had David Hughes not been discouraged by experts, the unit of frequency might have been called the "hughes" instead of the hertz</i>		

PRODUCT REVIEWS

GIZMO		5
<i>Including: Road Map Software for your PC; Instant Replay Multi-Standard VCR; and much more</i>		
HANDS-ON REPORT		22
<i>TSM Function Generator Kit</i>		
PRODUCT TEST REPORT	Len Feldman	27
<i>Funai TVCP 9T 9-Inch TV/Video-Cassette Player</i>		

COLUMNS

ANTIQUE RADIO	Marc Ellis	65
<i>Tips and tidbits</i>		
COMPUTER BITS	Jeff Holtzman	68
<i>Word BASIC</i>		
CIRCUIT CIRCUS	Charles D. Rakes	72
<i>More fun with Tesla coils</i>		
THINK TANK	John J. Yacono	75
<i>558 finale</i>		
HAM RADIO	Joseph J. Carr	78
<i>An antenna for DX'ing the low bands</i>		
DX LISTENING	Don Jensen	80
<i>The shortwave revival</i>		
SCANNER SCENE	Marc Saxon	82
<i>Drive-through sermons</i>		

DEPARTMENTS

EDITORIAL	Carl Laron	2
LETTERS		3
FACTCARDS		49
POPULAR ELECTRONICS MARKET CENTER		50A
FREE INFORMATION CARD		52
ELECTRONICS LIBRARY		84
NEW PRODUCTS		86
ELECTRONICS MARKET PLACE		93
ADVERTISER'S INDEX		96

Popular Electronics (ISSN 1042-170X) Published monthly by Gernsback Publications, Inc., 500-B Bi-County Boulevard, Farmingdale, NY 11735. Second-Class postage paid at Farmingdale, NY and at additional mailing offices. One-year, twelve issues, subscription rate U.S. and possessions \$21.95, Canada \$28.84 (includes G.S.T. Canadian Goods and Services Tax Registration No. R125166280), all other countries \$29.45. Subscription orders payable in U.S. funds only. International Postal Money Order, or check drawn on a U.S. bank. U.S. single copy price \$2.95. © 1992 by Gernsback Publications, Inc. All rights reserved. **Hands-on Electronics** and **Gizmo** trademarks are registered in U.S. and Canada by Gernsback Publications, Inc. **Popular Electronics** trademark is registered in U.S. and Canada by Electronics Technology Today, Inc. and is licensed to Gernsback Publications, Inc. Printed in U.S.A.

Postmaster: Please send address changes to **Popular Electronics**, Subscription Dept., P.O. Box 338, Mount Morris, IL 61054-9932.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, **Popular Electronics** publishes available plans or information relating to newsworthy products, techniques, and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, **Popular Electronics** disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Larry Steckler

EHF, CET

Editor-In-Chief and Publisher

EDITORIAL DEPARTMENT

Carl Laron

Editor

Robert A. Young

Associate Editor

John J. Yacono

Associate Editor

Byron G. Weis, K2AVB

Associate Editor

Teri Scaduto

Assistant Editor

Kathy Terenzi

Editorial Assistant

Marc Spiwak

Editorial Associate

Joseph J. Carr, K4IPV

Marc Ellis

Len Feldman

Jeffrey K. Holtzman

Don Jensen

Chris F. O'Brian

Charles D. Rakes

Marc Saxon

Contributing Editors

PRODUCTION DEPARTMENT

Ruby M. Yee

Production Director

Karen S. Brown

Production Manager

Marcella Amoroso

Production Assistant

Lisa Rachowitz

Editorial Production

ART DEPARTMENT

Andre Duzant

Art Director

Injae Lee

Illustrator

Russell C. Truelson

Illustrator

Jacqueline P. Cheeseboro

Circulation Director

Michele Torriilo

P-E Bookstore

BUSINESS AND EDITORIAL OFFICES

Gemsback Publications, Inc.

500-B Bi-County Blvd.

Farmingdale, NY 11735

1-516-293-3000

Fax: 1-516-293-3115

President: Larry Steckler

Customer Service/Order Entry

1-800-435-0715

7:30 AM - 8:30 PM EST

Advertising Sales offices listed on page 38

Cover photography by Diversified Photo Services

Composition by
Mates Graphics



Since some of the equipment and circuitry described in POPULAR ELECTRONICS may relate to or be covered by U.S. patents, POPULAR ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

CONSUMER ALERT

Even in good times, companies are always on the lookout for ways to improve their bottom line, and consumers are determined to find the best value for their dollars. Under economic conditions like the ones we currently face, those natural tendencies can be dramatically magnified. The result is that companies sometimes choose suppliers based more on cost than quality, and consumers sometimes bypass well-known brands in favor of less-expensive alternatives.

A product that provides comparable performance at a lower cost is a true bargain. By contrast, products that provide vastly inferior performance—or worse, that actually cause damage to something else—are no bargain at any price.

This month, **Popular Electronics** presents a report that anyone who buys or uses videotape must read. In it, Len Feldman—one of this country's best known consumer-electronics writers—reports on videotapes that at best provide mediocre performance, and at worst could possibly damage a VCR.

Backed by tests performed by Advanced Product Evaluation Laboratories, the article names names, and pulls no punches. It details how these tapes fall short, what to be alert for in brands other than those specifically mentioned, and how even the VHS logo provides no guarantee of acceptable performance.

If you buy or use videotape, this information is critical to the performance of your video gear. The story begins on page 31.

Carl Laron
Editor

A YOUNG READER'S REMARKS

I'd like to begin by saying that I think **Popular Electronics** is an excellent magazine, and that I've been following it for about a year now. I am 15 years old and I live in Airdrie, Alberta, Canada. That creates a great number of problems for me. First of all, almost every supplier of electronic goods mentioned in your magazine's "Market Center" is located in the United States.

When I order something, I must pay additional shipping fees, GST, duty, and any other applicable taxes in U.S. dollars, which ends up being quite expensive for a 15-year-old once the extra 19% is added for currency exchange. I enjoy and thrive on building and learning from as many **Popular Electronics** projects as I can, and would like to find suppliers who are located in Canada and are more accessible to me. I would greatly appreciate it if someone had a list of such suppliers.

Second, I'd like to say thanks to J.G. of Bridgeport, CT, whose

letter appeared in the July 1992 issue. I appreciate his encouragement of young people who wish to become engineers and who enjoy electronics as a hobby. We need all the encouragement we can get these days.

Finally, I'd like to send out a request to other readers. I have just ventured into the world of microcontrollers, and have purchased a Motorola M68HC11EVBU board. I've been trying to figure out the basics of the assembly language for the controller. I have been successful in creating programs that do such things as adding and subtraction, but I'd like to put the controller to more challenging uses, such as in automation applications for things in my room (door lock, voice recognition, etc.). I would appreciate any ideas or help

that anyone could offer.

Once again, thanks to **Popular Electronics** for all the support I've received from it in the past. I will continue to read it and build the projects for a long time to come.

Wesley d'Haene
450 Summerwood Place
Airdrie, Alberta
Canada T4B 1W5

HAVES & NEEDS

I need a Heathkit manual for an ignition analyzer model IO-20. I'm willing to pay copying costs and postage. Thanks a lot!

Ed Nell
103 Bar Harbor Road
Freehold, NJ 07728

Thank you for putting my letter in the May issue of **Popular Electronics**. I've already re-

ceived several letters, and I was able to get the schematic I needed.

Now I need a ribbon for an Adam Colecvision word processor that I bought in a thrift store. Perhaps you could help me with that also—although from now on I intend to specialize in old audio equipment.

By the way, your article on antennas in the May, 1992 issue (*Wire Beams: Gain on the Cheap*) was excellent.

Karl G. Maeder
2340 Tahoe Circle
Hemet, CA 92545

I've been reading **Popular Electronics** since it first came out in 1954. I need information or a book on how to use RF signal generators. Please help me out!

Daniel Seidler
3721 West 80th Street
Chicago, IL 60652

Train at HOME to be an Electronics Technician!

As the demand for computers and microprocessors in business, manufacturing and communications continues to grow, so does the need for qualified technicians. It's not unusual for experienced technicians to earn from \$30,000 to more than \$40,000 a year.* Now through Peoples College of Independent Studies you can train for this exciting field without interrupting your job or home life.

Choose From Five Programs of Study

- Electronics & Microprocessor Technology
- Industrial Electronics & Microprocessor Technology
- Communications Electronics with Microprocessor Technology
- Computer Servicing & Electronics Technology
- Specialized Associate Degree In Electronics Technology

Professional Equipment Is Included

Depending on the program you select, you'll perfect your skills using this advanced equipment, included in the price of tuition:

- IBM-Compatible Personal Computer
- Digital Multimeter
- Digital Logic Probe
- Elenco Oscilloscope
- Portable Cellular Telephone

(* Source: U.S. Bureau of Labor Statistics)



Exclusive Extras That Enhance Your Training

Peoples College introduces some training firsts to make your learning experience more complete:

- Accelerated Learning System — a scientifically proven study system that helps you learn faster and easier than ever before.
- Video Tutor Training Tapes — give you a permanent, visual record of informative lectures and close-up demonstrations.
- Experience Labs — professionally designed experiments that give you hands-on "bench" experience.
- Industry Certification Training Guide — provided with four of our programs. Prepares you for examinations you may take for your professional license or certification.

Easy Payment Plans — No Finance Charges

To help you get started on your education, Peoples College has reduced tuition rates and offers low monthly payment plans with no finance fees. So don't delay, call or write for more information today!

For COLOR CATALOG Mail Coupon or
Call TOLL FREE 1-800-765-7247

Programs offered only in United States, Canada, Puerto Rico and Virgin Islands. No Obligation. No sales person will call.

Our programs are accredited by the Accrediting Commission of the National Home Study Council

YES! I would like to know more about your training programs. Send a catalog to:

Name _____
Address _____
City _____
State _____ Zip _____

Phone # _____
PEOPLES COLLEGE
OF INDEPENDENT STUDIES
233 Academy Drive • P.O. Box 421768
Kissimmee, FL 34742-1768
Member of the Peoples Group E1192

GIZMO®

NOVEMBER 1992

A CHRONICLE OF CONSUMER ELECTRONICS



VOLUME 5,
NUMBER 11

Mapping Your Progress

STREET ATLAS USA. Published by: DeLorme Mapping, Lower Main Street, P.O. Box 298, Freeport, ME 04032. Price: \$ 169.
AUTOMAP. Published by: Automap, 9831 South 51st Street, Building C-113, Phoenix, AZ 85044. Price: \$99.95.
PC MAPS. Published by PC Maps Corporation, P.O. Box 581871, Houston, TX 77254. Price: \$99.

We remember a weekend trip we once took to Cape Cod, Massachusetts. Our decision to go was pretty much a spur-of-the-moment one. We didn't have time to get good maps, and assumed that our standard interstate-highway map and our general knowledge of geography would be sufficient. As it turned out, one of our most vivid memories of that vacation—one that we now laugh about—was of us getting hopelessly lost after we left the interstate in search of a gas station.

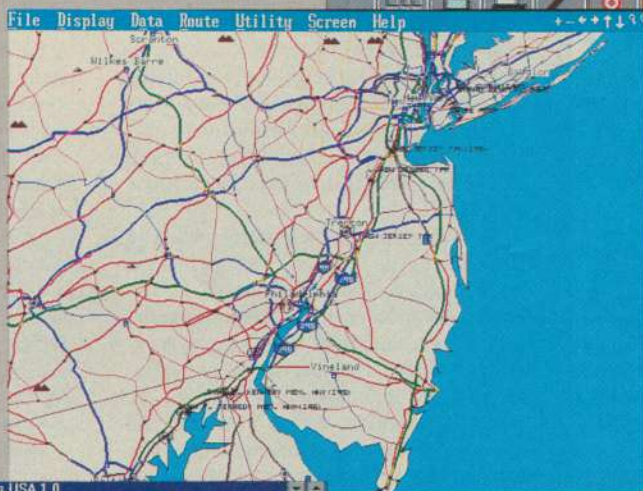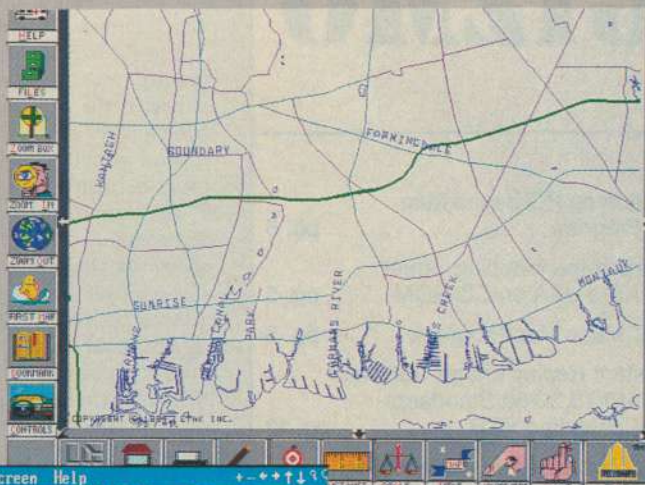
Another memory we have—and one about which we still don't laugh—is of a time we were planning a trip to a trade show in San Francisco. During the trip, we planned to stop by a couple of Silicon Valley businesses. But because we had never been there previously—and couldn't get any detailed maps locally—we had a hard time planning things out, and ended up wasting an entire day of our



West Coast trip.

And then there's the time we were trying to come up with a decent map that would direct friends to our house for a holiday party. We thought our hand-drawn maps were pretty good. The guests who got lost thought otherwise.

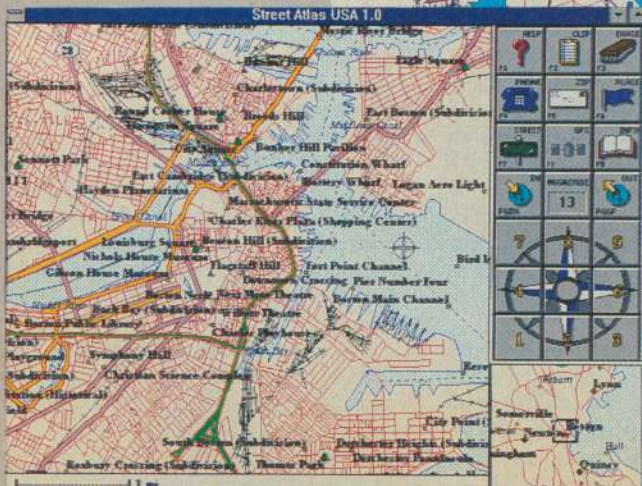We probably could have avoided all of those pitfalls with three interesting map programs: *Automap*, a U.S. trip-routing program; *PC Maps*, a local street map; and *Street Atlas USA*, a CD-ROM-based street atlas of the entire country.



STREET ATLAS USA

Our first reaction to Street Atlas USA was amazement. Now, we don't get amazed by technology very often because we see so much of it, we've been familiar with CD-ROM's for years, and we know that a disc can hold almost 700 megabytes of data, which is an extraordinary amount. But we had no idea that it was possible to fit a map of the United States—with details on every street—on a CD-ROM disc.

Street Atlas USA amazed us not only with the amount of data contained in "only" 450 megabytes on a CD-ROM, but also with the fact that the raw data for the disc came from the U.S. Census Bureau in files that were about 14 gigabytes long! DeLorme compressed the information, using a proprietary compression al-

TURN PAGE FOR CONTENTS

This month in GIZMO®

Automap PC-Based Map Program.....	pg. 5
DeLorme Mapping Street Atlas USA on CD-ROM.....	pg. 5
PC Maps Map Program.....	pg. 5
Instant Replay Image Translator 610IT3 50/60 Standards-Converting VCR.....	pg. 12
VidiPax Standards-Converting Service.....	pg. 14
Franklin Big League Baseball Encyclopedia.....	pg. 16
Universal Home Control One For All 4 Remote Control ...	pg. 20

Gizmo is published by Gernsback Publications, Inc., 500-B Bi-County Blvd., Farmingdale, NY 11735. Senior Writers: Chris F. O'Brian and Teri Scaduto. Contributor to this issue: Frank Barr, Advanced Product Evaluation Laboratories. ©Copyright 1992 by Gernsback Publications, Inc. Gizmo is a registered trademark. All rights reserved.

gorithm, into a 450-megabyte indexed database.

We all have various maps around the house. There's usually a world atlas (which is almost certainly out-of-date), a map of the U.S. showing major interstates, perhaps some regional maps for short vacations, and a local atlas that shows all local streets. Imagine having a local atlas for every county in the U.S. That's essentially what Street Atlas USA provides.

Although there are many businesses—trucking companies, for example—who would find Street Atlas USA valuable, almost half of the people who are buying the program are just normal people who like maps. (We fall into that category.) De-

Lorme could have priced the CD-ROM at whatever the company felt the market would bear. We're glad, and impressed, that they kept the price so reasonable.

Street Atlas runs under Windows and, of course, requires a CD-ROM drive. Color is an important component to the map displays, and we think a color monitor is essential. As with most Windows applications, a mouse is strongly recommended. You'll need about 2 megabytes of free space on your hard disk, because the automatic installation procedure copies some executable programs and dynamic link libraries to the drive, which improves performance.

The full-screen Street Atlas display is divided into three main sections. The largest is the map display. On the right-hand quarter of the screen are a "remote-control panel" and an inset low-detail overview map.


The main map can show detail in one of 16 resolutions, from Magnitude 3 (which shows the 48 contiguous states, most of Canada and Mexico, and a portion of Alaska), to Magnitude 18 (which shows an area of about one acre). The overview map always displays a resolution lower than the main map (in Magnitude 13, the overview is a world map), and indicates what's shown in the main-map display with a box.

Above the overview map window is a nine-key "compass" keypad. Clicking on any of the direction keys—or pressing the indicated number on your keyboard—lets you pan or scroll the map in that direction. You can also pan the map by clicking on part of the screen that will become the new center.

The top of the remote-control panel is a 12-button keypad that lets you operate the main program functions. You can, for example, zoom in or out by clicking on the appropriate buttons or by using the PGDN or PGUP keys. The magnitude or zoom-level of the main map is shown on the MAGNITUDE button, which is between the two zoom buttons. Unfortunately, you cannot click on the MAGNITUDE button and zoom to a given magnitude directly. You can, however, draw a box (using the mouse) around the area you would like to zoom into.

Other keys access the impressive search functions of Street Atlas. Three main choices are available: You can search by the name of a town, its 5-digit zip code, or the telephone area code and exchange. After you narrow the search area by one of those search methods, you can also search for a specific street name.

 Let's assume, for example, that you wanted to find where jazz saxophonist Charlie Parker grew up. You could click on Place, and enter the name of the town—Kansas City, KS. (If there is no exact match, a selection of choices that are al-



Street Atlas USA

with XMap™ System Software

Over \$5,000 worth of maps for just

\$169



Detailed, street-level maps of the entire USA on one CD-ROM

Every street in the USA is included

Comprehensive, seamless maps of every state

Highways, state routes, streets, back roads and their names

Close-up or distant views

Location by street name, phone exchange, zip code, or place name

Displays street addresses and city blocks in metropolitan areas

State boundaries, cities, towns, neighborhoods

Lakes, ponds, rivers, and rivers

Minimum requirements —

- Microsoft Windows 3.0 or higher
- VGA graphics
- Windows-compatible CD-ROM drive
- Mouse (recommended but not required)
- Single user version
- Network version available

DeLorme Mapping

Street Atlas USA, CD-ROM, \$169

100 North Main Street, Suite 200

Portland, Maine 04107 USA

For 24-hour toll-free

Copyright 1992 DeLorme Mapping Co., Inc.
The DeLorme Mapping Company is a registered trademark of DeLorme Mapping Co., Inc. All rights reserved.

CIRCLE 50 ON FREE INFORMATION CARD

phabetically closest will be displayed.) When you select the city or town, you will be presented with a map of the city at Magnitude 13, which provides a view of about 4 miles × 4 miles. You can then search for a given street—Freeman. To be found, the street must be in the area shown on the screen, although it may not be visible to you. You can even look up the locations of some of the nightclubs in Kansas and Missouri in which he used to play.

An alternative search method would be to enter the telephone area code and local exchange. We were interested in finding out where DeLorme Mapping's offices were located. Since we knew the company's telephone number, we simply entered the area code (207) and then the exchange (865). We were then presented with a 4 mile × 4 mile view of Freeport, Maine (the same view as if we had entered "Freeport, ME" in the Place submenu).

The third search method is by Zip code. Entering 04032 in the appropriate dialogue box would again bring us to a 16-square-mile view of Freeport.

The high-quality maps include more than just streets: Rivers, lakes, and some smaller bodies of water are visible, as are some parks, airports, colleges and universities, and points of interest. Railroad tracks are identified, although train stations, for the most part, are not. You can click on unlabeled points to find out what they are—although you won't always get an answer.

The weakest point of Street Atlas USA is its print capability—it doesn't have any. You can, however, save maps to the Windows clipboard, and then manipulate or print the image using a graphics program such as Windows Paintbrush.

Unfortunately, no map can ever be completely up to date—as soon as any map is published, it immediately starts to become out of date. Street Atlas USA, however, seems to come very close to being up-to-date. One easy test that we've found for maps is to try to locate Bi-County Blvd., the home of **Popular Electronics'** main offices. The street is relatively new, just over six years old. We couldn't find it, although an equally new adjoining street was shown. We can't really complain about the oversight—a check of 1992-edition street atlases available locally (from the Hagstrom and Geographica map publishers) didn't show either street.

The paper atlases did contain some information not contained in Street Atlas USA—public schools, and commuter rail stations, for example. Yet the CD-ROM atlas contained some information we couldn't find in our atlases, mostly the names of some small islands and creeks. Street Atlas USA does contain political boundaries, but not necessarily an indication of what the boundaries separate. For example, the boundary between Nassau and Suffolk counties on Long Island is shown, but when you click on it to find out what it is, "boundary" is all that is displayed.


It's easy for a critic to complain about features that could have been included in Street Atlas USA that are missing. Although we've done just that, we're extremely impressed by the product and its price. We're looking forward to seeing future versions of the program—especially one now in the works that will let you enter data from a GPS (global positioning satellite) receiver and find your location.

As impressive as Street Atlas USA is, it's not for everyone—not everyone needs a computerized street atlas of the entire country. Several local business people we showed the CD-ROM version to said they would indeed like to have it, but they'd rather have a similar product that covered only a specific area, and didn't require a CD-ROM drive. For them, another program, PC Maps might be the answer.

PC MAPS

PC Maps is a street-map program for IBM PC's and compatibles. Versions are available for more than 120 metropolitan areas. We examined two maps: One was of New York City and Hudson County, NJ and the second was of Long Island, NY. (The PC Maps package contains the program itself and one map database. Additional map databases are available for \$39.)

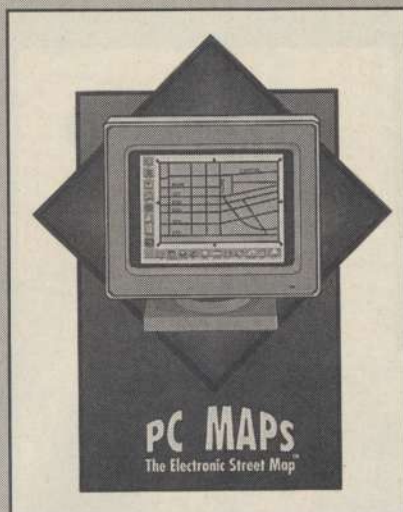PC Maps is based on development tools and electronic map databases that were created by Etak, Inc. of Menlo Park, California (the same company that created the database used in the Blaupunkt TravelPilot



CIRCLE 51 ON FREE INFORMATION CARD

car-navigation system we reviewed in our June 1992 issue)

In some respects, PC Maps is similar to Street Atlas USA. You can search for streets, re-center the map, and zoom in and out. PC Maps operates faster because it's not a Windows application, its search database is (naturally) smaller, and it doesn't rely on relatively slow CD-ROM drives.

PC Maps has relatively modest system requirements. Your PC must have 640 kilobytes of memory, it must be running MS-DOS 2.0 or higher, and it must have an EGA or VGA graphics adapter and monitor. A hard drive is a practical necessity: The individual city maps range in size from 1.29 megabytes for Reno, Nevada to 18.06 megabytes for "Large" Dallas-Fort Worth (there is also a map of "Small" Dallas-Fort Worth). Some other file sizes

for comparison are: Salt Lake City, 4.13 megabytes; Philadelphia, 9.0 megabytes; Indianapolis, 3.01 megabytes.


Although you can load more than one map database onto your hard drive, you can access only one at a time. For example, even though we used both the Long Island and the New York City maps—two adjacent areas—we had to switch databases when we got to the border of one or the other.

The PC Maps screen features menu bars along the left and bottom edges. The map occupies the rest of the screen, with the exception of a thin border around the map that contains scrolling "buttons" for panning the map.

Although a mouse can be used with PC Maps, it is not essential. We found ourselves using a combination of a mouse and the keyboard, because all of the menu icons can be accessed with a single keystroke. (Our description will assume that a mouse is used.)

The search functions are accessed with the FIND button, which brings up a dialogue box in which you can enter the address, street, cross street, and town. You need not completely fill in the search parameters, but you must enter at least a street name. If there is more than one match, you will be presented with a list from which you can select your choice. We entered "Main St." and were presented with a list of 25 possibilities—only the first 25 that PC Maps found in its Long Island database. Entering a cross street or town would have narrowed the search considerably.

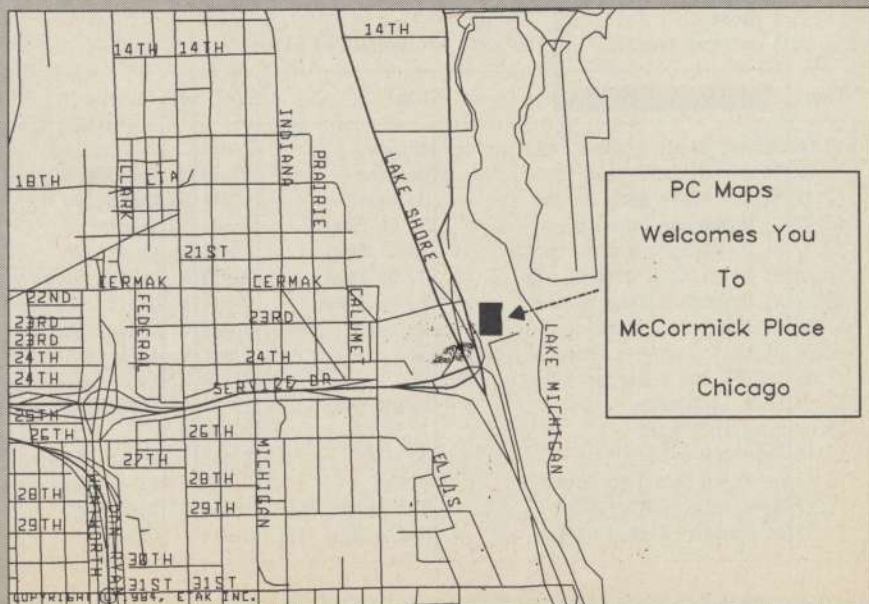Zooming can be handled in two ways. You can choose to ZOOM IN and ZOOM OUT from the menu bars, or you can draw a zoom box that lets you define the size of



PC Maps makes printing a custom map easy.

the area that you wish to see in more detail.


Five "bookmarks" can tag up to five map views, which allows you to quickly bounce back and forth between the five views. The bookmarks are only temporary, however. When you exit the program, they are not saved.

A "You're Here" command brings up an inset map that shows an overview of the main map is set in a larger geographical area. You can also bring up a grid or a scale to give you a quick idea of distances.

To determine distances more accurately, you can use the **DISTANCE** command, which lets you measure the distance between two points. You can string points together along your route to get a total distance. Unfortunately, you cannot scroll the map when you are measuring distances. That becomes inconvenient if you need to measure the distances along smaller streets, which become visible only when you zoom in sufficiently. You can, of course, measure the distances in one map, exit the distance mode, scroll the map, and re-enter the distance mode. Then, however, the program won't keep a running total of the distance measured.

When you zoom out, some streets disappear from the map. Others appear, but without their names. You can, however, point to any street to find its name. It's also possible to display full information at all zoom levels—assuming you have enough memory—but the screen becomes unreadable when you do.)

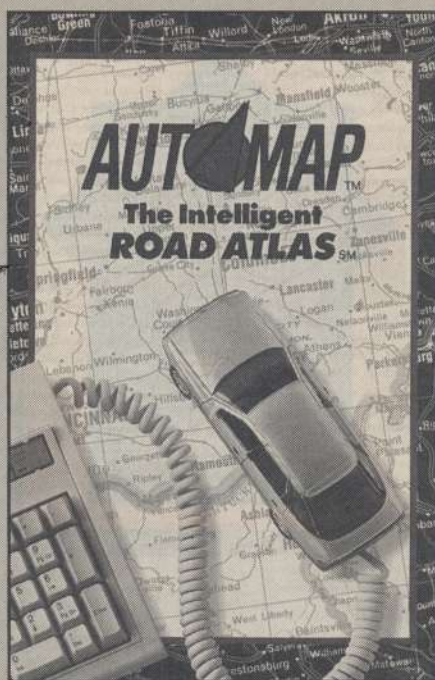One of the strong points of PC Maps is that it allows you to tailor the maps you define to your own requirements. You can add symbols—dots, pins or map tacks,



CIRCLE 52 ON FREE INFORMATION CARD

squares, and triangles—although you cannot change their size or orientation. You can also draw circles, rectangles, lines, and arrows of any size you choose. Text and titles can be added, too, but the program gives you no control over text size.

You can print your finished map to Epson or Hewlett-Packard LaserJet printers (or compatibles) in low- or high-resolution forms. If you are unhappy with the look of the map and want to customize it further, you can export the map as a PCX file, and

then use a graphics-editing program to tailor it further.

Using PC maps, we were able to print direction sheets to get friends to our homes, and business associates to our offices. (Like Street Atlas USA, PC Maps does not include the street on which the main office of Popular Electronics is located. We were able, however, to edit the map in PC Paintbrush to include the street.)

The two programs we've mentioned so far do an excellent job of finding the locations of streets and towns. But they can't necessarily tell you how to get from one place to another. There is, however, a program that can: Automap.

AUTOMAP

Automap is billed as "the intelligent road atlas." Designed for anyone planning a vacation or business trip, Automap asks where you're going, where you're starting from, the type of roads on which you want to travel, and any places you want to avoid. The program will then plan your route, and show you the results as an on-screen map, or as a list of directions.

The system requirements for Automap are rather modest. Any IBM-compatible PC with at least 512 kilobytes of memory and a hard disk with about 4 megabytes of free space should do. A wide variety of graphics adapters—from CGA and Hercules to super VGA—are supported, although we wouldn't recommend running the program on a PC with anything less than color EGA graphics. A wide variety of printers—from dot-matrix to color to laser—are also supported. A mouse is recommended.

The idea behind Automap is great. When we travel on a long car trip, we love to bring along maps, direction sheets and timetables. It makes the journey much more pleasant because we never feel that we're lost, we know how much longer we'll be driving, and we have something specific with which to answer the "are we there yet" questions. Maps are important enough to us that it is one of the main reasons we joined AAA. The AAA Triptik maps are superb and their route planners are very informative.

Automap doesn't come close to replacing the AAA services and maps, but it's an impressive program nonetheless. Not only can you enter your starting and ending points, you can select towns or some points of interest you want to visit on the way. You can display maps in varying levels of detail, and print out different versions with a minimum of effort. You might, for example, print one map showing the interstates on which you'll be traveling, and another one showing all of the parks and recreation areas you'll be passing on the way.

file edit route screen help F10-Menu F1-Help

references... route from Babylon to Baltimore

peeds...

courtesy lines... s 50 min. Distance 243 miles.

Time		Road	For	Di	Towards
12:00	DEPART Babylon (New York) on the	Unknown	3 mil		
12:07	At N Bay Shore take the	No name	3 mil N		Deer Park
12:10	At Deer Park stay on the	No name	4 mil SW		W Babylon
12:15	At W Babylon go onto	S. St Pkwy	2 mil SW		Levittown
12:17	At N Massapequa stay on the	S. St Pkwy	6 mil W		Levittown
12:24	At N Bellmore stay on the	S. St Pkwy	3 mil W		Valley Strea
12:27	At Uniondale stay on the	S. St Pkwy	9 mil W		Valley Strea
12:36	At Franklin Square go onto	Laurelton (Belt)	3 mil W		Valley Strea
12:38	At Valley Stream bear left onto	S27	4 mil W		(Jfk Int'l A
12:45	At Jfk Int'l Airport stay on the	S27	2 mil W		
12:47	Bear left onto	Shore Pkwy	13 mi SW		(Brooklyn)
13:07	Turn left onto	I278	7 mil W		
13:18	Turn off onto	No name	8 mil S		Perth Amboy
13:27	At Perth Amboy go onto	S440	8 mil W		Piscataway
13:37	Turn left onto	New Jersey Tpk	13 mi S		Vineland
13:51	At Spotswood stay on the	New Jersey Tpk	8 mil S		Vineland

Automap can print a detailed list of directions for your travels.

Graduate as a Fully Trained Electronics Professional!

If you want to learn about electronics, and earn a good income with that knowledge, then CIE is the best educational value you can receive.

CIE's reputation as the world leader in home study electronics is based solely on the success of our graduates. And we've earned our reputation with an unconditional commitment to provide our students with the very best electronics training.

Just ask any of the 150,000-plus graduates of the Cleveland Institute of Electronics who are working in high-paying positions with aerospace, computer, medical, automotive and communications firms throughout the world.

They'll tell you success didn't come easy...but it did come...thanks to their CIE training. And today, a career in electronics offers more rewards than ever before.

CIE'S COMMITTED TO BEING THE BEST...IN ONE AREA...ELECTRONICS.

CIE isn't another be-everything-to-everyone school. CIE teaches only one subject and we believe we're the best at what we do. Also, CIE is accredited by the National Home Study Council. And with more than 1,000 graduates each year, we're the

largest home study school specializing exclusively in electronics. CIE has been training career-minded students like yourself for nearly sixty years and we're the best at our subject....ELECTRONICS...BECAUSE IT'S THE ONLY SUBJECT WE TEACH!

CIE PROVIDES A LEARNING METHOD SO GOOD IT'S PATENTED.

CIE's AUTO-PROGRAMMED® lessons are a proven learning method for building valuable electronics career skills. Each lesson is designed to take you step-by-step and principle-by-principle. And while all of CIE lessons are designed for independent study, CIE's instructors are personally available to assist you with just a toll free call. The result is practical training...the kind of experience you can put to work in today's marketplace.

LEARN BY DOING...WITH STATE-OF-THE-ART EQUIPMENT AND TRAINING.

CIE pioneered the first Electronics Laboratory Course and the first Microprocessor Course. Today, no other home study school can match CIE's state-of-the-art equipment and

training. And all your laboratory equipment, books and lessons are included in your tuition. It's all yours to use while you study and for on-the-job after you graduate.

PERSONALIZED TRAINING...TO MATCH YOUR BACKGROUND.

While some of our students have a working knowledge of electronics others are just starting out. That's why CIE has developed twelve career courses and an A.A.S. Degree program to choose from. So, even if you're not sure which electronics career is best for you, CIE can get you started with core lessons applicable to all areas in electronics. And every CIE Course earns credit towards the completion of your Associate in Applied Science Degree. So you can work toward your degree in stages or as fast as you wish. In fact, CIE is the only school that actually rewards you for fast study, which can save you money.

SEND FOR YOUR CIE COURSE CATALOG AND WE'LL SEND YOU A FREE 24-PAGE CIE ELECTRONIC SYMBOLS HANDBOOK.

FREE!

SEND FOR YOUR CIE HOME STUDY COURSE CATALOG AND RECEIVE A FREE 24 PAGE CIE ELECTRONIC SYMBOLS HANDBOOK!

Includes hundreds of the most frequently used electronic symbols. Published exclusively by CIE for our students and alumni. Yours free when you request a CIE Course Catalog.



electronics

YES! I want to get started. Send me my CIE course catalog including details about the Associate Degree Program. (For your convenience, CIE will have a representative contact you - there is no obligation.)

AH34

Please print clearly

Name _____

Address _____

City _____ State _____

Zip _____ Age _____

Phone No. (____) _____

Check box for G.I. Bill Benefits

☐ Veteran ☐ Active Duty



1776 East 17th Street
Cleveland, Ohio 44114

A School of Thousands.
A Class of One. Since 1934.

Automap's user interface is through three main screens: the Map screen, Journey screen, and Table screen. The Map screen, obviously enough, shows a map. It is possible to plan your route by using the menu bar across the top of the screen, and by pointing to your starting and ending points. You may prefer, however, to enter the information in the Journey screen, where you type in your start points and destinations in text.

When your route is calculated, the result can be shown either on the Map (which shows the route by flashing the appropriate roads) or on the Table screen, which gives you a textual description of your route.

Let's say, for example, that you want to take a trip from Hope, Arkansas to Washington, DC, but you also want to pass through Daniel Boone National Forest in Kentucky. In the Journey screen (our preferred way to input such information), you would type in the start point of Hope (which won't be found unless you instruct the program to search through its database of smaller towns—according to the company, the database contains over 50,000 cities and towns). You could enter a starting time (which is useful because your direction sheet is printed out with the expected arrival times at various points). You then would enter your end point and any way points at which you want to stop. The only stop on this planned trip would be Daniel Boone National Forest (which the program again won't find unless you request it to search its database of "other features").

When you're ready to have Automap plan your route, you will be asked for the type of search you want: quickest, shortest, alternative, or a preferred route, in which your travel preferences (a dislike of interstates, for example) are taken into account.

We tried many hypothetical trips from our Long Island home base to various cities, including some of the major Canadian cities that are included in the database. For the most part, it chose reasonable routes. It duplicated some of the routes we've driven to get to different cities. And it got us into other cities in the way we probably would have chosen had we used a good interstate map. At the start point of the trip, however, it suggested routes that didn't make much sense. On many trips off Long Island, for example, it chose routes that would have taken us at least 15 minutes out of our way, or put us on heavily trafficked roads that we would have avoided at any cost. It didn't know the names of some major roads, and also didn't know about one of the two major ferry services serving Long Island. Some of those omissions are undoubtedly due to the programming being done in Britain using information from federal and state agencies in the U.S.

We found the program to be easy enough to use, although the menu structure can be a little bit confusing. To see more small towns on screen, for example, choosing "More Detail" wouldn't help. Choosing "Smaller Towns" from the Overlay menu (which is a submenu of the Data menu) would get you the display you wanted.

We did like the additional information available from the program's database. It's a simple matter to find out, for example, the population of states and cities, the number of licensed drivers and registered vehicles, and such traffic laws as whether seat belts are required. (Unfortunately right turns on red lights are not mentioned.) Tourist information numbers are also provided, which means that you'll be able to get the detailed information that you need to have a successful trip.

Finally, you can play games with Automap. You'll be quizzed, for example, on distances between cities, or asked to point to a given city on the map. That geography lesson alone might make the program worthwhile, and certainly makes it one that the whole family can use.


WRAPPING UP THE MAPS

Now that computer-mapping programs have hit the low-price popular market, are paper maps a thing of the past? We don't think so. But we will no longer rely solely on paper maps.

Each of the three programs has features that make it worthwhile. For example, we can certainly imagine having PC Maps available on a laptop in our car. It's a sensible way to schedule deliveries and to find your way around town.

Street Atlas USA, our favorite program of the three, is perfect for anyone who likes maps. (Almost half the sales of the disc so far have been to people who don't have any business or other pressing reason for having a street map of the entire country.)

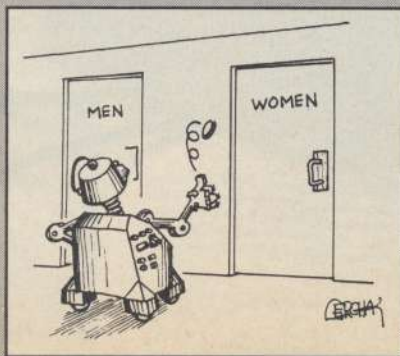Although Automap didn't live up to our initial expectations, we have to recommend it, too. Since many people find that half the fun of a vacation is in its planning, Automap will certainly make a lot of people happy. Its educational possibilities alone make it worth its cost. ■



Non-Standard VCR

IMAGE TRANSLATOR MODEL 610IT3 60/50 DIGITAL FRAME STANDARDS CONVERTER VCR. From Instant Replay, 2601 South Bayshore Drive, Suite 1050, Coconut Grove, FL 33133; 1-800-749-8779; \$795.

If it's your job to videotape the family reunion and send copies of the video to family members in various countries around the world once a year, your best bet probably would be to have the original professionally converted from NTSC to PAL or SECAM and copied. If, on the other hand, you're a foreign-film buff who relies on friends overseas to send you obscure titles on tape, or you work for a multinational corporation and frequently exchange videos for training, product demonstrations, and meetings with other offices, multi-standard VCR's might represent a more convenient and possibly more cost-effective solution.

Instant Replay sells a line of multi-standard VCR's that ranges from a portable \$600 unit to a \$2000 Super-VHS hi-fi unit. Our test unit was a middle-of-the-road-model, the two head VHS *Image Translator 610IT3*.

At first (and even second or third) glance at the Image Translator looks no different from any other front-loading VCR. The front panel is cleanly designed, with controls hidden behind a swing-down door; only the ON/OFF and STOP/EJECT buttons and the LCD readout are visible. Nor does opening the door give any clue to the VCR's multi-standard capabilities; hidden behind the door are the VCR/TV selector, play controls, the REC button, and channel up/down keys. The rear panel has nothing out of the ordinary—audio and video inputs and outputs, VHF/UHF antenna input and output, and a channel-3/4 switch. The remote control has 26 keys as well as a numeric keypad, but none of those is used to switch between video standards.

Not even the manual that accompanied our test unit mentioned the standards-conversion ability. It did, however, contain a one-page instruction addendum that was probably originally intended for a different model, since it says that "the Translator switch is located on the concealed front panel . . ." and "replaces the child lock switch." Our unit had neither a translator switch or a child-lock switch. We finally found an unlabeled toggle switch on the side of the unit. Experimentation revealed that moving it toward the front of the unit worked for NTSC, and pushing it backward was for PAL, and SECAM.

LABORATORY TESTS

The video frequency response of a VCR is a measurement of how accurately it can reproduce signals of different frequencies that it is called on to record. It is measured by recording a multiburst test signal, which contains bursts of several specific frequencies. The recorded signal is then played back and observed on a waveform monitor. In an ideal world, the frequency response of a VCR would be flat. In the real world, the response of a VCR drops off at higher frequencies.

As shown in the table and multiburst test patterns, the Instant Replay Image Translator did a pretty good job in the NTSC mode. Its frequency response was down 2.25 dB at 2 MHz, and 11.3 dB at 3 MHz. Using a PAL test tape, its frequency response was measured to be down 9.86 dB at 2 MHz, and 13.4 dB at 3 MHz. Although the PAL results are significantly worse than the NTSC results, those numbers are equivalent to those of many standard VCR's we've seen.

The signal-to-noise ratio is a measurement of the amount of unwanted noise on a fixed, flat-field video signal. A red field, used in our lab tests, is usu-

ally preferred to measure the chroma signal-to-noise ratio. AM chroma measurements indicate the strength of the color signal, while the PM chroma tests indicate the purity of the color signal. Interestingly, the measurements made for the PAL test tape yielded the highest results. The NTSC record/playback results are lower than we would expect to see.

The luminance signal-to-noise measurements indicate the brightness and detail that you can expect to see in recorded videos. The measurements on the Image Translator were unexceptional at best.

On a brighter note, the Image Translator offered good stairstep linearity, deviating no more than 2% from perfect linearity. Its performance was worse, but definitely acceptable, in the PAL playback mode.

The audio measurements show a reasonably poor signal-to-noise ratio and THD performance, and acceptable frequency-response characteristics.

In summary, if not for the multi-standard capabilities of the Image Translator, we would not be overly impressed by its performance.

TEST RESULTS—VIDEO SECTION*

Frequency Response (@2.0 MHz)

NTSC record/play out	-2.25 dB
PAL test tape play	-9.86 dB

Signal-to-Noise Ratios

Red Field Chroma	
NTSC AM	39.7 dB
NTSC PM	36.2 dB
PAL AM	41.0 dB
PAL PM	36.1 dB
Luminance	
50 IRE	
NTSC	33.2 dB
PAL	35.1 dB

TEST RESULTS—AUDIO SECTION (NTSC)

Output Level

(0 dB reference level, 1 kHz)	0.49 volts, 1.53% THD (SP)
	0.45 volts, 2.04% THD (SLP)

Signal/Noise ("A" weighted)

41.4 dB (SP) 42.2 dB (SLP)


Flutter

0.17% avg; 0.20% pk (SP)
0.32% avg; 0.40% pk (SLP)


ADDITIONAL DATA

Weight	8¾ pounds
Dimension (H × W × D)	3½ × 14½ × 11½ inches
Power Requirement	16.5 Watts
Fast Forward Time (T-120)	3:53
Fast Rewind Time	3:10

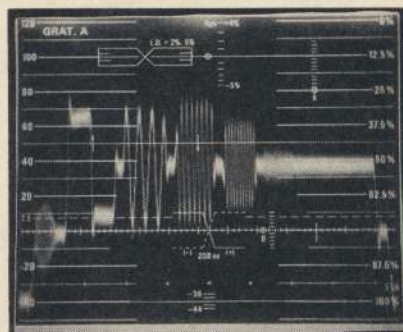
*All PAL measurements are made with a PAL test tape.



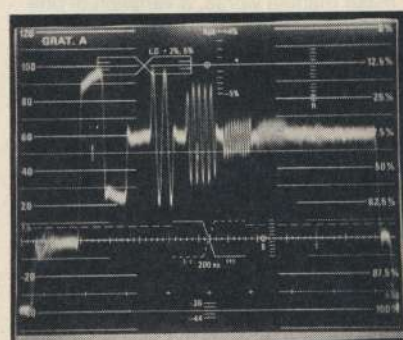
The multiburst pattern shows the acceptable frequency response performance of recorded NTSC signals.



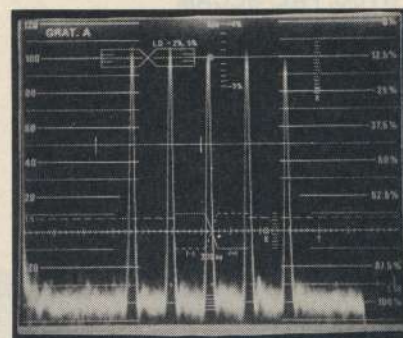Playing back a PAL test tape yielded response results that were significantly worse than those obtained from NTSC recordings, but still acceptable.



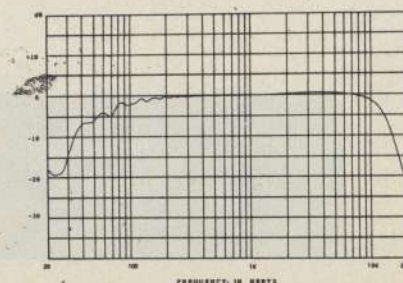Measurements made when playing back a PAL test tape showed acceptable stairstep linearity.



The frequency response of the audio section of the Image Translator for NTSC recordings in SP mode.

Video Standards: Parlez-vous PAL?

Anyone who travels internationally expects to encounter communication problems in foreign countries, due to the different languages used. Savvy travelers are also aware of the problems caused by trying to use American electrical appliances in Europe, because of the differences in voltage and frequency of the power lines. To minimize some of those problems, travelers often carry multilingual dictionaries and voltage converters.

Perhaps not so well known is that similar barriers exist between televisions around the world, which operate under one of three different broadcast standards—NTSC, PAL, or SECAM—or, to make matters worse, a variation of one of those three. In the 1990's, when world travel, multinational corporations, and widespread immigration have made the world seem smaller, and when camcorders and VCR's have made video a portable medium, it seems ridiculous to have different standards. Hindsight is always 20/20, but when video standards first were introduced—in the years following World War II—there was no talk of the "global village" and television was still a local medium. No one thought about people using video cameras to send tapes of the grandchildren to relatives in foreign countries, or large corporations making training tapes to be used in branch offices in various countries.

NTSC, PAL, SECAM

It took three years of negotiations for NTSC, named after the National Television System Committee, finally to be declared a uniform standard in the United States by the FCC in 1953. The NTSC standard uses a scanning rate of 60 cycles per second, which corresponds to the frequency of the AC power lines in the United States. Each

1/60-second image, called a field, is made up of either even or odd lines drawn by the picture tube's electron gun. Each pair of fields makes a single frame—a full resolution image with 525 scan lines, that is actually a combination of the odd and even fields that have been interlaced.

The PAL (or Phase Alternate Line) standard, developed to match the 50-cycles-per second AC power available in Europe, Asia, and Africa, is a 25-frame-per-second system. With the slower frame rate, there is more time to transmit a higher resolution picture—625 lines—while still using the same bandwidth for broadcasting. SECAM (for *Sequentiel Couleur avec Memoire* or color sequence with memory) also is a 25-frame-per-second system.

So, right from the beginning—in the days of black-and-white, vacuum-tube sets—two factors were incompatible: resolution and field frequency. The advent of color television only made matters more complicated. While it made sense at the time to make color television standards backward-compatible, so that black-and-white TV's could display a monochrome image from the color broadcasts, that simply introduced a third incompatibility: chrominance, or color information.

All color television systems use the same basic scheme. The color information or chrominance is made up of three signals representing television's primary colors—red (R), green (G), and blue (B)—that are combined with each other and with the black-and-white (or luminance) information.

The NTSC system transmits only the luminance, R, and B signals. A decoder in the TV tuner then derives the G signal using the mathematical relationship between the color components. Some problems resulted from that solution,

however—ones that were serious enough to inspire the nickname "Never Twice the Same Color" for NTSC. The NTSC color subcarrier, which uses amplitude modulation (AM), is in the middle of the luminance spectrum; that sometimes results in interference—usually in the form of shimmering patterns that are most obvious when someone on screen is wearing a checkered jacket. The noise added to the color signal during transmission adversely affects NTSC signals. Finally, TV decoder phase-shifting changes the tint, making manual tint-controls a requirement on NTSC sets.

Based on the assumption that any two adjacent lines have the same phase distortion, the PAL system compensates for tint changes by shifting the phase of every other line by 180 degrees. The receiver then averages the phase from successive lines, canceling out undesired phase changes and eliminating the need for manual tint controls.

The SECAM standard is based on the same number of scan lines and frame rate as does PAL, but frequency modulation (FM) is used to process the video signal before transmission, although the final composite signal is broadcast in AM. The SECAM color-encoding technique is also different in that each scan line contains information about only one primary color. The next line contains the second color, and the missing third color is derived from the previous lines by the receiver.

If you bring your travel iron along on your European vacation, a simple voltage adapter allows it to run on the different electrical system. Unfortunately, there's no little add-on adaptor that allows you to watch videos recorded on an NTSC VCR on a PAL or SECAM TV and VCR. To get a clear color picture, three factors must match: scan rate

The standard must be selected while the power is off or you'll have no success watching non-NTSC tapes unless you unplug the unit from the wall and reset it. The VCR can produce a 525-line, 60-Hz NTSC signal from a 625-line, 50-Hz videotape. The converted output is compatible with all NTSC TV's and can be recorded by an ordinary VCR for standards-conversion purposes (although you can't make dupes of copy-protected tapes). SECAM tapes play back in black-and-white only.

We were able to try out the conversion capability using foreign commercial tapes: the German version of Eddie Murphy's *Coming to America*, *Der Prinz aus Zamunda* in PAL, and a French version of a horror flick called *Possession: The New War of the Worlds* in SECAM. In addition,




CIRCLE 53 ON FREE INFORMATION CARD

VIDEO STANDARDS (continued)

(number of frames per second), resolution (number of scanning lines), and chrominance (color signals). PAL and SECAM are somewhat compatible, since they have the same resolution and scan rate, but usually the color information is lost when you try to play one type of tape on the other type of system. When you try to view an NTSC tape on a PAL or SECAM VCR, the result is a scrambled picture and garbled sound—unless you have a multi-standard VCR, or have the tape professionally converted to the correct standard. In this month's **Gizmo**, we take a hands-on look at one multi-standard VCR, the Instant Replay 610IT3 Image Translator 50/60. Another option is the VidiPax conversion service.

People who occasionally need to send a videotape overseas—sending their parents in Europe videos of their grandchildren at their birthday parties and Christmas, for instance—would be better off having those tapes professionally converted to PAL or SECAM than using an expensive multi-standard VCR. The conversion process is complex and costly for small-scale local shops to handle, so professional video-conversion services often were difficult to locate and expensive once found, charging up to \$100 for an hour of videotape.

VidiPax International (P.O. Box 2, Eldred, NY 12732) offers a convenient and relatively inexpensive alternative. Similar to the prepaid processing mailers that are commonplace in the film-developing industry, the VidiPax mailers can be purchased at electronic, video-rental, photography, and drug stores around the country. (For a dealer near you, call 914-557-3600.) The mailers are then used to send a videotape to VidiPax, where it will be converted to either PAL or SECAM. An order form printed in

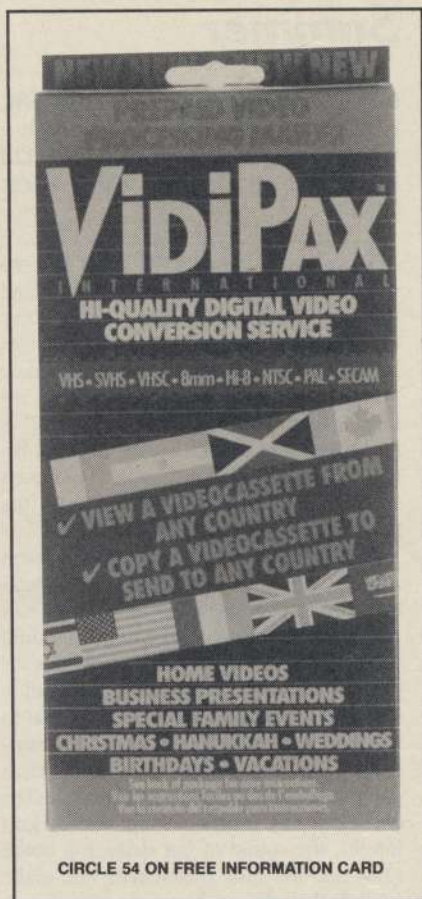

English, French, and Spanish is included. You don't even have to specify which standard; just tell VidiPax in which country it will be played, and they will convert it to the correct standard. A week or two later, you'll receive both your original and the converted duplicate by UPS. We had good results when

we had VidiPax duplicate a video test-standards tape into both PAL and SECAM. (Details appear in the Instant Replay VCR article.)

VidiPax uses a complex digital technique to convert the tapes. Remember, three areas of incompatibility must be overcome: resolution, field frequency, and color information. Instead of simply cutting off some of the video, as is done in some multi-standard VCR's, VidiPax uses digital interpolation to take care of the differences in resolution. The video lines are digitized, and then the lines that should be added or subtracted are averaged, or interpolated.

Differences in field rates are reconciled by the process in a similar manner, by digitizing and interpolating fields in the time domain. A technique that is called motion-vector analysis tries to anticipate motion and selectively interpolate using different algorithms to reduce visual artifacts.

Chrominance transcoding is done by keeping track of the color information for each video line and encoding it in the new standard in the final digital-to-analog stage of the conversion process. The content of that line will be determined by the scanning line and field frequency that has occurred.

Although the standards-conversion process is fairly complex, and involves sophisticated equipment, by performing the standards conversions at one central location the price can be kept to a reasonable level. The \$39.95 mailer is good for up to one hour of digital conversion. Each additional hour of tape converted costs \$7.50 more, and duplicate tapes cost \$15 each. Once the processing is complete, your original tape and the converted version are returned to you by VidiPax. The company will also convert from VHS to 8mm at no additional charge. ■

we had our own tapes that had been converted using the VidiPax standards-conversion service (see box). For test purposes, we first made a tape of a laserdisc called "A Video Standard" (published by Reference Recordings), which contains video test patterns and audio and video test signals that let you determine the accuracy of your equipment's reproduction. We sent that tape off to VidiPax, where copies were made in both PAL and SECAM.

The results were nowhere near perfect video in either PAL or SECAM mode, although the quality of PAL tapes was somewhat better than that of SECAM tapes, even without considering the lack of color in the SECAM version. SECAM tapes had poorer resolution and noticeably poorer audio quality. The PAL tapes, while

better than those recorded and played back in SECAM, suffered in comparison to NTSC tapes. The most noticeable and annoying problem was a picture that bounced continually—something not indicated in our laboratory tests. Playing with the sharpness control on the back of the unit helped to get the color level correct—but that control isn't even mentioned in the manual (or shown on any of the equipment drawings), and its placement is anything but convenient.

Whether you're using the Image Translator VCR to watch videos recorded in PAL, SECAM, or NTSC, or simply using it to tape your favorite TV shows, the unit offers many features that you'd expect to see on a decent VCR—but certainly not everything you'd expect to see on a \$795 unit. There are some trade-offs for the

standards-converting capability. The Model 610IT3 is a two-head unit, and lacks hi-fi stereo sound, which we consider important. Instant Replay does offer other standards-converting VCR's with all the bells and whistles—Dolby Surround Sound, S-VHS, four heads—but at an even higher price.

The model that we tested was not completely Spartan; it did offer some valuable convenience features. On-screen programming is used to set the date and time (you can call up a monthly calendar screen that has today's date flashing or a time/date screen); to add or delete channels either manually or automatically. Each function is easy enough to accomplish, and those who get easily flustered by VCR programming will appreciate on-screen prompts such as "To end, push program." You can

set the timer recording for single events, or to record the same show every day or every week. You can also use one-touch recording to set the VCR to record in half-hour time increments up to 11:30 PM on the next day.

Although each of those recording methods is quite easy to use, we did encounter some problems caused by power interruptions. If the power interruption occurred in the middle of recording, the Image Translator VCR stopped and didn't come back on when power was restored. If it was programmed to tape shows later, that information was lost. And, as much as we hate being confronted by a host of LED's flashing "12:00" each time the power is restored, it's better than the Image Translator's solution, which is to display the wrong time (the correct time minus the five minutes it took for power to be restored). It's all too easy to not notice the time discrepancy and end up missing the first five minutes of the next show you tried to tape.

On the other hand, the Model 610IT3 has a feature that we particularly liked: time search. Time search allows you to fast forward and rewind by specific lengths of time. Say, for instance, that the family had to go out on a Wednesday evening and you set the VCR to record everyone's favorite game show *Jeopardy* (7:00-7:30), a documentary that your daughter had to watch for a social studies assignment (6:00-7:00), and *Beverly Hills 90210* for the kids (9:00-10:00). Instead of rewinding the tape and fast-forwarding through *Jeopardy* to get to the documentary that she had to watch, your daughter could rewind it, set the time search for 30 minutes, and the VCR would automatically bring the tape to the beginning of the documentary. That feature works in reverse, too. If your daughter decided she'd rather watch *Beverly Hills 90210* first, she could set the timer search to rewind for one hour.

All in all, the Image Translator VCR was easy and convenient to use. Most of its functions could be operated intuitively, and the remote control featured well-marked, well-placed keys. When we used the Image Translator as an everyday VCR, taping and playing back television shows, we had few complaints. When using it as a standards-converting VCR, however, some problems arose. We recognize the complexity involved in the standards conversion process, and appreciate having the ability to view PAL and SECAM videotapes in the U.S., even if the quality wasn't great. The poor picture and sound quality didn't bother us as much as the poor placement of the standards-conversion controls and the lack of instructions about using that feature, which, after all, is its claim to fame.

The Toys of Summer

BIG LEAGUE BASEBALL ELECTRONIC ENCYCLOPEDIA. Manufactured by: Franklin Electronic Publishers, Inc., 122 Burrs Road, Mt. Holly, NJ 08060. Price: \$129.95.


We are not big fans of baseball—we seldom watch games on television, and pay only fleeting attention to the scores and standings printed in the sports pages each day. We consider ourselves Yankee fans, but we couldn't name this year's infield without help. ("Fair-weather fans" is probably more accurate—we can still recall the entire Yankee lineups, and even some of their jersey numbers, from the spectacular 1977 and 1978 seasons!)

Yet whenever we travel during the warm months, on either business trips or vacations, we try to catch a major-league ball game. There's something about attending a live baseball game that transcends simply watching a sporting event. Baseball is so firmly entrenched in our culture that to be there is to experience a bit of Americana. We love the sameness of each game—the classic duels between pitcher and batter, the teamwork of a closely knit infield, the sound of bat striking a home run—and the little differences that make each ball park and home-team audience unique. We love listening to the fans in neighboring seats (who are almost always more knowledgeable and more vocal than us) discuss strategy, tell tales of other games, and throw around statistics and

sometimes-scathing comments. (Fans can be far more entertaining than sportscasters. Our favorite line: The guy sitting in front of us, responding to someone's remark about a batter known for taking his time at the plate, said, "Yeah, he's what you might call a human rain delay.")

Even though baseball doesn't have the fast action and excitement of hockey, football, or basketball, it has a history that lives on in tradition, in legend, in stories handed down for generations—and in statistics. There were unbeatable teams, classic games, historic hits, and larger-than-life heroes. And true baseball fans, be they absent-minded professors or high-school dropouts, can remember who won the series in 1952; can rattle off statistics about every player on the 1967 White Sox; and can explain the meaning of RBI, HR, E, AB, ERA, and a host of other statistical abbreviations. Perhaps it's baseball's leisurely pace that's allowed the time for such intense examination of games and teams past—after all, the fans and sportscasters need something to discuss during pitching changes or when a "human rain delay" steps up to the plate!

Now even folks like us can have baseball facts and figures at our fingertips at all times, thanks to *Franklin's Big League Baseball Encyclopedia Model HR-61*. Those facts and figures include more than 620,000 batting statistics, 270,000 pitching stats, and biographical information about every player in the history of major league baseball. Moreover, you can manipulate the data in the Baseball Encyclopedia to discover who was the all-time leader in home runs (Hank Aaron, 755) or who had the worst batting average in the American League in 1971 (Dean Chance,

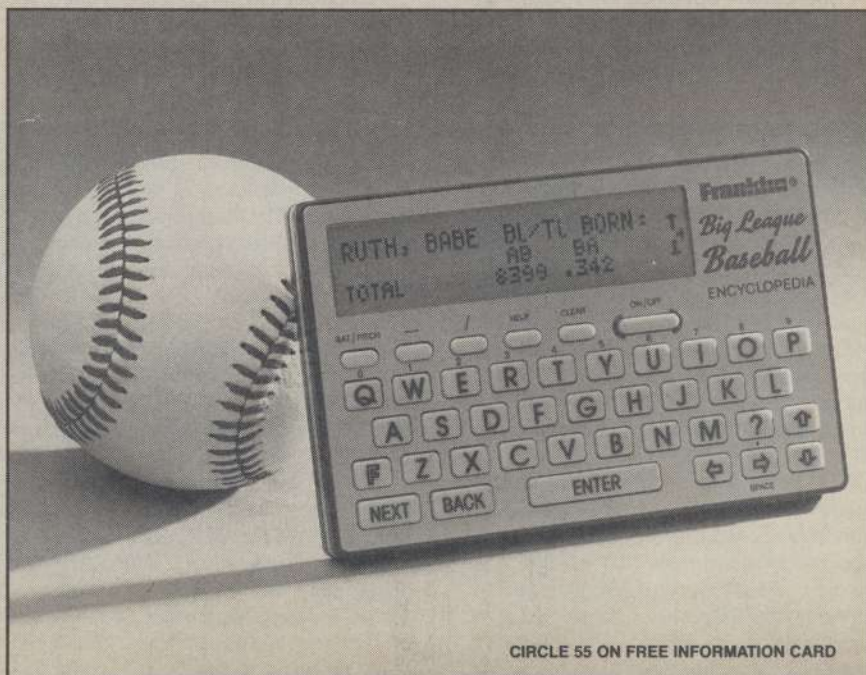

CIRCLE 55 ON FREE INFORMATION CARD

47st. Photo®

The latest in electronics is only a phone call away! 1-800-221-7774

In N.Y. or if busy call: 1-718-722-4750. Please mention code ES892.



AIWA CSD-EX1
PORTABLE LCD
RADIO CASSETTE CD PLAYER

- High power output
- Power saving switch plus auto stop
- 20-selection random programmable memory CD
- AM wide/FM stereo tuner

(AIW-427)
Sugg. Retail \$179.95

Our Price
\$139.95



AIWA NSX-330
30W/ch HI-FI MINI COMPONENT
SYSTEM WITH SURROUND SOUND

- Super T-bass

Includes:

- 3-preset graphic equalizer
- 5-band spectrum analyzer
- Wireless remote
- FM/AM tuner with 32-station random preset
- Dual auto reverse cass. w/Dolby B NR
- Optical digital output terminal
- 3-way speaker (AIW-424)

Sugg. Retail \$560.00

Our Price
\$399.95



AIWA XP-7
PORTABLE CD PLAYER
WITH IN CAR USE

- 1-bit dual D/A converter
- 8-times oversampling digital filter
- Optical digital output terminal
- 24-random programmable memory
- Heat-resistant for in car use
- Random play with 3-way repeat

Includes: Rechargeable battery BP-50, stereo headphones with remote control, AC adaptor recharger, and connection cord. (AIW-420)

Sugg. Retail \$280.00

Our Price
\$249.95



CANON E-63
8mm CAMCORDER WITH
8:1 POWER ZOOM

- High speed shutter
- 180° FlexiGrip
- 2-lux low light
- Sports finder
- Wireless Remote (CAN-6300)

BONUS!
Free case
with purchase
of E-63
\$59 Value!

Super Value!



PANASONIC RQ-S35V
AM/FM STEREO CASSETTE
PLAYER WITH AUTO REVERSE

- Ultra compact size
- Digital synthesizer tuner with 7AM/7FM presets
- S-XBS & Dolby NR
- LCD tape/radio display
- Dual clock/alarm functions
- One button wired remote

Includes: Rechargeable battery and charger. (PAN-2754)

Sugg. Retail \$209.95

Our Price
\$169.95



SONY WM-WX50
WALKMAN®
STEREO CASSETTE
PLAYER

WIRELESS HEADSET!

- Broadcasts up to 9 ft.
- Auto reverse Mega Bass 2x sound system with variable control
- Dolby NR (SON-3483)

Sugg. Retail \$249.95

Our Price
\$179.95



SHARP IQ-8400
ELECTRONIC ORGANIZER

- 256 KB memory
- Typewriter style keyboard
- Hi-contrast 40 char. by 8 line screen
- Month/week & day calendar
- 3 phone directories
- Business Card function (SHA-8400)

Sugg. Retail \$499.95

Our Price
\$319.95



PANASONIC KX-T4300
CORDLESSPHONE WITH
ANSWERING MACHINE

- 10 channel access • Rubber antenna
- Tone/pulse • 2-way paging
- 10-number speed dial • Message alert
- LED readout
- 11-function tone remote
- Auto logic operation. (PAN-4300)

Sugg. Retail \$199.95

Our Price
\$159.95



PANASONIC KX-T9000
900MHz POCKET-SIZED FOLDING
CORDLESSPHONE

- Operates on 902/928MHz
- Sound Charger technology
- 30ch auto scan • Auto Intercom
- 2 interchangeable batteries
- 2-way paging & auto intercom
- 10, 20 digit no. auto dial
- Handset Auto switch to 'talk' mode (PAN-9000)

Sugg. Retail \$499.95

Our Price
\$399.95



CASIO BP-100
BLOOD PRESSURE
MONITOR WATCH

- Water resistant to 50 meter
- 12/24-hour formats
- 3 multi-function alarms
- Altimeter, Depth meter & Barometer
- Countdown alarm
- 1/100 stopwatch (CAS-826)

Sugg. Retail \$169.95

Our Price
\$129.95



SONY XVT-600
ADD PRO STYLE SUPERIMPOSED
TITLES TO YOUR VIDEOS!

- 15 color picture computer superimposes picture title or background to video
- Draw lines, add color—endless possibilities!

(SON-409)

Sugg. Retail \$600

SALE!
\$109.95



PANASONIC CTP-2066S
20" STEREO MONITOR-RECEIVER
WITH S-VHS INPUT (Over 500
lines horizontal resolution)

- Audio/Video input jacks
- Unified TV/VCR remote
- Clock, Sleep-timer & on-timer (PAN-2796)

Sugg. Retail \$499.95

SALE!
\$357.95

- Cameras
- Darkroom Supplies
- Video Equipment
- Televisions
- Hi-Fi Stereo Equipment
- Portable/Personal Audio
- Telephones
- Cellular Phones
- Computer Equipment
- Business Machines
- Calculators/Organizers
- Electronic Games
- Watches/Sunglasses
- Small Home Appliances
- Jewelry

Visit our superstores at:

67 West 47th Street **115 West 45th Street**

Bet. 5th & 6th, NYC CA. LIC. #800189-691860

Bet. 6th & B'way, NYC CA. LIC. #800191-811628

1-212-921-1287

Sun. 10:00-5:00, Mon.-Thurs. 9:30-6:00, Fri. 9:30-2:00, Closed Saturday

A New York Landmark for over 26 years!

Mail Order Dept.:
455 Smith Street, Brooklyn, N.Y. 11231

G1192

Toll-free line is open
SUN. 10-5, DAILY 8-7, FRI. 8-2
Local lines are open
SUN. 10-5, DAILY 9:30-6, FRI. 9:30-2

OVERNIGHT DELIVERY
to any point in the
continental USA
AVAILABLE
at additional cost

0 for 21). If you're more interested in heavy players than heavy hitters, you can even find out which ball player weighed the most (Walter "Jumbo" Brown, 295 pounds).

Weight isn't a problem for the Big League Baseball Encyclopedia, however. Bearing no resemblance to those hefty, old-fashioned books of baseball stats with complex cross-referencing systems, the electronic version is sized to fit in a shirt pocket, and weighs only five ounces. It comes with a protective vinyl cover and a quick reference card that provides operating pointers when the manual isn't at hand. Searches can be initiated in several ways, and cross-referencing is done at the push of a button.

You can search for statistics by keying in (on the QWERTY-style keypad) the player's name (first, last, or both), the team name or city, or the league. Even nicknames will work: Catfish, for James "Catfish" Hunter, for instance. And Franklin's built-in phonetic spell-checker will correct misspelled players' names and offer alternatives for guesses.

When an individual player is called up, Big League Baseball's three-line, 24-character LCD readout will show his full name on the first line. Arrow keys are used to scroll across the line, which also includes BL/TL (bats left/throws left for a southpaw) or BR/TR; birth and death (if applicable) dates; weight; and height. The second line displays headings for the columns of statistics that follow: for pitchers, IP (innings pitched), ERA (earned-run average), W and L (wins and losses), SV (saves), ER (errors), SO (strike outs), H (hits); for batters, AB (at bats), BA (batting average), HR (home runs), RBI (runs batted in), H (single-base hits), 2B (doubles), 3B (triples), R (runs scored), and SB (stolen bases). Career totals are displayed on the third line. Each subsequent line shows the year, team, and league, and the players statistics for that year.

When searching by team, you can key in the team name to see a complete year-by-year history of the team. Typing in "Red Sox" will call up first the 1901 Boston Red Sox (A) (for American League), followed by team-total batting averages and then individual players' averages (Cy Young batted .209 that year). A press of the BAT/PITCH key calls up the pitching stats. A press of the NEXT key brings up the next year. If a team has played in more than one city, a list of options will appear. Typing in "Dodgers" brings up the choices "1958-91 LA Dodgers" and "1890-1957 Bro Dodgers," for instance. Similarly, typing in "NY" calls up the team choices: 1903-91 NY Yankees, 1962-91 NY Mets, 1883-1957 NY Giants, and 1876 NY Mutuals—a team that none of the native New Yorkers

here at Gizmo had ever heard of. There's no need to scroll through fifty screens if you want to take a look at the 1950 Yankees; you can simply type in "1950 Yankees" to go directly to that year.

Once you've called up a team, cross-referencing to individual players is a snap. You simply move the cursor to the player whose stats you want to see and press ENTER. A press of the BACK key returns you to the team-info screen.

You can find teams' win/loss records and final league standings for any year by typing "AL" or "NL" followed by the year, and can see complete stats for any of those teams by pointing the cursor at them and pressing ENTER. You can also find out the results of any World Series by typing in "WS" and the year.

All of those functions are simply the basics of the Big League Baseball Encyclopedia. Its compact size, easy cross-referencing, and automatic spell correction do set it apart from any written baseball encyclopedia. But the unit's electronic search capabilities, which allow you to create your own statistical lists, make it truly unique.

Typing in "MAX" or "MIN" before any stat abbreviation will result in a list of the players with the most or least; that works for all pitching and batting stats, as well as biographical information (age, height, and weight). You can find out maximum and minimum ratios—for example, most home runs per at bats, by typing in "Max HR/AB."

The results of those two examples are quite different. The most-home-runs list comes as no surprise, starting off with baseball legends Hank Aaron, Babe Ruth, and Willie Mays. The players with the most home runs per at bats are not as well known—Frank O'Connor was up at bat twice and hit one homer, Luke Stuart and Jeff Bittiger were each one for three.

You can further hone your search by adding limiters—"GT" for greater than or "LT" for less than. To discover who has the most home runs and has a batting average under .250, you would type in "MAX HR BA LT .250" and find Dave Kingman (442 home runs, .2359 average) at the top of the list. You can use years or teams (or both) as qualifiers separately from, or in addition to, "MIN/MAX" and "GT/LT." For instance, "MAX HR BA LT .250 METS 1969" would create a list with Ed Kranepool (11 homers, .2380 average) at the top. Each list can contain up to 30 names. To learn more about any player in a list, you can move the cursor to his name and press the enter key to cross-reference.

When you consider the number of qualifiers and statistics contained in Big League Baseball, you'll soon realize that the possibilities are close to endless—at least, you're far more likely to run out of

curiosity long before it runs out of possible list combinations.

We do have a few complaints, however. First, we weren't crazy about either the keyboard layout or the tactile response of the keys. The ENTER key was in the space normally occupied by the space bar, which created some problems, and the number keys run from zero through nine instead of one through zero as they would on a standard keyboard. Second, we strongly feel that the players' field positions should have been included. Third, we would like to have seen included statistics on walks—there have been quite a few players known for their ability to draw bases on balls.

The Big League Baseball Encyclopedia does a great job of providing pitching and hitting stats; perhaps it's too much to ask for fielding stats as well. Yet even though baseball drama revolves around the pitcher and the batter, it's often fielding that makes or breaks a game. With the electronic encyclopedia, you can call up the Chicago Cubs in the early years of the century and find Joe Tinker, Johnny Evers, and Frank Chance on the roster, but you won't learn anything about the famous Tinker-to-Evers-to-Chance double-play combination.


In a similar vein—although we're not sure if this is a plus or a minus—some of the unit's answers to our inquiries were intriguing enough to send us to the written books (and to call our fathers) for more details than could be provided by the statistically oriented electronic encyclopedia. For instance, our search for the major leaguer who weighed the least came up with Eddie Gaedel, who weighed 65 pounds and was only 3 feet, 7 inches tall! Still more perplexing, we learned that in his one season with the St. Louis Browns in 1951 he had no at bats—in fact, all his stats were zeros. It turns out that Browns' owner Bill Veeck brought in a dwarf to force a walk. Gaedel was at bat once, crouched over the plate to present the pitcher with a six-inch strike zone, and drew a walk. Outraged baseball commissioner Ford Frick quickly called an end to Gaedel's major-league career.

Of course, baseball is a unique amalgam of statistics and stories, and Big League Baseball provides the quickest statistics that we've ever seen. In fact, its good points far surpass its drawbacks, even for people who aren't obsessed with the game. Because it's so easy to use, you never get bogged down or frustrated. The manual clearly explains how to set up complex questions, the quick-reference card provides reminders, and there's even on-screen help to get you out of any potential jams. We loved the nostalgia of calling up favorite teams, checking out what was happening in the years in which we were born, and perusing the careers of favorite players. ■

Your choice for only \$9.95

when you join the Electronics Engineers' Book Club

Your source for . . .

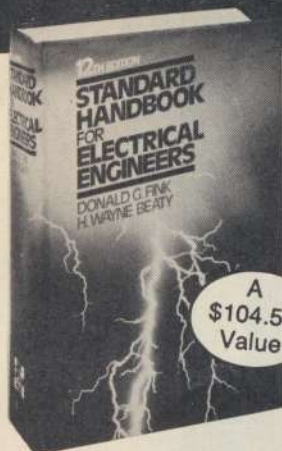


A
\$104.50
Value

STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 12th Ed.

Edited by Donald G. Fink
and H. Wayne Beaty

- the essential on-the-job reference for Electrical Engineers
- latest information on rapidly changing areas such as nuclear power and high-voltage transmission systems
- all the essentials including circuits, telecommunications, power distribution and electrical standards
- Written and compiled by 115 recognized experts

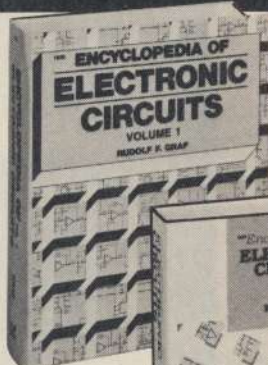2,248 pp., 1,863 illus. and tables
Order #020975



A
\$120.00
Value

THE ENCYCLOPEDIA OF ELECTRONIC CIRCUITS—Volumes 1 & 2


by R.F. Graf

These comprehensive sourcebooks put over 1,900 of the latest and most useful circuit designs at your fingertips. The format, generously illustrated and cross-referenced, is organized for quick access to 108 distinct categories.

Volume 1—768 pp., 1762 illus.

Volume 2—744 pp., 728 illus.

Order #585785

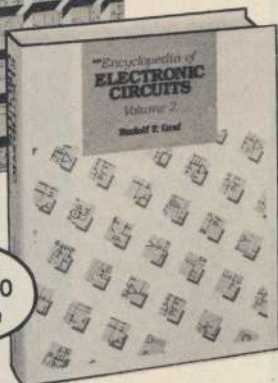

A
\$105.00
Value

ELECTRONICS ENGINEERS' HANDBOOK, 3rd Ed.

by Donald G. Fink
and Donald Christiansen

This fully revised and updated edition of the standard desktop reference shows you how to use the latest design and cost-cutting solutions at work in the industry today. You'll find a wealth of new material on electronic systems design, computer systems and digital recording, telecommunications, process control, laser technology, and CAD of electronic circuits.

2,258 pp., 1,800 illus.

Order #9255H

As a member of the Electronics Engineers' Book Club . . .

. . . you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off of regular publishers' prices. If you want the Main Selection do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. Your only obligation is to purchase 3 more books during the next 2 years, after which you may cancel your membership at any time.

A shipping/handling charge and sales tax will be added to all orders. All books are hardcover. (Publishers' Prices Shown) ©1992 EEBC

If coupon is missing, write to:

Electronics Engineers' Book Club, Blue Ridge Summit, PA 17294-0860

ELECTRONICS ENGINEERS' BOOK CLUB

Blue Ridge Summit, PA 17294-0860

YES! Please rush me the book(s) indicated below for just \$9.95 plus shipping/handling & tax. Enroll me as a member according to the terms outlined in this ad. If not satisfied, I may return the book(s) within ten days without obligation. A shipping/handling charge and sales tax will be added to all orders.

- ☐ Standard Handbook for Electrical Engineers, 12th Ed. #020975
- ☐ Encyclopedia of Electronic Circuits, Volumes 1 & 2 #585785
- ☐ Electronics Engineers' Handbook, 3rd Ed. #9255

Name

Address

City/State

Zip Phone

Valid for new members only, subject to acceptance by EEBC. Canada must remit in U.S. funds. Applicants outside the U.S. and Canada will receive special ordering instructions.

PPIF1192

that you might decide to buy a few years down the road.

Universal's One For All 4 remote uses a patented RAM (random-access memory) chip that has the ability to be upgraded as you upgrade your equipment (and even upgraded to cover your very old components). The upgrade, while fairly easy to accomplish (it involves running a cable between a One For All remote and a computer that provides new product codes), must be done at Universal or one of its service centers, which is a bit inconvenient for users. But the company is so sure of its ability to match your equipment (with the exception of Bang & Olufsen products, which use a different IR frequency than any other products on the market), that they offer a double-your-money-back guarantee.

We had no problem entering the codes for a Sanyo VCR and Zenith TV using the sequence TV (OR VCR) - A - B - C - followed by the three-digit code listed in the manual. Unfortunately, we gained control of only the most basic functions of the two units. We were unable to access any on-screen menus for timed-taping, source selection, or any of the other functions that we frequently use. (That's the big advantage that the more complicated learning remote controls have over the ROM and RAM-based ones: By programming them key-by-key, you can replicate every function of the original remote.) We were also unable to find a code corresponding to the Instant Replay standards-converting VCR that we review elsewhere in this issue.

Universal provides a toll-free number for just such dilemmas. We were helped by a pleasant woman who informed us that although the All For One remotes are intended solely for basic operations, it is sometimes possible to access more sophisticated functions using various series of letters and numbers. Because they don't work for all models, the manual doesn't mention them. We lucked out with our VCR and TV: pressing VCR - A - 1 - 0 brought up our on-screen programming menu, allowing us to set the timer to record our favorite shows. We were able to operate the TV's picture-in-picture using a similar sequence, but we still couldn't get it to control some of the less-frequently-used functions. That could present a major problem for people whose sets lack front-panel controls for some of the more sophisticated functions—lose the original remote, and you're out of luck.

As far as the Instant Replay deck goes, neither our customer-service rep nor her manager could find any reference to it. She suggested that we try to "search the library." According to the manual, it's possible that the correct code for a piece of equipment is already in the All For One 4, but listed under a different manufacturer.

You can search the entire library of devices by turning on the device, pressing A - B - VCR - C - POWER, and alternating between C and POWER until the VCR turns off. Although it might be necessary to repeat C - POWER as many as 50 times, the process doesn't take long. Once the device turns off, pressing the "A" key locks in the code. Unfortunately, searching the library didn't work with the Instant Replay VCR. (We suppose we could have tried to return the One For All 4 for "double-our-money"—but that wouldn't work with a unit that we'd only borrowed! Besides, it works quite well on the equipment that we use every day.)

Although it's called the All For One 4, the remote control can be used with only three video devices—a TV, a VCR, and a cable box. The fourth device key, labeled AUX on All For One 4's that are sold without the Home Control Center, is now labeled HOME CONTROL and is used to control lights and appliances.

Setting up the Home Control Center is no more difficult than preparing the remote for use with video equipment. The set comes with one command-center module, one appliance module, and one lamp module. Each command-center module can control as many as 16 lamp and appliance modules, which can be purchased separately for under \$20. The command center is plugged into any standard wall outlet that's in the room where you would normally use the remote to control your video devices—probably either the family room or bedroom. Each module must be given its own unit code, which allows the command center to distinguish it from other modules. A screwdriver is needed to turn the selector on the front of each module to the desired number. The accessory modules then can be plugged into any outlets in the house or yard, and the devices to be controlled then plug directly into the modules. Once everything is plugged in, you program a home-control code in the same manner that you set the video-gear codes, using one of the three-digit codes provided in the manual.

Once the set up is complete, by aiming the remote control at the command center, you can remotely turn appliances and lights on and off. The infrared signals from the remote control activate the command center, which passes commands to the modules through your home's AC wiring. (You can also skip the remote control and use the keypad on the command-center module to directly control up to eight lights or appliances.) To remotely turn on the lamp that's connected to lamp module one, for instance, you would press HOME CONTROL - 1 - ON (the CHANNEL-UP key doubles as the ON control; CHANNEL DOWN and OFF also share a key). Other buttons on the remote control allow you to dim lights

and to simultaneously turn on every light and to turn off every light and appliance that's hooked up to the system. It's not possible to turn on every appliance at once because some unwanted consequences can result if the remote is used carelessly. For instance, you wouldn't want to accidentally turn on a coffee maker that had no water in its carafe. The manual suggests attaching a label on which you've recorded the module number of each device under control to the back of the remote control for quick reference—and to make sure that you do not accidentally turn the wrong appliance on or off.


We didn't need a reference chart, because our test package came with only one light and one appliance module. We first tried it in the office, to control a desk lamp and a fan. Everything worked exactly as promised, and it didn't take long for the keystroke sequences to become second nature. Available outlets are at a premium in our office, and when we had to unplug the control module in order to plug our printer back in, for some reason the appliance module began to turn the fan on and off by itself at unpredictable intervals. That problem was remedied by resetting the command control module.

The outlet situation in our media room is somewhat better, and we didn't have the same problem there. Actually, even in our rather limited configuration (we used the system to control two lamps in the room), the Home Control Center One For All 4 both provided the convenience of one using remote for both TV and VCR and offered an excellent introduction to home automation. We particularly liked a feature called "Punch-Thru," which lets you operate several video devices simultaneously without having to repeatedly change device keys. For instance, if the last device key pressed was CABLE, you can still control the volume and mute keys on the TV and the VCR's play, pause, fast forward, reverse, and TV/VCR keys. We also liked being able to use a single remote control to either mute the TV or pause the VCR and turn up the lights whenever the phone rang while we were watching TV. We imagine that, with the addition of more modules, the ability to turn off the room lights, outside lights, and the upstairs ones that somehow were left on before dinner all at the push of a button, and then to turn on the bedroom lights also would be quite convenient.

We're sure that you can think of quite a few things around your own home that could be added to a home-control system like this one—and we're also sure that that's just what Universal intended. Let timid consumers get their feet wet with remote control of one lamp and one appliance, and once they're hooked, they'll come back for more.



TSM FUNCTION-GENERATOR KIT

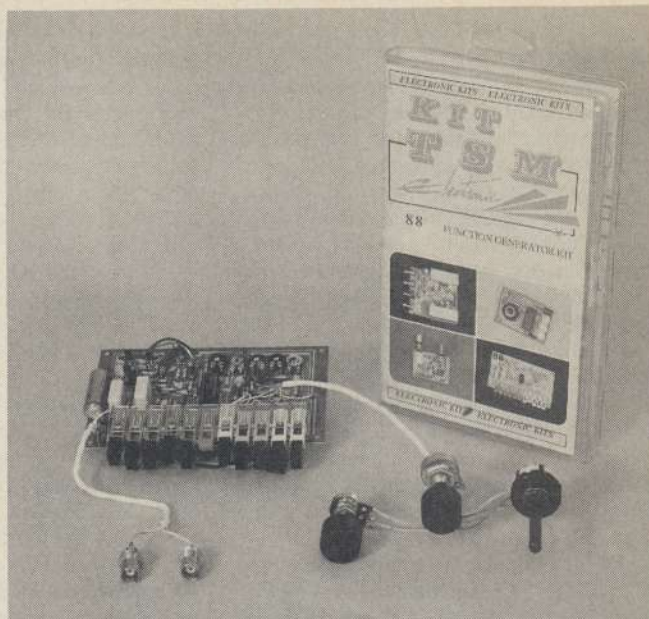

CIRCLE 119 ON FREE INFORMATION CARD

As user-built test equipment goes, this unit will perform well, but only for the builder who knows what he's doing.

It doesn't take much experience in electronics to teach you the value of a well-stocked test bench. Fortunately, by the time most of us have out-grown the multimeter-only phase of our hobby, we've gained enough skill to build at least some pieces of test equipment.

The *TSM Function-Generator Kit No. 88* seems just right for that level of experience—when you've already cut your teeth and need to take the next step. Unlike most TSM kits, the Function-Generator is not suitable for a rank beginner due to some idiosyncrasies in its assembly instructions. I'll point those out as I proceed to help those that wish to give the kit a try. The irregularities in the instructions should not significantly hamper the efforts of a seasoned kit builder. If you feel you fit that description, and don't mind a bit of a challenge, then read on . . .

Features. The specifications of the TSM Function Generator are appropriate for typical enthusiast use: It is capable of producing squarewaves, triangle waves, sawtooth waves, or sinewaves over a frequency range of from 8 Hz to 200 kHz, with signal amplitudes ranging from 1 mV to 1 volt. However, bear in mind that you really

need an oscilloscope to calibrate the unit's sinewave output. The lack of an oscilloscope will not prevent you from calibrating the other waveforms, though.

It should be mentioned that the signal output is AC coupled. The unit has a synchronization output in addition to its signal output. That eliminates the need for putting a tee connector on the signal output to connect it to a frequency counter or the synchronization input on an oscilloscope. Further, since the "sync" signal is not amplified by the unit's output circuitry, you needn't worry about it overdriving the input stage of a frequency counter. This little feature comes in real handy during calibration (which I'll get to a little later in this article) as well as regular use.

Oddly, except for the label "Synch" [sic] near that output on the unit's schematic diagram, this useful feature is not mentioned or explained anywhere in the documentation. If I didn't understand the circuit's operation from the schematic, I would have had trouble determining what the output is for.

Almost everything you need is supplied with the kit. However, you will need to add a 12-volt DC, 300-mA

power supply, two or three connectors (depending on whether your power supply requires a mating connector), an enclosure, and some wire to make the unit functional. (By the way, a tiny amount of wire is supplied in the kit, but it is not enough for all the on-board jumpers let alone the off-board controls and connectors.)

Of course, adding the obligatory power-on LED would be nice too. Purists might wish to add a power switch as well, but there is a multi-pole switch (used to set the amplitude scale) that has an unused section and an undesignated switch position that can be used for that purpose. Your kit might also require an additional knob for one of the controls, as one of the controls that came with my unit was too large for any of the supplied knobs. Alternatively, you can drill out one of the supplied knobs to suit that control. It's modifications like those that require some experience in electronics to recognize and take advantage of—they are not mentioned in the instructions.

On the plus side, the components and the circuit board are all high quality. The PC board is single sided and has a color-coded silk-screened pattern—one color for component

Learn to troubleshoot and service today's computer systems as you build a powerful 386sx/20 MHz computer!

NEW!
386sx/20 MHz
computer, 40 meg
hard drive!

Train the NRI way—and learn to service all computers as you build your own powerful West Coast 386sx/20 MHz computer, now with 1 meg RAM, 40 meg IDE hard drive, and exciting new diagnostic hardware and software!

Jobs for computer service technicians will almost double in the next 10 years according to Department of Labor statistics, making computer service one of the top growth fields in the nation.

Now you can cash in on this exciting opportunity—either as a full-time industry technician or in a computer service business of your own—once you've mastered electronics and computers the NRI way.

Get real-world skills as you train with and keep a powerful 386sx-based computer system plus Microsoft® Works software

Only NRI gives you hands-on training with the finest example of state-of-the-art technology: the powerful new West Coast 386sx/20 MHz computer. As you assemble this fully IBM PC/AT-compatible machine, you actually see for yourself how each section of your computer works.

You assemble and test your computer's "intelligent" keyboard, install the power supply and 5¼" high-density floppy disk drive, then interface the high-resolution monitor.

Your hands-on training continues as you install a powerful 40 meg IDE hard drive—today's most-wanted computer peripheral—now included in your course to dramatically increase your computer's data storage capacity while giving you lightning-quick data access.

Plus you now work with today's most popular integrated software package, Microsoft Works, learning to use its word processing, spreadsheet, database, and communications utilities for your own personal and professional applications.

But that's not all!

NEW! Ultra-X diagnostic hardware and software for fast, accurate troubleshooting

Now you train with and keep the latest in diagnostic hardware and software: the extraordinary R.A.C.E.R. plug-in diagnostic card and QuickTech menu-driven software, both from Ultra-X. Using these state-of-the-art tools, you learn to quickly identify and service virtually any computer problem on XT, AT 80286/80386, and compatible machines.



Only NRI gives you such confidence-building, real-world experience. Only NRI gives you both the knowledge and the professional tools to succeed as today's in-demand computer service technician.

No experience needed...NRI builds it in

With NRI training, you learn at your own convenience in your own home. No classroom pressures, no night school, no need to quit your present job until you're ready to make your move.

NRI starts you with the basics of electronics and computers, building on that foundation step by step until you have the knowledge and skills you need for success.

And all throughout your training you've got the full support of your personal NRI instructor and the entire NRI technical staff, always ready to answer your questions and help you achieve your training goals.

Send for your FREE catalog today!

Send today for NRI's big, free catalog that describes every aspect of NRI's innovative computer training, as well as hands-on training in other growing high-tech career fields.

If the coupon is missing, write to: NRI Schools, McGraw-Hill Continuing Education Center, 4401 Connecticut Avenue, NW, Washington, DC 20008.

IBM and AT are registered trademarks of the IBM Corporation. R.A.C.E.R. and QuickTech are registered trademarks of Ultra-X, Inc. West Coast is a member of the Syntax Group.

SEND CARD TODAY FOR FREE NRI CATALOG

NRI Schools

McGraw-Hill Continuing Education Center
4401 Connecticut Avenue, NW, Washington, DC 20008




- | | |
|---|---|
| ☒ Check one FREE catalog only | ☐ Computer Programming |
| ☐ MICROCOMPUTER SERVICING | ☐ PC Software Engineering Using C |
| ☐ TV/Video/Audio Servicing | ☐ Desktop Publishing & Design |
| ☐ Telecommunications | ☐ Word Processing Home Business |
| ☐ Industrial Electronics & Robotics | ☐ Bookkeeping & Accounting |
| ☐ Security Electronics | ☐ Air Conditioning, Heating, & Refrigeration |
| ☐ Electronic Music Technology | ☐ Building Construction |
| ☐ Basic Electronics | ☐ Small Engine Repair |
| | ☐ Automotive Servicing |

☐ For career courses approved under GI Bill, check for details.

Name (please print) _____ Age _____

Address _____

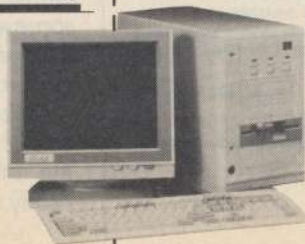City/State/Zip _____ Accredited Member, National Home Study Council _____ -18-112



SUPER 12 HOUR RECORDER

CALL TOLL FREE

Modified Panasonic Slimline.
6 hrs per side
120 TDK tape furnished.
AC/DC Operation.
Quality Playback.
Digital Counter.
Durable Lightweight Plastic.



\$119.00*

PHONE RECORDING ADAPTER

Starts & Stops Recorder
Automatically When
Hand Set is Used.
Solid State!



FCC Approved

\$28.50*

VOX VOICE ACTIVATED CONTROL

Solidstate Adjustable
Sensitivity. Voices &
Sounds Activate Recorder
Adjustable Sensitivity
Provisions for Remote
Mike



\$28.50*

* Add for ship. & handling. Phone Adapter & Vox
\$2.00 each, Recorders \$5.00 each. Colo. Res add
tax. Mail Order, VISA, M/C, COD's OK. Money Back
Guar. Qty Disc. available. Dealer inquiries invited.
Free data on other products.

AMC SALES INC. 193 Vaquero Dr.
Boulder, CO. 80303
Phones (303) 499-5405 1-800-926-2488
FAX (303) 494-4924
Mon-Fri 8-5 MTN. TIME

CIRCLE 6 ON FREE INFORMATION CARD

outlines and designations, another color for the foil traces. The screen work makes board-stuffing and troubleshooting (if any is needed) pretty easy.

The controls also bear special mention; they are very nice. The waveform and frequency switches are ganged pushbuttons, just like the kind you would find on a manufactured function generator, so they are particularly pleasing. If you do a good job machining and labeling your enclosure (which will not be covered in this article), the unit can be made to look store-bought. The first step, of course, is to build the unit itself, which I'll discuss now.

Construction. Building TSM kits is usually pretty easy, and, with a few exceptions, the Function-Generator Kit followed suit. Oddly, there are some helpful soldering hints, pin-outs, parts-identification tips, and a color-code chart printed onto the binder of the TSM kit case, apparently to assist beginners. That's odd because a beginner requiring *that* much support would probably find the kit frustrating

to build and calibrate because the instructions are poorly translated (I don't know what language they're translated from).

The literature that pertains to the kit itself is written in a "build it, adjust it, and use it" style—it doesn't contain any circuit theory. It does describe how to stuff a generic component into the board and advises that you install the components in the order that they appear in the parts list to avoid any difficulty. If you don't follow that sound advice you could end up covering the holes for some of the jumpers (referred to as "straps") with the rather large switch assemblies used by the unit.

However, this simple advice is made a little difficult to follow because of the Parts List. One problem with the Parts List was the use of commas in place of decimal points for some of the parts. For example, 6.8 was written 6,8 in some places. Also, many of the component values are specified as a range rather than a single value. For example, fixed resistor R10 could be any value from 180k to 200k. When faced with such ambiguous information an inexperienced builder might be tempted to match each part with its listing before stuffing anything into the board, blowing an evening just taking inventory. Of course, a more experienced hobbyist would solve this kind of puzzle by stuffing the *entire* board, prior to soldering. That way if you've placed a part incorrectly, it will become obvious before any soldering is done and can be easily corrected.

That bit of strategy behind us, there were a few more bridges (albeit, somewhat inconsequential to someone with experience) to cross while stuffing the board. For example, some of the holes for the non-polarized capacitors were spaced so close together that those components could not lay flat on the board. That increases their lead length, introducing additional stray inductance into the circuit. I suspect that that problem somewhat reduced the overall effectiveness of the completed function generator, as I'll point out later.

Once the on-board components were in place, I turned my attention to the off-board parts. Everything went pretty smoothly with the exception of

(Continued on page 88)

THIS SPACE CONTRIBUTED AS A PUBLIC SERVICE

A defense against cancer can be cooked up in your kitchen.

There is evidence that diet and cancer are related. Follow these modifications in your daily diet to reduce chances of getting cancer:

1. Eat more high-fiber foods such as fruits and vegetables and whole-grain cereals.
2. Include dark green and deep yellow fruits and vegetables rich in vitamins A and C.
3. Include cabbage, broccoli, brussels sprouts, kohlrabi and cauliflower.
4. Be moderate in consumption of salt-cured, smoked, and nitrite-cured foods.
5. Cut down on total fat intake from animal sources and fats and oils.
6. Avoid obesity.
7. Be moderate in consumption of alcoholic beverages.

No one faces cancer alone.

AMERICAN CANCER SOCIETY



\$429

AN ECONOMICAL KEYBOARD-CONTROLLED KEPCO BENCH POWER SUPPLY 75 WATTS

Choose from four Digital Power Supplies: 0-12.5V @ 6A, 0-24V @ 3A, 0-40V @ 2A or 0-125V @ 0.5A. Each one offers precise, repeatable voltage control with two current ranges. Fully protected for overvoltage or overcurrent.

Bonus: You can program the output from your PC's serial port (RS232 software included) and read back too!

The DPS is an affordable professional instrument and belongs on your bench.

Want more info? Ask for "DPS" brochure, 146-1768. Call-write-fax: Dept. MXS-77. Kepco Inc. 131-38 Sanford Avenue, Flushing, NY 11352 USA • Tel: (718) 461-7000 • Fax: (718) 767-1102. Use your VISA or MASTERCARD. Immediate delivery, 5-year warranty.



CIRCLE 10 ON FREE INFORMATION CARD

PRODUCT TEST REPORTS

By Len Feldman

Funai TVCP 9T 9-Inch TV/Video Cassette Player

How many times have you been away from home and wished you could rent and watch a videotape on a small, high quality TV set that's light enough to carry with you on a trip? Better still, wouldn't it be nice if that same TV set had a built-in video-cassette player, so you wouldn't have to both- er hooking up a separate VCR when you wanted to watch a tape? Well, Funai Corporation (100 North Street, Teterboro, NJ 07608) has come up with just such a combination unit.

CIRCLE 20 ON FREE INFORMATION CARD



The Funai TVCP 9T combination TV/video-cassette player.

The TVCP 9T features a 2-rotary-head playback system. All three speeds (SP, LP, and EP) can be accommodated. If you insert a tape, power is turned on automatically and, if the safety tab on the tape has been removed, playback begins. At the end of the tape, the tape rewinds automatically,

is ejected, and, unless "repeat playback" has been selected, the unit turns itself off.

The feature most likely to attract travelers to this unit is its two-way power capability, which lets you power the unit with standard AC voltage or from your car battery using the supplied car-battery cord. Since this TV set is likely to be moved from place to place, it is equipped with a "degaussing button," which corrects color by counter- ing the magnetic influence caused by nearby appli- ances. The remote control supplied with the TVCP 9T lets you operate all the tape-transport controls, change TV channels, and adjust the volume level from your viewing chair. An on-screen display of se- lected channels and other operating functions makes control adjustment fool- proof. High-speed picture search in either direction is possible when watching a tape, as is "freeze frame" or still-picture viewing. The fre- quency-synthesized TV tuner incorporated in this product can be tuned to any of 155 TV or cable channels, and random ac- cess to any numbered channel is possible, as is programming of the tuner to receive only those chan- nels available in your area.

CONTROLS

Pushbuttons beyond the right side of the TV screen include the power switch and channel and volume

up/down buttons. The vid- eo-cassette insertion slot is located below the screen, with a stop/eject button lo- cated to the left and below the tape slot. A swing-down door discloses controls as- sociated with the video player as well as less-often- used controls associated with the TV set itself. With the door flap closed, play and tape-in indicator lights are visible on its front surface. When opened, access is gained to the rewind, play, fast forward and still buttons of the player, as well as to controls that adjust tracking, brightness, contrast, color, and tint. Also found here are the auto-repeat selec- tor and a switch that selects either broadcast or cable TV frequencies for the TV tuner.

For private listening, a headphone jack is found on the left side panel of the cabinet. The rear panel of this combination unit houses the previously men- tioned degaussing button, connection points for either the AC-line cord and the car-battery DC-supply cord, audio and video input and output jacks, and a con- nector for a 75-ohm antenna transmission line.

TEST RESULTS

Advanced Product Eval- uation Labs (APEL) measured the performance of this unit both in terms of its capabilities as a TV monitor/receiver, and in terms of its operation as a video-cassette player. In the latter case, all measure-

Earn Your B.S. Degree in ELECTRONICS or COMPUTERS



By Studying at Home

Grantham College of Engineering, now in our 42nd year, is highly experienced in "distance education"—teaching by correspondence—through printed materials, computer materials, fax, and phone.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand but complete and thorough lesson materials, with additional help from our instructors.

Our Computer B.S. Degree Program includes courses in BASIC, PASCAL and C languages—as well as Assembly Language, MS DOS, CADD, Robotics, and much more.

Our Electronics B.S. Degree Program includes courses in Solid-State Circuit Analysis and Design, Control Systems, Analog/Digital Communications, Microwave Engr, and much more.

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Write or phone for our free catalog. Toll free, 1-800-955-2527, or see mailing address below.

Accredited by
the Accrediting Commission of the
National Home Study Council

GRANTHAM
College of Engineering
Grantham College Road
Slidell, LA 70460


ments were made at the SP tape speed and, since this unit is a player only (as opposed to the usual VCR player/recorder), APEL used a prerecorded test tape.

The maximum usable luminance for the TV screen measured 63 foot-lamberts, which, while not the brightest for a TV set of this tube size, was bright enough to view pictures in normal room lighting. Horizontal resolution measured 280 lines. (Maximum resolution possible for broadcast TV is about 330 lines.) The transient response was very good, as was color quality. Black level retention was a somewhat below average 70%, while overscan (the amount of picture deliberately extended beyond the screen width) was only 4%. TV-tuner sensitivity was very good, with reception at fringe-area signal strengths remaining quite acceptable. As for the audio section of the TV receiver, audio output via the separate output jacks was 0.43 volts at 0.04% distortion, with distortion decreasing to an even lower 0.03% when audio levels were backed down to -10 dB below reference level. Audio signal-to-noise ratio measured 68 dB, while the audio frequency response

extended from 26 Hz to 13 kHz.


APEL used a prerecorded test tape made on Sony Pro-X tape to measure the performance of the tape player section of this TV/player combination. Using a multiburst test signal, frequency response was down by 6.64 dB at 2.0 MHz, or about average for a standard VHS format VCR operating at its SP speed. Red field chroma (color) signal-to-noise ratio measured 43.2 dB for AM noise and 34.9 dB for phase-modulation (PM) noise. The luminance (brightness) signal-to-noise ratio ranged from 43.4 dB to 43.8 dB, depending upon the reference luminance level at which APEL made the measurements. Color accuracy as indicated by a vectorscope, was very good.

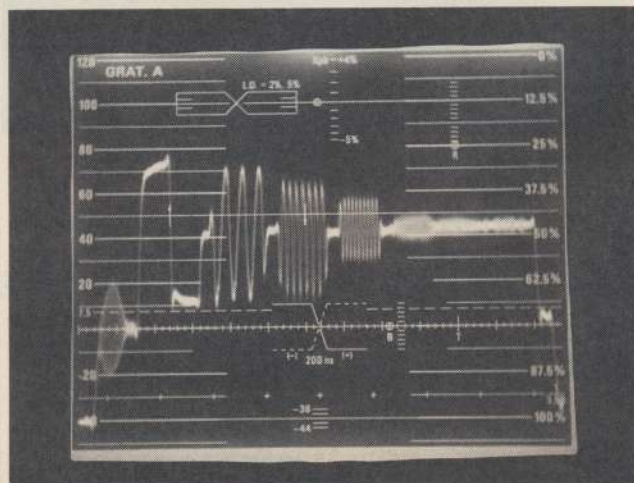Turning to the audio section of the tape player, APEL measured an audio output of 0.36 volts at a harmonic distortion level of 1.25%—again, about what one would expect from a VHS-format machine. Frequency response during playback of the test tape extended from 150 Hz to 13.4 kHz, while distortion at a -10 dB playback level was only 0.59%. Fast forward time for a 2-hour (T-120) tape was 3



Using a multiburst test signal, response was down 6.64 dB at 2 MHz. That is about average for a VHS machine.

The Amazing Maze.

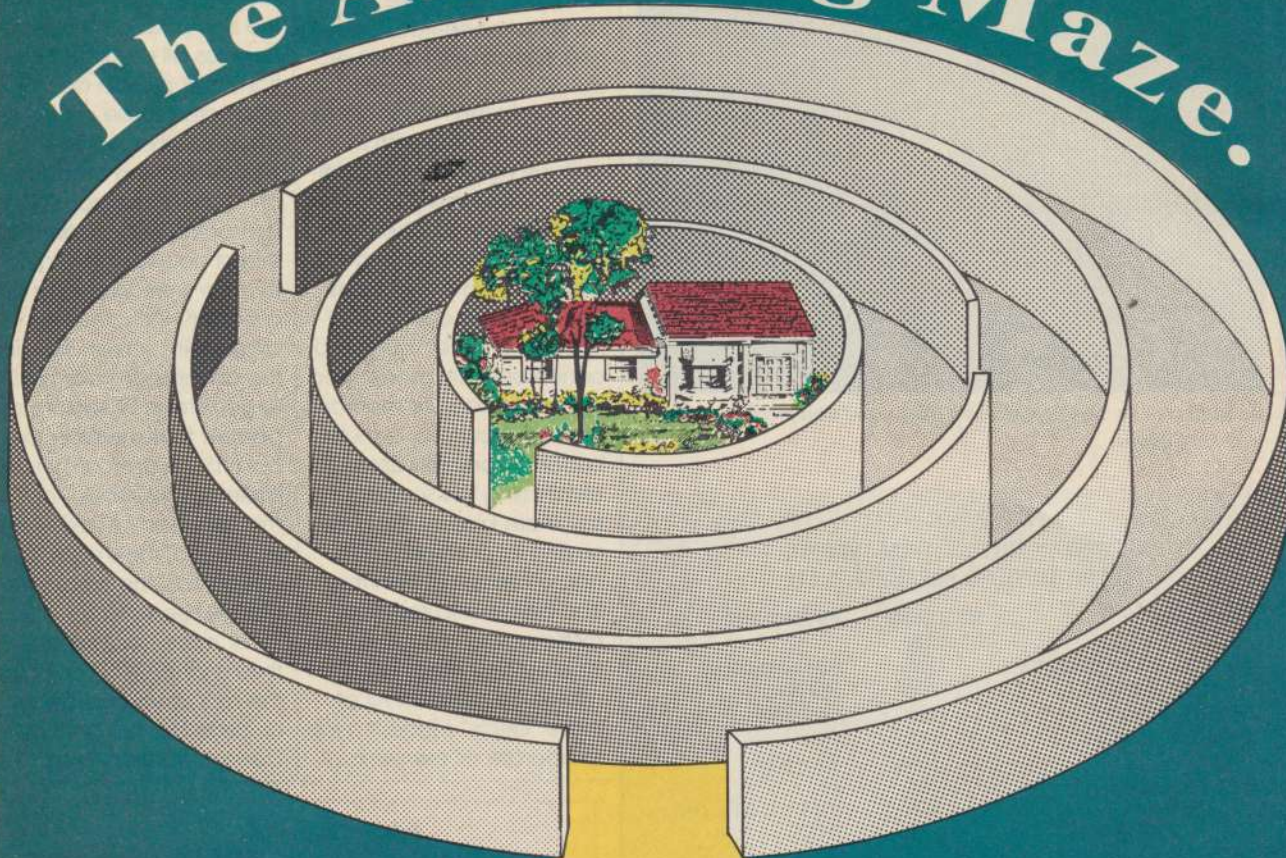

**YOUR HOME . . .
the television series,
will help guide you through it.**

For most families . . . our homes are the biggest purchase we'll ever make. From time to time we've all thought about making changes to our homes. By watching the YOUR HOME television series, you can catch all of the latest ideas and trends designed to get you through the maze of products that will enhance the beauty, functionality, and quality of the time that you spend at home. Whether you're building a dream kitchen or attempting to create the home theater experience, from the simple to the exotic, YOUR HOME has a wealth of great ideas. It's like going to the world's biggest home and garden store each and every week.

Tune into upcoming shows to check out the best and brightest in home products and services:

**MCINTOSH LABORATORY
INC.**

The ultimate in home audio gear
for the true audiophile.

ROBERT H. PETERSON CO.
Decorative Gas Fireplace Logs.

SONY CORP.

STR-Audio Video Receiver with
Dolby Pro Logic.

TOSHIBA

Large Screen Television for the
true home theater experience.

UNELKO CORP.

Invisible Shield, Water and soil
repellent and protectorant.

Check your local cable listing for the time and channel number in your area.

A presentation of

WJMK • 2424 N. Federal Highway • Boca Raton, FL 33431 • (407) 367-0703

BAD VIDEOTAPES

BY LEN FELDMAN

Theoretically, any videotape bearing the VHS logo must have passed certain stringent tests developed by JVC, the inventors of the VHS video-recording format. In fact, JVC conducts ongoing tests to ensure that its tape manufacturing licensees maintain a proper level of quality in their video cassette tapes. But what happens if some maverick overseas manufacturers decide to bypass the licensing procedure and simply produce and market videotape of inferior quality and illegally apply the VHS logo to such products? Even worse, what happens if reputable firms buy such tape from unqualified manufacturers and then, in all innocence, have it packaged under their own familiar brand names? What's an unwary consumer to do?

It recently came to our attention that several tapes bearing unfamiliar brand names, all of them manufactured in mainland China, were competing in the marketplace against more familiar, well established tape brands. Further investigations disclosed that of the dozen questionable brands found, nearly half were not even licensed by JVC to carry the VHS logo. The following brands bear the trademark illegally: Haili, Mustang, Supra, Treasury, and Windsor. While the remaining seven brands are all licensed by JVC, the owners of those brand names do not, in fact, actually manufacture videotape. That means they are buying their tape from other manufacturers, some of whom may be the very same manufacturers who are using the VHS logo illegally and who, as our exhaustive tests show, are incapable of making videotape of

These videotapes may bill themselves as "high grade," but their performance is decidedly low grade—and some could actually damage your VCR!

acceptable quality. By way of comparison, we also measured the performance of three well-known, high-quality standard VHS tapes: TDK High Standard, Sony ES, and Scotch EG. It's important to note that we purposely selected these companies' standard

(and lowest priced) videotapes whereas nearly all of the "Made in China" tapes are billing themselves as "High Grade" (hence higher priced) tapes!

A brief summary of our findings with respect to each of the dozen "Made in China" tapes can be found later on in this article. A more detailed analysis can be found by consulting Table 1, which shows the test results for three samples of each tape. Let's now examine how those tests were performed, and what the numbers mean.

Test Procedures and Lab Measurements. The videotape testing was conducted by APEL (the Advanced Product Evaluation Laboratories). APEL tape tests were performed with three samples of each type of tape. The results shown in Table 1 represent the average performance of all three tapes. Prior to testing, all of the tapes were put into an environmentally controlled room at a temperature of 70°F and a relative humidity of 60% for at least 48 hours. These conditions were maintained during the tests as well, since many of the measurements are temperature and humidity dependent. Before actually measuring each tape, each cassette was bulk erased and "exercised" to prevent any settling of the tape. Each deck was thoroughly cleaned after each tape sample was tested to reduce any contamination between the tape samples.

How We Tested the Tapes. All samples were tested for video performance as well as for audio performance. Audio tests were confined to conventional



TABLE 1
VIDEO MEASUREMENTS

Tape Type	S/N Ratios		Dropouts @ -18 dB						Frequency Response (dB)					Signal Loss (dB)	
	Luma	Chroma		Beg		Center		End		0.50 MHz	1.25 MHz	2.00 MHz	3.00 MHz		3.58 MHz
		AM	PM	5μs	15μs	5μs	15μs	5μs	15μs						
Laser HQ Plus	48.1	44.1	39.7	127	79	37	21	86	57	0.0	1.3	-0.2	-3.7	-2.8	0.1
Certron High Grade	47.9	43.1	39.1	208	130	83	52	521	334	0.0	1.5	0.0	-3.2	-2.5	0.6
Tozai Prem. Grade	46.8	38.5	35.8	999	837	607	319	852	446	0.0	1.2	-0.5	-3.4	-2.6	0.1
Recoton High Grade	48.5	43.9	39.7	93	54	61	30	159	103	0.0	1.4	0.0	-3.2	-2.5	0.1
Treasury Prem. Grade	46.8	42.3	38.1	166	86	174	106	185	118	0.0	1.5	0.5	-2.7	-1.9	0.0
Windsor Super H.G.	46.6	38.6	36.9	309	190	134	81	941	547	0.0	1.1	-0.6	-3.7	-3.0	0.2
Silver Shadow H.G.	47.6	42.7	39.0	999	385	72	48	105	73	0.0	1.4	0.0	-3.2	-2.5	0.3
Gemini High Grade	46.8	41.6	38.3	106	69	165	115	384	248	0.0	1.3	-0.5	-3.0	-2.2	0.1
Haili	47.6	38.1	34.7	988	563	999	576	999	658	0.0	1.6	0.8	-1.5	-0.7	0.2
Universal Super HG	47.2	40.6	38.0	192	80	155	81	246	150	0.0	1.5	0.0	-2.5	-1.8	0.6
Supra	39.7	30.6	27.5	999	565	826	392	999	821	0.0	0.3	-3.9	-6.8	-6.4	0.0
Mustang Super HG	47.5	42.4	38.8	583	409	75	43	999	476	0.0	1.2	-0.3	-3.5	-3.1	0.3
Reference Tapes (for comparison purposes)															
TDK High Standard	48.4	43.1	39.3	21	13	17	9	23	13	0.0	1.3	-0.3	-3.6	-2.8	0.2
Sony ES	47.9	42.8	39.2	28	15	15	6	23	12	0.0	1.3	-0.5	-3.9	-3.2	0.2
Scotch EG	49.4	43.9	39.7	26	16	11	3	10	3	0.0	1.3	0.0	-3.3	-2.9	0.6

AUDIO MEASUREMENTS

Tape Type	Output @3% THD (volts)	THD -10dB (%)	S/N Ratio A-weighted (dB)	Uniformity (dB)		Bandwidth (-3dB)	
				Left	Right	Low, Hz	High, kHz
Laser HQ Plus	0.77	0.15	50.6	0.2	0.7	42.5	11.2
Certron High Grade	0.71	0.17	49.4	0.3	0.6	43.2	11.9
Tozai Prem. Grade	0.80	0.15	51.6	0.6	1.1	43.0	11.0
Recoton High Grade	0.79	0.15	51.2	0.2	0.4	43.1	11.7
Treasury Prem. Grade	0.76	0.15	50.4	0.3	0.4	43.8	11.0
Windsor Super HG	0.71	0.17	48.6	0.4	0.6	43.7	11.9
Silver Shadow HG	0.69	0.16	49.7	0.3	0.6	43.0	11.6
Gemini High Grade	0.81	0.15	51.1	0.7	0.9	43.0	10.8
Haili	0.99	0.16	51.8	0.9	1.2	41.7	9.5
Universal Super HG	0.80	0.18	52.0	0.7	1.4	41.8	9.5
Supra	0.59	0.24	47.1	1.1	1.1	42.4	12.2
Mustang Super HG	0.79	0.18	50.5	0.3	0.4	43.1	11.5
Reference Tapes (for comparison purposes)							
TDK High Standard	0.75	0.15	51.2	0.2	0.4	42.5	10.9
Sony ES	0.82	0.17	51.7	0.2	0.2	43.1	10.7
Scotch EG	0.93	0.15	53.6	0.2	0.2	43.1	10.9

or edge-track recording and playback because the VHS Hi-Fi recording mode is not particularly dependent upon tape quality. Five major video-performance characteristics were measured: luminance (brightness) signal-to-noise ratio, chroma (color) signal-to-noise ratio, dropouts, video frequency response, and signal loss after repeated playings.

Video S/N Ratios. Luminance, or brightness signal-to-noise ratios, were measured with a reference recorded gray level of 50 IRE units. Each tape was then played back and the un-weighted noise was measured over a bandwidth extending from 10 kHz to 4.2 MHz, without the chrominance (color) trap at 3.58 MHz.

Chroma signal-to-noise ratio tests were made using a red test-color field corresponding to the colors of a 75% amplitude, color-bar pattern. Both amplitude modulation (AM) and phase modulation (PM) chroma noise were measured over a bandwidth extending from 100 Hz to 500 kHz.

Video Frequency Response. Video frequency response is directly related to picture detail and resolution. The more uniform the response, and the higher the frequency to which it extends, the sharper and more detailed the picture you will be able to record and playback, assuming that your VCR's own frequency response is as good as or better than that of the tape you use.

To measure that important characteristic, APEL used a multi-burst test signal consisting of five bursts at discrete frequencies of 0.5 MHz, 1.25 MHz, 2.0 MHz, 3.0 MHz, and 3.58 MHz. The color-burst signal normally associated with that group of test signals was removed in order to prevent activating the color circuitry of the VCR. That circuitry, when activated in most VCR's, removes all frequencies above 3.58 MHz.

Dropouts. Perhaps the most important characteristic relating to videotape performance is the dropout count in a specified time period. Dropouts cause brief bursts of noise on your TV screen when you play back your tapes. Dropouts of very short du-

ration can often be mistaken for noise, but in fact they represent imperfections in the tape where the video signal actually "drops out" or is substantially lowered in amplitude. Longer dropouts of 15 microseconds or more show up as highly visible and annoying horizontal streaks in a picture being played back. Tape dropouts were measured at three different locations on each tape. Generally, a higher dropout count can be expected near the beginning and end of a tape, while the lowest dropout count should occur near the center.

In our tests, a gray field of 50 IRE units was recorded at each section of the tape for one minute. The tape was played back and any signal reduction of 20 dB or more was counted as a dropout. Duration of the dropout was also measured, and dropouts were divided into short (5 microseconds) and long (15 microseconds or more) categories.

Signal Loss. Some tapes begin to lose some of their signal with repeated playings. Obviously, if you plan to record an event or a program that you'd like to play over and over again and preserve for a long time, you will want to choose a tape that exhibits a low signal loss with repeated playings. In our measurements, each recorded cassette was played back ten times and the percentage of RF signal loss was measured.

Audio Bandwidth. One of the most important qualities of any audio recording is uniform frequency response or audio bandwidth. Because of the very narrow track and the slow longitudinal speed of videotape, its audio frequency response cannot be expected to be as good as that of even a low-cost audio cassette used in a relatively low-cost audio cassette deck. Nevertheless, some of the tapes tested exhibited somewhat better audio frequency response than did others. Dropouts can affect audio performance just as they can affect video performance. Since the audio track is positioned near the edge of the tape, audio dropouts can often be more serious than video dropouts if the magnetic coating is not uniform out to the very edge of the tape. In our tests of audio performance, a nominal "0-dB" reference level was deter-



Fig. 1. Tapes carrying the Supra brand were the noisiest tested, with video dropouts exceeding 1000-per-minute.

mined by recording a 1-kHz signal that, when played back, produced 3% total harmonic distortion. The audio signal level available under those conditions was noted and it was against that reference level that other measurements were made.

Total Harmonic Distortion. Total harmonic distortion, or THD, was measured using a 1-kHz signal at a level 10 dB below the reference level. The lower the percentage, the better the tape in this regard. All of the tapes measured well below 0.5% under these test conditions, but there was still a fair degree of variation between them, with Supra offering the poorest readings (0.24%), and Laser HQ, Tozai Premium Grade, Recoton High Grade, Treasury Premium Grade, and Gemini High Grade offering the lowest distortion (0.15%).

Audio Signal-to-Noise Ratio. Audio S/N was measured by first making a recording with the inputs to the VCR shorted. The tape is then played back through an A-weighting network, and the level of noise measured is expressed as a number of dB lower than the reference level established earlier. The higher the dB number, the better the signal-to-noise ratio. All of the

tapes except the Supra samples did quite well; better in fact than the capability of most VHS VCR's. In other words, with any of these tapes, the audio signal-to-noise ratio is likely to be a function of your VCR or camcorder rather than of the tape itself.

Uniformity. Audio uniformity measures the tape's ability to reproduce a steady-state audio tone (of 1 kHz) recorded at a constant amplitude for a period of three minutes, on both stereo channels. Variations in output level and even intermittent muting can occur for tapes that exhibit severe dropout characteristics and this is reflected in the test results. The poorest performer in this regard was the Supra tape. That should come as no surprise when you examine the high dropout count of these particular samples.

With that groundwork now out of the way, let's turn our attention to the tapes themselves and look at the highlights of our test results.

Laser HQ Plus. While the long term (15 μ s or more) dropout count at the center of these tapes was the lowest of the dozen tapes tested, it was still many times greater than that of any of the reference tapes tested for comparison. Furthermore, dropouts at the

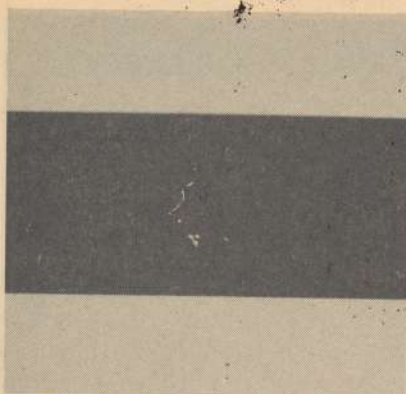


Fig. 2. Two of the three samples of Mustang Super High Grade tape had seriously damaged sections of tape.

beginning and end of the tapes were far beyond acceptable levels. Other video and audio characteristics were, on the whole, acceptable and comparable to those of the three reference tapes. This brand, as well as Certron, Gemini, and Recoton, previously used tape purchased in Hong Kong and Taiwan. All four brands appear to be using mainland China tapes in selected grades only.

Certron High Grade. Here is a tape brand that, in previous tests, yielded far more acceptable dropout numbers. This is typical of a tape distributor who is probably purchasing raw tape from a variety of sources, some better than others. In the case of the current "Made In China" batch tested by APEL, dropout counts were far beyond acceptable limits, both at the ends of the tape and in its center. Were it not for this important failing, other performance characteristics might have been deemed acceptable.

Tozai Premium Grade. Here's a case where APEL simply "stopped counting" short-term dropouts when the count reached over 1000! In addition, this tape exhibited uniformity problems during audio performance measurements.

The investigation, testing and research referred to in this article was conducted solely by the author. The test results, opinions and conclusions are those solely of the author and do not reflect those of the publisher. The publisher makes no representations as to the completeness or accuracy of the investigation, testing, research, test results, opinions or conclusions expressed by the author herein and disclaims any and all responsibility with respect thereto.

Recoton High Grade. As was true of the Laser HQ Plus samples, Recoton seems to control quality a bit better than the less familiar brands tested by APEL. Nevertheless, dropout counts for this so-called "High Grade" tape, even at its center, were higher than that of the low-cost reference tapes used for comparison purposes.

Treasury Premium Grade. This brand of tape is distributed by Thrift Drug Stores. While not apparent from the "averaged" figures shown in our charts, there was tremendous inconsistency among the three samples tested. For example, one sample actually exhibited acceptable long-term dropout counts at the center of the tape (35), while the poorest sample showed 221 dropouts for the same section of tape. There was considerable variation among the three samples in other audio and video performance characteristics as well.

Windsor Super High Grade. This tape, like so many of the other "Made In China" samples, exhibited very high video dropouts, especially at the beginning and ends of the tape. Video signal-to-noise ratios were also below average compared with the standard, low-cost, name-brand tapes measured for comparison purposes.

Silver Shadow High Grade. This brand is distributed exclusively by Woolworth. Two of the three samples tested had extremely high video dropouts and poor uniformity. While the third sample had lower dropout counts at the ends of the tape, but higher center-tape dropouts. In short, there was little consistency in the quality of these tapes from one sample to the next.

Gemini High Grade. Like the Certron and Recoton samples discussed above, previously measured samples of this tape brand made in Hong Kong or Taiwan, exhibited far better performance than the currently measured "Made in China" samples. The current samples were high in dropout counts even at the center of the tape, although other measured parameters compared favorably with the reference standard-grade tapes measured by APEL for comparison purposes.

Haili. These samples were among the worst of all the "Made In China" brands tested by APEL. Dropouts were extremely high over the entire length of all three samples tested. In addition, there were uniformity problems during testing of audio performance. In short, this tape exhibited not a single redeeming feature!

Universal Super High Grade. According to our investigations, this brand of "Made In China" tape has probably been on the market longer than any of the other brands tested. Its most serious problem was poor uniformity, but the samples also exhibited high dropout counts and poor audio bandwidth, as well as higher than average signal loss with repeated playings.

Supra. This brand is sold at Pathmark Supermarkets. APEL had to purchase 11 samples to try to find three that could be tested without damaging the VCR test bed. Video dropouts measured in excess of 1000-per-minute. (See Fig. 1.) These tapes proved to be the noisiest of any tested, both in terms of video and audio signal-to-noise ratios.

Mustang Super High Grade. Two of the three samples tested had seriously damaged sections of tape. (See Fig. 2.) Furthermore, one sample's tape broke while playing in the VCR and had to be repaired before it could be tested. Another sample's damaged tape section had to be removed before testing could be completed.

The Bottom Line. It should be abundantly clear from these test results that Mainland China has not yet mastered the technology required to produce high-quality (or even acceptable quality) videotape cassettes. Here we have a classic case of "buyer beware." Often, these tapes are sold alongside more established and recognizable, quality brands. By assigning "high grade" labels to them and pricing them at levels normally charged for "standard" grades made by reputable, recognized domestic, Japanese, Hong Kong, and Taiwanese tape makers, distributors of these off-brand tapes hope to appeal to uninformed buyers. Don't fall into the trap!

CHOOSING and USING



AUDIO and VIDEO TAPE

Select the best tape for any recording job, and ensure that the life of that recording does not end too soon.

Audio and videotape is so common nowadays that nearly everyone uses it on a regular basis. It's unfortunate though, that so many people using tapes don't know how to properly care for them—because tapes can have a very short lifespan if they're not taken care of. There's a lot you should know about tapes that will greatly lengthen their usable life. And if having your tapes in good working order for years to come is important to you, then there's also a lot you should know about what to look for when buying them in the first place.

Magnetic tape is made by coating a thin yet strong "ribbon," or tape, with a layer of magnetic-oxide particles. To record a signal, as the tape passes over the record head in a tape deck, the head arranges the polarity of the magnetic particles in a way that represents the signal. During subsequent playback of the tape, the magnetic particles recreate the original signal

BY MARC SPIWAK

as the tape passes over the playback head.

Contrary to what many people believe, a recording on any kind of magnetic tape, digital or otherwise, is never absolutely permanent—especially if the recording will be repeatedly played back. Even though audio and video cassettes have tabs that can be removed to prevent accidental erasure, the coating of magnetic particles on the tape tends to deteriorate over time. Furthermore, playback actually wears away at the tape surface as the tape rubs up against the heads. (That's one reason why CD's are praised as being "indestructible." Nothing but a laser beam physically comes in contact with the recorded area of the disc to wear it out.)

We don't want you to get the impression that the recordings you make today will be gone in just a few

years. Tapes stored in a sealed vault kept at precise temperature and humidity levels could probably be saved for your great grandchildren. The problem is that few people are going to go through all that trouble to preserve their tapes. Even so, there have been cases where master tapes have survived for many years, only to have the magnetic coating disintegrate as it is played back. Don't worry, though—with proper care, good quality tapes should deliver many years of entertainment.

Videotape Formats. Before we talk about how to care for videotape, let's first discuss what you should look for when buying videotapes. To begin with, there are many different videotape formats, with different kinds of cassettes.

As far as most consumers are concerned, VHS is today's king of the hill. Most people use VHS for their home-video recording and it's also by far the



VHS cassettes are by far the most common videotapes in use today. Many different grades of this tape are available.



VHS-C cassettes are much smaller than their VHS counterparts, yet they can be played in a standard VHS deck using an adapter that resembles a full-sized VHS cassette. Camcorders that use VHS-C cassettes can be made smaller and lighter, but the standard length of a VHS-C tape is only 20 minutes.



8mm cassettes are even smaller than VHS-C, and they can record two hours of video.

most rented format. Unfortunately, even though VHS is the most common format, it has a poor horizontal resolution—about 240 lines. The horizontal resolution translates into the maximum number of pixels, or individual dots that can be produced (or in this case recorded) on one horizontal line of video; the more dots, the sharper the picture.

Super VHS, or SVHS, has higher horizontal resolution—over 400 lines—but it must be viewed on a monitor with an "S" input to achieve the full benefits of the format. SVHS is not very popular at all. That's probably because you can never record a cleaner picture than

what you receive, and for the signal quality most people receive from cable or broadcast TV. VHS is more than adequate. SVHS decks can record in both VHS and SVHS modes, depending on what type of tape is used. VHS and SVHS cassettes look the same, but special magnetic formulations are used in SVHS tapes to achieve higher frequency recording. A slight physical difference between the two cassettes prevents an SVHS deck from recording in the SVHS mode if a VHS tape is loaded. Obviously an SVHS recording can be played back only on an SVHS deck.

Another variation of VHS is VHS-C (or

VHS-Compact), which is a format that was developed for use in camcorders. Basically, a VHS-C cassette is a miniature version of a VHS cassette, and it contains the same kind of tape, but in a length of only 20 minutes. That smaller cassette size allows manufacturers to downsize VHS-type camcorders considerably. The VHS-C cassettes can be played back in a conventional VHS deck using an adapter that resembles a full-sized VHS cassette. There's also an SVHS-C format, which is Super VHS tape in a C-sized cassette.

The newest videotape format is 8mm. Although its resolution is about the same as VHS, 8mm uses a much narrower tape than any of the VHS formats to provide two full hours of recording on a small cassette. The format was developed for use in very compact camcorders. Full-sized 8mm decks are also available for home use. They eliminate the wear and tear of playing back all of your 8mm tapes on your expensive 8mm camcorder. Unfortunately, the lack of readily available pre-recorded material has limited the commercial success of 8mm home decks.

A variation of 8mm, called "Hi8," has the same horizontal resolution as SVHS. But again, to see the improved resolution, playback requires an "S" input on the TV monitor.

While Beta is still used in some professional applications, and by some videophiles, the format has pretty much died as far as typical consumers are concerned. Very few places (if any) still rent Beta tapes, and blank tapes are becoming harder to find.

Selecting Videotape. All of the formats we've discussed have a special logo which should be printed on the box. The logo indicates that the tape meets certain specifications, regardless of who made it, and you shouldn't purchase a tape that does not bear the proper logo. Figure 1 shows what the logos look like.

Just as important as the logo is that you buy a good name brand tape that you've had good experiences with. Stay away from cheap no-name tapes that not only don't last very long, but may also damage your deck. A low-grade videotape can have a poor, flaky magnetic coating that will quickly wear away during recording



If you want to record music, these cassettes are the way to go. Perhaps the new DCC's will finally make these obsolete.



Fig. 1. These logos should be printed on the box of each format. Do not purchase a tape that does not bear the proper logo.

and playback—taking audio and video along with it. As the coating wears out, it'll leave heavy oxide deposits on the heads and other internal parts of the VCR. That can shorten the life of your VCR.

Evidence of a poor-quality tape, or one that's very worn out, is the presence of numerous dropouts, or white streaks running horizontally through the picture, and excessive video noise in general. Even if you have good luck with one no-name tape, another tape from the same manufacturer may turn out to be horrible—there's often very little quality control. And the cost advantage of no-name tapes can be as little as a dollar. Is it really worth it to save a dollar in exchange for a short-lived movie and extra wear and tear on your VCR? (For more on that topic, see "Bad Videotapes" elsewhere in this issue.)

For many of the formats we've mentioned, no matter who the manufacturer is, you'll find many different grades of tape; standard, high-standard, high-grade, super high-grade, professional, and so on. The manufacturer will list the recommended uses for the particular grade of tape. Standard-grade tape from a well-known

manufacturer is usually more than adequate for everyday use—and certainly much better than any no-name tape. Despite any differences in formulation, there's often very little observable difference between standard and high-grade tape from the same manufacturer.

And note that you do not need any special "Hi-Fi" tape to record Hi-Fi. An all-time favorite movie or irreplaceable camcorder event might be worth investing in Hi-Fi-grade tape, but any decent-quality VHS tape will do fine most of the time. You do, of course, need a Hi-Fi VCR to record Hi-Fi.

General Practices. There are a few procedures and practices that should be followed to consistently make better recordings. For example, one thing you should consider when recording is the tape speed. Most VCR's can record at two speeds, and many can record at three. That allows you to record 2, 4, or 6 hours of video on a standard T-120 tape. The tradeoff is that the picture and audio quality decrease as you slow down the tape—the picture more so than the audio. Prized recordings should always be done at the fastest speed.

Once you've made some prized videotapes, you'll certainly want to be able to get the most out of them. That can only be done if you maintain your VCR according to the manufacturer's recommendations. Cleaning the heads is mostly what's involved, and there are many different ways to do that. (A snowy picture is usually evidence of dirty heads—or worn out heads.) It's always best to follow the manufacturer's recommendations as to which head-cleaning method you should use. Because a VCR is a very complex device, those less technically inclined should leave maintenance to a professional. Even those who are technically inclined should consult and understand one of the many books and articles on the topic before attempting a VCR maintenance task such as head cleaning.

Many problems can arise when playing videotapes. Sometimes a problem is due to the VCR, but it can also be due to the video cassette. If you encounter a problem with one tape, recreate the conditions using a different tape and see if the problem goes away. If so, the problem is more than likely due to the tape and not the VCR.

Damaged tape—scratched, creased, etc.—can cause a picture to be unstable and contain various flaws. A stretched-out videotape can cause the top of the picture to wave back and forth. If a tape keeps stopping when you play, fast forward, or record, it could be due to binding within the cassette. If a VCR loads in a tape and then shuts down, it could be that the tape is wound too loosely. Should you find that you can't easily get a cassette to eject from the VCR, leave it in and have it properly serviced. Forcefully removing it can damage the VCR and/or the tape. Also, if a cassette seems to be making a lot of noise, it's best not to use it anymore. As a general rule of thumb, if your VCR has trouble with only one or two tapes, then the trouble is probably due to those tapes. If your VCR has trouble with most or all tapes, then the VCR is probably in need of maintenance or repair.

Audio-Tape Types. The audio cassette has been extremely popular for a long time. Four kinds of tape are available: all in the same type of cas-

sette. However, most cassette decks can't record and play all four types of tape. Check your owner's manual to determine which types of tape your deck can use.

The first kind of tape is called "Type I," which is standard, or normal-bias tape. It's coated with a layer of ferric oxide, and can be used in any tape deck. Type II is high-bias tape, with a chromium dioxide magnetic layer. It's also referred to as CrO₂, or chrome tape. A deck must have a high-bias setting to use chrome tape. A seldom-seen type III, or ferrichrome tape (FeCr), contains a mixture of both ferric oxide and chromium dioxide. The most advanced tape today, type IV, uses a layer of metal particles. However, to use it, the deck must have metal capability for recording and/or playback.

Concerning no-name audio cassettes: as with video tapes, our advice is don't buy them. And if you stick to a good brand, normal-bias (type I) tape is fine for most applications. As you go from type I to type IV, the signal-to-noise ratio, frequency response, and price increase. So select blank audio tapes according to your taste and budget. Today's best audio cassettes, using various noise-reduction schemes, and a good-quality deck, can capture nearly the full frequency response of a CD, with noise levels that are hardly noticeable.

Two last audio-tape formats worth mentioning are DAT, or Digital Audio Tape, and the soon-to-come DCC's, or Digital Compact Cassettes. DAT's have been around for quite some time, but were plagued with political problems in this country due to their ability to make near-perfect copies of CD's. They have not become popular, though, perhaps due to their high price and limited demand. The newer DCC decks will be able to make a digital recordings on DCC's and be able to play your old-style cassettes as well. Only time will tell if this new format will catch on.

Helpful Hints. Once you've captured all the subtleties of your favorite music on cassette, you will no doubt want to hear all those subtleties every time you play the tape. As with videotape, to do that you must keep your tape deck clean according to the manufacturer's recommendations. All

parts in the tape path, including the heads, will develop oxide and dirt deposits on them over time. Oxide on the playback head will degrade the quality of the playback. If the record head is dirty, you'll be producing poor recordings to begin with. Dirt on the mechanical parts of the deck in the tape path can cause the deck to eat tapes, which is obviously not a good thing. Try to stay away from cassettes that are supposed to clean your deck simply by playing them—many of these "tapes" are very abrasive and do more harm than good. It's best to use plain old alcohol and cotton swabs (do not use rubbing alcohol that may contain additives that will leave a residue—use pure isopropyl alcohol only). Sometimes the manufacturer will also recommend that the heads be demagnetized. If so, a head demagnetizer is probably available where you purchased the deck.

If your deck is clean and in proper working order, and you still have trouble with a particular cassette, it's probably the cassette itself. A damaged cassette should obviously not be used. Also, a cassette that is very noisy when it operates (squeaky, for example) is a sure sign of trouble, and you should stop using it. If your deck keeps stopping while playing a particular tape, the tape is probably wound unevenly inside the cassette, causing it to stick. Sometimes you can remedy the problem by fast-forwarding and rewinding the tape a couple of times. If that doesn't help, you should discard the tape. Again, the same rule of thumb applies here: if your tape deck has trouble with just a few tapes, then the tapes are most likely at fault. If it has trouble with most or all tapes, then it's the deck.

Care of Magnetic Tape. Now that we know what to look for when buying magnetic tape, let's take a look at what you can do to make your audio and videotapes last as long as possible—aside from keeping your equipment in tip-top shape. Number one is to avoid touching the magnetic tape itself. Oil from your fingertips will damage the oxide.

When you go to play a tape that has been sitting in a warm and damp or cold and dry environment, it's best to wait a couple of hours before playing it. Otherwise, condensation can

form on the tape. That can damage the tape itself, as well as the player.

It's also good if you try to minimize stops, fast forwards, and rewinds. Those actions put extra mechanical stress on the tape, which, over time, can stretch and distort—distorting the audio and video along with it.

Never overuse a tape. If you start to notice dropouts where parts of the audio or video are missing, the tape has had it. If you continue to use such a tape, it will probably begin to leave excessive oxide deposits in your deck. A tape that has gone through more than 200 record/playback cycles should be put out to pasture.

When you watch or listen to a tape, it's best to play the entire tape from beginning to end without stopping. Then store it without rewinding it. That's because a tape is wound on the reel with an even amount of tension when it is done slowly in the play mode, and it is best to store a tape when it is evenly wound. Tapes that are stored for long periods without being used should probably be rewound and played through at least once a year. That prevents the windings of tape from sticking to each other.

When you do store a tape, store it vertically. Storing a tape horizontally can damage the edges of the tape. Never store tapes in direct sunlight, and don't leave them in your car. Although you probably don't have much control over these next two items, tapes are best stored at a temperature of about 70 degrees Fahrenheit, and a relative humidity of about 50 percent. Note, however, that heat and humidity are worse for tapes than a cold and dry environment.

Last but not least, it's a good idea to keep tapes away from magnetic fields created by things like speakers and TV's. Actually it would be hard to damage a tape by resting it on top of a TV set or speaker—as proof, we've all probably done that at one time or another. However, long-term storage of a tape on top of a TV might eventually damage it. Airport metal detectors also create potentially damaging magnetic fields. However, the X-ray machines do not.

That's about all we have to say about magnetic tape. If you follow the guidelines we've provided, your tapes should last a lifetime—and maybe even your children's lifetime as well! ■

Today's consumers are offered an ever increasing variety of wireless gadgets, many of which operate in the 46- and 49-MHz FM bands. Walkie-talkies and cordless telephones are but two examples of that. Operating those gizmos is usually very easy. But simply operating them teaches you relatively little about what makes them tick. One way to learn about how such devices work is to build, maintain, and repair a few of those wireless "thingamajigs."

In this article, we are going to show you how to build a low-power transmitter that can be used with any compatible receiver: cordless telephones, walkie-talkies, baby monitors, etc. The 49-MHz FM Transmitter described in this article, which is powered from a standard 9-volt battery, is capable of outputting 16 mW (milliwatts) of RF power. The circuit contains a voltage-controlled crystal oscillator (VCXO) to

Build a 49-MHz FM Transmitter

Learn some of the principles behind wireless communications by building this simple FM transmitter

BY DAN BECKER



ensure RF-carrier stability. That helps to prevent signal drift.

In a frequency-modulated (FM) transmission, the RF carrier frequency (49.890 MHz in our case) must deviate (vary) in direct proportion to the amplitude of the audio or voice signal.

Circuit Description. Figure 1 is a schematic diagram of the 49-MHz FM Transmitter. The circuit consists of an audio amplifier, a low-pass filter, three RF stages, and a regulated-DC power supply.

The audio picked up by the microphone (MIC1) is fed to U2-a (half of an LM358 dual op-amp), which is configured as a non-inverting audio amplifier, the gain of which (approximately 500) is determined by R1 and R28. Capacitor C6 modifies the gain of the audio amplifier, effectively turning it into a high-pass filter. That results in a 13-dB gain at 100 Hz that increases 6-dB-per-octave to yield 33 dB at 1000 Hz.

In order to keep the audio bandwidth below 20 kHz (± 10 kHz), the output of U2-a is fed to a low-pass filter, consisting of R7/C9. Together the low-pass filter and audio amplifier yield an overall cutoff frequency of about 4 kHz. The resulting signal is then coupled through R8 and R9 to the base of Q1—a buffer stage built around a 2N3904 general-purpose NPN transistor that's configured as a boot-strapped voltage follower. The output Q1 is fed back via C11 to the R8/R9 junction; that prevents Q1 from loading the low-pass filter.

The output of Q1 (taken from its emitter) is fed through R10 (which provides a means of adjusting the peak deviation) to a crystal-controlled Colpitts oscillator comprised of Q2, L1, D1, XTAL1, and several support components. Figure 2 shows a simplified schematic diagram of a Colpitts oscillator. In that circuit, capacitors C16 and C17 and inductor L provide feedback to Q2's input. However, a feed-

back network made with a conventional inductor would have a Q (quality factor) well below 100, allowing oscillation over a wide band of frequencies. That would make the output signal very unstable. To increase the oscillator's tuning sharpness (Q) and, by extension, its frequency stability, a quartz-crystal resonator is used. Inductor L represents the net result of three separate components: crystal XTAL1, tuning coil L1, and varactor diode D1.

The operation of a quartz crystal is best explained by a simplified equivalent circuit, like the one shown in Fig. 3. That model consists of a series-resonator network made up of C_m , L_m , and R_m , with a parallel capacitor, C_o , shunting the crystal's terminals. At the crystal's series-resonant frequency, the equal and opposite reactances of C_m and L_m cancel each other out, leaving the equivalent series resistance R_m .

However, our Colpitts oscillator requires an inductor between C16 and C17. Therefore, as with any series-resonant circuit, as the applied signal increases in frequency, inductive reactance dominates. Therefore, the crystal resonator is manufactured so that the desired operating frequency is slightly above the crystal's series-resonant frequency. That provides the needed inductor, but one with a Q of several thousand, which sharply tunes the feedback network to a single frequency.

Refer back to Fig. 1. In order to generate an FM signal, it is necessary to modulate the oscillator's frequency. The audio signal from the microphone is used as the modulating source. Diode D1, with a junction capacitance that's inversely proportional to the voltage between its anode and cathode, provides a convenient mechanism for varying the

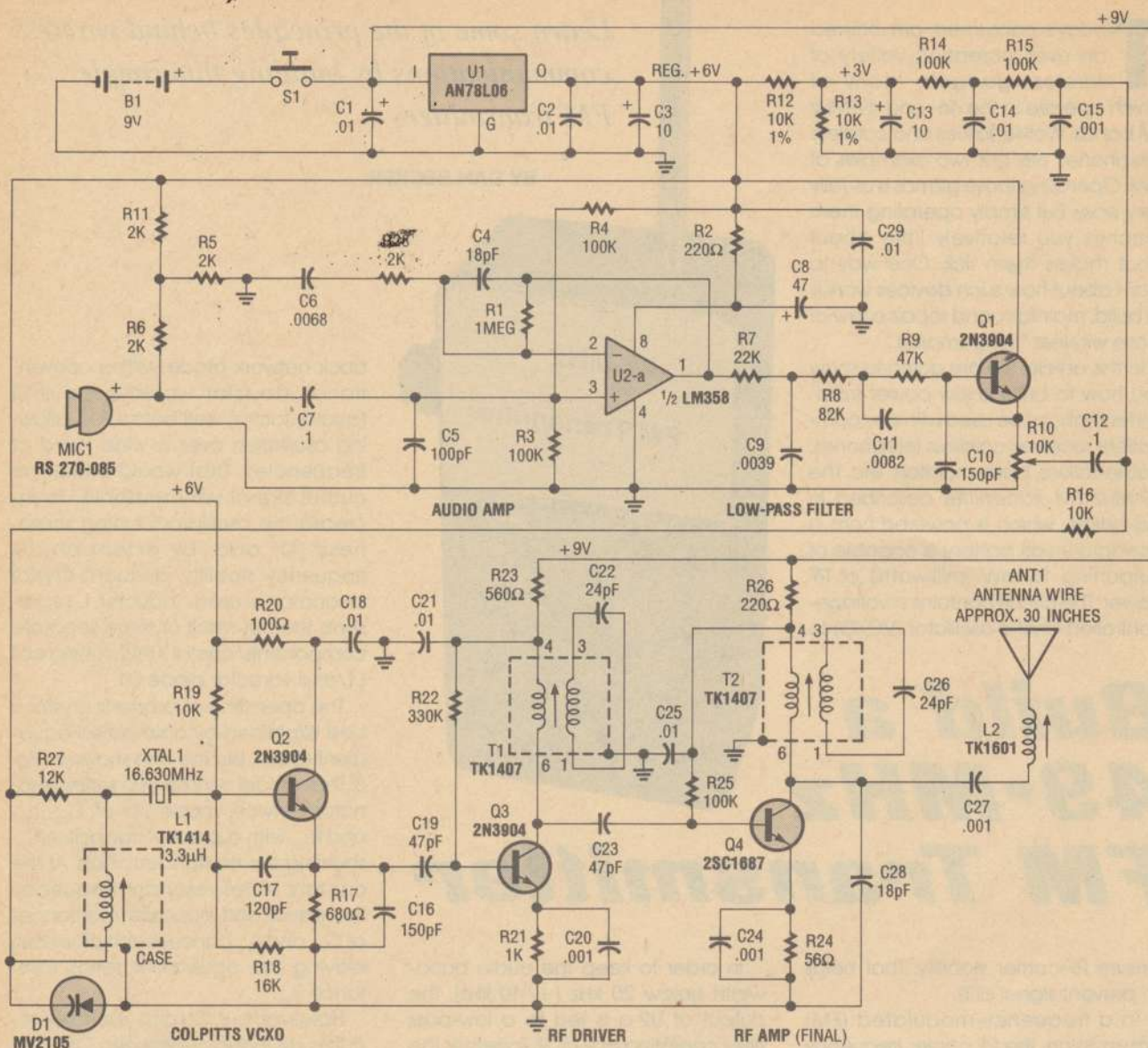


Fig. 1. The 49-MHz FM Transmitter consists of an audio amplifier, a low-pass filter, three RF stages, and a regulated-DC power supply.

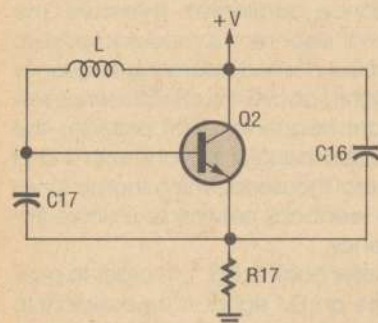


Fig. 2. Shown here is a simplified schematic diagram of a Colpitts oscillator. In that circuit, capacitors C16 and C17 and inductor L provide feedback to Q2's input. Inductor L represents the net result of three separate components: crystal XTAL1, tuning coil L1, and varactor diode D1.

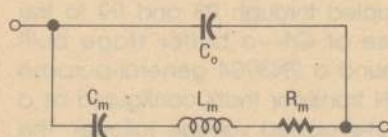


Fig. 3. The operation of a quartz crystal is best explained through this simplified equivalent circuit, consisting of a series-resonator network made up of C_m , L_m , and R_m , with a parallel capacitor, C_o , shunting the crystal's terminals.

resonant frequency of the oscillator's feedback network.

However, since D1 lowers the net inductive reactance of the crystal, L1 is included in the circuit to compensate for the loss. Inductor L1 can also be used to adjust the oscillator to the

desired center frequency. Resistor R27 lowers the Q of L1, preventing spurious oscillations that may be caused by L1 resonating with the crystal's shunt capacitance.

Voltage divider R12/R13, along with a pair of low-pass filters (consisting of R14 and C14, and R15 and C15), set D1's quiescent point to 3 volts; that yields a junction capacitance (which varies by about 2-pF/volt of audio signal) of approximately 16 pF. Thus the audio-signal frequency modulates the oscillator. Because it is easier to vary the frequency of a 16-MHz crystal oscillator than that of a 49-MHz crystal oscillator, the circuit operates on the third sub-harmonic of the output fre-

quency. For example, if a 49.890-MHz transmitter signal is desired, a 16.630-MHz crystal would be selected. Because Q2's output is rich in harmonics, the next stage is tuned so that it amplifies only the third harmonic (49.890 MHz) and ignores the 16.630-MHz fundamental frequency.

Since the third harmonic produces three times as much deviation as the oscillator's fundamental frequency, varying the fundamental frequency by ± 1.67 kHz yields a ± 5 kHz deviation at 49.890 MHz. That greatly reduces the demand on our reactance modulator. The output of oscillator is fed to the emitter-base junction of Q3 (an RF driver stage) through C19. By making C19 small (47 pF), Q3's low input impedance does not load or detune the oscillator. Resistors R21-R23 set Q3's quiescent DC emitter current to a fraction of a milliamp. However, drive from Q2 automatically increases that current to a few milliamps, producing significant RF-power gain. Capacitors C20 and C21 bypass RF current to prevent degenerative feedback.

A resonant tank circuit, comprised of T1 and C23, filters Q3's highly distorted collector current by creating a high impedance at 49-MHz, but a low impedance at the oscillator's fundamental and second harmonic. That allows Q3's collector to drive Q4 with a reasonably clean, 49.890-MHz signal through C23. The next RF-output stage, built around Q4, works pretty much like the Q3 driver stage. However, DC bias resistors R24-R26 are noticeably smaller than their Q3 counterparts. That causes a larger DC emitter current, and results in greater RF gain.

As with Q3, a resonant-tank circuit (consisting of T2 and C26) filters Q4's somewhat-distorted collector current. A reasonably clean output signal is taken from Q4's collector, and used to drive the antenna. The antenna-loading coil, L2, is used to tune out capacitive reactance, allowing Q4 to see a more resistive load. Capacitor C27 blocks Q4's DC collector voltage, while coupling its RF output to the antenna. Capacitor C28 improves the impedance match between Q4's output and the antenna, in addition to suppressing any spurious VHF emissions.

Power for the circuit is supplied by a

PARTS LIST FOR THE 49-MHZ FM TRANSMITTER

SEMICONDUCTORS

U1—AN78L06 6-volt, 100-mA, low-power voltage regulator, integrated circuit
U2—LM358N low-power dual op-amp, integrated circuit
Q1, Q2, Q3—2N3904 general-purpose NPN silicon transistor
Q4—2SC1687 RF-amplifier, NPN silicon transistor
D1—MV2105, 15pF at 4-volts, varactor tuning diode (Motorola)

RESISTORS

(All fixed resistors are 1/4-watt, 5% units, unless otherwise noted.)

R1—1-megohm
R2, R26—220-ohm
R3, R4, R14, R15, R25—100,000-ohm
R5, R6, R11—2000-ohm
R7—22,000-ohm
R8—82,000-ohm
R9—47,000-ohm
R10—10,000-ohm, trimmer potentiometer
R12, R13—10,000-ohm, 1%
R16, R19—10,000-ohm
R17—680-ohm
R18—16,000-ohm
R20—100-ohm
R21—1000-ohm
R22—330,000-ohm
R23—560-ohm
R24—56-ohm
R27—12,000-ohm
R28—2000-ohm

CAPACITORS

C1, C2, C14, C18, C21, C25, C29—0.01- μ F, ceramic-disc
C3, C13—10- μ F, 16-WVDC, tantalum
C4, C28—18-pF, ceramic-disc
C5—100-pF, ceramic-disc
C6—0.0068- μ F, metallized-film
C7, C12—0.1- μ F, metallized-film
C8—47- μ F, 16-WVDC, electrolytic
C9—0.0039- μ F, metallized-film
C10, C16—150-pF, ceramic-disc
C11—0.0082- μ F, metallized-film
C15, C20, C24, C27—0.001- μ F, ceramic-disc
C17—120-pF, ceramic-disc
C19, C23—47-pF, ceramic-disc
C22, C26—24-pF, ceramic-disc

ADDITIONAL PARTS AND MATERIALS

L1—TK1414 3.3- μ H, 7.96 MHz Toko coil
L2—TK1601 1.6- μ H, 25.2-MHz Toko antenna-loading coil
T1, T2—TK1407 0.41- μ H, 49-MHz Toko RF transformer
MIC1—Electret microphone element
XTAL1—16.630-MHz, 32-pF parallel-resonant crystal
B1—9-volt alkaline transistor-radio battery
S1—SPST momentary contact pushbutton switch
Printed-circuit materials, antenna (27-inch whip or length of #22 wire), enclosure, 8-pin DIP socket, wire, solder, hardware, etc.

9-volt battery (B1). Alternatively, the circuit can be operated from any 9-volt DC source that's capable of supplying about 20 mA or so.

When S1 is pressed, 9-volts DC is applied across C1 to voltage regulator U1. Capacitor C1 protects U1's input from stray RF and voltage spikes. Integrated-circuit U1 regulates its 9-volt input to deliver 6-volts DC to all of the circuit except for the RF driver and final stages. If a regulator were not used, the RF carrier frequency could drift or change as the battery voltage decreased with age. Capacitors C2 and C3 minimize the noise and voltage spikes that are often generated by low-cost voltage regulators like U1.

Construction. The author's prototype was assembled on a printed-circuit board that measures about

1 $\frac{15}{16}$ by 2 inches. A full-size template of the printed-circuit artwork is shown in Fig. 4. Once you've etched your own board and gathered the parts listed in the Parts List, construction can begin. Most of the specified component values are not critical; so if your junkbox contains a reasonably close value to the one specified, use it. If you have a reasonably well-stocked parts bin, you probably already have more than half (if not all) of the passive components.

A parts-placement diagram for the printed-circuit board is shown in Fig. 5. It is recommended that an IC socket be provided for U2. Before you begin assembling the project, it is important that you decide at what frequency the circuit is to operate. The frequencies shown in Table 1 correspond to the 46- and 49-MHz cordless-tele-

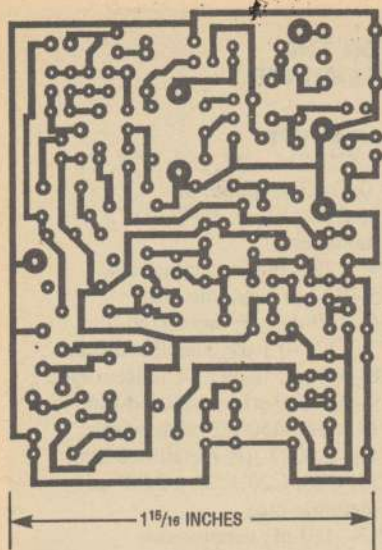


Fig. 4. The author's prototype was assembled on a printed-circuit board that measures about $1\frac{15}{16}$ by 2 inches. This full-size template of the printed-circuit artwork is provided so that you can etch your own printed-circuit board.

phone channels. However, many of those frequencies are also used by walkie-talkies, baby monitors, and numerous other wireless and experimental devices. To determine the required crystal frequency for the transmitter, divide the given channel frequency by three.

Once you've decided on the frequency of operation for your transmitter and obtained the required crystal, assembly can begin. Start by installing an IC socket where U2 is indicated in Fig. 5, and then install the passive components surrounding the socket. When assembling the circuit, mount all of the components close to the circuit board to keep lead length (and thus its reactance) to a minimum. Note: Because of the density in component placement, most of the resistors are mounted vertically.

Also note that except for the three electrolytic and the two metallized-film capacitors, all of the capacitors are low-voltage ceramic-disc units. After the passive components have been installed, mount and solder the semiconductors in place. Connect the positive lead of the battery connector in series with a SPST switch, making sure that that subassembly has sufficient (but not over abundant) lead length to reach the switch's mounting location. Connect that subassembly to the points on the board

shown in Fig. 5. Finally, connect lengths of wire to the board where MIC1 and ANT1 are indicated.

The next step is to prepare the enclosure. Any enclosure of sufficient size can be used to house the 49-MHz FM Transmitter; just remember that the enclosure should have sufficient room to accommodate the circuit board as well as the off-board components (S1, ANT1, B1, and MIC1).

The first step in preparing the enclosure is to select a site on or within the enclosure for the off-board com-

TABLE 1—FREQUENCY ALLOCATION

CHANNEL	BASE TRANSMITTER (MHz)	HANDSET TRANSMITTER (MHz)
1	46.610	49.670
2	46.630	49.845
3	46.670	49.860
4	46.710	49.770
5	46.730	49.875
6	46.770	49.830
7	46.830	49.890
8	46.870	49.930
9	46.930	49.990
10	46.970	49.970

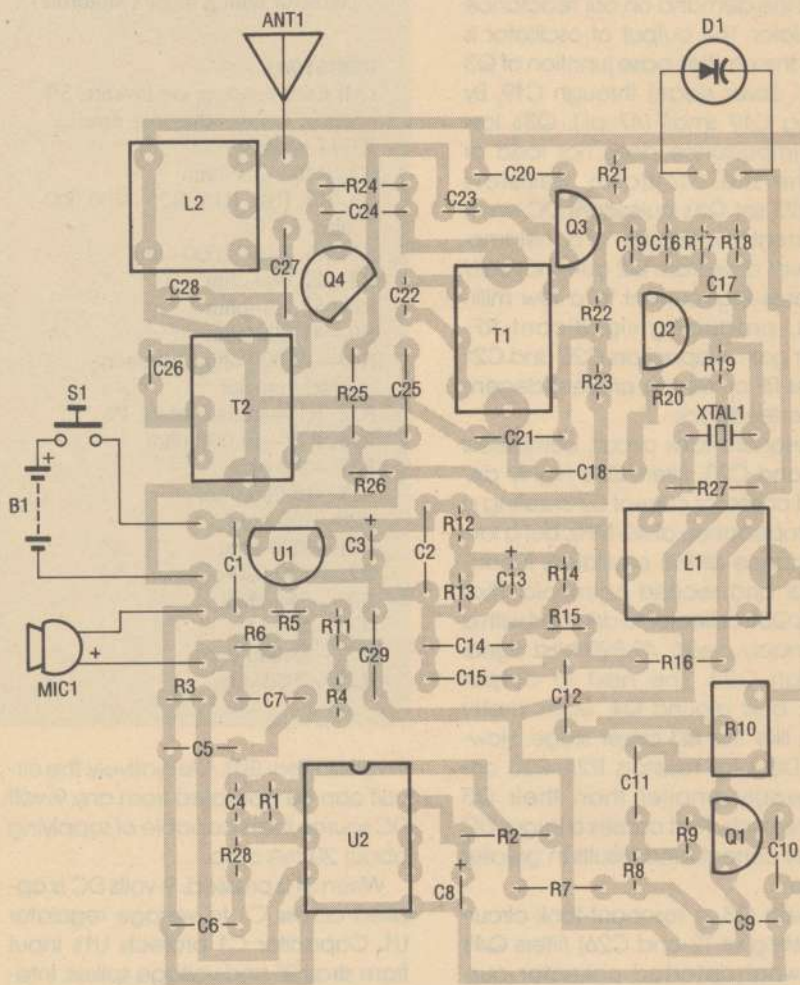


Fig. 5. Assemble the printed-circuit board using this parts-placement diagram as a guide. It is recommended that an IC socket be provided for U2. Before you begin assembling the project, however, it is important that you decide on what frequency the circuit is to operate and to select a crystal accordingly.

ponents—S1, MIC1, and ANT1. Drill holes at the selected sites for the components that will be located there. Mount the off-board components to the enclosure, and connect them to the circuit using the previously installed hook-up wire.

Note: If you intend to power the circuit from an alternate power source

(a wall adapter, for example), install a 10- μ H miniature RF choke in series with each supply lead, and then connect the positive lead in series with an SPST switch.

If you intend to use a telescoping whip antenna, be certain that it includes mounting hardware. Most

(Continued on page 92)

Using a cable-ready VCR as a tuner can, in many cases, save the cost of renting a cable box. Unfortunately, doing so means always having to turn two units (both the TV and VCR) on or off due to the lack of switchable accessory outlets. Admittedly, that's a minor annoyance, but it is a constant one. Tiring of that inconvenience, I came up with the *VCR/TV Auto-Switch* described in this article.

What the VCR/TV Auto-Switch does is monitor the baseband-video output of your VCR. When a video signal is detected, the VCR/TV Auto-Switch automatically turns on your TV set or video monitor. Note, however, that this approach will not work with a television that stores channel or volume information in a volatile memory.

How It Works. A schematic diagram of the VCR/TV Auto-Switch is shown in Fig. 1. The circuit is comprised of a 24-volt center-tapped transformer (T1), a 1-amp, 100-PIV fullwave bridge rectifier (BR1), and two 12-volt regulators (U1 and U2), which form a dual-polarity, regulated, power supply; a dual BiFET op-amp (U3) and a general-purpose NPN silicon transistor (Q1), which form the basis of a signal detector/trigger circuit; a 12-volt relay (K1); two AC sockets (SO1 and SO2); and a few additional components.

A voltage divider formed by R5 and R6 provides a very small positive offset to the inverting inputs of both U3-a and U1-b to help prevent false triggering. The circuit takes its input from the baseband-video output of your VCR via PL2 (an RCA plug that mates with the video-output jack of the VCR). When switches S1 and S2 are in the positions shown and the VCR is turned off, no signal is applied to the circuit (through PL2), so the input to op-amp U1-a is at zero volts, forcing its output low. That low is applied to the non-inverting input of U3-b, forcing its output low. The low output of U3-b holds Q1 at cutoff, keeping relay K1 from energizing, and the TV connected to SO2 from turning on. Note that when there is no signal present, the output of U3-b swings close to the negative supply rail, producing a negative voltage that exceeds the emitter-base breakdown voltage of Q1. Diode D2's



Build an Automatic Power Switch for your TV

Add an accessory outlet to your video system that turns on your TV whenever your VCR is turned on

function is to block the negative going output of U3-b, thereby preventing damage to Q1.

On the other hand, when the VCR is turned on, a baseband-video signal is applied to the circuit at PL2. That signal is routed to the non-inverting input of U3-a, causing the output of that op-amp to swing positive. The output of U3-a is fed through diode D1 (which passes only the positive portion of the signal), causing C11 to charge. Diode D1 also prevents the charge on C11 from being discharged through U3-a during U3-a's negative-going output transition. The charge on C11 is bleed off via R7 during the negative-going output transition and power is removed from the circuit. The C11/R7 combination also forms a glitch filter, which provides a short time-delay that prevents a momentary signal loss from cycling the television or monitor off and on.

The output of U3-a is applied to the

non-inverting input of U3-b, causing its output to go high. That high is applied to the base of Q1 through D2 and R8, causing Q1 to turn on.

When Q1 conducts, it, in turn, completes the ground path for the relay, causing it to energize. With the relay energized, AC line voltage is applied to SO2, automatically turning on the TV. Diode D3 is used to protect Q1 from the inductive kickback (spikes) caused by the relay's collapsing field. Without that protection, an inductive spike could cause Q1 to short, turning it into a three-legged Zener diode. That would result in the TV being on continually.

Switch S1 allows you to choose between auto and manual operation. When S1 is placed in the MANUAL position and S2 is set to the ON position, a positive voltage from the power supply is applied to the non-inverting input to U3-a, causing the TV to turn on as if the circuit were in the auto mode

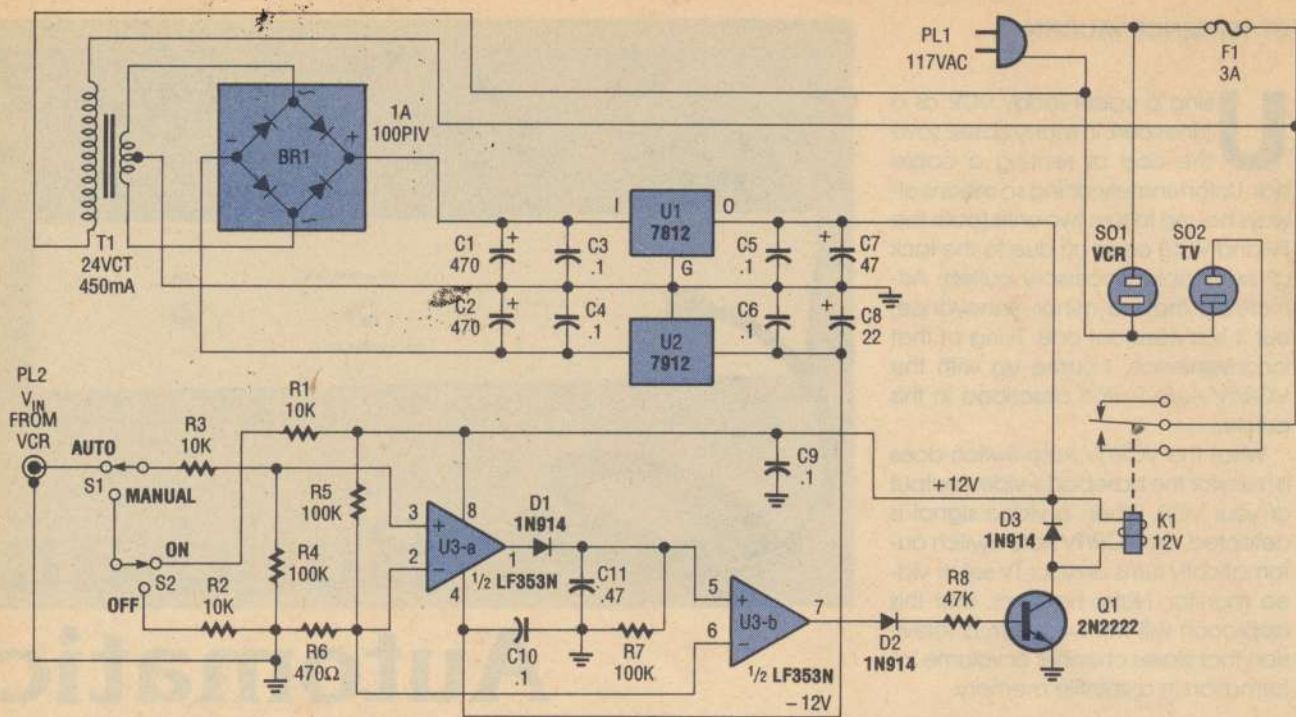


Fig. 1. The VCR/TV Auto-Switch is comprised of a 24-volt center-tapped transformer (T1), a 1-amp, 100-PIV, fullwave bridge rectifier, and two 12-volt regulators (U1 and U2), which form dual-polarity, regulated, power supply; a dual BiFET op-amp (U3) and a general-purpose NPN silicon transistor (Q1), which form the basis of a signal detector/trigger circuit; a 12-volt relay (K1); two AC sockets (SO1 and SO2); and a few additional components.

and a video signal from the VCR were present.

Construction. As shown in the photo, the author's prototype of the VCR/TV Auto-Switch was assembled on a section of copper-clad experimenter's board and point-to-point wiring was used to make the component interconnections. When assembling the circuit, all of the standard project-building precautions apply: Keep all leads as short as possible, and all power-supply bypass capacitors (C3-C6, C9, and C10) should be mounted as close to their respective IC's as possible. It is also recommended that an IC socket be provided for U3 (the op-amp).

Because 117-volts AC is applied to the circuit board via the relay, the board must be securely mounted on standoffs. In addition, wire connections to the relay should be made with wire of sufficient size to handle the AC-line voltage. Instead of enlarging the pre-drilled holes in the experimenter's board to accommodate 18-gauge (line-cord size) or heavier wire, the author used dual strands of 20-gauge hook-up wire for the relay, which is more than equal to a single 18-gauge

wire. Mount the relay to the board and connect short lengths of wire to the relay contacts. Do not connect the relay-contact wires to SO2 and the AC line at this point; you will be instructed when to do so later on, during the checkout procedure.

Note that the circuit contains two AC sockets (SO1 and SO2): The two sockets are actually a single, standard duplex AC wall-outlet. The socket

should be of the type that has break-away tabs between the two outlets. As shown in the schematic diagram, the cold (or neutral, large-spade side) remains as normal; however, the two hot tabs have been separated, with the hot side of SO1 going directly to the AC line, and the hot side of SO2 going to the relay's wiper.

For safety reasons, it is also important that the duplex socket (which is



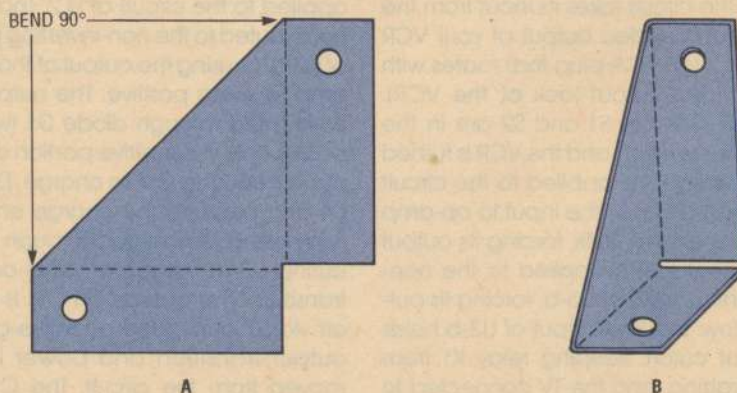


Fig. 2. For safety reasons, it's also important that the duplex socket mounted to the rear panel of the enclosure be able to withstand power-cord insertion force without the case flexing and possibly forcing the AC wiring to contact the case or other components. To that end, reinforcing brackets fabricated from scraps of sheet aluminum were placed at one end (either end) of the outlet, although placing brackets at both ends makes for a much sturdier project.

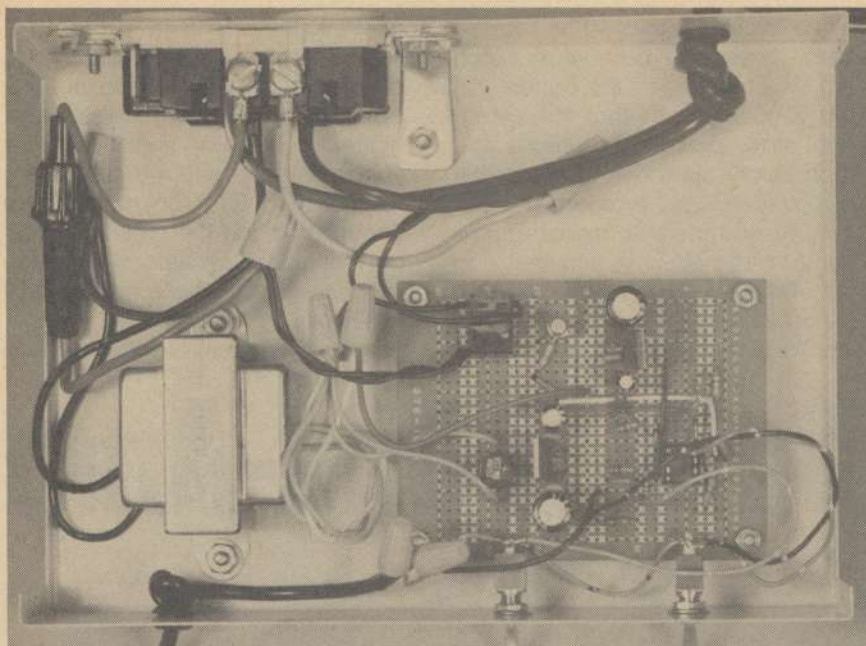

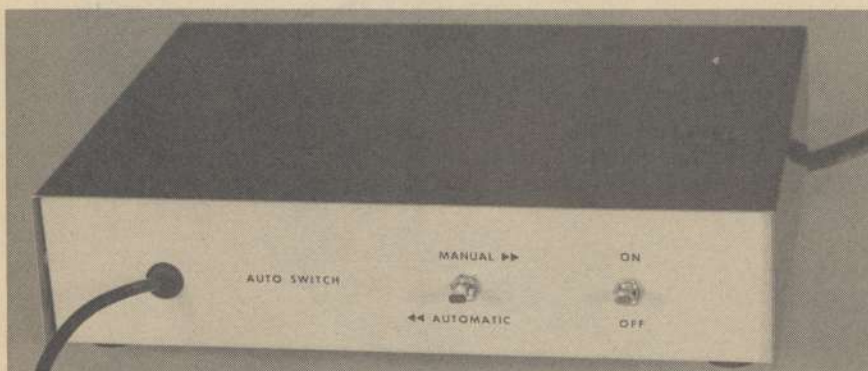Here is an inside view of the VCR/TV Auto-Switch. In the prototype, fuse F1 is not the board-mounted type; instead the author chose to use an in-line fuse. The enclosure for the project has enough space for the circuit board, as well as all of the off-board components.



Once the project enclosure has been drilled, labels can be affixed to the front and rear panels to indicate switch functions, and outlet designations.

mounted to the rear panel of the enclosure in the prototype) be able to withstand the power-cord insertion force without the case flexing and possibly forcing the AC wiring to contact the case or other components. To that end, reinforcing brackets fabricated from scraps of sheet aluminum were placed at one end (either end) of the outlet, although placing brackets at both ends makes for a much sturdier project. Figure 2 gives details on how to fabricate the bracket(s).

Since the project is intended to be in constant use, it does not have a power switch; however, adding one certainly wouldn't hurt anything. It is essential that a polarized AC power cord be used to connect the circuit to

the AC source. That's because the relay can interrupt only one line and that really should be the hot (small spade) side of the AC line cord. Modern electronics gear (particularly VCR's and TV's) may (and often do) also require the correct polarity. A three-wire plug and cord (with the ground wire connected to the case) is even better for PL1.

When it comes to PL2, you have a couple of options: You could use a jack instead of a plug for PL2, and use an RCA patch cord to connect the circuit to your VCR; or you can do as the author did, cut the connector from one end of a patch cord and connect the wires directly to the circuit board. With the latter arrangement, you could simply plug the unit

PARTS LIST FOR THE VCR/TV AUTO-SWITCH

SEMICONDUCTORS

- U1—7812 12-volt, 1-amp, positive voltage regulator, integrated circuit
- U2—7912 12-volt, 1-amp, negative voltage regulator, integrated circuit
- U3—LF353N or TL082 dual BiFET op-amp, integrated circuit
- Q1—2N2222A general-purpose NPN silicon transistor
- D1-D3—1N914 general-purpose, small-signal diode
- BR1—1-amp, 100-PIV, full-wave bridge rectifier

RESISTORS

- (All resistors are 1/4-watt, 5% units.)
- R1-R3—10,000-ohm
 - R4, R5, R7—100,000-ohm
 - R6—470-ohm
 - R8—47,000-ohm

CAPACITORS

- C1, C2—470- μ F, 35-WVDC, electrolytic
- C3-C6, C9, C10—0.1- μ F, 50-WVDC, monolithic-ceramic or ceramic-disc
- C7—47- μ F, 35-WVDC, electrolytic
- C8—22- μ F, 35-WVDC, electrolytic
- C11—0.47- μ F, 35-WVDC, tantalum

ADDITIONAL PARTS AND MATERIALS

- T1—24.6-volt, center-tapped, 450-mA transformer
- F1—3-amp, fast-acting fuse
- K1—SPDT 12-volt relay (Omron G2E-184P, All Electronics catalog #RLY 787)
- S1, S2—SPDT toggle switch
- PL1—Polarized AC power plug with line cord
- PL2—Video dubbing (patch) cord, see text
- SO1, SO2—117-volt duplex AC outlet
- Experimenter's board, enclosure, fuse holder, 8-pin socket, standoffs, strain-reliefs or grommets, wire, solder, hardware, etc.

into the VCR's baseband-video output.

If you opt for the latter arrangement, cut off one of the RCA plugs and carefully remove one inch of the thin outer insulation, exposing the braided sheath. Bend the cable at the end of the insulation and spread the braid away from the bend. Pull the inner cable through the opening in the braid. Strip about 1/2 inch of insulation from the inner cable. Connect

(Continued on page 89)

Have you ever been frustrated by your digital multimeter when trying to measure resistance below one ohm? If so you're probably not alone because most meters will only measure resistance down to the nearest 0.1 ohm. Well, in this article we'll show you how to build a DMM accessory that will enable you to accurately measure a resistance down to the nearest 0.0001 ohm. The unit injects a precise amp of current into the resistance to be tested. Then you simply use your DMM to measure the voltage drop produced by the injected current. With typical meters, resistances from 1 ohm to 0.0001 ohm can be measured with the aid of the current injector.

You should be able to find many uses for the unit. I have used it to measure shunt resistors, circuit-board-trace re-

sistance, relay/switch contact resistance, and motor/transformer winding resistance. You can even use it to determine a wire's gauge by measuring its resistance per unit length or to test diode rectifiers or transistors at 1 amp.

The circuit is powered by two "C" cells, B1 and B2. A pushbutton switch (S1), which connects the batteries to the circuit, ensures that the system only draws power momentarily. The momentary operation of the switch also discourages prolonged measurement times, increasing the number of measurements that can be taken before the batteries need to be replaced. The large 100- μ F capacitor (C1) helps dampen transients

flows into the inductor (L1) from the 3-volt battery supply. When pin 7 turns off, the energy stored in the inductor emerges as a short voltage pulse, higher in amplitude than the supply voltage. Those voltage pulses are routed to a filter capacitor (C3) through a diode (D1). With the component values chosen, the voltage produced at C3 ranges from about 9 to 12 volts.

The current-control section uses a

If your multimeter is stumped when it comes to reading very low resistance, then this is the multimeter accessory you should build to extend its range.

It has some nice features. For example the injector circuit is powered from two "C" cells and features a power-on LED that doubles as a weak-battery indicator. Should the batteries need to be replaced, the LED will fail to turn on during operation.

How it Works. Figure 1 contains the schematic diagram for the One-Amp Current Injector circuit. The unit can be divided into three main sections: power supply, current controller, and battery-voltage monitor. Let's examine the power-supply section first.

Build a One-Amp



Current Injector

BY DAVID A. JOHNSON

caused by the heavy DC current drawn from the battery during operation.

Because much of the unit's electronic circuits function better at more than 3-volts, the circuit contains a simple flyback voltage converter. It is based on a CMOS version of the classic 555 timer (U1) wired as a non-standard astable oscillator. When pin 7 of the timer (used as an active-low output in this circuit) turns on, current

power MOSFET (Q1) to set the amount of current passed through the unknown resistance (R_x). By controlling the voltage applied to the gate terminal of the FET, it can be made to behave as a variable resistor and can, therefore, vary the current as needed.

For that reason, one comparator in an LM393 IC supplies the FET with a gate-control voltage. That section of the IC has been configured to operate as an operational amplifier with

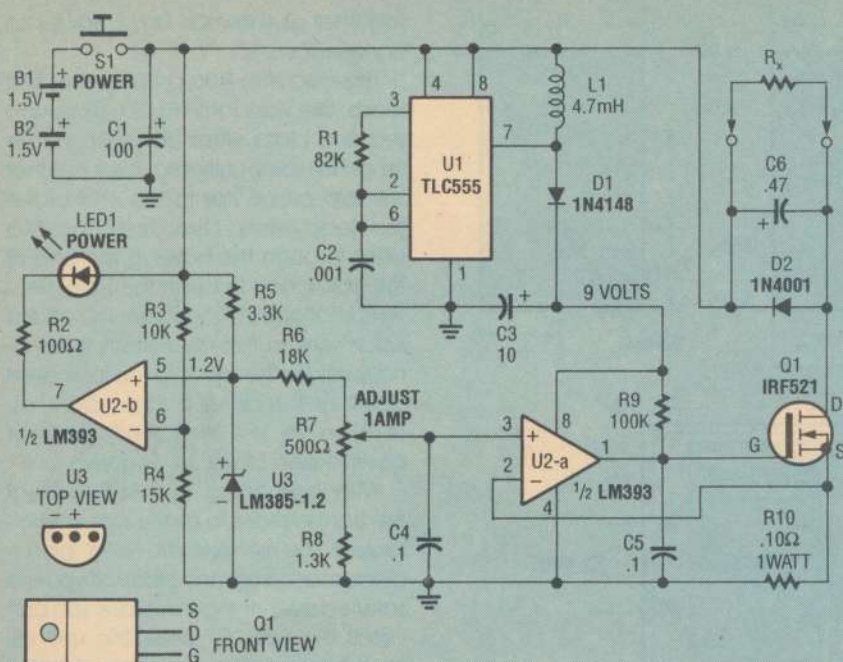


Fig. 1. The current injector can be broken down into three sections: the power supply (containing a DC-to-DC converter), a current-control circuit, and a battery monitor.

the aid of a resistor (R9) and a capacitor (C5). The two components form a filter network that helps stabilize the voltage fed to the FET. A regulated voltage, developed by a voltage-reference IC (U3) and a resistor (R5), is connected to the noninverting input of U2-a through a voltage-divider network consisting of R6, R7, and R8. The noninverting-input voltage sets the voltage level controlling the FET. Potentiometer R7 allows you to select the value of the noninverting-input voltage so you can precisely adjust the injector's output current to 1-amp.

The injector's output current, which passes through the unknown resistance and the FET (Q1), is also forced through an internal current-monitoring resistor (R10). The voltage developed across R10 is therefore proportional to the injector's output current. The current-monitoring voltage produced by R10 is fed to the inverting side of the control IC (U2-a). So the IC's output supplies the gate of the FET with the correct voltage to maintain the unit's output current at a fixed level.

Diode D3 and capacitor C6 are wired across the output terminals as protection. They absorb any energy that may be sent back to the circuit if you happen to measure a resistor with a large inductance.

The battery-monitor section also

performs an important task. With two fresh "C" cells installed in the unit, a nominal 3-volts is supplied to the current control circuit. However, during operation, the battery voltage will drop. The unit will continue to operate properly as long as the battery voltage remains above 2-volts. The battery monitor's job is to light the power LED (LED1) as long as the battery voltage remains above 2-volts. Should the circuit need new cells, the LED will fail to turn on.

To do its job, the battery monitor uses the second half of the dual-comparator IC (U2-b). It is wired as a classic voltage comparator. The regulated voltage from the voltage reference IC (U3) is compared to a voltage developed by a voltage divider (made of R3 and R4) that is connected to the cells. As long as the voltage from the divider is greater than the reference voltage, the output of the comparator remains low, turning on the power indication LED.

Construction. As illustrated in Fig. 2, the unit's circuitry is housed in a project box (the author's was plastic) that you can purchase from almost any electronic-parts supply store. Using the figure as a guide, first glue a two "C"-cell holder to the inside bottom of the box, with the holder pushed to one end. Drill two $\frac{5}{32}$ -inch holes

PARTS LIST FOR THE ONE-AMP CURRENT INJECTOR

SEMICONDUCTORS

- U1—TLC555CP CMOS oscillator timer, integrated circuit
- U2—LM393N dual comparator, integrated circuit
- U3—LM385BZ-1.2 voltage reference, integrated circuit
- Q1—IRF521 or IRFZ12, 50-volt, 0.3-ohm power FET
- D1—1N4148 general-purpose diode
- D2—1N4001 1-amp, 50-PIV rectifying diode
- LED1—Light-emitting diode, red, super-bright T-1 $\frac{1}{4}$ style

CAPACITORS

- C1—100- μ F, 10-WVDC, aluminum electrolytic
- C2—1000-pF, 50-WVDC, ceramic or Mylar
- C3—10- μ F, 25-WVDC, aluminum electrolytic
- C4, C5—0.1- μ F, 50-WVDC, ceramic or Mylar
- C6—0.47- μ F, 50-WVDC, Mylar

RESISTORS

- (All fixed resistors are $\frac{1}{4}$ -watt 5% units unless otherwise indicated.)
- R1—82,000-ohm
- R2—100-ohm
- R3—10,000-ohm
- R4—15,000-ohm
- R5—3300-ohm
- R6—18,000-ohm
- R7—500-ohm multi-turn trimmer potentiometer (Digi-Key CEG52 or equivalent)
- R8—1300-ohm
- R9—100,000-ohm
- R10—0.1-ohm, 1-watt, (Digi-Key SC1A0.1 or equivalent)

ADDITIONAL PARTS AND MATERIALS

- B1, B2—alkaline "C" cell
- L1—4.7-mH choke coil (Digi-Key TK4320 or equivalent)
- S1—Normally open, SPST, momentary-contact switch
- Printed-circuit or perfboard, LED holder, 2 "C"-cell holder, enclosure, transistor heat sink, red and black hook-up wire, alligator clips (or equivalent), solder, etc.

through the other end of the box to allow the injector's two current-carrying wires to exit. Then drill a $\frac{3}{8}$ -inch hole for the power switch and a $\frac{1}{4}$ -inch hole for an LED holder through the top cover of the box. With the holes drilled, you can then install the

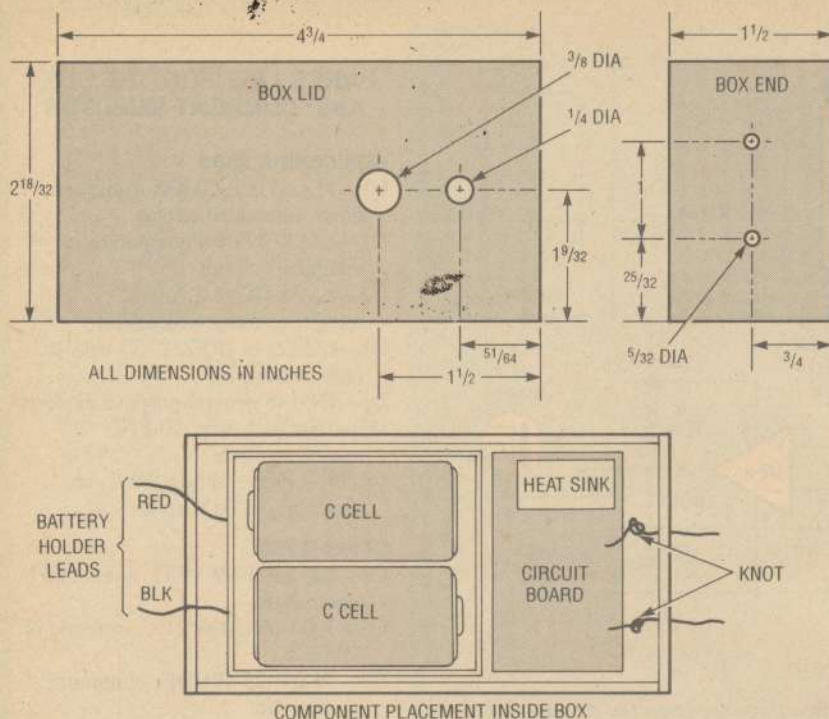


Fig. 2. If you drill your enclosure to these specifications you'll make the task of final assembly a lot easier. Remember to use a holder for the LED.

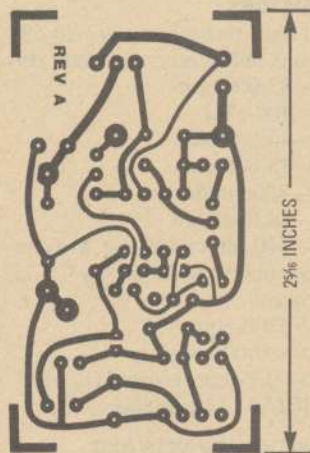


Fig. 3. Using this foil pattern to generate a printed-circuit board will make the assembly of your own current injector a snap.

power switch and the LED (with a holder) in the top of the box.

Next, you'll need to build the rest of the circuit on a suitable platform. The circuit is not complicated and could easily be built breadboard-style. Alternatively, if you wish to, you can etch your own printed-circuit board using the foil pattern shown in Fig. 3. Consult the parts-placement drawing (see Fig. 4) for the correct component placement, being careful to note the orientation and polarity of the components.

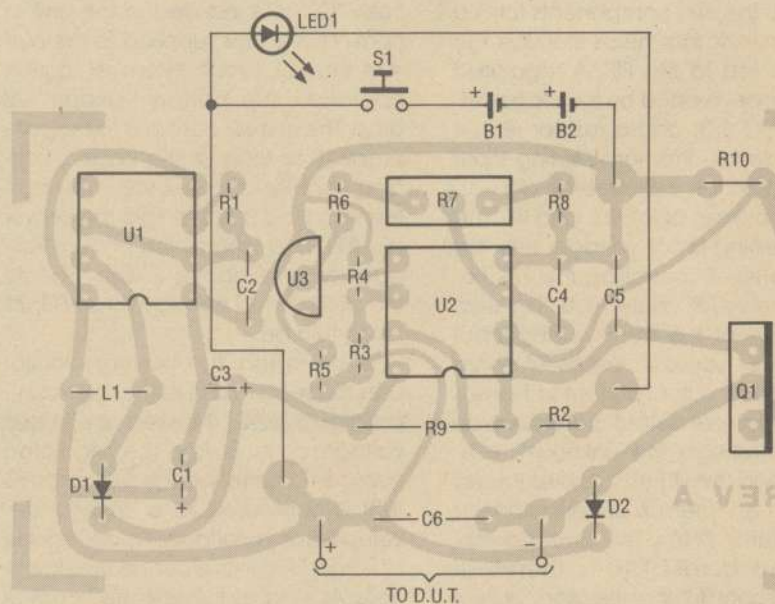


Fig. 4. Follow this diagram to stuff the circuit board. Be sure to orient all the polarity-sensitive parts properly as you proceed.

When you install the FET (Q1), make sure that its body is about 0.15 inches above the board and that it is properly heat-sunk. Once you have soldered all the parts in place, carefully inspect the board for solder splashes, shorts, and misplaced components before moving on.

Next, use pieces of small gauge (No. 28–24) wire to connect the circuit board, battery holder, LED1, and S1

together as shown in Fig. 4. Solder all connections.

The next step is to prepare two test leads. Use standard No. 20–18 gauge red and black wires about 36 inches long. First solder alligator clips or other suitable probe tips to the end of the test lead wires. Next, feed the two wires through the holes in the end of the box. Once through the hole, tie a tight knot about 1 inch from the end of each wire to act as a strain relief. Finally, solder the leads to the indicated points on the circuit board, paying attention to the polarity—red for positive and black for negative.

With everything installed, inspect the connections to make sure you followed the schematic and parts-placement diagram exactly. If you are satisfied everything is in order, you can install the two "C" cells. The unit still must be calibrated, so do not install the lid at this time.

Unit Calibration. You will need a good digital multimeter to accurately

calibrate the unit. Before connecting the injector's output to the digital multimeter's leads, make sure the meter is set to measure DC amps (usually on a 2-amp scale), and not DC milliamps. **If you mistakenly set the multimeter to the milliamp or microamp scale, the 1 amp of current from the injector could blow the meter's protection fuse.**

(Continued on page 89)


Popular ElectronicsTM Market Center

Paperback Books

GREAT PAPERBACKS AT SPECIAL PRICES

☐ **COMPUTER HOBBYISTS
HANDBOOK—BP251—
\$8.95**

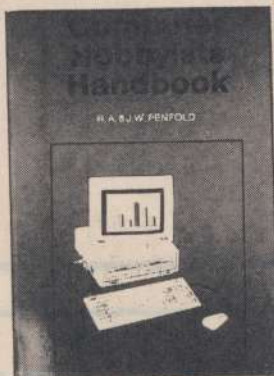
Subjects covered include microprocessors and their register sets; interfacing serial, parallel, monitor, games and MIDI ports; numbering systems, operating systems and computer graphics. While the book is aimed at the computer hobbyist, it should also prove useful to anyone who intends to use a computer to follow their interests.




☐ **INTERNATIONAL RADIO
STATIONS GUIDE—
BP255—\$9.95**

Provides the casual listener, amateur radio DXer and the professional radio monitor with an essential reference work designed as a guide for the complex radio bands.

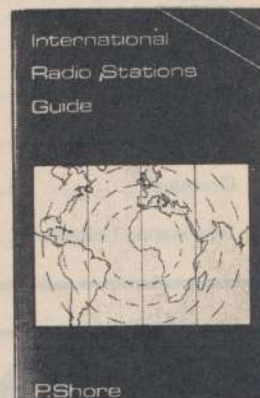Includes coverage on Listening to Short Wave Radio, ITU Country Codes, Worldwide Radio Stations, European Long Wave and Medium Wave Stations, Broadcasts in English and more.



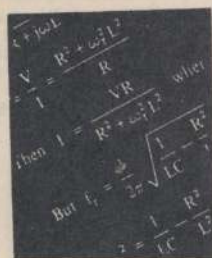**Further
Practical
Electronics
Calculations and
Formulae**
F.A. WILSON



☐ **FURTHER PRACTICAL
ELECTRONICS
CALCULATIONS—
BP144—\$9.00**

450 pages crammed full of all the formulae you are likely to need. Covers Electricity, Electrostatics, Electromagnetism, Complex Numbers, Amplifiers, Signal Generation and Processing, Communications, Statistics, Reliability, Audio, Radio Systems, Transmission Lines, Digital Logic, Power Supplies. Then there's an appendix of Conversion Factors, Mathematical Formulae and more.



☐ **WIRELESS &
ELECTRICAL
CYCLOPEDIA—ETT1—\$5.75**

A slice of history. This early electronics catalog was issued in 1918. It consists of 176 pages that document the early history of electricity, radio and electronics. It was the "bible" of the electrical experimenter of the period. Take a look at history and see how far we have come. And by the way, don't try to order any of the merchandise shown, it's unlikely that it will be available. And if it is, the prices will be many times higher.

ELECTRONIC TECHNOLOGY TODAY INC.
P.O. Box 240, Massapequa Park, NY 11762-0240

Name _____
Address _____
City _____ State _____ Zip _____

**SHIPPING CHARGES IN
USA AND CANADA**

\$0.01 to \$5.00	\$1.50
\$5.01 to \$10.00	\$2.50
\$10.01 to 20.00	\$3.50
\$20.01 to 30.00	\$4.50
\$30.01 to 40.00	\$5.50
\$40.01 to 50.00	\$6.50
\$50.01 and above	\$8.00

**SORRY No orders accepted
outside of USA & Canada**

Total price of merchandise	\$ _____
Shipping (see chart)	\$ _____
Subtotal	\$ _____
Sales Tax (NYS only)	\$ _____
Total Enclosed	\$ _____

All payments must be in U.S. funds

Number of books ordered ☐



FAMOUS BRAND SOLDER

0.25" dia. solid core, 29T/70L.
5 lb. spool. **\$19.95**

Other solders in stock,
including rare types.

VHF PISTON TRIMMER

10 KV, 5-12 pF, teflon dielectric. PolyFlon No. VC 10-12-05. **\$19.95 each**

5.25" FLOPPY DISKS

Premium quality.
DSDD, 360K, notched, with sleeves.
100 for \$19.95

45 MHz SAW FILTER

Murata Erie No. SAF45-MA80Z.

Two for \$9.95



MODULAR WALL POWER SUPPLY

16 VAC, 500 mA
Two for \$4.95

STAINLESS STEEL HARDWARE

Popular sizes used in electronic work. Assorted. May contain capscrews, Phillips. Sizes 4-40 and up. **3 lbs. \$5.99**

PLASTIC PROJECT BOX

Measures approx. 5" x 3" x 1". Features inlays, outlays, overlays, rubber feet and a PC board full of goodies inside. **3 for \$4.95**



PHOTOMULTIPLIER POWER SUPPLY

1000V @ 1 mA. Power Technologies Inc. model BR12-2RA. New. **\$29.95 each**

RESISTOR RIOT

1/8, 1/4, 1/2 Watt, power, precision, fixed, adjustable, etc. Thousands of pieces. **5 lbs. for \$4.95**



3-PIN DIN MALE

**99¢ each
12 for \$9.95**

KEYPAD CONTROLLERS

For use with Atari 2600 video computer system game programs. Part #CX50. Set of two. **\$9.95**



MINI RELAY ASSORTMENT

5V, 12V, 24V coils, unused, tiny to thumb-nail sizes, mixed. **25 for \$9.95**

SOUNDCAN Alarm or Amplified Speaker

The latest in alarm technology from England. It listens to the total environment and is able to distinguish between "hostile" and "friendly" sounds. It is designed to detect the sounds of a break-in.

Fully self-contained with its own rechargeable batteries, in case of power failure the unit will run for up to 24 hours. Entry delay - 30 seconds. Exit delay - 15 seconds. When set for maximum sensitivity, range covers 25,000 cubic feet. Duration of alarm approximately 10 minutes.

Inside attractive box is a keyswitch, 4" 5 Watt pm speaker, 6AA nicads and holder, 10VDC modular power supply and a PC board full of transistors, IC's and other goodies.

These units are from a distress sale, appear new, tested good, with instructions for simple conversion to portable, amplified speaker. **\$19.95**

100 GAUSS CRESCENT MAGNET

Shown approx. 75% size.
\$6 for \$9.95



STANDOFFS

Popular sizes and styles used in electronics. **100 for \$4.95**

MICROWAVE VCO

1.3-2.3GHz, 10mW output, small (1" x 1" x 3/8"), Z-Comm #C600. With data sheet. **\$39.00 each
3 for \$100.00**



CANON DESKTOP FULL PAGE SCANNER

300 x 300 dpi. With I/O card, cable and software. **\$249.00**



400V 25A BRIDGE

\$3.99 each

800 PIV, 1A DIODE

100 for \$9.95



SUPER QUALITY FOOT SWITCH

From medical equipment supplier. Great for musical applications. Key your transmitter, mute TV, radio or telephone. Well constructed, metal case and non-slip pads top and bottom. Has SPST switch and includes 6' cord with 5-pin DIN plug. **\$9.95 each or 3 for \$24.00**



RADAR DETECTOR

Famous brand, used, working condition. **\$24.95 each**



EUROPEAN STYLE POWER CORDS

For computers and test equipment.
Your Choice - \$3.00 each

50 Lb. CARE PACKAGE


Surplus goodies from Silicon Valley. This is not junk, just material we've acquired in quantities too small to catalog: electronic and mechanical subassemblies for everything from robots to rockets. Assortments may include IC's, caps, connectors, bearings, diodes, hardware, circuit boards, cables. Weird and wonderful stuff. Every selection is different. **50 lbs \$49.95**

9" ROD ANTENNA

With treaded hole at bottom.
Two for 99¢

ELECTRET CONDENSER MIKE

Shown approx. actual size.
99¢ each

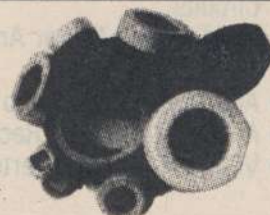

TOROID CORE ASSORTMENT

May contain tape wound, powdered metal, ferrite material cores, different sizes. **20 for \$4.95**

When in Reno, Nevada

Visit

ASCI Electronics

ALLTRONICS
2300 Zanker Road • San Jose, CA 95131

VISA - MC - AMEX cards accepted, Minimum order \$15.00. California residents add 8.25% sales tax. Shipping additional on all orders.

Phone (408) 943-9773 • Fax (408) 943-9776

Visit Our
Retail Store
M-F 9 - 6
Sat. 10-3

ADVERTISERS INDEX

Free Information No.	Page	Free Information No.	Page	Free Information No.	Page
29	Ace Communications 50O	33	Interactive Images 50F	—	P.C. Boards 50Z
34	All Electronics 50C	—	Internt'l Micropower 50D1	—	P.E. Factcards 50J
35	Alltronics 50A1	37	JDR Microdevices 50P	—	P.E. Reprint Bkst. 50T
—	C&C Specialties 50C1	—	JP Video 50F1	42	Prairie Digital 50T
30	C&S Sales 50R	25	Kelvin 50K	—	Science Probe! 50E1
—	CLAGGK Monitor 50L	—	Mental Automation 50H	—	Seattle Film Works 50D
36	Consumertronics 50H	—	Microthinc 50Z	39	Silicon Valley Surplus 50X
—	Datak 50Z	—	MCM Electronics 50Z	—	Spy Supply 50Y
—	EDE 50D1	38	MWK 50J	31	United Electronic Supply 50W
—	Electronic Tech. Today 50A	26	Ocean State Electronics 50M	40	Viejo Publications. 50V
—	47th St. Photo 50C1	27,28	Optoelectronics 50I, 50U	41	WPT 50L
—	Greenleaf 50H	—	OWI 50J	32	Xandi 50B
—	Information Unlimited 50E				

XANDI Electronics

**SATISFACTION
GUARANTEED!**

The use of surface mount technology makes this the smallest FM transmitter you can buy! This is not a toy, it out performs most units on the market today. Our E-Z-kit has all the surface mount parts pre-assembled to the circuit board.

XST500(E-Z) E-Z Kit \$39.95

The Use of surface mount technology makes this the smallest telephone transmitter you can buy. Powered by the phone line, it can transmit a phone conversation upto 1/4 mile. Our E-Z kit has all the surface mount parts pre-assembled to the circuit board.

XSP250(E-Z) E-Z Kit \$29.95



The XTR100 Tracking Transmitter transmits a continuously beeping tone that can be received by any FM receiver. Can be used for games, contests, or as an anti-theft device.

XTR100(C) Kit \$39.95



The XFM100 FM transmitter has a range of upto 1 mile. It works with any standard FM receiver. It contains a built in high gain two stage audio amplifier for maximum sensitivity.

XFM100(C) Kit \$35.95




The XTT100 is a battery powered phone transmitter with a range of upto one mile. It only transmits when the phone is being used in order to conserve battery life.

XTT100(C) Kit \$35.95



The XBD200 quickly locates hidden transmitters from 1 to 2000 MHz by emitting an audio output proportional to the transmit level.

XBD200(C) Kit \$44.95

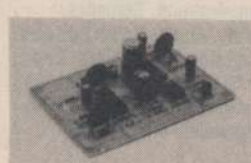

Use the XPS100 to call your home from any other phone and listen in using the built in microphone and amplifier.

XPS100(C) Kit \$45.95



The XPB1 is a telephone transmitter capable of transmitting to any FM receiver up to a 1/4 mile away. Powered by the telephone line it requires no batteries.

XPB1(C) Kit \$29.95

WE ACCEPT VISA, MC, CK, MO
COD PLEASE ADD \$6.00
CALL 1-602-829-8152 OR
WRITE FOR A CATALOG

**TOLL FREE
PHONE ORDERS
1-800-336-7389**

**MAIL ORDERS TO:
XANDI ELECTRONICS
BOX 25647
TEMPE, AZ 85285-5647**

GET THE LATEST ADVANCES IN ELECTRONICS

WITH A SUBSCRIPTION TO

Electronics Radio Combined with Electronics® NOW®



Electronics Now gives you exciting articles like:

- Buyer's Guide to Digital Oscilloscopes
- Build A Scanner Converter
- Single-Chip Voice Recorder
- Build A MIDI Interface for your PC
- Troubleshoot Microprocessor Circuits
- Build A High-Power Amplifier for your Car
- Add Music On Hold to your Phone
- All About Binaural Recording
- VGA-to-NTSC Converter

ENJOY THE WORLD OF ELECTRONICS EACH MONTH!

Subscribe to the best electronics magazine—the one that brings you the latest high-tech construction projects, feature articles on new technology, practical troubleshooting techniques, circuit design fundamentals, and much more.

Electronics Now looks to the future and shows you what new video, audio and computer products are on the horizon. What's more you'll find helpful, monthly departments such as Video News, Equipment Reports, Hardware Hacker, Audio Update, Drawing Board, Computer Connections, New Products, and more. All designed to give you instruction, tips, and fun.



FOR FASTER SERVICE CALL TODAY

1-800-999-7139

DON'T DELAY SUBSCRIBE TODAY!

Just fill out the order card in this magazine and mail it in today.

5PL23

ALL ELECTRONICS CORP.

Small Neodymium Magnet

Small, powerful neodymium magnet. Irregular shape approx. 0.64" X 0.7" X 0.1" thick. Strong for its size. CAT# MAG-5 \$1.50 each




Digital Voice Module

Ming# DVM-108. Digital recording module especially suited for reproducing verbal messages. Ideal for HAM contesting, memo recorder, verbal alarm system etc. Requires a minimum of external wiring. Up to 8 different phrase channels. Built-in 200 mW audio amp. 1 Megabit of DRAM memory, for up to 32 seconds of recording. Condenser or dynamic mike input. Board size: 3 3/4" X 2" X 1" high. Includes memory chips which require installation. Microphone and other external components not included. CAT# DVM-108 \$25.00 each




A.C. Line Cord

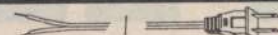6' Black 18/2 A.C. power cords. SPT-1 insulation. Polarized plug. CAT# LCAC-7 2 for \$1.00 • 100 for \$45.00 • 1000 for \$400.00



Car Lighter Coil Cord

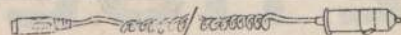

Automotive cigar lighter plug with replaceable 5 amp fuse. Quality, retractable coil cord extends to approximately 6 feet. Terminates with a 5 pin DIN plug which can be cut-off. Ideal for battery charger or running 12 Volt devices from car battery. CAT# CLP-18 \$1.50 each • 10 for \$12.50

Piezo Element

3 Wire Piezo Element. Taiyo Yuden Co. # CB358BKRA. Self-excited piezo electric diaphragm. 1.40" diameter x 0.021" thick. Resonant resistance: 400 ohms. 5" color-coded leads. CAT# PE-12 \$1.00 each 10 for \$8.50 • 100 for \$65.00



L.E.D.'s


Surface mount LED chip.

Clear when off, green when lit. Very tiny - whole unit is 0.115" X 0.055" X 0.05" thick. 1mm (0.04") lens diameter. Gold-plated mounting surfaces for superior conductivity. CAT# SMLED-2 10 for \$2.00 100 for \$18.00 1000 for \$140.00



Standard JUMBO

Diffused T 1-3/4 size (5 mm)

 

RED CAT# LED-1 10 for \$1.50 • 100 for \$13.00
GREEN CAT# LED-2 10 for \$2.00 • 100 for \$17.00
YELLOW CAT# LED-3 10 for \$2.00 • 100 for \$17.00

REDUCED PRICES FLASHING LED

W/ built in flashing circuit 5 volt operation. T 1-3/4 (5mm)




RED 50c each
CAT# LED-A 10 for \$4.75
GREEN 75c each
CAT# LED-4G 10 for \$7.00
YELLOW 75c each
CAT# LED-4Y 10 for \$7.00

LED HOLDER

Two piece holder. CAT# HLED 10 for 65c




ELECTROLUMINESCENT BACKLIGHTS

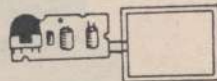

At last! A low cost electroluminescent glow strip and inverter. These brand-new units were designed to backlight small LCD TVs made by the Citizen Watch company. The inverter circuit changes 3 or 6 Vdc to approximately 100 Vac, the voltage required to light the glowstrip. Luminescent surface area is 1.7" X 2.25". The strip is a salmon color in its off state, and glows white when energized. The circuit board is 2.2" X 1". Glow strip and circuitry can be removed easily from plastic housing. Ideal for special lighting effects.

Citizen# 92TA operates on 3-6 Vdc
CAT# BLU-92 \$3.50 each
LARGE QUANTITY AVAILABLE
10 for \$32.00 • 100 for \$275.00

LCD Display 16 Character X 2 Line

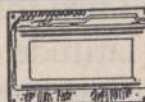

Hitachi# LM052L

Built-in controllers and drivers. Operate on 5 Vdc power. 4 or 8 bit operation. Spec. sheets and instructions included. Display size: 2.53" X 0.55". Module size: 3.15" X 1.42". Character size: (5 X 7 dots) 2.95mm X 3.8mm. CAT# LCD-5 \$12.00 each

Flash Units



NEW compact flash assemblies from a camera manufacturer. Operates on 3 Vdc. Measures 2 1/2" X 1 1/4". Ideal for use as a strobe, warning light or attention getter. Includes a hook-up diagram. CAT# FSH-1 \$3.75 each • 10 for \$35.00 100 for \$325.00

12 Volt 2 Amp Transformer


Same as Mouser #41FG020. 12 VCT, 2 Amp power transformer. 2" X 2.35" X 2.10". 2.90" mounting centers. Pigtail leads. CAT# TX-122A \$4.00 each 10 for \$37.50



Rechargeable Batteries (nickel-cadmium)

Size	Volt	Amp	Cat#	1-5	10
AAA	1.20	180 mAh	NCB-AAA	\$1.50	\$13.50
AA	1.20	500 mAh	NCB-AA	\$2.00	\$18.50
AA w/ Solder Tabs	1.20	500 mAh	NCB-SAA	\$2.20	\$20.00
Sub C w/ Solder Tabs	1.20	1200 mAh	NCB-SC	\$4.25	\$40.00
C	1.20	1200 mAh	NCB-C	\$4.25	\$40.00
C Heavy Duty	1.25	1800 mAh	HDNCB-C	\$5.25	\$42.50
D	1.20	1200 mAh	NCB-D	\$4.50	\$42.50
D Heavy Duty	1.25	4000 mAh	HDNCB-D	\$7.00	\$65.00

Motor Speed Controller And Timer

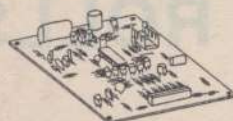

With a minimum of external wiring, this, PC board will control the speed and duration of a 120 Vac motor or other load up to 300 watts. When activated, motor will operate for 10, 20 or 40 minutes or continuously at high, medium or low speed. To simplify hook-up we recommend using our membrane keypad, (CAT# KPM-12 \$1.25 each) which, with slight modification, works well with this device. Instructions included. CAT# MSC-5 \$3.00 each

With a minimum of external wiring, this, PC board will control the speed and duration of a 120 Vac motor or other load up to 300 watts. When activated, motor will operate for 10, 20 or 40 minutes or continuously at high, medium or low speed. To simplify hook-up we recommend using our membrane keypad, (CAT# KPM-12 \$1.25 each) which, with slight modification, works well with this device. Instructions included. CAT# MSC-5 \$3.00 each

12 VDC STEPPER MOTOR



Airpax# A83712-M1
12 Vdc, 36 ohm coil, 15 degree/step. 2.25" dia. X 0.95" thick. 0.25" shaft X 0.6" long. CAT# SMT-9 \$6.00 each

ORDER TOLL FREE 1-800-826-5432

Call Or Write For A Free 64 Page Catalog Outside the U.S.A. send \$2.00 postage.

FAX (818) 781-2653 • INFORMATION (818) 904-0524

Minimum Order \$10.00 • All Orders Can Be Charged To Visa, Mastercard Or Discover Card • Checks and Money Orders Accepted By Mail • California, Add Sales Tax • No C.O.D. • Shipping And Handling \$3.50 for the 48 Continental United States • All Others Including Alaska, Hawaii, P.R. And Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MAIL ORDERS TO: ALL ELECTRONICS CORP. • P.O. BOX 567 • VAN NUYS, CA 91408

DISCOVER

VISA



47st. Photo[®]

The latest in electronics is only a phone call away! **1-800-221-7774**

In N.Y. or if busy call: 1-718-722-4750. Please mention code ES892.



AIWA CSD-EX1
PORTABLE LCD
RADIO CASSETTE CD PLAYER

- High power output
- Power saving switch plus auto stop
- 20-selection random programmable memory CD
- AM wide/FM stereo tuner

(AIW-427)
Sugg. Retail \$179.95

Our Price
\$139.95



AIWA NSX-330
30W/ch HI-FI MINI COMPONENT
SYSTEM WITH SURROUND SOUND

- Super T-bass

Includes:

- 3-preset graphic equalizer
- 5-band spectrum analyzer
- Wireless remote
- FM/AM tuner with 32-station random preset
- Dual auto reverse cass. w/Dolby B NR
- Optical digital output terminal
- 3-way speaker

(AIW-424)
Sugg. Retail \$560.00

Our Price
\$399.95



AIWA XP-7
PORTABLE CD PLAYER
WITH IN CAR USE

- 1-bit dual D/A converter
- 8-times oversampling digital filter
- Optical digital output terminal
- 24-random programmable memory
- Heat-resistant for in-car use
- Random play with 3-way repeat

Includes: Rechargeable battery BP-50, stereo headphones with remote control, AC adaptor recharger and connection cord. (AIW-420)

Sugg. Retail \$280.00

Our Price
\$249.95



CANON E-63
8mm CAMCORDER WITH
8:1 POWER ZOOM

- High speed shutter
- 180° FlexiGrip
- 2-lux low light
- Sports finder
- Wireless Remote (CAN-6300)

BONUS!
Free case
with purchase
of E-63
\$59 Value!

Super Value!



PANASONIC RQ-S35V
AM/FM STEREO CASSETTE
PLAYER WITH AUTO REVERSE

- Ultra compact size
- Digital synthesizer tuner with 7AM/7FM presets
- S-XBS & Dolby NR
- LCD tpae/radio display
- Dual clock/alarm functions
- One button wired remote

Includes: Rechargeable battery and charger. (PAN-275)
Sugg. Retail \$209.95

Our Price
\$169.95



SONY WM-WX50
WALKMAN®
STEREO
CASSETTE
PLAYER

WIRELESS HEADSET!

- Broadcasts up to 9 ft.
- Auto reverse Mega Bass 2x sound system with variable control
- Dolby NR (SON-3483)

Sugg. Retail \$249.95

Our Price
\$179.95



SHARP IQ-8400
ELECTRONIC ORGANIZER

- 256 KB memory
- Typewriter style keyboard
- Hi-contrast 40 char. by 8 line screen
- Month/week & day calendar
- 3 phone directories
- Business Card function (SHA-840G)

Sugg. Retail \$499.95

Our Price
\$319.95



PANASONIC KX-T4300
CORDLESSPHONE WITH
ANSWERING MACHINE

- 10 channel access • Rubber antenna
- Tone/pulse • 2-way paging
- 10-number speed dial • Message alert
- LED readout
- 11-function tone remote
- Auto logic operation. (PAN-4300)

Sugg. Retail \$199.95

Our Price
\$159.95



PANASONIC KX-T9000
900MHz POCKET-SIZED FOLDING
CORDLESSPHONE

- Operates on 902/928Mhz
- Sound Charger technology
- 30ch auto scan • Auto Intercom
- 2 interchangeable batteries
- 2-way paging & auto intercom
- 10, 20 digit no. auto dial
- Handset Auto switch to 'talk' mode (PAN-9000)

Sugg. Retail \$499.95

\$399.95



CASIO BP-100
BLOOD PRESSURE
MONITOR WATCH

- Water resistant to 50 meter
- 12/24-hour formats
- 3 multi-function alarms
- Altimeter, Depth meter & Barometer
- Countdown alarm
- 1/100 stopwatch (CAS-826)

Sugg. Retail \$169.95

Our Price
\$129.95



SONY XVT-600
ADD PRO STYLE SUPERIMPOSED
TITLES TO YOUR VIDEOS!

- 15 color picture computer superimposes picture title or background to video
- Draw lines, add color—endless possibilities! (SON-409)

Sugg. Retail \$600

SALE!
\$109.95



PANASONIC CTP-2066S
20" STEREO MONITOR-RECEIVER
WITH S-VHS INPUT (Over 500
lines horizontal resolution)

- Audio/Video input jacks
- Unified TV/VCR remote
- Clock, Sleep-timer & on-timer (PAN-2796)

SALE!
Sugg. Retail \$499.95
\$357.95

- Cameras
- Darkroom Supplies
- Video Equipment
- Televisions
- Hi-Fi Stereo Equipment
- Portable/Personal Audio
- Telephones
- Cellular Phones
- Computer Equipment
- Business Machines
- Calculators/Organizers
- Electronic Games
- Watches/Sunglasses
- Small Home Appliances
- Jewelry

Visit our superstores at:

67 West 47th Street **115 West 45th Street**
Bet. 5th & 6th, NYC CA. LIC. #600189-691860 Bet. 6th & 8way, NYC CA. LIC. #800191-811628

1-212-921-1287

Sun. 10:00-5:00, Mon-Thurs. 9:30-6:00, Fri. 9:30-2:00, Closed Saturday

A New York Landmark for over 26 years!

Toll-free line is open
SUN. 10-5, DAILY 8-7, FRI. 8-2
Local lines are open
SUN. 10-5, DAILY 9:30-6, FRI. 9:30-2

OVERNIGHT DELIVERY
to any point in the
continental USA
AVAILABLE
at additional cost

Mall Order Dept.:
455 Smith Street, Brooklyn, N.Y. 11231

MC1192

FREE

2 ROLLS

35mm Film

*Rave Reviews
from the
Photo Magazines*

Try this Exciting New Film!

"While (this film) has sharpness and fine grain competitive with other films of its speed, its main forte is color reproduction.

Nuances of color are held in the

prints; You can see the difference between

cherry red and tomato red"

Photographic Magazine



**100%
Satisfaction Guaranteed**

Now you can try the 35mm film *Photographic Magazine* calls the best 200 ASA print film in the World! For Free. To introduce you, we'll send you two rolls Free. Fine grain, rich color, wide exposure latitude — perfect for everyday shots. Shoot in bright or low light — indoors or outdoors. And you can order prints, slides, or both, from the same roll — without the high cost of slide film! Try this remarkable film today.

**Prints or
Slides
from
the same
roll**

SEND ME 2 ROLLS FREE!

☐ Rush me two 20-exposure rolls of your highly acclaimed 35mm film, one each at 200ASA and 400 ASA. Enclosed is \$2.00 for shipping. Limit 2 rolls per household.

FIRST NAME

LAST NAME

ADDRESS

CITY

STATE

ZIP

Mail to: Seattle FilmWorks
1260 16th Ave. W.
P.O. Box 34056
Seattle, WA 98124-1056

24526

©1991 Seattle FilmWorks. Free film offer does not include developing. Process SFW-XL.




GRABS SIGNALS FROM PHONE LINE:

CALLER I.D. - COMPUTER Interface

CHEAP SOFTWARE SAVES CALLS




SEE WHO IS CALLING BEFORE ANSWERING PHONE! PREVENT UNAUTHORIZED ACCESS MODEM, BBS, 3-FT PHONE CORD + 3-FT RS232 CABLE. UNIT HAS NO DISPLAY, USES COMPUTER SCREEN INSTEAD (SOME COM PORT SOFTWARE REQUIRED).
PCASSY/W/SEPERATE CABLES IMC4K \$39.95
FULLY ASSEMBLED/TESTED IMC4A \$45.50
SOFTWARE SHOWS CALL DATE, TIME, AREA CODE, PHONE NUMBER. SAVES ALL CALLS TO DISK. "IBM COMPATIBLE" COMPUTER OR LAPTOP
TSR "POP-UP-WINDOW" SOFTWARE IMC4SW \$7.50
(CALLER I.D. NOT AVAILABLE EVERYWHERE YET - CHECK WITH YOUR LOCAL TELEPHONE COMPANY.)

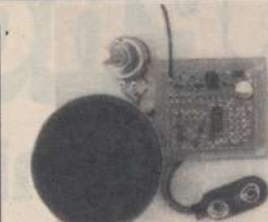

RF DETECTOR/TRANSMITTER TUNER DEVICE IS 4X AS SENSITIVE AS ANY UNIT UNDER \$100.00. PUT IT IN A BOX, ADD EXT. ANT. - MAKES A GOOD TRANSMITTER LOCATOR USE TO TUNE SMALL TRANSMITTERS. HIGHEST PITCH MEANS STRONGEST RF IMC4RF \$38.00

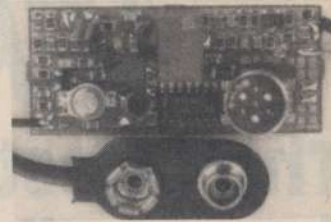CALLER I.D. GUIDEBOOK THEORY AND CIRCUITS. EVEN HAS SCHEMATIC FOR CALLER I.D. SIGNAL GENERATOR (REQUIRES SEPARATE 1200 BAUD SERIAL DATA SOURCE AND POWER SUPPLY). COVERS SINGLE & MULTIMESSAGE FORMAT AND NAME DELIVERY.
IMC4B \$18.50 (\$13.95 WITH IMC4A or K)



REALLY DIFFERENT MINIATURE SURFACE MOUNT TRANSMITTERS HAVE CRYSTAL-CLEAR SOUND. 25-TURN TUNING IS STABLE. RANGE ABOUT 500 FT. ROOM MICROPHONE VERSION IMC4F \$39.95
AUTO-SWITCH PHONE VERSION IMC4T \$39.95
(SURFACE MT. COMPONENTS PRE-ASSEMBLED)

International MicroPower Inc.
65 Palm Drive
Camarillo, CA 93010
1-800-992-3511
ORDERS ONLY MC or VISA Accepted
(Sorry, we do NOT print a catalog.)

56 PAGES - EASY
TO UNDERSTAND

CALLER I.D. Guidebook

INCL 8 PAGES OF
SCHEMS & DIAGRAMS

PE MARKET CENTER CLASSIFIEDS

Cable Aids Test

Orders only
1-800-452-7090

Information
(213) 867-0081

Test chips for JERROLD, TOCOM, ZENITH, S.A. & more. Fully activates units in just minutes. Easy installation. Zenith only \$39.95ea. Most others only \$50ea.

No Ch. miles. Not for use in cable co. owned equip. For use as a test aid only.

CABLE TV

"BULLET" BUSTER. Protect your cable box against the infamous "bullet." The "Bullet" Buster acts as an electronic shield. Installs in-line in seconds. Don't wait until it's too late! \$19.95 plus \$3.00 S&H. ELECTROMAN, Dept. RE, PO Box 24474, New Orleans, LA 70184.

TRI-BI PROBLEMS? Flashing? Intermittent scrambling? Black lines? Don't throw that Tri-Bi away! VIDEOTRON can modify them for the Starcom 6 and 7 systems. \$25.00 per unit shipped. Jerrold 400 and 450 converters factory reconditioned with new remotes. \$55.00 single, \$50.00 5/lot. 400 and 450 remotes \$15.00 each. All units tested before shipping. Send check or M/O to VIDEOTRON, 6315 Nebraska St., Hammond, IN (219) 989-9789.

CABLE STEALTH: protect yourself from descrambler detection and stop the "bullet." Preset and tested, only \$24.99 plus \$4.00 S&H. Money order or COD orders only. BALDWIN ELECTRONICS, Box 9291, Balto., MD 21222-0291.

COMPUTER SOFTWARE

THOUSANDS OF IBM SHAREWARE PROGRAMS. \$3.00 S&H for 2 disks full plus catalog disk. American Software, PO Box 509, Suite M6, Roseville, MI 48066-0509.

IBM COMPUTER PROGRAMS \$1.99! Windows, business, home, games, fonts, art UNCONDITIONALLY GUARANTEED. Free catalog 1 (800) 723-0658 Ext. 119.

ELECTRONICS SOFTWARE. From \$2.00 per disk. IBM 5.25". Free catalog on disk. GENERIC SOFTWARE, POB 502, Dayton, OH 45401.

EXPLORE OUR incredible software catalogs which include fascinating rentals, the newest shareware, affordable public domain, sizzling movies and pictures. Plus super specials of the month with prices that are slashed-to-the-bone! Plenty of success-guaranteed video and audio programs too! But wait! There's more, just mention Popular Electronics and we will throw in 6 powerful programs (our choice). Just include \$3.00 (refundable) for shipping 2-360K disks, or \$3.50 (refundable) for shipping 2-720K disks, and you'll get our 3 part storehouse of knowledge catalogs above, plus the 6 powerful IBM compatible programs free! You only send shipping!! **BEACH RADIO**, Dept., PE, PO Box 548, Boston, MA 02112-0548.

MISCELLANEOUS ELECTRONICS FOR SALE

GOVERNMENT SURPLUS test equipment, and parts. Free catalog. EF Electronics, Box 326, Aurora, IL 60507.

REMOVE TAMPER resistant security screws, deluxe 30-pc. set \$29.95 plus \$4.50 S&H. Send SASE for more information. **Sunset Electronics**, 12145 Alta Carmel Ct., Suite 250-139, San Diego, CA 92128.

SURVEILLANCE

COUNTERSURVEILLANCE Electronic Devices
Miniature Transmitter Kits.. \$29.95
Voice Changers, Phone Scramblers, Vehicle Tracking, Phone Recording Systems, Bug & Phone Tap Detectors, & More!

CALL IDENTIFIER device • displays callers phone number before you answer with date & time of call...\$49.95

FOR CATALOG SEND \$5.00 TO...
EDE P.O. Box 337, Buffalo, NY 14226 (716) 691-3476

AUDIO-VIDEO-LASERS

IBM PC and laptops video digitizer. Connects to camcorder. 640 by 480 resolution. 256 gray levels \$89.98. Demo disk \$3.00. Information \$1.00. Colorburst, Box 3091, Nashua, NH 03061. Phone (603) 891-1588.

COMPUTER HARDWARE

IBM PC and laptops video digitizer. Connects to camcorder. 640 by 480 resolution. 256 gray levels \$89.98. Demo disk \$3.00. Information \$1.00. Colorburst, Box 3091, Nashua, NH 03061. Phone (603) 891-1588.

EDUCATION

LEARN TO EARN. Increase your income with electronic skills. Courses written for easy learning. Most courses \$49.50 or less. Electronic parts and equipment also sold. Send \$2.00 for catalog to A&A Products, Rt 1, Box 482-L, Rockdale, TX 76567.

BARCODES BARCODES BARCODES they are everywhere you look! Now you can get in on an industry that is growing by 20% each year with **THE BARCODE COURSE**. This course comes complete with a detailed barcode textbook, portable barcode reader, RS232 interface and barcode printing software for only \$149.95 + \$7.00 S&H. OBR Inc., RR3 Box 47-7, Carbondale, IL 62901. (618) 549-7100.

ANTIQUE ELECTRONICS

TUBES, PARTS (Old stock from closed or bankrupt Radio-TV stores). Extensive listings in 16 page illustrated catalog: \$2.00. Don Diers, 4276 North 50th Street #MC4, Milwaukee, WI 53216-1313.

EXERCISE

Does Your Heart Good.

American Heart Association

AMAZING ELECTRONIC PRODUCTS and KITS

NEW CONCEPT! Mystery Levitating Device



Remember War of the Worlds? Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or great science project.
ANT1K Easy to Assemble Kit / Plans \$19.50

Combination Solid State Tesla Coil & Variable 100,000VDC Generator




Experiments Using Tesla Coil:
• Plasma in a Jar/Tornado, Furnace
• Kirlian Photography
• Wireless Energy Transmission
• Induction Fields • Pyrotechnic Effects
• Corona and Brush Discharge
• Energizer for Neon Plasma Tubes

Experiments Using Hi Volts DC:
• Plasma Blaster Driller/Cutter
• Anti-Gravity/Force Fields
• Ion Reaction Motors
• Lightning Generation
• High Ion Source
• Ozone For Air Purification
• Electrification of People & Objects
• Particle Accelerators/Atom Smashing
• High Energy Capacity Charging

HVM7 Plans Complete System \$15.00
HVM7K Complete System Kit/Plans \$174.50
TCL4K Tesla Coil Only Kit/Plans \$99.50
115/19AC Wall Adapter for 115AC \$15.50


Table Top Tesla Coil

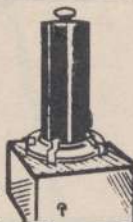**Spectacular -
A Real Attention Getter!**
• 250,000 Volts! • 7-10" Sparks!
Energy even passes through windows. Great for science projects, displays, advertising.



Highly spectacular devices produces visible, audible bolts of lightning appearing to flash in the air. Causes certain materials to burn from within and glow, lights bulbs without wires, produces induction fields, St Elmo's fire corona. Clearly demonstrates high frequency high voltages yet terminal may be touched by user during operation with a metal object. 115VAC operation only.
BTC3 Plans ... \$15.00 BTC3K Kit/Plans \$299.50
BTC30 Assembled and Tested \$399.50


Plasma Fire Saber

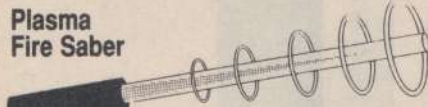

Produces the spectacular effect that captured the fantasy of millions of movie fans. Visible plasma field is controlled by grip pressure and adjusts saber length. Active energy field produces weird & bizarre effects. Excellent for special effects. Specify photon blue, neon red, phasor green, or starfire purple.
PFS2 Plans \$8.00 PFS2K Kit/Plans \$49.50
Special Offer PFS20 Assembled reg \$89.95, \$59.50

Solar Power Devices

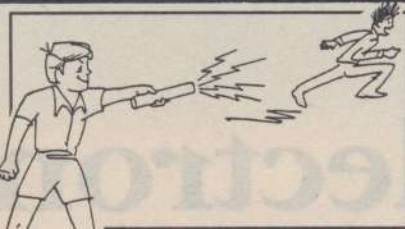Build a fence shocker, solar motor, light, bug zapper, batt charger, etc. **SOL1 4", 2 Amp Cell w/Plans .. \$8.50**
SOL2 6x12", 14 V Cell w/Plans \$7.50



Shocker Force Field / Vehicle Electrifier

Neat little device allows you to make hand and shock balls, shock wands and electrify objects, charge capacitors. Great pay back for those wise guys who have wronged you!
SHK1KM Easy To Assemble Electronic Kit . \$24.50

100,000V Intimidator / Shock Wand Module

Build an electrical device that is effective up to 20 feet. May be enclosed for handheld, portable field or laboratory applications.
ITM2KM Easy to Assemble Electronic Kit ... \$49.50
ITM2 Plans Only; Credit-able to Kit \$10.00

Ion Ray Gun - Projects charged ions that induce shocks in people & objects without any connection! Great science project as well as a high tech party prank.

IOG3 Plans \$10.00 IOG3K Kit/Plans \$69.50

Invisible Pain Field Generator

Shirt pocket size electronic device produces time variant complex shock waves of intense directional acoustic energy capable of warding off aggressive animals, etc.
IPG7 Plans \$8.00 IPG7K Kit / Plans \$49.50
IPG70 Assembled \$74.50

Homing / Tracking Transmitter

Beeper device, 3 mile range.
HOD1 Plans \$10.00 HOD1K Kit/Plans \$49.50

Listen Thru Walls, Floors

Highly sensitive stethoscope mike.
STETH1 Plans ... \$8.00 STETH1K Kit/Plans \$44.50

3 Mile FM Wireless

Mike - Subminiature!
Crystal clear, ultra-sensitive pickup transmits voices and sounds to FM radio. Excellent security system, warns of intrusion. Become your neighborhood disk jockey! Monitor children and invalids.
FMV1 Plans \$7.00 FMV1K Kit/Plans . \$39.50

Telephone Transmitter - 3 Miles!

Automatically transmits both sides of a telephone conversation to an FM radio. • Tunable Frequency
• Undetectable on Phone • Easy to Build & Use
• Up to 3 Mile Range • Only transmits during phone use
VWPM7 Plans \$7.00 VWPM7K Kit/Plans \$39.50

ElectroMagnetic Coil Gun

Projects a metal object over a considerable distance. Become part of and perhaps contribute to this exciting new concept of weaponry.
EML2 Plans \$8.00 EML2K Kit/Plans \$99.50



NEW! Amazing GlowTron!

Projects visible energy. Operates on safe, low voltage to produce spectacular lighting effects. Neon & fluorescents glow without wires!
GTRON Ready to Use \$29.50



TV & FM Joker / Jammer - Shirt pocket device allows you to totally control and remotely disrupt TV or radio reception. Great gag to play on family or friends. Discretion required.

EJK1KM Easy to Assemble Electronic Kit . \$19.50

Visible Beam Laser

High brightness red HeNe laser visible for miles. **Produce your own light show!** Projects a beam of red light clearly visible under most circumstances. Can be used to intimidate by projection of a red dot on target subject. Also may be used to "listen in" utilizing our laser window bounce method #LLIS1 below. **Easy to Build Modules Produce A Working Visible Laser:**
LAS1KM Kit w/1mw Laser Tube, Class II . \$69.50
LAS3KM Kit w/2.5mw Laser Tube, Class IIIA \$99.50



"Laser Bounce" Listener System

allows you to hear sounds from an area via a lite beam reflected from a window or other similar object. System uses our ready-to-use LATR1 Laser Terminator gun site as the transmitter. The receiver section is supplied as an easy-to-build kit, including our cushioned HS10 headsets. **Order # LLIST20 System, includes our LATR1 Ready-to-Use Laser Gun Site, LLR1K Special Receiver Kit, and HS10 Headset, all for only \$299.50**

5mw Visible Red Pocket Laser

Utilizes our touch power control!
VRL3KMX Kit / Plans \$119.50

See In The Dark Viewing

Device uses invisible infrared illumination for seeing in total darkness. Excellent for low cost night vision, along with observing lasers and other IR sources. Functional unit, many useful applications.
SD5 Plans \$10.00
SD5K Kit / Tube / Plans \$299.50
GPV10 Ready to Use Viewer \$499.50
6032A Tube / Plans to build your own ... \$99.50



INFORMATION UNLIMITED


Dept PEM10, Box 716, Amherst, NH 03031
Phone: 603-673-4730 FAX 603-672-5406
MC, VISA, COD, Checks Accepted. Please Add \$5.00 Shipping & Handling

Catalog

with many more items
**FREE with Order,
Or Send \$1 P&H**



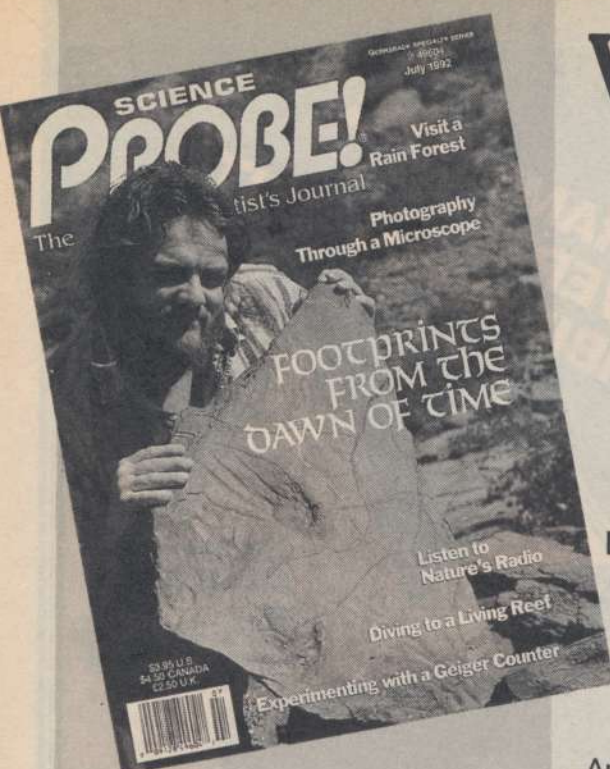**Order by Mail,
or by 24 Hour
Orders-Only Phone:
800-221-1705**



Welcome to...

SCIENCE PROBE!®

The Amateur Scientist's Journal

Embark on an irresistible new journey into the realm of mystery, challenge, and exploration! The perfect magazine for the budding scientist, the serious amateur, the professional who would like to relax, and those who simply want to gaze at the stars.

Science PROBE! — the *only* magazine devoted entirely to Amateur Scientists! If you are fascinated by science in all its many forms... if you can't stay away from a microscope, telescope, calipers, or test tube — we invite you to share the wonders in every issue of **Science PROBE!** You will join a community of Amateur and Student Scientists who enthusiastically seek scientific knowledge or follow scientific pursuits for their own sakes and not merely as a profession.

Obtain your next issue of **Science PROBE!** by visiting a quality Newsstand, Convenience Store, or Supermarket or by reserving your personal copy through the mail by completing the coupon below.

From your very first issue of **Science PROBE!** you will be involved in a world of scientific facts, experiments, and studies pursued by amateur scientists who are university students, investors, academicians, engineers, or office workers, salesmen, farmers—whose *quest* is to probe into the mysteries of science and reveal them to all.

Plan to become a **Science PROBE!** reader!

Articles to appear in upcoming issues of **Science PROBE!** are:

Inside Internet—A Scientific Computer Network
Make your own Seismometer
Operate a Solar-Powered Weather Station
Assemble a Solid-State Portable Barometer
The Bicycle—A Traveling Scientific Laboratory

If you're fascinated by science in all its many forms, if you are compelled to experiment and explore, then **Science PROBE!** is your kind of magazine!

For Faster Service—Call Today:
1-800-777-5489

Science PROBE!
 500-B Bi-County Boulevard
 Farmingdale, NY 11735

7PL21

Please forward my copy of **Science PROBE!** as soon as it comes off the press. I am enclosing \$3.50-U.S.A. (\$4.23-Canada-includes G.S.T.) plus \$1.00 for shipping and handling. Better still, please enroll me as a subscriber and send the next four (4) quarterly issues of **Science Probe**. I am enclosing \$9.95-U.S.A. (Canada: \$16.00—includes G.S.T.)

☐ Next Issue Only ☐ Next Four Issues (1 Year)
 Offers valid in the U.S.A. and Canada only. No foreign orders.

Name _____

Address _____

City _____


State _____

ZIP _____

All Orders payable in U.S.A. Funds only.

ON SALE AT QUALITY NEWSSTANDS, CONVENIENCE STORES AND SUPERMARKETS
GET YOUR COPY TODAY—\$3.50-U.S.A.—\$3.95-Canada

The Electronics Lab in a Computer!

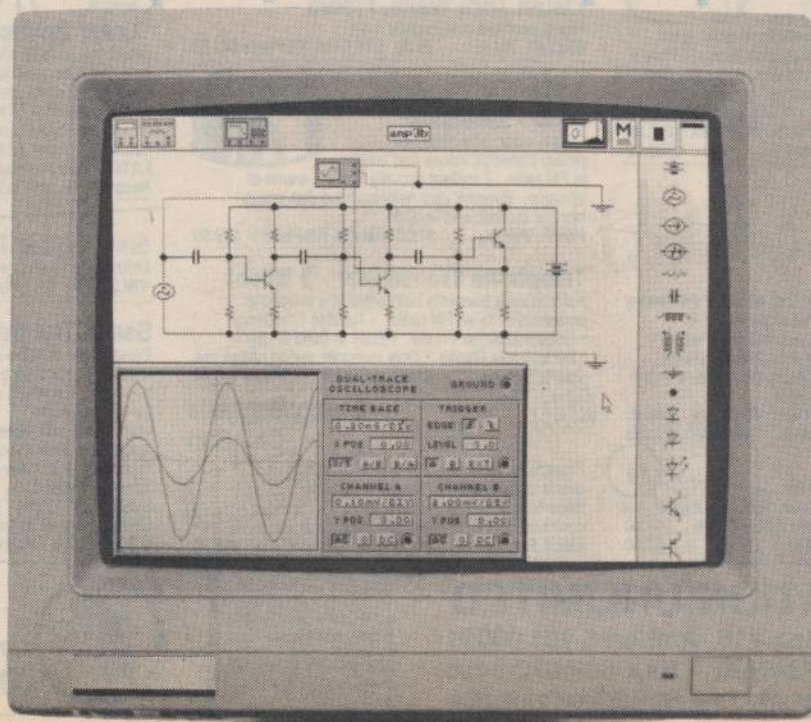

Testing an analog three-stage amplifier with the simulated oscilloscope.

HOT! NEW!

- DESCRAMBLERS
- CONVERTERS
- COMBINATION UNITS

SCIENTIFIC ATLANTA 8590

Features

- Wireless Remote Control
- Favorite Channel Recall
- Parental Lockout
- Volume Control

**BRAND NEW
1 YEAR
WARRANTY**

\$259⁰⁰ 6-10 **\$275** 1-5

SCIENTIFIC ATLANTA 8580

Features

- Wireless Remote Control
- Favorite Channel Recall
- Parental Lockout

**BRAND NEW
1 YEAR
WARRANTY**

\$199⁰⁰ 6-10 **\$225** 1-5

**WE'LL BEAT
ANY PRICE!**

ADD ON DESCRAMBLERS

	1-5	6-10
FTB-3	49.00	39.00
TVT OR TBI	55.00	47.00
SA-3	59.00	49.00
KN12-3	59.00	49.00
P 10-3 OR PIO-3+	59.00	47.00
MLD1200-3	49.00	39.00

CONVERTERS

	1-5	6-10
PANASONIC 1453G	75.00	65.00
JERROLD DQN7-3	75.00	65.00
JERROLD 400	49.00	39.00

LATEST DESCRAMBLER MODELS

Add On Descrambler for all JERROLD Systems (Except Base Band) Guaranteed to Work Anywhere Coast to Coast (Model JD-3)

\$125 6-10
\$159 1-5

Add On Descrambler For All PIONEER Systems. Guaranteed to Work Anywhere Coast to Coast. (Model PD-3)

\$125 6-10
\$159 1-5

Add On Descrambler For All SCIENTIFIC ATLANTA Systems (Except 8570, 8590, 8600). Guaranteed to Work Anywhere Coast to Coast. (Model SAD-3)

\$89 6-10
\$119 1-5

**JP
VIDEO**

1470 OLD COUNTRY ROAD,
SUITE 315 - P.E.
PLAINVIEW, NY 11803
NO NY SALES

FREE COLOR CATALOG!

1-800-950-9145

Electronics Workbench®

Powerful software to build and simulate
analog and digital circuits.

Building and testing circuits is fast and easy with *Electronics Workbench*. Just click-and-drag with a mouse to add parts, run wires, and adjust instruments. The traces on the simulated instruments are the same as you'd get on real equipment.

Electronics Workbench really is an electronics lab in a computer. It's ideal for learning about electronics, experimenting, and prototyping circuits.

Includes:

- **Analog Module** with passive and active components including transistors, diodes, and op-amps; a function generator, an oscilloscope, a multimeter and a Bode plotter.
- **Digital Module** with gates, flip-flops, adders, a word generator, a multimeter, a logic analyzer and a unique logic simplifier.

DOS Professional Version - \$299


Macintosh Version - \$199

(416) 361-0333

Interactive Image Technologies Ltd.

908 Niagara Falls Boulevard,
North Tonawanda,
NY 14120-2060

Fax (416) 368-5799

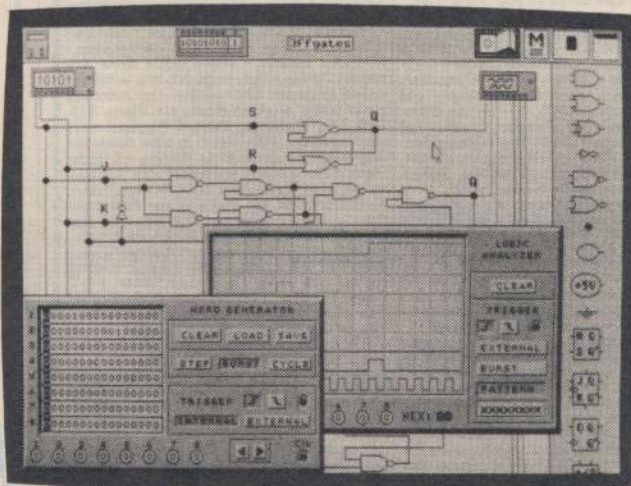

Testing a gate implementation of three different flip-flops.

"Electronics Workbench is pretty amazing."

- Jerry Pournelle, Ph.D., InfoWorld

"... Electronics Workbench is a marvelous learning and teaching tool for the study of electronics."

- Art Salsberg, Editor-in-Chief,
Modern Electronics Magazine

"Building a circuit is simple and intuitive."

- Jeff Holtzman, Computer Editor,
Radio-Electronics Magazine

"... if you're trying to learn electronics, you can do 10 times as many experiments with Electronics Workbench..."

- Jerry Pournelle, Ph.D., BYTE



Electronics Workbench Professional Version runs on any IBM AT or PS/2 or true compatible with 640 KB RAM; Microsoft-compatible mouse; EGA/VGA graphics; hard disk; MS-DOS 3.0 or later. Monochrome version also available. Macintosh Version (monochrome only) runs on Macintosh Plus or greater. All trademarks are the property of their respective owners. Prices are in US dollars. Offer valid in the USA and Canada only.

TOP SECRET



CONSUMERTRONICS

2011 Crescent Dr., P.O. Drawer 537
Alamogordo, NM 88310

Add \$4 S/H (USA, Canada). All items in stock. COD (UPS cash only), VISA, MasterCard OK. New Catalog is \$2 with order, \$4 without. In business since 1971. As seen on TV, etc. John Williams - former Lockheed Senior Engineer, NMSU Professor of Computer Science, NIH Health Physicist. Educational purposes only.

*All software supports all IBM-PC compatible systems (8086 - 80486)

VOICE LINES: 8AM - 9PM MST, Mon - Sat
FAX (orders only): 24-hour, 7 days/week

(505) 434-0234, 434-1778

FAX: (505) 434-0234 (if you get answering machine press #4, then #1 any time)

Off-The-Shelf HARDWARE

Van Eck Systems, Automated Tempest Module, KX Radar Emitter, Voice Disguiser, Shriek Module, Hearing Assistant, EM Countermeasure, TENS, 6th Sense Communicator, Bumper Beeper, Subliminal Mixer/Amp, Super MWO, Hieronymus Machine, Neurophone, MU Magnetometer, Dwelling Security System, Levitator, Stealth Paint - more! See details in new Catalog.

SPECIAL PROJECTS

We design, build, repair, modify, maintain and/or consult on any device, system, process, project (electrical, electronic, computer, phone, mechanical, optical, automotive). Invention prototyping. Confidentiality guaranteed. Describe and include \$25 fee (does not obligate you). Time and cost estimates in 7-10 days.

CELLULAR PHONE MANUAL

How cellular phones are designed, operated, re-programmed. How cellular systems are vulnerable to hack attacks, and countermeasures. Comprehensively describes modifying NAMs and ESNs (includes specific info. on 30+ popular models), scanning, scanner restorations (includes UHF TV method), freq and channel allocations, roaming, tracking, ECPA - more! \$39.

VOICE MAIL BOX HACKING

How Voice Mail Box (VMB) systems are used and the specific ways they are hacked. Includes ASPEN, MESSAGE CENTER, BIX, EZ, SYDNEY, PHONE MAIL, AUDIX, etc. Absolutely required for all users and sysops! \$29

PHONE COLOR BOXES

As designed by Phone Phreaks! 15 phone color boxes described. Dozens of circuits, simulator programs. Plus call forwarding, conferencing, phreak history, 50 useful and legal phone circuit plans - more! \$29.

COMPUTER PHREAKING

TROJAN HORSES, VIRUSES, WORMS, etc. and countermeasures. Includes disk with 360K of hacker text files and utilities, and legendary FLUSHOT+ protection system (Ed. Choice, PC Magazine). Dozens of computer crime and abuse methods and countermeasures. How systems are penetrated. BBS advice, password defeats, glossary - much more! Manuals + Disk* \$39.

BEYOND VAN ECK PHREAKING

Eavesdropping on VDT and TV video signals using an ordinary TV! Documented in security industry literature. Range up to 1KM. Plans include both the CONSUMERTRONICS and the original TOP SECRET VAN ECK designs! \$29.

CRYPTANALYSIS TECHNIQUES

Five powerful menu-driven crypto programs (in .COM and their .BAS sources) to analyze, decrypt "secure" ciphertexts. Worked-out examples. Recommended in prestigious COMPUTERS & SECURITY. Manual + Disk* \$29.

ABSOLUTE COMPUTER SECURITY

Dozens of simple, versatile, secure methods and tips. Plus our invulnerable Cipher Program (in .COM and its .BAS source). Plus \$1,000 CIPHER CONTEST ciphertext and rules. Manual + Disk* \$24.

HARD DRIVE MANUAL

Covers all hard drive and controller implementations (emphasis on PCs). How to select, interface, initialize, set up, use, maintain, troubleshoot and repair them. How to protect them from mistakes, sabotage, prying eyes and sticky fingers. How to recover damaged and lost files. How to prevent crashes to begin with. Includes software reviews. Loaded with information, advice, tips. \$29.

DISK SERVICE MANUAL

Maintain, troubleshoot, repair, adjust, align floppies Without special equipment or software. 3.5"/5.25"/8", PC/XT/AT/386/486, Apple, Commodore, etc systems. All floppies need regular upkeep. \$29. DISK DRIVE TUTORIAL: Theory, practical facts on floppy drives, disks, including many tips, recommendations, formatting, interfacing, FDC, etc. \$19. Both \$39.

AUTOMATIC TELLER MACHINES

ATM crimes, abuses, vulnerabilities and defeats exposed! 100+ methods detailed, include: Physical, Reg. E, cipher, PIN compromise, card counterfeiting, magnetic stripe, false front, TEMPEST, Van Eck, tapping, spoofing, inside job, super-cool, vibration, pulser, high voltage - others. Case histories, law, countermeasures, detailed security checklist, labeled internal photos, figures. ATMs contain up to \$250,000 in cash! Recent \$350,000 ATM crime spree still unsolved! \$39.

CREDIT CARD SCAMS

Cardholders, merchants and banks suffer \$ Billions in losses annually because of credit card fraud. Describes every known means of credit card fraud and scams. Protect yourself! \$29.

CONS & SCAMS

Cons & scams (legions) Americans of \$100+ billion per year! The most comprehensive survival manual on cons & scams of all kinds - from the classic to the high-tech. Details on 100s and their many variations. Protect yourself! \$29.

STOPPING POWER METERS

As reported on CBS "60 MINUTES": How certain devices can slow down - even stop - watt-hour meters - while loads draw full power! Device simply plugs into one outlet and normal loads into other outlets. Also describes meter creep, overload droop, etc. Plans. \$19. THE I.G. MANUAL: External magnetic ways (applied to the meter itself) to slow down and stop watt-hour meters while drawing full loads. Plans. \$19. KW-HR METERS: How watt-hour meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow and stop meters by others. \$19. Any 2, \$33. All 3, \$47.

HIGH VOLTAGE DEVICES

HV devices plans: Stun Gun, Taser, Prod, Cane, Flasher, Blaster, Zapper, Audio/RF/Radar Jammer, Jacob's Ladder, Plasma & Van de Graaff Gens., Fence Charger, Geiger Counter, Ozone Gen., Fish Stunner, Plant Stim., Kirlian, more! Shocking! \$29.

UNDER ATTACK!

Electromagnetic Interference and Electronic Weapon Attacks can cause: Cancer, birth defects, and profound psychological, neurological, cardiovascular and immune system disorders! Destructive to people, animals, plants, equipment! Includes ACTUAL CASES OF EM ATTACKS ON PEOPLE (we investigated) - more common than believed! Includes how to verify and pinpoint EMI and electronic attack sources, and specific countermeasures. \$29.

EM BRAINBLASTER

Tutorial and plans for powerful ELECTROMAGNETIC WEAPONS and LAB DEVICES. Optimum circuits, freqs, waveforms, duty cycles, intensities. Comprehensive. \$29.

RADIONICS MANUAL

Exciting electrical, electronic and electromagnetic therapeutic, diagnostic and preventive devices (mostly experimental). History, descriptions, plans (dozens), availabilities of Radionics Devices from early to modern. While drugs cost \$ Hundreds, electricity costs pennies! \$29.

ROBOFONE AUTODIALER

Powerful, versatile, menu-driven "Wargames" autodialer lets you dial any quantity (up to 10K) or mix of local/long distance numbers in any order, over any length of time, whether busy or answered (your choice) and log the times, commands and results to monitor, printer and/or disk. Quick-dial directory of up to 600 numbers, BUSY redial options. Direct modem command and control. All Result Codes, including VOICE and RINGING. Optional shell to terminal program upon CONNECT. Exit to menu or DOS (for batching). Manual + Disk* \$29.

SOFTWARE PROTECTION SYSTEM

Unique system that highly discourages costly software piracy while not interfering with legit archival copies. No known way to defeat. No special equipment required. Simple and automatic to install on your distributed software. Compatible with all other copy-prevention systems. Manual + Disk* \$59.

SECRET & SURVIVAL RADIO

Optimum survival and security radio equipment, methods, freq allocations and voice/data scrambling/encoding. Includes small receivers/transmitters, telemetry, antenna optimizations, remote monitoring and control, security, surveillance, and ultrasonic, fiberoptic and infrared commo. 70+ circuit plans, tables. \$29.

STEALTH TECHNOLOGY

Police radar is fascinating! It also has error rates of 10-20%! Every known error mode - stealth method and material used to minimize radar reflections - tactic and strategy to fight unjust radar tickets (that cost you \$100s in insurance and risk cancellation) - methods to detect and jam signals - fully described! \$29.


ROCKET'S RED GLARE

How to design and build solid-propellant amateur and survival rockets. Emphasis on formulation, manufacture, installation of propellants, motors, igniters, etc. Includes list of commonly available materials, and the design of launch pads and test beds and their electronics. \$29.

Low Cost CAD Software

for the IBM PC and Compatibles

Now for DOS and Windows™

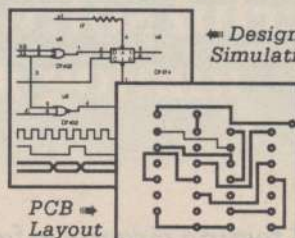

- * Easy to use schematic entry program (SuperCAD) for circuit diagrams, only \$99. Includes netlisting, bill of materials, extensive parts libraries, dot matrix printer output. More parts, HPGL plotter and laser printer output available separately or in enhanced CAD package (SuperCAD+) for only \$199. New Windows version available.
- * Powerful, event-driven digital simulator (SuperSIM) allows you to check logic circuitry quickly before actually wiring it up. Works directly within the SuperCAD editor from a pull-down menu and displays results in "logic analyzer" display window. Starting at \$99, this is the lowest cost simulator on the market. Support for PALs, a larger library, and a separate interactive logic viewer are available in full-featured SuperSIM+ for only \$395. Library part models include TTL, CMOS and ECL devices. New Windows version available.
- * Circuit board artwork editor and autorouter programs, starting at \$99 each. Produce high quality artwork directly on dot matrix or laser printers. Separate plotter driver available for \$49. You can do both single or double-layer boards with plated through holes. Includes drill hole listing utility. Autorouter accepts netlists and placement data directly from the SuperCAD schematic editor.
- * All software comes with complete documentation and 30-day money-back guarantee.

Write or call for further information and free demo disks:

MENTAL AUTOMATION, INC.

Mental Automation, Inc.

5415 - 136th Place S.E.

Bellevue, WA 98006

(206) 641-2141

FAX (206) 649-0767



CABLE TV

Converters & Descramblers

Compatible with

Jerrold, Scientific Atlanta,
Pioneer, Oak, & Hamlin
Equipment

BRAND NEW!

90-DAY GUARANTEE

LOWEST PRICES

Volume Control & Parental Lockout Available

Greenleaf Electronics

1-800-742-2567

NO ILLINOIS SALES

It is not the intent of Greenleaf Electronics to defraud any pay television operator and we will not assist any company or individual in doing the same.

NO PROBLEM

You want a bargraph & a full range counter – Optoelectronics can deliver!

\$199.

*Don't Wait,
This Offer Can't Last!
No discounts, No trade-ins.*

Now for a limited time only, \$160. off the list price. for our Full Range Model 2810 with bargraph – plus:

- Full range -10Hz to 3GHz.
- LCD display (daylight visibility).
- True state-of-the-art technology with the high speed ASIC.
- NiCads & Charger included.
- Ultra-high sensitivity.
- 4 fast gate times.
- Extruded metal case.
- Compatible with MFJ207.

Suggested options

TA100S:

Telescoping Whip Antenna.....\$ 12.

CC30

Vinyl Carry Case.....\$ 15.

BL28:

EL Backlight for use in roomlight and low light.....\$ 45.

TCXO 30:

Precision ± 0.2 ppm 20 to 40°C temp. compensated time base\$100.

**Made in
the USA**



Universal
Handi-Counter™
Model 3000, \$375. and
Bench Model 8030, \$579.
Both offer frequency,
period, ratio and time
interval.

OPTOELECTRONICS

Call for free catalog - Factory Direct Order Line:

1-800-327-5912

FL (305)771-2050 • FAX (305)771-2052

5821 NE 14th Ave. • Ft. Lauderdale, FL 33334
5% Ship/Handling (Max. \$10) U.S. & Canada.
15% outside continental U.S.A.
Visa and Master Card accepted.

CIRCLE 27 ON FREE INFORMATION CARD

R U ↑ 2 the Challenge?



From budding enthusiasts to electronic whizzes, robot fanciers won't be able to resist the challenge to assemble our new series of OWI's educational electronic robot kits.

If you liked MOVITS, you're ready for the next step. OWIKITS have NO pre-assembled parts. It's up to you to solder your own circuit boards and create one the many kits available from OWI.

Take the Challenge. Let the adventure begin.



OWI Incorporated

1160 Mahalo Place
Compton, CA 90220
310.638.4732
FAX: 310.638.8347
1.800.638.1694
E & K Kroeger, Inc.
416.752.4382

Canadian Distributor:


LASERS

HELIUM NEON FROM \$19
ARGON * BOOKS
CO² * PLANS
OPTICS * LIGHTSHOWS
LASER DIODES
LASER POWER SUPPLIES



LASER USES:
HOLOGRAPHY * LIGHTSHOWS
PRINTING * COMMUNICATION
WEAPON SIGHTS * ALIGNMENT
ALARMS * POINTERS
CUTTING * CONSTRUCTION

FREE CATALOG 1-800-356-7714

 

198 LEWIS COURT
CORONA, CA 91720

CIRCLE 38 ON FREE INFORMATION CARD

FACTCARDS



■ ALL YOU NEED to know about electronics from transistor packaging to substitution and replacement guides. FACTCARDS numbers 34 through 66 are now available. These beautifully-printed cards measure a full three-by-five inches and are printed in two colors. They cover a wide range of subjects from Triac circuit/replacement guides to flip-flops, Schmitt triggers, Thyristor circuits, Opto-Isolator/Coupler selection and replacement. All are clearly explained with typical circuit applications.

■ WANT TO EXPAND your knowledge of electronics? Do it the easy way

by studying the Electronics Fact Cards. Do you travel to and from your job each day? Drop a handful of cards in your pocket before you leave, and the bus becomes a schoolroom! At home, you can build some of the projects and not only have fun building and using them, but learn how they work at the same time.

■ YOU'LL BE AMAZED both at how rapidly you learn with these cards, and how easy it is to understand. These new cards are available right now. Don't miss out. Send your check or money order today.

FACTCARDS—Facts at your fingertips for Experimenters and Project Builders!

- ☐ Please send one copy of FACTCARDS at \$3.50. Shipping \$1.00 (U.S. and Canada only).
- ☐ Please send _____ copies of FACTCARDS. Total cost is sum of copy price and First Class postage and handling cost multiplied by number of card sets ordered.

New York residents add sales tax to total cost of each order.

Please print

Allow 6-8 weeks for the material to arrive.

(Name)

(Street Address)

(City)

(State)

(Zip)

Detach and mail today:
CLAGGK Inc.
P.O. Box 4099
Farmingdale, NY 11735

All Payment must be in U.S. Funds!

**Jampacked with
information at your
fingertips**

FROM

\$19⁹⁵

Standard

\$199⁹⁵

High Performance

GREAT
VALUE!**Standard Features - Models 100, 150, 200 & 400**

- AC & DC VOLTAGES ● DC CURRENT ● RESISTANCE
- CONTINUITY TESTER - Buzzer ● DIODE TEST ● 3 1/2 Digit LCD
- LOW BATTERY INDICATOR ● ACCURACY +/- 0.5% RDG

Kelvin Meters backed by a
2 Yr Warranty - Parts & Labor

100 Basic



150 Basic+



200 Advanced

PRO 400



BATTERY TEST

KELVIN
990087
100 Basic
\$19⁹⁵

TRANSISTOR hFE
BATTERY TEST

KELVIN
990090
150 Basic+
\$29⁹⁵

TRANSISTOR hFE
CAPACITANCE
AC/DC CURRENT
KELVIN
990091
200 Advanced
\$39⁹⁵

20MHz FREQ
COUNTER
AC/DC CURRENT
CAPACITANCE
LOGIC TEST
TRANSISTOR hFE
LED TEST -
VERIFY GOOD/BAD
KELVIN
990092
PRO 400
\$69⁹⁵

Protective Cases

For Models 100, 150, 200 \$4.⁹⁵ (990088)
Case For Model Pro 400 \$9.⁹⁵ (990094)

Model 92
PERFORMANCE PLUSModel 93
DIAGNOSTIC PLUSModel 95
ENGINE ANALYZER PLUS**Standard Features - Models 92, 93, 94 & 95**

- DC/AC VOLTMETERS ● AC/DC CURRENT ● OHM METER
- FREQUENCY COUNTER to 4 MHz ● AUDIBLE CONTINUITY TESTER
- DIODE TESTER ● MAX/MIN AVERAGE MEMORY RECORD
- RELATIVE MODE ● 10A HIGH-ENERGY FUSE PROTECTION
- DATA HOLD ● AUTO SLEEP & AUTO POWER OFF

PERFORMANCE PLUS

Model 92 # 990109

\$119⁹⁵

Complete with above **Standard Features** plus
WATER RESISTANT (92 & 94 Models only),
2 YEAR WARRANTY, YELLOW HOLSTER,
PROBES, BATTERY, FUSE, STAND

DIAGNOSTIC PLUS

Model 93 # 990110

\$149⁹⁵

Complete with **Standard & Model 92 Features** plus
LOGIC PROBE, CAPACITANCE TESTER,
TRANSISTOR TESTER, TEMPERATURE
TESTER & K-TYPE PROBE, HIGH VOLTAGE
WARNING BUZZER

ENGINE ANALYZER PLUS

Model 95 # 990112

\$199⁹⁵

Complete with **Standard & Model 92 Features** plus
TEMPERATURE, TACHOMETER & DWELL
ANGLE TESTER, DUTY CYCLE, 10 MEGA
OHM IMPEDANCE, ANALOG BAR GRAPH,
K-TYPE TEMP PROBE, ALLIGATOR CLIP
TEST LEADS, INDUCTIVE PICKUP CLIP,
6' TEST LEADS & CARRY CASE

KELVIN
ELECTRONICS

10 HUB DRIVE
MELVILLE, NY
11747

M/C & VISA

(800) 645-9212

Established 1945

(516) 756-1750

(516) 756-1763/FAX

The Ultimate Meter

TRUE RMS - LCR - Hz - dBm



12 INSTRUMENTS IN ONE - DC VOLTMETER, AC VOLTMETER,
OHMMETER, AC CURRENT, DC CURRENT, DIODE TESTER, AUDIBLE
CONTINUITY TESTER, dBm, FREQ COUNTER, CAPACITANCE METER,
INDUCTANCE METER, LOGIC PROBE

0.1% ACCURACY
on DC Voltages

Water
Resistant

\$199⁹⁵

MODEL 94
#990111

10 MEGA OHM IMPEDANCE:
RELATIVE MODE / DATA HOLD
MAX/MIN AVERAGE MEMORY RECORD
10A HIGH-ENERGY FUSE PROTECTION
AUTO SLEEP & AUTO POWER OFF with Bypass

COMES COMPLETE WITH
YELLOW HOLSTER, PROBES,
BATTERY, FUSE, STAND

Freq Counter to 20 MHz

Cases for 90 Series Meters

Regular Padded Zippered ... \$9.⁹⁵ (#990116)

Deluxe Padded Zippered ... \$14.⁹⁵ (#990115)

This meter is designed in
accordance with relevant safety
requirements as specified in IEC-
3348, UL-1244 and VDE-0411.

For your Heart's sake get **PULSE STICK II**

Your very own sophisticated pocket health monitor, PULSE STICK II, checks your pulse rate quickly and accurately anywhere. Regular monitoring of your pulse rate during exercise will enable you to plan an exercise regimen suitable for your stage of fitness. Pulse stick II provides an early warning that you may be exceeding your own capabilities.

PULSE STICK II photoelectrically measures the changes

Only
\$39⁹⁵

in the pulsed intensity of infrared radiation emitted by superficial blood vessels below the skin of the thumb. The time intervals between pulses are automatically measured and analogued by the micro-processor based circuitry and displayed in a liquid-crystal display (LCD).

Before attempting any exercise program, consult your doctor. Ask for guidance regarding the recommended safe pulse ranges for your exercise program. Follow your doctor's instructions carefully.



Uses three AA dry cells
supplied with PULSE STICK II




Ideal for running, walking and
aerobic training programs!

FCC LICENSE PREPARATION

General Radiotelephone
Radiotelegraph
Amateur Radio Licenses

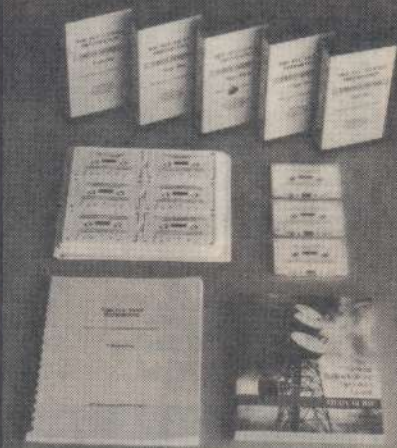We offer the most up-to-date study materials available. Our formats include: tests, audio programs, and video programs. Q & A Disks



WPT PUBLICATIONS

7015 N.E. 61st Ave.
Vancouver, WA 98661
(206) 750-9933

CIRCLE 41 ON FREE INFORMATION CARD



You Need Tree City USA

City trees add the soft touch of nature to our busy lives. They cool our cities, fight pollution, conserve energy, give wildlife a home, and make our neighborhoods more liveable.

Support Tree City USA where you live. For your free booklet, write: Tree City USA, The National Arbor Day Foundation, Nebraska City, NE 68410.



The National
Arbor Day Foundation

PSII-2

☐ **YES!** Please send me _____ PULSE STICK II at \$39.95 each. Price includes shipping and handling charges.

Total amount of order \$ _____

☐ Check or Money Order enclosed. Make check payable to **CLAGGK Inc. PULSE STICK II Offer**

Charge my ☐ Visa ☐ MasterCard

Account No. _____

Exp. Date _____ / _____

Credit Card

Signature _____

Print Name _____

Address _____

City _____ State _____ Zip _____

No telephone orders or C.O.D. Signature required on credit card orders. All prices include postage and handling. Payments in U.S.A. funds only. New York residents must include local applicable sales taxes. No foreign orders.

Mail orders to CLAGGK Inc. Pulse Stick II Offer, P.O. Box 4099, Farmingdale, NY 11735.

Telephone orders to 1-516-293-3751.

FAX orders to 1-516-293-3115.

OCEAN STATE ELECTRONICS

PROFESSIONAL, AMATEUR, OR COMMERCIAL — WE'RE YOUR ONE STOP ELECTRONIC SOURCE
CALL OR WRITE FOR OUR FREE 112 PAGE CATALOG 1-401-596-3080

DELUX CODE KEY



Adjustable, heavy duty brass base with ball bearing pivots. Designed for hard usage. 3/16" plated contacts.

\$10.75

MASTERING THE MORSE CODE

This book teaches the beginner how to learn the Morse Code. Some of the topics covered are Rules for practicing the Morse Code, the code alphabet, how to send and receive code, how to build and hook up a code practice oscillator. 32 pages.

\$2.50

CODE PRACTICE OSCILLATOR & MONITOR IN KIT FORM OR WIRED

A solid-state code practice oscillator and monitor that uses the latest IC circuitry. It contains a 3" built-in speaker, headphone terminals, a volume control and a tone control. It is a attractively packaged with a two color panel. With the addition of a few parts, the unit can easily be converted into CW monitor. It can therefore be used as an operating aid after the code has been learned.



Kit **\$19.95**
Wired **\$24.95**

LINEAR IC'S

NE555	.25
NE564	1.75
LM733N	.65
LM741	.30
UA7805	.39
UA7812	.39
UA7820	.49
UA7824	.49
UA7912	.75
LM317T	.69

TRANSISTORS

PN2222A	.07
2N2222A	.35
2N3055	.69
2N3553	2.75
2N3563	.35
2N3856	1.00
2N3904	.10
2N3906	.15
2N4401	.15
MPF102	.29



MAGNET WIRE

Plain enamel. Solid bare copper. For winding coils, transformers and toroids. Prices for 1/4 lb. spools.

#14	3.25	#24	3.70	#34	4.80
#16	3.30	#26	3.75	#36	4.90
#18	3.35	#28	3.85	#38	4.95
#20	3.55	#30	4.00	#40	5.10
#22	3.65	#32	4.40		

TOROIDS

IRON	FERRITE
T-25-2	FT37-43
T-25-6	FT37-61
T-37-6	FT37-77
T-37-12	FT50-43
T-50-2	FT50-61
T-50-3	FT50-77
T50-6	FT82-43
T68-0	FT82-67
T68-2	FT82-68
T68-6	FT114-61
T80-2	FT140-43
T200-2	FT240-61

WE STOCK A COMPLETE LINE OF TOROIDS AND BEADS.

Q-DOPE



Solution of pure polystyrene in solvents. Dries fast and leaves a clear, protective coating on toroids, coils and transformers, with no or minimal effect on inductive values. May also be used as a cement for molded or fabricated items made of polystyrene.

(Bottle with Brush 2 fl. oz. 59 ml) **\$3.75**

CD22402E

CMOS LSI Sync Generator **\$9.95**



MAKE CIRCUIT BOARDS THE NEW, EASY WAY WITH TEC-200 FILM

JUST 3 EASY STEPS:

- Copy circuit pattern on TEC-200 film using any plain paper copier
- Iron film on to copper clad board
- Peel off film and etch

Convenient 8 1/2 x 11 size

With Complete Instructions

5 SHEETS	\$6.25
10 SHEETS	\$10.75
20 SHEETS	\$16.25



REGULATED POWER SUPPLIES 13.8 VDC

Perfect for ham equipment, CB's, car stereo's and other 13.8 VDC items. LED on indicator, short circuit protection. Binding post output.



3 AMP	\$29.50
4 AMP	\$39.50
6 AMP	\$46.50
10 AMP	\$79.50
20 AMP	\$119.50
30 AMP	\$149.50

MINI-CIRCUITS SBL-1 DIODE RING MIXER



Double balance Mixer
LO/RF - 1-500MHz
RF DC - 500 MHz

\$6.75

MINIATURE TOGGLE SWITCHES 3A 125V Solder Terminals

SPDT	ON-ON	\$1.25
DPDT	ON-ON	\$1.50



DIGITAL CAPACITANCE/INDUCTANCE METER



DIGITAL LCR METER measures inductance, capacitance and resistance. At Last! An LCR meter that everyone can afford. Now you can measure coils, transformers, chokes from 1µH to 200H. Capacitors from 1 pfd to 200 mfd and resistors from 1 ohms to 200 meg ohms. All in one handheld instrument.

MODEL LCR-1801 **\$119.95**

VERNIER DIALS



1-1/2" Diameter 0-10 Marking	\$8.25
1-1/2" Diameter 0-100 Marking	\$9.25
2" Diameter 0-100 Marking	\$10.25

SIGNETICS NE602AN



Balanced Mixer/OSC. Popular IC among experimenters for building DC and super-het receivers.

\$2.49 BUY 3 OR MORE ... **\$2.25**

200 WATT INVERTER

Plugs into your lighter and runs:




- Ham Equipment
- Lights
- Soldering Iron
- Computer
- Power Tools
- Shaver
- 13" TV with VCR
- MUCH MORE

Model: POW 200
Input: 10 to 15 volts DC
Output: 115 volts AC true RMS
Power: 400 Watts peak
200 Watts for 2 minutes
140 Watts continuously
5" x 2.6" x 1.7"

\$99.95

QRP CW TRANSCEIVER KIT

- Covers 14.0 MHz to 14.1 MHz on 20 M or covers 7.0 MHz to 7.150 MHz on 40M
- Available on 20M or 40M band
- Superior Superhet
- Single signal receiver
- CW crystal ladder filter
- VFO tuning with vernier dial
- RIT w/critter detent control
- Very effective AGC
- Selectable audio filter
- Sidetone Oscillator
- 2-3 watts of RF output
- Semi break-in
- 12VDC operation
- Custom pre-painted, punched & silkscreened cabinet
- 100% complete kit with instructions. Nothing else to buy!
- Measures (HWD): 2 1/4" x 6 1/4" x 6"
- Weight 24 oz.

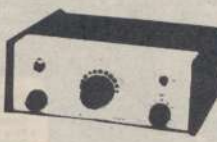

QRP-20	20M VERSION	\$149.95
QRP-40	40M VERSION	\$149.95

SIGNAL INJECTOR/TRACER KIT

This handy tester is both a signal generator and receiver. As a generator use it to check out an amplifier, stage by stage. Also tests AM radio IF and RF stages. As a receiver you can pin point where a defective part exists. Will transmit and receive simultaneously.



\$18.95

LOGIC PROBE KIT

Hand held Digital Logic Probe provides convenient and precise use in the measurement of logic circuits. It displays logic levels (high or low), pulses and voltage transients down to 300 nanoseconds. High intensity LED readouts provide instant response to the logic state.



\$18.95

TRIMMER CAPACITOR ASSORTMENT

Top Quality. May contain some two and three gang as well.

10 pcs. **\$1.50**



VERNIER DRIVE



American made 6:1 vernier drive. Has dual plate mounting flange with two tapped holes (2-56) for dial mounting. Input & output mate with 1/4" shaft.

\$10.75

6146B POWER TUBE

Most Popular Power Tube Used in HF Transmitters

MFG SYLVANIA **\$16.95** Each



CALL US FOR ALL YOUR TUBE NEEDS

DATAMARK DRY TRANSFER TITLES AND MARKINGS (LETTER AND NUMBER SHEETS)

Each set covers a specialized area of electronics. Title sets contain five 3 1/4" x 5" title sheets and one letter-number sheet. The three alphabet sets contain six sheets of letters and numbers in an assortment of black, white and gold. All titles 1/8" high.



AUDIO, TV AND HI-FI

Titles cover the audio broadcast, recording and stereo areas.

K58B Black (K58W White) Audio Titles **\$4.95**

AMATEUR RADIO AND CB

Set is designed for marking all RF and communications equipment

K59B Black (K59 White) Amateur Radio Titles **\$4.95**

TEST AND INDUSTRIAL

Has numerous titles for marking scopes, meters, analyzers, plotters and most other test equipment. Also used for labeling industrial control system panels.

K61B Black (K61W White) Test and Industrial Titles **\$4.95**

MARKS AND SWITCH PATTERNS

Contains rotary switch patterns, arrows, lines, graduations and numbers. Single set contains both black and white sheets. (Black and White assortment)

K62 Marks and Switch Patterns **\$4.95**

ALPHABETS AND NUMERALS, 1/8", 1/4", 1/2"

Sets have 3 black, 2 white and 1 gold sheet of letters and numbers.

K63 1/8" Letters and Numbers **\$4.95**

K64 1/4" Letters and Numbers **\$4.95**

K65 1/2" Letters and Numbers **\$4.95**

Call 1-800-866-6626 ORDERS ONLY

(Catalog requests can not be taken on toll free number.)

8 a.m. - 6 p.m. EST
Monday through Friday

OR WRITE TO:

Ocean State Electronics,
P.O. Box 1458, Westerly, R.I. 02891

OR FAX TO: LOCAL CALLS USE

(401) 596-3590 596-3080

If paying by CREDIT CARD include Card No.

and Expiration Date

Mail in orders please include \$4.00 shipping

CANADA \$7.00 - OVERSEAS \$12.00

Minimum order \$10.00

R. I. Residents add 7% Sales Tax

ORDERS RECEIVED BY 1:00 PM EST—

SHIP SAME DAY!

FREE SHIPPING ON ALL MAIL IN ORDERS

OVER \$25.00.

NOT VALID WHEN COMBINED W/CAT. ORDERS.

Applies to UPS Ground in Continental U.S. Only.

PRICES SUBJECT TO CHANGE




EDGEWISE MOUNT S-METER/SWR

200µA movement. Scale reads signal 0-50db. Has two ear flanges with holes for mounting.

Measures approx. 1 1/2"W x 1 1/4"D x 7/8"H. **\$4.00**

200µA movement. Scale reads both signal (0-30db) and SWR. Same mounting as above.

 Measures 1 3/8"W x 1 1/4"D x 3/4"H. **\$4.00**



MULTIVOLTAGE AC ADAPTER


Rated 500MA
Input 117VAC
Output 3V, 4.5V, 6V,
7.5V, 9V, 12V DC
Polarity switch
Universal plug



\$5.95

RECTIFIER DIODES

1N4001	.09
1N4002	.09
1N4003	.10
1N4004	.10
1N4005	.12
1N4006	.15
1N4007	.17
1N5400	.20
1N5401	.20
1N5402	.20
1N5404	.25
1N5406	.25
1N5407	.25
1N5408	.25

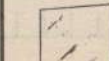

COPPER CLAD PC BOARDS

One oz. copper, phenolic base
Single sided

7" x 5"

8" x 6"

\$1.50

\$2.00

Enter A World Of Excitement with a Subscription to

Popular Electronics®

Get the latest electronic technology and information monthly!

Now you can subscribe to the magazine that plugs you into the exciting world of electronics. With every issue of Popular Electronics you'll find a wide variety of electronics projects you can build and enjoy.

Popular Electronics brings you informative new product and literature listings, feature articles on test equipment and tools—all designed to keep you tuned in to the latest developments in electronics. So if you love to build fascinating electronics, just fill out the subscription form below to subscribe to Popular Electronics...It's a power-house of fun for the electronics enthusiast.

EXCITING MONTHLY FEATURES LIKE:

- ☐ **CONSTRUCTION**—Building projects from crystal sets to electronic roulette
- ☐ **FEATURES**—Educational training on digital electronics, Ohm's Law, Antennas, Communications, Antique Radio, Simplified Theory
- ☐ **HANDS-ON-REPORTS**—User test comments on new and unusual consumer products
- ☐ **SPECIAL COLUMNS**—Think Tank, Circuit Circus, Computer Bits, DX Listening, Antique Radio, Amateur, Scanner Scene

PLUS: ALL OUR GREAT DEPARTMENTS!

You'll get 12 exciting and informative issues of Popular Electronics for only \$18.95. That's a savings of \$23.05 off the regular single copy price. Subscribe to Popular Electronics today! Just fill out the subscription order form below.

CREATE A HIGH-VOLTAGE MINIATURE TORNADO

Popular Electronics

NEW GEAR COMING AT YOU

Get your first look at wide-screen TV's, recordable video-discs, "full-motion" picturephones, "shock-proof" CD players, and the rest of the new generation of high-tech electronic products

POP-UP OUTDOOR LIGHTS

Build a walkway lighting system that ducks out of your way for mowing and other gardening chores

WIRE BEAMS:

GAIN ON THE CHEAP
These antenna designs work where others fail

BUILD YOUR OWN HIGH-VOLTAGE CAPACITORS

Can't find or afford that special capacitor for your Tesla coil or other high-voltage project? Then build your own using our easy-to-duplicate, low-cost designs

Product Reviews

- Sensual A/V Amplifier
- Memorex Extended-Play Personal Stereo
- Plug 'N Power Computer Interface
- Zenith 27-inch Surround-Sound TV
- And More

Save
55%
Off The Regular
NEWSSTAND
Rate

FOR FASTER SERVICE CALL TODAY

1-800-827-0383

(7:30AM-8:30PM)

EASTERN STANDARD TIME

Popular Electronics SUBSCRIPTION ORDER FORM

P.O. Box 338, Mt. Morris IL. 61054

YES! I want to subscribe to Popular Electronics for 1 Full year (12 Issues) for only \$18.95. That's a savings of \$23.05 off the newsstand price.

(Basic Subscription Rate—1 yr/\$21.95)

☐ Payment Enclosed ☐ Bill me later

Please charge my: ☐ Visa ☐ Mastercard

Acct. #

Signature

Exp. Date

PLEASE PRINT BELOW:

NAME

ADDRESS

CITY

STATE

ZIP

Allow 6 to 8 weeks for delivery of first issue. U.S. Funds only.

In Canada add \$6.68 Postage (Includes G.S.T.). All Other Foreign add \$7.50 Postage.

APEL2

Communications Radios

SCANNER & SHORTWAVE

AOR ARI000XC \$429.00

AM Broadcast
to Microwave
1000 Channels

500KHz to 1300MHz coverage in a programmable hand held. Ten scan banks, ten search banks. Lockout on search and scan. AM plus narrow and broadcast FM. Priority, hold, delay and selectable search increments of 5 to 995KC. Permanent memory. 4 AA ni-cads and wall plus cig charger included along with belt clip case and ant. & earphone.
Size: 6 7/8 x 1 3/4 x 2 1/2. Wt. 12 oz.



AR2500 \$499.00

2016 Channels
1MHz to 1300 MHz
Computer Control

62 Scan Banks, 16 Search Banks, 35 channels per second. Computer control for logging and spectrum display. AM, NFM, WFM, & BFO for CW/SSB. Priority bank, delay/hold and selectable search increments. Permanent memory. DC or AC with adaptors included.
Size: 2 1/4 H x 5 5/8 W x 6 1/2 D. Wt. 1 lb. Mtng brkt & Ant incld.



AR3000 \$1095.00

100KHz to 2036MHz
400 Channels

Extreme coverage, excellent sensitivity, plus processor controlled band pass filtering and attenuation to eliminate interference. AM, NFM, Wide FM, LSB, USB, CW modes. RS232 control. Lockout in search. 4 priority channels. Delay & hold & Freescan modes.
Size: 3 1/7 H x 5 2/5 W x 7 7/8 D. Wt. 2 lbs. 10 oz. Ant. & AC/DC pwr cords included.



Free Shipping and Handling
25 Day Satisfaction Guarantee
Toll Free Service and Support
No Credit Card Surcharges
Full Warranties

SCANNERS

AOR AR900 \$269.00

Lo, Hi, Air, UHF, 800
100 Channel Hand Held

5 Scan & 5 Search banks with permanent memory. Extremely compact. Unrestricted 800 coverage. Permanent memory, Delay, Hold, Priority. Supplied with Antennas, Charger, Ni-Cad Batts, Belt Clip.



Bearcat BC760 \$269.95

Lo, Hi, Air, UHF, 800
100 Channel Mobile

Five banks of 20 channels, weather scan, delay, priority, and search. AC/DC power cords, Ant., and mtng brkt included.



Bearcat BC200XLT.....	\$259.95
AOR AR950.....	\$259.00
Bearcat BC55XLT.....	\$119.95
Bearcat BC560XLT.....	\$99.95
AOR AR880.....	\$149.00
Bearcat BC210XLT.....	\$149.95
Bearcat BC70XLT.....	\$129.95
Bearcat BC590XLT.....	\$199.95
Bearcat BC855XLT.....	\$199.95
Bearcat BC147XL.....	\$99.95
Bearcat BC172XL.....	\$139.95
Bearcat BC800XLT.....	\$249.95

2 - WAY

RH256 \$319.00


REGENCY/RELM

Keyboard programmable 16 channel 25watt transceiver with receive scan. Program CTCSS tone, range 148-162MHz. Mic, mtng brkt, DC cord included.
Size: 6 1/2 W x 10 1/2 D x 2 1/2 W Wt. 64 oz.
RSP Prog. Hand Held VHF.....\$419.00
HR3500 10 mtr Mobile.....\$249.00
Ranger Marine Mobile.....\$159.00
Ranger Marine Hand Held.....\$179.00



SHORTWAVE

SONY ICF2010 \$349.00

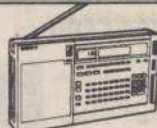

The top selling shortwave receiver. Covers 150KHz to 30.0MHz with 76 to 108 FM and 116 to 136MHz Air. Keyboard programmable with 32 memories. Synchronous detection and selectable IF bandwidth.
Size: 6 1/4 H x 11 3/8 D x 2 1/16 D Wt. 3 lbs 12 oz.
Kenwood R5000.....\$879.00
Grundig SAT650.....\$849.00
Grundig SAT500.....\$499.00
Kenwood RZ1.....\$499.00
Sangean ATS803A.....\$174.00

ACCESSORIES

Wide Band Preamp GW-2 \$89.00



Improve sensitivity of any receiver. -3 to +25db gain, adjustable. GaAsFET design, >1.5db NF, 100KHz to 1500MHz coverage. 9VDC power, battery included.
Size: 3H x 1 7/8 W x 1 1/8 D Wt. 5oz. BNC cntrs.

Interference Filter MPIF \$59.00

Filters interference from TV, FM broadcast, Paging and Cellular.
Size: 3 H x 1 7/8 W x 1 1/8 D Wt. 5 oz. BNC cntrs.

Wide Coverage Base Antenna DA300 \$99.50

25-1200MHz RX. TX or RX. 37" high. N adaptor with 50 ft. of cable to BNC adaptor.

Antennas, power adaptors, computer programs. Call for details.

WARRANTIES & SERVICE


Extended warranties available for many units. Call toll free for details. Service available for many scanners and transceivers by ex-factory technicians. Call toll free for cost estimates.

To Order Call 1-800-445-7717

In All 50 States and Canada. 24 Hours a Day. Fax Orders: 1-800-448-1084, 24 Hours a Day.
ACE Communications Monitor Division 10707 E. 106th Street, Fishers, IN 46038
Int'l Voice# 317-842-7115. Int'l Fax# 317-849-8794.

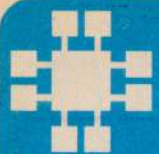Service and Support Lines: Mon-Fri 9 a.m. to 9 p.m., Saturday 10-4 EST
MasterCard, Visa, American Express, Check, Approved P.O.'s & C.O.D. (add 5.00)
Price, specifications and availability subject to change.





JDR Microdevices®

2233 Samaritan Drive, San Jose, CA 95124

BUY WITH CONFIDENCE FROM JDR!

- 30-DAY MONEY BACK GUARANTEE
- 1 YEAR WARRANTY
- TOLL-FREE TECH SUPPORT

CALL FOR YOUR FREE JDR CATALOG TODAY!

FOR PC'S, SOFTWARE, MONITORS, DISK DRIVES, KEYBOARDS, MODEMS, CABLES, CONNECTORS, ICS, COMPONENTS, PROGRAMMERS, TEST EQUIPMENT, TOOLS & MORE!



16-BIT VGA CARD

- 8/16-bit 8088 or 286/386/486 compatible
- 640 x 480 in 16 colors
- 320 x 200 in 256 colors
- 256Kb video RAM



\$49⁹⁵

- MCT-VGA-16** \$49.95
MCT-VGA-1024+ 1024x768, 512 Kb VGA card \$149.95
MCT-IDEFH 16-bit IDE hard/floppy controller \$29.95
MCT-IDEIO 16-bit IDE floppy/hard multi I/O \$69.95
MCT-AIO Serial/parallel/game port card \$49.95
MCT-AIO+ Two NS16550 serial/par/game port \$89.95
MCT-FDC-HD 1.44Mb floppy controller \$49.95
MCT-FDC-ED 2.88Mb 4-floppy controller \$79.95
GATEKEEPER PC security card \$49.95
PCODE Diagnostic display card \$49.95

CONNER 84Mb DRIVE PACKAGE

- CP-30084 84Mb, 19ms IDE hard drive, 16-bit floppy/hard disk controller, cables and instructions



\$319

HDKIT80 \$319

IDE HARD DRIVES

PART #	BRAND	CAP.	SPD.	TYPE	PRICE
CP-3000	Conner	42Mb	28ms	3.5" IDE	\$199
ST-351A	Seagate	42Mb	28ms	3.5" IDE	\$209
CP-30084	Conner	84Mb	19ms	3.5" IDE	\$299
ST-3096A	Seagate	88Mb	16ms	3.5" IDE	\$319
CP-30104	Conner	120Mb	19ms	3.5" IDE	\$379
ST-3144A	Seagate	131Mb	16ms	3.5" IDE	\$399
CP-3204F	Conner	212Mb	16ms	5.25" IDE	\$599

FLOPPY DRIVES

- FDD-1.44A** 1.44Mb, 3.5", Beige \$79.95
FDD-2.88A 2.88Mb, 3.5", Beige \$149.95
FDD-1.2 1.2Mb, 5.25", Beige \$89.95
FDD-360 360Kb, 5.25", Black \$79.95

UNIVERSAL PROGRAMMER

- Programs EPROMs, EEPROMs, microprocessors, PROMs, PAL/GALs and other PLDs; tests logic & memory devices
- Optional adaptors available for PLCC, PGA, QFP and multiple DIP devices
- Includes host adaptor card and cable



MOD-EMUP \$699.00

EPROM PROGRAMMER

- Programs 24-32 pin EPROMs & EEPROMs from 16K-1024K
- Hex to OBJ converter
- Vpp 5, 12.5, 12.75, 13, 21 & 25V



MOD-MEP* \$119.95

MOD-MEP-4* 4-EPROM programmer unit \$169.95

MOD-MAC Host adaptor card & cable \$29.95

*Note: Requires host adaptor card

EPROM ERASER

- Quickly and simultaneously erases up to 4 standard EPROMs



DATASER II \$39.95

1024 X 768 NON-INTERLACED VGA PACKAGE

- 0.28mm dot pitch non-interlaced monitor
- High-resolution VGA card
- Resolution up to 1024 x 768 in 256 colors*
- 512Kb video RAM expandable to 1Mb

\$499⁹⁵



- VGA-PKG-1024N** \$499.95
VGA-PKG-1024+ 1024x768 interlaced VGA pkg. \$469.95
VGA-PKG 640x480 interlaced VGA pkg. \$349.95
VGA-MON-1024 1024x768 interlaced monitor \$349.95
VGA-MON-1024N 1024x768 non-interlaced mon. \$389.95

* Note: Requires 1Mb RAM for 1024 x 768 in 256 colors

ENHANCED KEYBOARD

\$49⁹⁵



BTC-5339 101/102-key enhanced layout \$49.95

3-BUTTON MOUSE

- Accuracy 290-1450 DPI
- Opto-mechanical design
- Universal 3.1 compatible

\$14⁹⁵

JDR-MOUSE-3 \$14.95
MOUSE-PAD \$4.95

DYNAMIC RAM

PART #	SIZE	SPEED	TYPE	PRICE
41256-80	256K x 1	80ns	DIP	1.69
41256-60	256K x 1	60ns	DIP	2.39
414256-80	256K x 4	80ns	DIP	4.95
1MB-80	1M x 1	80ns	DIP	5.99
1MB-60	1M x 1	60ns	DIP	6.49
41256A98-80	256K x 9	80ns	SIMM	14.95
41256A98-60	256K x 9	60ns	SIMM	16.95
421000A98-10	1M x 9	100ns	SIMM	39.95
421000A98-80	1M x 9	80ns	SIMM	45.95
421000A98-60	1M x 9	60ns	SIMM	49.95
424000A98-80	4M x 9	80ns	SIMM	169.95
424000A98-60	4M x 9	60ns	SIMM	174.95

MATH CO-PROCESSORS

Each co-processor includes a manual, software guide and Intel's lifetime warranty.



PART #	SPEED	PRICE	PART #	SPEED	PRICE
8087	5MHz	89.95	80387-SXP	33MHz	199.95
8087-2	8MHz	129.95	80387-DXP	≤25MHz	119.95
80287-XL	12MHz	94.95	80487-SX	20MHz	499.95

BREADBOARD ON-A-CARD

- Solderless breadboard with I/O, decode & timing circuitry



PDS-601 8-bit card \$79.95

PDS-611 16-bit version \$89.95

WIRE-WRAP PROTOTYPE CARDS

JDR-PR2 8-bit with I/O decode layout \$29.95

JDR-PR10 16-bit with I/O decode layout \$34.95

PORTABLE IC TESTER


- Tests the following 14 to 20-pin devices: 74 series TTL, 40 & 45 series CMOS & 41/44 series DRAM up to 1Mb
- Identifies unknown part numbers



MOD-HIC \$129.95

MOTHERBOARDS

NEW LOWER PRICE!

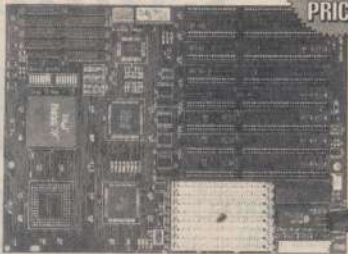

25MHZ CACHE 486SX \$499⁹⁵

- 25MHz Intel 80486SX CPU • 64Kb cache memory on board (expandable to 256Kb) • Expandable to 32Mb on-board using 256Kb, 1Mb or 4Mb SIMMs (ØKb installed) • Includes Intel's "Vacancy" socket

- MCT-M486SX-25** \$499.95
MCT-M486-50 Mini-size 50MHz cache 486 \$1295.00
MCT-M486-33 Mini-size 33MHz cache 486 \$895.00
MCT-C386-40 Mini-size 40MHz cache 386 \$379.95
MCT-C386-33 Mini-size 33MHz cache 386 \$349.95
MCT-M386SX-25 Mini-size 25MHz 386SX \$199.95
MCT-M286-16 Mini-size 16MHz 286 \$149.95
MCT-M286-12 Mini-size 12MHz 286 \$129.95
MCT-TURBO-10 Mini-size 10/4.77MHz 8088 \$69.95

UPRIGHT CASE

\$99⁹⁵

- Accommodates std. motherboards
- Mounts 3 floppy and 4 hard drives
- 2 digit LED display

- CASE-100A** \$99.95
P5-250TW 250W p. supply \$129.95
P5-300TW 300W p. supply \$149.95
CASE-50 Mini 286-style case \$59.95
CASE-70 Std. 286-style case \$89.95
CASE-120 \$199.95
 Mini-upright case w/200W power supply



POWER SUPPLIES

- U/L approved
- 110/220V, 50/60Hz



- P5-150** 8088 150 watt \$69.95
P5-200X 8088 200 watt \$89.95
P5-200 286/386/486 200 watt \$89.95
P5-250 286/386/486 250 watt \$129.95
P5-300 286/386/486 300 watt \$149.95

2400 BAUD MODEM

\$49⁹⁵

- Internal data modem
- Hayes AT compatibility
- Incl. ProComm software



MCT-241 \$49.95

2400 BAUD EXTERNAL MODEM

- 2400/1200/300 baud • Just 6.25 x 3.8 x 2 inches

PRO-24ME \$89.95

9600 BAUD EXTERNAL MODEM

- CCITT V.42bis/V.32/V.22bis/Bell 212A & Hayes AT compatible • Asynchronous / synchronous

VIVA-96E \$349.95

FAX/MODEM SWITCH

- Save phone line charges! • Supports fax, modem, phone and answering machine from 1 phone line

FAXM-SWITCH \$119.95

FAX-SWITCH Without modem connection \$89.95



ORDER TOLL-FREE 800-538-5000

FAX ORDERS 800-538-5005

TECHNICAL SUPPORT 800-538-5002

NOW ORDER 24 HOURS A DAY!

KEY CODE: 1255



JDR Microdevices®

2233 Samaritan Drive, San Jose, CA 95124

BUY WITH CONFIDENCE FROM JDR!

- 30-DAY MONEY BACK GUARANTEE
- 1 YEAR WARRANTY
- TOLL-FREE TECH SUPPORT



TTL LOGIC

PART#	PRICE	PART#	PRICE	PART#	PRICE
7400					
7400	0.29	74LS02	0.25	74LS191	0.49
7402	0.29	74LS04	0.25	74LS193	0.59
7404	0.29	74LS08	0.25	74LS221	0.59
7406	0.35	74LS10	0.25	74LS240	0.89
7407	0.35	74LS14	0.39	74LS241	0.89
7408	0.35	74LS20	0.25	74LS244	0.89
7410	0.29	74LS30	0.25	74LS245	0.89
7412	0.49	74LS32	0.25	74LS251	0.49
7414	0.49	74LS38	0.35	74LS253	0.49
7416	0.35	74LS40	0.29	74LS257	0.39
7417	1.19	74LS42	0.39	74LS273	0.69
7418	0.49	74LS51	0.25	74LS293	0.59
7419	0.49	74LS73	0.35	74LS367	0.39
7420	0.49	74LS74	0.29	74LS368	0.39
7421	0.79	74LS75	0.29	74LS373	0.69
7422	0.49	74LS83	0.49	74LS374	0.69
7423	1.99	74LS85	0.49	74LS682	1.99
7424	0.49	74LS86	0.25		
7425	0.49	74LS90	0.39		
7426	0.59	74LS93	0.39	74500	0.29
7427	0.59	74LS107	0.39	74502	0.29
7428	1.49	74LS112	0.35	74504	0.29
7429	0.59	74LS123	0.49	74508	0.29
7430	0.69	74LS125	0.39	74532	0.35
7431	0.69	74LS126	0.39	74538	0.39
7432	0.89	74LS138	0.39	745138	0.49
7433	0.89	74LS151	0.39	745151	0.59
7434	1.19	74LS153	0.39	745153	0.59
7435	1.29	74LS155	0.49	745157	0.79
7436	0.89	74LS157	0.39	745161	1.29
7437	1.49	74LS163	0.49	745163	0.59
7438	0.89	74LS173	0.39	745244	0.99
7439	1.49	74LS174	0.39	745373	0.99
7440	0.25	74LS175	0.39	745374	0.99

VOLTAGE REGULATORS

PART #	PRICE	PART#	PRICE	PART#	PRICE
UA78540	1.95	7815K	1.39	7915T	0.59
78L05	0.49	7824T	0.49	7915K	1.49
7805T	0.49	7824K	1.39	7924T	0.59
7805K	1.39	79L05	0.69	7924K	1.49
78M05C	0.29	7905T	0.59	LM317T	0.57
7806T	0.49	7905K	1.49	LM323K	3.60
7808T	0.49	7906T	0.59	LM337K	3.60
7812T	0.49	7908T	0.59	LM337T	0.87
7812T	0.49	7912T	0.59	LM338K	6.25
7812K	1.39	7912T	0.59	LM350K	4.25
7815	0.49	7912K	1.49	LM350T	3.60
7815T	0.49	7915	0.69	LM723	0.49

NEC V-20 SERIES

The NEC V-20 can improve performance by up to 30%! Pin compatible with the 8088.

- Uses supersuper of 8088 instructions
- High speed address calculation in hardware
- Low power CMOS design

PART#	PRICE
V20	6.95
V20-8	8.95
V20-10	10.95

LINEAR

PART#	PRICE	PART#	PRICE	PART#	PRICE
LM301	0.39	LM380	0.69	LM711	0.79
LM307	0.49	LM380N-8	1.49	LM723	0.49
LM308	0.69	LM393	0.49	LM741	0.29
LM309K	1.49	LM555	0.29	LM747	0.69
LM311	0.59	LM556	0.49	LM748	0.69
LM317K	1.99	LM558	0.99	LM1458	0.39
LM318	1.19	LM565	0.99	LM1488	0.49
LM324	0.35	LM566	1.49	LM1489	0.49
LM339	0.49	LM567	0.69	LM3900	0.49
LM358	0.49	LM709	0.59	LM3909	1.49

LIGHT EMITTING DIODES

PART #	DESCRIPTION	PRICE
MAN72	7-SEGMENT .3" COMMON ANODE LED	0.99
MAN74	7-SEGMENT .3" COMMON CATHODE LED	0.99
LED-JR	JUMBO T1-3/4 RED LED	0.10
LED-JG	JUMBO T1-3/4 GREEN LED	0.14
LED-JY	JUMBO T1-3/4 YELLOW LED	0.14

EPROMS

PART#	SIZE	SPEED	Vpp	PINS	PRICE
2732A	4096x8	250ns	21V	24	3.95
2764	8192x8	450ns	12.5V	28	3.95
2764-250	8192x8	250ns	12.5V	28	3.95
2764-200	8192x8	200ns	12.5V	28	4.49
27128A-200	16384x8	200ns	12.5V	28	4.95
27256	32768x8	250ns	12.5V	28	4.95
27C256	32768x8	250ns	12.5V	28	5.95
27512	65536x8	250ns	12.5V	28	5.95
27C101-20	131072x8	200ns	12.5V	32	8.95
27C101-15	131072x8	150ns	12.5V	32	9.95

STATIC RAM

PART#	SIZE	SPEED	PINS	CMOS	LP	PRICE
HM6116-2	2048x8	120ns	24	Y	N	2.95
HM6116LP-4	2048x8	120ns	24	Y	Y	2.95
HM6116LP-3	2048x8	150ns	24	Y	Y	3.25
HM6116LP-2	2048x8	120ns	24	Y	Y	3.95
HM6264LP-15	8192x8	120ns	28	Y	Y	3.95
HM6264LP-12	8192x8	120ns	28	Y	Y	4.95
HM6264LP-10	8192x8	100ns	28	Y	Y	5.95
HM43256LP-15	32768x8	150ns	28	Y	Y	4.95
HM43256LP-12	32768x8	120ns	28	Y	Y	5.95
HM43256LP-10	32768x8	100ns	28	Y	Y	6.95

PALS

PART#	SPEED	PINS	IN	OUT	I/O'S	FUNCTIONS	PRICE
16L8	35ns	20	10	2	6	AND-OR INV	2.95
16R4	35ns	20	8	4	4	AND-OR INV	2.95
16R6	35ns	20	8	6	2	AND-OR INV	2.95
20L8	40ns	24	14	2	6	AND-OR INV	2.95
20R4A	25ns	24	12	4	2	AND-OR INV	3.49
20R6	40ns	24	12	6	2	AND-OR INV	2.95
20R8	40ns	24	12	8	-	AND-OR INV	2.95
20X8	50ns	24	10	8	2	AND-OR-XOR INV	2.95
20L10	40ns	24	10	12	2	AND-OR INV	2.95

GALS

PART#	SPEED	PINS	REPLACES	IN	OUT	PRICE
16V8	35ns	20	10L8 TO 16R8	8	8	2.49
16V8-15	15ns	20	10L8 TO 16R8	8	8	2.95
20V8	35ns	24	14L8 TO 16R8	20	8	3.49
20V8-15	15ns	24	14L8 TO 16R8	20	8	4.95
22V10	35ns	24	PGM OUTPUTS	22	10	6.95
22V10-15	15ns	24	PGM OUTPUTS	22	10	19.95

8000 SERIES MICROPROCESSORS

PART #	PRICE	PART #	PRICE	PART #	PRICE
8155	3.95	8742	19.95	80486-33	599.00
8224	2.95	8748	8.95	8087	89.95
8237-5	4.49	8749	9.95	8087-2	129.95
8251A	3.49	8755	24.95	8087-1	189.95
8253-5	2.95	8088	4.95	80287-XL	94.95
82C55-5	3.95	8088-1	9.95	80387-SXP	119.95
8257-5	3.49	80286-12	21.95	80387-DXP	199.95
8272	4.95	80286-16	49.95	80487-SX	499.95
8741	9.95	80386-33	299.95	ODP486-SX20	449.95

RS-232 BREAKOUT BOX \$34.95

- Ten bi-polar LEDs monitor TF, RD, RTS, CTS, DSR, CD, TC, RC, DTR and TC signals (2 spare)
- 24 switches for breakout and patching
- Includes jumper wires
- Requires no battery

BRBOX-B0 \$34.95

SOLDER STATION \$59.95

- 60 watts thermostatically controlled heat from 200-900°F
- Solder gun, gun-rest & cooling tray

168-3C \$59.95

SOLDER/DESOLDER STATION

- Oil-free vacuum pump
- Adjustable temperature (200°-900°F) and vacuum (0.60cm/Hg)

XY9995D \$399.95

JDR INSTRUMENTS

ALL JDR INSTRUMENTS CARRY A 2 YEAR WARRANTY

35MHZ OSCILLOSCOPE

- Exceptionally bright CRT
- TV sync filter
- Delayed & single sweep modes
- Fast 10ns rise time

MODEL-3500 \$499.95

MODEL-2000 20MHz version, no delay \$389.95

100MHZ MULTIFUNCTION COUNTER

- Range: 10Hz to 10MHz direct, 10MHz to 100MHz prescaled by 10
- Period measurements: 10Hz to 2.5MHz±1 count accuracy
- Time base: 10MHz
- 8 digit LED display with decimal point

DFC-100 \$179.95

DFC-1000 1 GHz version \$199.95

DFG-600 Sweep function generator \$189.95

DOS-600 Audio oscillator/counter \$189.95

3.5 DIGIT DMM \$79.95

- Basic DC accuracy ±0.25%
- DC voltage: ±1mV-1000V; AC voltage: ±1mV-750V; AC/DC current: 1µA - 20A
- Resistance: ±1Ω - 20MΩ
- Input impedance: 10MΩ • 28 ranges

DMM-300 \$79.95

DMM-150 3.5 digit DMM with 14 ranges \$29.95

LP-100 Logic probe \$17.95

LP-200 Pulsar probe \$19.95

D-SUBMINIATURE CONNECTORS

TYPE	ORDER BY	CONTACTS				
		09	15	25	37	50
SOLDER CUP	MALE DBxxP	.45	.59	.69	1.35	1.85
	FEMALE DBxxS	.49	.69	.75	1.39	2.29
R/A PC SOLDER	MALE DBxxPR	.49	.69	.79	2.27	—
	FEMALE DBxxSR	.55	.75	.85	2.49	—
W/W SOLDER	MALE DBxxPWW	1.69	2.56	3.89	5.60	—
	FEMALE DBxxSWW	2.76	4.27	6.84	9.95	—
ID5	MALE IDEBxxP	1.39	1.99	2.25	4.25	—
TYPE	FEMALE IDEBxxS	1.45	2.05	2.35	4.49	—
HOODS	METAL MHODxx	1.05	1.15	1.25	—	—
	PLASTIC HOODxx	.39	.39	.39	.69	.75

IC SOCKETS DIP CONNECTORS

TYPE	ORDER BY	CONTACTS						
		08	14	16	20	24	28	40
SOLDERTAIL	xx PIN ST	.11	.11	.12	.18	.20	.22	.30
WIREFRAME	xx PIN WW	.59	.69	.69	1.09	1.49	1.69	1.99
ZIF	ZIF-xx	—	.69	.69	.95	1.05	1.15	1.45
TOOLED	AUGATxx	.55	.59	.69	.85	.99	1.09	1.29
TOOLED WW	AUGATxxWW	1.30	1.80	2.10	2.50	3.15	3.70	5.40

IDC CONNECTORS AND CABLE

TYPE	ORDER BY	CONTACTS				
		20	26	34	40	50
SOLDER HEADER	IDHxxS	1.29	1.68	2.20	2.58	3.24
R/A HEADER	IDHxxSR	1.35	1.76	2.31	2.72	3.39
W/W HEADER	IDHxxWW	2.98	3.84	4.50	5.28	6.63
R/A W/W HEADER	IDHxxWR	3.28	4.22	4.45	4.80	7.30
HEADER SOCKET	IDSxx	.65	.75	.75	1.19	1.19
RIBBON HEADER	IDMxx	5.50	6.25	7.00	7.50	8.50
IDC EDGE CARD	IDExx	.55	.75	.89	1.29	1.69
RIBBON CABLE	RCxx	.30	.39	.51	.60	.75

To order, insert the number of contacts in the position marked "xx" of the "order by" part number listed. Ex: a 15-pin right angle male PC solder part would be DB15PR.



NOW ORDER
24 HOURS
A DAY!

CALL TOLL FREE

1-800-292-7711

1-800-445-3201 (Can.)

ELENCO PRODUCTS AT DISCOUNT PRICES

**48 HOUR
SHIPPING**

DIGITAL METERS



**True RMS 4 1/2
Digit Multimeter
M-700T**

\$135

.05% DC Accuracy
.1% Resistance
with Freq. Counter
Data Hold



**Multimeter with
Capacitance &
Transistor Tester**

\$55 CM-1500B

Reads Volts, Ohms
Current, Capacitors,
Transistors and
Diodes / with Case
Big 1" Display



**Digital Capacitance Meter
CM-1550B**

\$58.95

9 Ranges
.1pF-20,000uF
.5% basic acy.
Zero control w/ Case
Big 1" Display



**Digital LCR Meter
LC-1801**

\$125

Measures:
Coils 1uH-200H
Caps .1pF-200uF
Res .01-20M



**Digital Multimeter
M-1000**

\$25

.3 1/2 Digit
.7% Accuracy
Reads:
AC/DC volts
resistance,
DC current & Diodes

QUALITY AMERICAN MADE POWER SUPPLIES



**High Current Power Supply
XP-800**

\$295

Digital
Volt/Amp Meters

Fully regulated, 0-122VAC @ 2A, 0-40VAC @ 10A or 0-30VDC @ 10A. Fully variable, Short circuit protected.



**Digital Triple Power Supply
XP-765**

\$289

0-20V @ 1A
0-20V @ 1A
5V @ 5A

Fully regulated, Short circuit protected
with 2 limit control, 3 separate supplies
XP-660 with Analog Meters \$195



Quad Power Supply XP-580

\$69.95

2-20V @ 2A
12V @ 1A
5V @ 3A
-5V @ .5A

Fully regulated and short circuit protected



**Triple Power Supply XP-620
Assembled \$75
Kit \$49.95**

2 to 15V @ 1A,
-2 to -15V @ 1A
(or 4 to 30V @ 1A)
and 5V @ 3A

All the desired features for doing experiments.
Features short circuit protection, all supplies.

GENERATORS & VIDEO PRODUCTS



**Function Generator
Blox
#9600**

\$28.95

Provides sine, triangle, square wave
from 1Hz to 1MHz
AM or FM capability

Kit \$26.95



**Color Convergence Generator
SG-250**

\$89.95

Kit \$69.95
Finest in the industry
10 rock steady patterns
RF & Video output



**Wide Band Signal
Generators
SG-9000**

\$129

RF Freq 100K-450MHz AM Modulation
of 1KHz Variable RF output
SG-9500 w/ Digital Display &
150MHz built-in counter \$249



**GF-8016 Function Generator
with Freq. Counter**

\$249

Sine, Square, Triangle, Pulse, Ramp,
.2 to 2MHz, Freq Counter .1-10MHz
GF-8015 without Freq. Meter \$179

EDUCATIONAL KITS - FUN & EASY TO BUILD

Robotic Arm Kit



Model Y-01 \$48.95

Teaches basics of robotics. Arm
grabs & releases, lifts & lowers, &
pivots from side to side

AM/FM Transistor Radio Kit

with Training Course
Model AM/FM 108

\$26.95

14 Transistors ♦ 5 Diodes
Easy to build because
schematic is
printed right on the PCB
Makes a great school project

Learn to Build and Program Computers with this kit

Includes: All Parts,
Assembly and
Lesson Manual



Model
MM-8000

\$129.00

Starting from scratch you build a complete system.
Our Micro-Master trainer teaches you to write into
RAMs, ROMs and run a 8085 microprocessor, which
uses similar machine language as IBM PC.

LASER KITS

Build your own laser. This great kit in-
cludes all parts needed to build a class
II laser. Safe to use, output is under one
milliwatt. Kit includes a new He-Ne
1.125 dia x 5.75" long laser tube. Comes
with building instructions, schematic and
all parts.

Model LK-1 \$79.95

Specifications LK-1:

Input voltage 12VDC @ 1.25 amp
Output voltage 2-3KV @ 3-4.5mA
Trigger voltage 6-8KV
Laser power 1 milliwatt
Laser tube type helium - neon
Laser tube size 1.125" dia x 5.75" long

Mirror & Motor Kit

This unique kit allows you to project
laser patterns on the ceiling or walls.
You change the patterns by varying the
speed of the motors. The kit comes com-
plete with 2 motors, 2 front surface mir-
rors, 2 motor brackets and 1 power
rheostat control to vary speed of the
motor.

Model LM-1 \$19.95

XK-500 Digital / Analog Trainer

A complete mini-lab for building, testing, prototyping analog and digital circuits
Elenco's Digital/Analog Trainer is specially designed for school projects, with 5 built-in power
supplies. Includes a function generator with continuously variable, sine, triangular, square wave
forms. All power supplies are regulated and protected against shorts.

Power Supplies

- Variable Power Supply
- +1.25 to 20VDC @ .5 Amp
- (+1.25 to 20VDC @ 1 Amp)
- -1.25 to -20VDC @ .5 Amp
- (-1.25 to -20VDC @ 1 Amp)
- +12VDC @ 1 Amp
- -12VDC @ 1 Amp
- +5VDC @ 1 Amp
- 30VAC Center tapped @ 15VAC at 1 Amp

Analog - Section

- Function Generator Sine, Triangular, Square wave forms
- Frequency adjustable in five ranges from 1 to 100KHz
- Fine frequency adjust
- Amplitude adjust
- DC offset
- Modulation FM-AM

Digital - Section

- Eight data switches
- Two no bounce logic switches
- 8 LED readouts TTL buffered
- Clock frequency 1 to 100KHz
- Clock amplitude 5VPP square wave

Breadboards

- 2 breadboards, each contain: 840 tie points (total 1,680)



\$149.95 Assembled \$119.95 Kit

WE WILL NOT BE UNDERSOLD

UPS SHIPPING: 48 STATES 5%

IL RES 7.5% TAX (\$3 min \$10 max)

OTHERS CALL

C&S SALES INC.

1245 ROSEWOOD, DEERFIELD, IL 60015

FAX: 708-520-0085 • (708) 541-0710



15 DAY MONEY BACK GUARANTEE

2 YEAR WARRANTY

WRITE FOR FREE CATALOG

CIRCLE 30 ON FREE INFORMATION CARD

**LOWEST
PRICES
GUARANTEED**

ELENCO & HITACHI SCOPES AT DISCOUNT PRICES

**48 HOUR
SHIPPING**


ELENCO OSCILLOSCOPES

- 25MHz and 40MHz Dual Trace, Dual Trigger
- 10 MS/S Sampling Rate (DS-203)
- Vert Sensitivity from 1mV/Div to 5V/Div
- Sweep Rate from 10nS/Div to 15/Div
- Hold-off, X-Y Operation
- TV Sync Triggering
- 6" CRT with Internal Graticule
- Includes Probes
- 2 Year Warranty



**S-1325 25MHz
Dual Trace Oscilloscope**

\$349

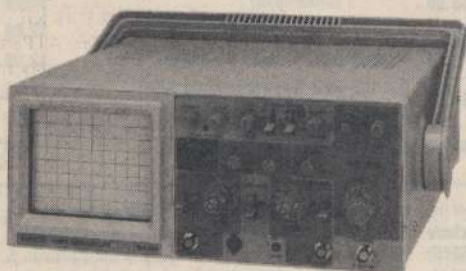

**S-1340 40MHz
Dual Trace Oscilloscope**

\$495

**DS-203 20MHz, 10MS/S
Digital Storage Oscilloscope**

\$775



S-1360 60MHz Delayed Sweep (not shown) \$775

- 2K word per channel
- Plotter output
- 8 bit vert resolution
- 2048 pts hor. resolution
- Much more

All scopes include probes, schematics, operators manual and 3 year (2 years for Elenco scopes) world wide warranty on parts and labor. Many accessories available for all Hitachi scopes. Call or write for complete specifications on these and many other fine scopes. 1x, 10x scope probes: P-1 65MHz \$17.95 P-2 100MHz \$21.95

SPECIAL BUY HITACHI V-212



20MHz
2 Channel
Includes probes

\$409

Hitachi Popular Series

A favorite of field service personnel and education institutions around the world, these scopes have a reputation of quality and reliable performance. With dual channels, $\pm 3\%$ accuracy and 1mV/div sensitivity they have become the standard in portable analog oscilloscopes.

V-525 - 50MHz, Cursors	\$995
V-523 - 50MHz, Delayed Sweep	\$975
V-522 - 50MHz, DC Offset	\$875
V-422 - 40MHz, DC Offset	\$775
V-223 - 20MHz, Delayed Sweep	\$695
V-222 - 20MHz, DC Offset	\$625

Hitachi Compact Series Scopes

This series provides many new functions such as CRT Readout, Cursor measurements (V-1085/1065/665), Frequency Ctr (V-1085), Swepttime Autoranging, Delayed sweep and Tripper lock using a 6-inch CRT. You don't feel the compactness in terms of performance and operation.

V-660 - 60MHz, Dual Trace	\$1,149
V-665 - 60MHz, DT, w/cursor	\$1,345
V-1060 - 100MHz, Dual Trace	\$1,395
V-1065 - 100MHz, DT, w/cursor	\$1,649
V-1085 - 100MHz, QT, w/cursor	\$1,995
V-1100A - 100MHz, Quad Trace	\$2,195
V-1150 - 150MHz, Quad Trace	\$2,695

Hitachi RSO Series

(Portable Real-time Digital Storage Oscilloscopes)

RSO's from Hitachi feature roll mode, averaging, save memory, smoothing, interpolation, pretriggering, cursor measurements. These scopes enable more accurate, simpler observation of complex waveforms, in addition to such functions as hardcopy via a plotter interface and waveform transfer via the RS-232C interface. Enjoy the comfort of analog and the power of digital.

VC-6023 - 20MHz, 20MS/s	\$1,695
VC-6024 - 50MHz, 20MS/s	\$1,995
VC-6025 - 50MHz, 20MS/s	\$2,195
VC-6045 - 100MHz, 40MS/s	Call
VC-6145 - 100MHz, 100MS/s	Call

C&S SALES INC.
1245 Rosewood
Deerfield, IL 60015
708-541-0710 Fax: 708-520-0085




**CALL TOLL FREE
1-800-292-7711**

1-800-445-3201 (Can)

**15 Day Money Back Guarantee
2 Year Warranty**

WRITE FOR FREE CATALOG

Prairie Digital, Inc.

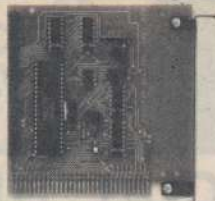

PC DATA ACQUISITION SYSTEM - \$79


INCLUDES SOFTWARE ON 5.25" FLOPPY
MODEL 30-FOR 386'S, XT'S, AT'S, PS2
MODEL 25 & 30'S.

FEATURES:

- ★ 24 LINES OF PROGRAMMABLE INPUT/OUTPUT
- ★ 8 BIT ANALOG TO DIGITAL CONVERTER
- ★ 8 CHANNEL ANALOG MULTIPLEXOR
- ★ 12 BIT CMOS COUNTER
- ★ EASY INTERFACE TO ALL POPULAR LANGUAGES
- ★ OPTIONAL 7 CHANNEL 50V DRIVER AVAILABLE FOR ADDITIONAL \$5

APPLICATIONS:

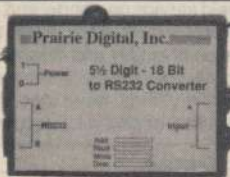- ★ CONTROL RELAYS, LIGHTS & MOTORS
- ★ MEASURE TEMPERATURE, PRESSURE, LIGHT LEVELS, & HUMIDITY
- ★ INPUT SWITCH POSITIONS, THERMOSTATS, & LIQUID LEVELS
- ★ GREAT FOR ROBOTICS, SERVO CONTROL LOOPS



MODEL 70 18 BIT (5.5 DIGIT) A/D WITH RS232 INTERFACE \$239


INEXPENSIVE - Equivalent resolution of 51/2 digit DVMs costing over \$1000! FAST - 16.7 to 133 ms/conversion depending on resolution and mode

MULTI-CHANNEL CAPABILITY - Up to 32 model 70's can be daisy chained together off of 1 serial port

SOFTWARE - Virtual instrument software features easy pull down menus, mouse support, CGA, EGA, VGA support. Will log to screen, printer, or disk data file for easy import to spreadsheets and graphic programs. Source code included (QuickBasic)

\$239 COMPLETE (- Includes software on floppy, PC cable, 9 volt wall mount power supply and manual)

\$199 WITHOUT - Software and cable

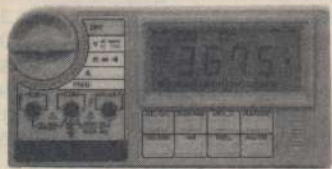

MODEL 150 TRUE RMS DMM W/RS232 PORT - \$149

INCLUDES RS232 PC CABLE AND SOFTWARE ON 5.25" FLOPPY

- ★ LARGE 3 3/4 DIGIT DISPLAY (3.999 VS. 1.999 FOR 3 1/2 DIGIT METERS)
- ★ RS232 SERIAL INTERFACE COMMUNICATES WITH COMPUTERS AND PRINTERS
- ★ MEASURES AC-DC VOLTAGE AND CURRENT, FREQUENCY, RESISTANCE
- ★ 20 AMP CURRENT RANGE, 30 Hz TO 40 KHz FREQUENCY RANGE
- ★ DIODE TEST AND AUDIBLE CONTINUITY

SEND CHECK, MO, VISA, MC
INCLUDE \$8 FOR SHIPPING & HANDLING

Prairie Digital, Inc.

846 Seventeenth Street
Prairie du Sac, Wisconsin 53578
Tel: (608) 643-8599 Fax: (608) 643-6754

Popular Electronics

REPRINT BOOKSTORE

- ☐ 222 Popular Electronics (1992 back issues) \$5.00
Write in issues desired _____
- ☐ 221 Popular Electronics (1991 back issues, Jan., Mar. not available) \$5.00
Write in issues desired _____
- ☐ 220 Popular Electronics (1990 back issues) \$5.00
Write in issues desired _____
- ☐ 119 Popular Electronics (1989 back issues) \$5.00
Write in issues desired _____
- ☐ 118 Hands-On Electronics (1988 back issues) \$5.00
Write in issues desired _____
- ☐ 117 Hands-On Electronics (1987 back issues) \$5.00
Write in issues desired _____
- ☐ EH92 Experimenters Handbook (1992) \$5.00
- ☐ EH91 Experimenters Handbook (1991) \$5.00
- ☐ EH90 Experimenters Handbook (1990) \$5.00
- ☐ EH88 Experimenters Handbook (1988-89) \$5.00
- ☐ EH87 Experimenters Handbook (1987) \$5.00
- ☐ HH92 Hobbyist Handbook (1992) \$5.00
- ☐ HH91 Hobbyist Handbook (1991) \$5.00
- ☐ HH90 Hobbyist Handbook (1990) \$5.00
- ☐ HH89 Hobbyist Handbook (1989) \$5.00
- ☐ 212 Radio-Electronics (1992 back issues) \$5.00
- ☐ 211 Radio-Electronics (1991 back issues) \$5.00
Write in issues desired _____
- ☐ 210 Radio-Electronics (1990 back issues) \$5.00
Write in issues desired _____
- ☐ 109 Radio-Electronics (1989 back issues) \$5.00
Write in issues desired _____
- ☐ 108 Radio-Electronics (1988 back issues) \$5.00

Write in issues desired _____

- ☐ 107 Radio-Electronics (1987 back issues) \$5.00
Write in issues desired _____

REPRINTS

REPRINTS

- ☐ 169 Think Tank (133 Circuits) \$3.50
- ☐ 169A Think Tank Vol. 2 \$3.00
- ☐ 168 Fact Cards (#34-66) \$4.00
- ☐ 168C Fact Cards (#67-99) \$3.50
- ☐ 168D Fact Cards (#100-132) \$3.50
- ☐ 167 Designing With IC's \$4.00
- ☐ 166 Collected Works of Mohammed Ulysses Fips (62 pages, April Fools Collection) \$5.00
- ☐ 165 How to Repair CD Disc Players \$5.00
- ☐ 164 Modern Electronics (April 1908) \$3.00
- ☐ 163 Receiving Satellite TV \$5.00
- ☐ 162 Build Your Own Satellite TV Receiver \$5.00
- ☐ 161 Descrambling (Feb. 1984) \$4.00
- ☐ 160 New Ideas - 42 Circuits \$3.50
- ☐ 159 Low Frequency Receiving Techniques Building and using VLF Antennas \$5.00
- ☐ 158 Electro Importing Co. Catalog (Circa 1918) \$5.95
- ☐ 157 All About Kits \$2.00
- ☐ 156 How To Make PC Boards \$2.00
- ☐ 155 IBM Typewriter To Computer \$2.00
- ☐ 154 How To Repair VCR's \$3.50
- ☐ 150 Pay TV Decoder (1981) \$3.00

To order any of the items indicated above, check off the ones you want. Complete the order form below, **include your payment**, check or money order (DO NOT SEND CASH), and mail to **Claggg Inc.**, Reprint Department, P.O. Box 4099, Farmingdale, NY 11735. Please allow 4-6 weeks for delivery.

If you need a copy of an article that is in an issue we indicate is unavailable you can order it directly from us. We charge 50¢ per page. Indicate the issue (month & year), pages and article desired. Include payment in full, plus shipping and handling charge. Make checks payable to Claggg Inc.

ARTICLE _____

PAGES _____

MONTH _____

YEAR _____

TOTAL PAGES _____

@50¢ each

TOTAL PRICE _____

MAIL TO: **Claggg Inc.**

Reprint Bookstore, P.O. Box 4099, Farmingdale NY 11735

All payments must be in U.S. funds

SHIPPING CHARGES IN USA & CANADA

\$0.01 to \$5.00	\$1.50	\$30.01 to 40.00	\$5.50
\$5.01 to \$10.00	\$2.50	\$40.01 to 50.00	\$6.50
\$10.01 to 20.00	\$3.50	\$50.01 and above	\$8.00
\$20.01 to 30.00	\$4.50		

Total price of merchandise \$ _____

Shipping Charge (see chart) \$ _____

Subtotal \$ _____

Sales Tax (New York State Residents only) \$ _____

Name _____

Total Enclosed \$ _____

Address _____

City _____ State _____ Zip _____

PE1192

OPTOELECTRONICS

BRINGING YOU INNOVATIVE PRODUCTS
FOR 18 YEARS

3000 - Our Best Handi-Counter®

10Hz - 3GHz Multifunction Counter, includes: •Bargraph
•6 Functions • ± 1 PPM TCXO •NiCads & Charger

\$375. (options: BLB30 \$75, TXCO30 \$100.)

8030 - Bench/Portable Multifunction Counter

10Hz - 3GHz Extremely High Sensitivity, High Resolution
and Accuracy, includes: •Bargraph • ± 1 PPM TCXO

•Two Inputs •Adjustable Trigger Level •Trigger Variable
•Hold Button

\$579. (options: BLB90 \$75,
TCXO9 ± 1 PPM TCXO \$135.)



APS104

Our Active
Preselector
will
unbelievably
boost your
counter's ability
to detect
frequencies up to
10 times the
distance. Tunable
over 5 octaves.

\$995.



PC10 PC Based Multifunction Counter

Operates under Windows 3.1.
("C" Library available)

•Instantly tunes a receiver •Data Logging
•10 Digit •10Hz - 2.4GHz

\$199. (options: AP10H - Dual
High Impedance Amplifier
Head Unit \$199.)

Both PC10 & AP10H \$379.

**YOU
CAN'T HIDE
IT'S COMING
IN THE FALL
OF '92**

**Factory Direct Order Line
1-800-327-5912**

(305) 771-2050 • FAX (305) 771-2052
30 Day Money Back Guarantee

5821 NE 14th Ave. • Ft. Lauderdale, FL 33334
5% Shipping Handling. (Maximum \$10) U.S. & Canada.
15% outside continental U.S.A. In Florida add 6% sales tax
Visa and MasterCard accepted.

BIG PROFITS IN VIDEO REPAIR!

**WORK FROM HOME-EARN \$85 HR!
-NO EXPERIENCE NECESSARY-**

Only requirement: That you possess average mechanical ability and a desire to learn

With the tens of millions of VCRs and Camcorders in use, there currently is a serious shortage of trained techs to perform cleaning and repair jobs on these popular devices... Learn

how **you** can start your own **highly profitable, Home-Based** video servicing business...

And since up to 95% of all VCR and Camcorder malfunctions are due to a simple mechanical or electro-mechanical failure, you need not spend months or even years of complicated study before starting paid, professional service work!

Let Viejo's Training Program show you how!



Train at
Home in your
Spare Time!

CALL
TOLL-FREE

1-800-537-0589

or mail coupon today!

VIEJO PUBLICATIONS, INC.

4470-107 Sunset Blvd., Suite 600
Los Angeles, CA 90027

Yes! Rush me your **FREE OPPORTUNITY KIT** today!
(Check appropriate box)

- ☐ VCR Repair
- ☐ Camcorder Repair
- ☐ Advanced VCR Repair
- ☐ Fax Machine Repair

Name _____

Address _____

City/State _____ Zip _____

Dept. PE

THIS LAND

Gave us our past...

It can give us our future

Help protect America's soil and water today.



We owe it to our children.

Find out what you can do.

Call 1-800-THE SOIL to get your free kit.

United States
Department of
Agriculture

Soil
Conservation
Service



CIRCLE 40 ON FREE INFORMATION CARD

WHOLESALE SPECIALS

LIMITED QUANTITIES

CABLE CONVERTERS

Blow Out!!

XL - 103

550 MHZ - 86 Channel **\$89.95** each

TOP CHANNEL ROLLOVER,
LAST CHANNEL MEMORY, SUB-
CHANNEL 0+1 CAPABILITY,
FAVORITE CHANNEL, SURGE
PROTECTION, 4 db AMP,
DECODER COMPATABLE,
STD/HRC SWITCHABLE, ONE
YEAR REPLACEMENT
WARRANTY, A/B TWINLINE
OPTIONAL

\$70.00 each - 5 Lot

\$65.00 each - 10 Lot

\$57.00 each - 20 Lot

\$52.00 each - 50 Lot

\$50.00 each - 100 Lot

VIEWSTAR IS HERE

MXC-2520-525 MHZ remote volume
remote volume control
Audio/video Baseband **\$119.95** ea.
Output, decoder loop **\$90.00** 5 lot
Parental Lockout **\$85.00** 10 lot
Favorite channel **\$80.00** 20 lot
Remote Fine tuning
'Universal' Decoder Compatible

NEW "NORTH COAST"

'Excel' 66 channel remote **\$99.95** ea.
Fine tune remote,
60 min. Sleep timer **\$80.00** 5 lot
Display dimmer
Favorite channel **\$75.00** 10 lot
Parental Lockout,
HRC/STD Remote **\$70.00** 20 lot
Selectable Twinline A/B Select Optional
AMERICAN MADE Keep OUR People Working

UNITED ELECTRONIC SUPPLY

P.O. BOX 1206 PE • ELGIN, ILLINOIS 60121

24 Hour Service

(708) 697-0600

Mon - Fri 8:30 - 5 pm - CST

PE MARKET CENTER CLASSIFIEDS

PLANS-KITS-SCHEMATICS

HAM RADIO KITS & ASSEMBLIES for various QST & 73 construction articles. For catalog, send legal size SASE w/52 cents postage to A & A Engineering, 2521 W. LaPalma #K, Anaheim, CA 92801.

FM STEREO BROADCASTER kit. This kit outperforms the competition. Transmitter will broadcast any audio signal from a CD player, VCR, or cassette player to FM stereo radios throughout your home and yard. All the complex circuitry is in the unique BA1404 integrated circuit. Tunable across the FM band, runs on 1.5 to 12 volts DC. Complete kit of PC board and components for \$24.00. **TENTRONIX**, Dept. PM1192, 3605 Broken Arrow, Coeur d'Alene, ID 83814.

NI-CAD ZAPPER can rejuvenate those unchargeable NI-CAD batteries. Instructions, schematic and parts list to construct NI-CAD Zapper: \$5.00. **TENTRONIX**, Dept. PM1192, 3605 Broken Arrow, Coeur d'Alene, ID 83814.

MAGNETIC AMPLIFIER. Solid state amplifier without semiconductors or vacuum. Amplifies through the use of magnetic fields. Plans \$10.00, kit (plans + one amplifier) \$20.00. **Electroman**, Dept. PE, PO Box 24474, New Orleans, LA 70184.

FLAME SPEAKER. Finally, a speaker with no moving parts! Omnidirectional sound, with higher frequency response than conventional loudspeakers. No diaphragm or voice coil. Plans, \$10.00. **Electroman**, PO Box 24474, Dept. PE, New Orleans, LA 70184.

68HC11 MICROCONTROLLER design manual. Interfacing, schematics, software algorithms, PCB artwork. Rush \$10.00. **AJR Circuits**, 42073 Addison, Canton, MI 48187.

BUILD YOUR own robot! Complete plans \$12.00, details \$1.00. Key Publications, Box 971, Elfers, FL 34680.

RADIO CONTROL CAR STARTER. Build and assemble a radio controlled starter for your car. Start your car from inside the house. For plans and instructions send \$10.00 to Jeff Cox, 1418-B Forestdale Blvd., #201, Birmingham, AL 35214-3016.

100 PIECE GRAB BAG, flyer of electronic goodies. \$2.00 Lynn Johnson, Box 51268, San Jose, CA 95151-1268.

INSTRUCTION FOR PLACING YOUR AD!

HOW TO WRITE YOUR AD

TYPE or PRINT your classified ad copy **CLEARLY** (not in all capitals) using the form below. If you wish to place more than one ad, use a separate sheet for the additional ads (a photocopy of this form works well). Choose a category from the list below and write that category number into the space at the top of the order form. If you do not specify a category, we will place your ad under Miscellaneous or whatever section we deem most appropriate.

We cannot bill for classified ads. Payment in full must accompany your order. We do permit repeat ad or multiple ads in the same issue, but in all cases, full payment must accompany your order.

WHAT WE DO

The first two words of each ad are set in bold caps at no extra charge. No special positioning, centering, dots, extra space, etc. can be accommodated.

RATES

Our classified ad rate is 40¢ per word. Minimum charge is

\$6.00 per ad per insertion (15 words). Any words that you want set in bold or caps are 10¢ each extra. Bold caps are 20¢ each extra. Indicate bold words by underlining. Words normally written in all caps and accepted abbreviations are not charged as all-caps words. State abbreviations must be Post Office 2-letter abbreviations. A phone number is one word.

CONTENT

All classified advertising in the **PE Market Center** is limited to electronics items only. All ads are subject to the publisher's approval. We reserve the right to reject or edit all ads.

DEADLINES

Ads received by our closing date will run in the next issue. For example, ads received by June 18 will appear in the October issue that is on sale in August. No cancellations permitted after the closing date. No copy changes can be made after we have typeset your ad. **NO REFUNDS**, advertising credit only. No phone orders.

AD RATES: 40¢ per word, Minimum \$6.00.

Send your ads with payment to:

Popular Electronics Market Center, 500-B Bi-County Blvd. Farmingdale, NY 11735

CATEGORIES

100 — Antique Electronics	330 — Computer Software	570 — Plans-Kits-Schematics
130 — Audio-Video-Lasers	360 — Education	600 — Publications
160 — Business Opportunities	390 — FAX	630 — Repairs-Services
190 — Cable TV	420 — Ham Gear For Sale	660 — Satellite Equipment
210 — CB-Scanners	450 — Ham Gear Wanted	690 — Security
240 — Components	480 — Miscellaneous Electronics For Sale	710 — Telephone
270 — Computer Equipment Wanted	510 — Miscellaneous Electronics Wanted	720 — Test Equipment
300 — Computer Hardware	540 — Music & Accessories	

CLASSIFIED AD COPY ORDER FORM

Ad No. 1—Place this ad in Category # _____

1 - \$6.00	2 - \$6.00	3 - \$6.00	4 - \$6.00	29 - \$11.60	30 - \$12.00	31 - \$12.40	32 - \$12.80
5 - \$6.00	6 - \$6.00	7 - \$6.00	8 - \$6.00	33 - \$13.20	34 - \$13.60	35 - \$14.00	36 - \$14.40
9 - \$6.00	10 - \$6.00	11 - \$6.00	12 - \$6.00	37 - \$14.80	38 - \$15.20	39 - \$15.60	40 - \$16.00
13 - \$6.00	14 - \$6.00	15 - \$6.00	16 - \$6.40	Ad No 1—Total words _____ x .40 per word = \$ _____			
17 - \$6.80	18 - \$7.20	19 - \$7.60	20 - \$8.00	All Caps words _____ x .10 per word = \$ _____			
21 - \$8.40	22 - \$8.80	23 - \$9.20	24 - \$9.60	Bold words _____ x .10 per word = \$ _____			
25 - \$10.00	26 - \$10.40	27 - \$10.80	28 - \$11.20	Bold Cap words _____ x .20 per word = \$ _____			
				TOTAL COST OF AD No. 1 \$ _____			

Total classified ad Payment \$ _____ enclosed.

[] Check [] MasterCard [] Visa (\$15.00 minimum credit card order)

Card # _____

Expiration Date ____ / ____

Signature _____

Name _____

Phone _____

Address _____

City State Zip _____

\$49
Four motor kit with computer interface



\$99
High speed Closed loop Galvo kit Squares to 180 hz, & Circles to 900 hz



FREE
catalog of Kits

Silicon Valley Surplus
1273 Industrial Prkwy West
Bldg 460
Hayward, Ca .94544-7025
510-582-6602

CIRCLE 39 ON FREE INFORMATION CARD

CELLULAR TELEPHONE MODIFICATION HANDBOOK

How do you reprogram a cellular phone?


- Descriptions of cellular phones' vulnerabilities !
- Techniques for decoding and changing cellular phones' NAMS and ESN's
- Where to buy programming devices
- Chip supplier's phone numbers
- Instructions on how to change phone numbers on all models
- Cellular phone manufacturer's ESN codes

Complete Manual only
\$79.95

M.O. or C.O.D. to

SPY Supply

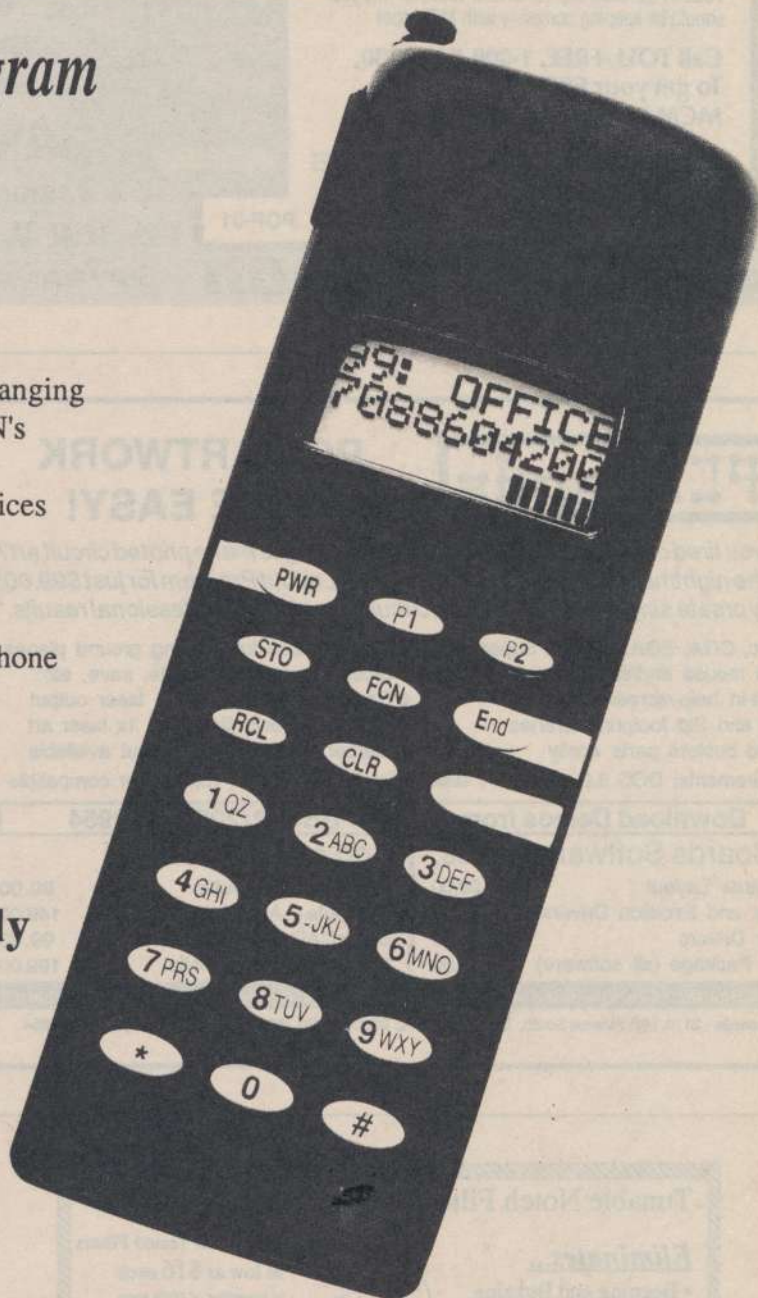7 Colby Court Suite 215
Bedford, NH 03110
(617) 327-7272



Sold for educational purposes only

SAMS **AKRO-MILS** **Rocket** **American International** **'PRO**

UPS **EMINENT** **GC** **COMMODORE** **ACR** **LE Channel** **SONY** **Panasonic** **ICA DUN** **DIAMOND** **LIQUID TOOL** **Multi-tool**

MCM Electronics
We Can't Help Mentioning A Few Names
 Although name-dropping is usually frowned upon, we'll risk it so you'll know the kind of company we keep... and that you can get almost any part you could ever want from our huge MCM Catalog. Choose from more than 17,000 items, most of them ready to ship within 24 hours! Talk to friendly, knowledgeable sales reps, get technical help when you need it and enjoy convenient, TOLL-FREE ordering. All GREAT reasons why you should be keeping company with MCM too!

Call TOLL-FREE, 1-800-543-4330,
To get your FREE
MCM Electronics Catalog

MCM ELECTRONICS
 650 CONGRESS PARK DR.
 CENTERVILLE, OH 45459-4072
 A PREMIER Company

POP-01

Switchcraft **PRO-LUXE** **RCA** **PYRAMID**

A M S E V **GE** **AUTOPAGE** **MITSUBISHI** **Chemtronics** **CORAL** **MG** **DECISION** **MATSUS** **CANY** **FISHER Welle**

PE MARKET CENTER CLASSIFIEDS

PRINTED CIRCUIT KIT

ER-4 PHOTO ETCH™ kit lets you copy art from this magazine onto your PC board. Includes everything but exposure bulbs. Shipped UPS to your street address for \$43.00.

ER-19 EXPOSURE BULB SET FOR ER-4. Contains 3400°K reflector flood and 4800°K long wave UV lamp for ordinary 120V socket. Shipped UPS to your street address for \$18.45. **FREE CATALOG** of dry transfers and PC supplies. Write or phone **DATAN**, 55 Freeport Blvd, Sparks, NV 89431. 702-359-7474 FAX: 702-359-7494.

BUSINESS OPPORTUNITIES

CASH FOR TRASH. Turn that electronic scrap into cash. \$2.00 Lynn Johnson, Box 51268, San Jose, CA 95151-1268.

EASY BUSINESS Earn up to \$1000.00/wk repairing VCRs from home. 4 hour video training tape shows you how. Send \$39.95 to VCR Training, 3975 Jane Street, Box 21057, Downsview, Ont., Can. M3N 3A3.

PUBLICATIONS

MARCONI SALAD and Tesla Taters! ElectroMeals Cookbook, available just in time for holiday gift giving. The perfect present for the Ham's mate. 125+ recipes, \$12.00 plus \$3.00 S&H. **ELECTROMAN**, Dept PE, Box 24474, New Orleans, LA 70184.

PCBoards

PCB ARTWORK MADE EASY!

"Are you tired of laying down tape or wire wrapping to make printed circuit art? End the nightmare with the PCBoards Circuit Layout Program for just \$99.00! Easily create single or double-sided circuit boards with professional results."

- Herc, CGA, EGA, VGA, & SuperVGA
- Use mouse and/or keyboard
- Built-in help screens
- Dip and Sip footprint libraries
- Build custom parts easily
- Copper flood for building ground planes
- Block move, copy, rotate, save, etc.
- Comes with dot-matrix & laser output
- Make your own films with 1x laser art
- Gerber and Excellon output available

Requirements: DOS 3.0 or later, 1 disk drive, 384k of RAM, IBM-PC or compatible

Download Demos from our 24hr BBS at (205) 933-2954

PCBoards Software Prices:

PCBoards Layout	99.00
Gerber and Excellon Drivers	49.00
Plotter Drivers	49.00
Demo Package (all software)	10.00

Add on Software:

PCRoute Autorouter	99.00
PCRoute+ Autorouter	149.00
SuperCAD Schematic	99.00
SuperCAD+ Schematic	199.00

Use PCBoards, PCRoute, and SuperCAD as a "system" to create pcb art from a schematic!

PCBoards - 2110 14th Avenue South, Birmingham, AL 35205 / Ph. (800)473-PCBS Fax (205)933-2954

Tunable Notch Filters and Telephone Recording Equipment

Eliminates...

- Beeping and Buzzing
- Severe Interference

Micro Thinc.
 P.O. Box 63-6025
 Margate, FL 33063

Assembled and Tested Filters

as low as \$16 each
 in quantities of 10 or more



Kit Filters
 as low as \$8 each
 in quantities of 21 or more

Brochure \$1

(305)-752-9202

RADON. THE HEALTH HAZARD IN YOUR HOME THAT HAS A SIMPLE SOLUTION.

Call
1-800-SOS-RADON
 to get your Radon
 test information.



*Here is a circuit that
leaves no doubt as to
whether someone
has been trying
to reach
you*

BY STEVEN M. O'KELLEY

Recently, telephone companies began offering a new type of service; Electronic Voice Mail. Intended as a replacement for the answering machine, the service leaves a greeting and records messages from callers when a subscriber is unable to answer the phone. Typically, Voice Mail is activated after a preset number of rings to allow subscribers time to answer a call when they are at home.

Instead of using magnetic recording tape, the service records and stores the caller's message in digital form at the telephone-switching office. The user can then retrieve messages using any Touch-Tone telephone.

Even though Voice Mail has some nice advantages over its mechanical counterpart, there is still some room for improvement. For example, when a message has been left, the system lets you know by pulsing the first few seconds of dial tone when you pick up the handset. That means that someone who is in and out several times a day has to pick up the phone each time to check for messages.

While a device that automatically does this would be complex, the next best thing is easy. The simple circuit—dubbed the *Tel-Tale*—described in this article will detect when someone has called and flash an LED to alert you to check for messages.

How It Works. A schematic diagram of the Tel-Tale is shown in Fig. 1. The circuit is built around a couple of low-cost IC's: an H11C4 optoisolator/coupler with an SCR output (U1) and an LM3909 LED flasher (U2). The circuit is



Build A Voice-Mail Alert

connected to the phone line's tip (green) and ring (red) wires in the same manner as any extension phone.

When the phone is on hook, there is about 48 volts DC across the line. A neon lamp (NE1) is connected in series with the tip conductor. Because NE1 requires about 60 volts to conduct, the circuit represents a high impedance to the line and no current flows. When a call is made to the covered line, a ring voltage—about 90 volts AC at 20 Hz—is applied to the telephone line by the telephone-switching office. During half of the cycle, current flows from the ring line through R1, D1, NE1, and C1 to the tip line. During the other half cycle, the current reverses and the LED portion of U1 conducts, triggering its internal SCR, allowing a small amount of current to flow through the SCR and R2. That current flow causes capacitor C2 to begin charging.

Integrated circuit U2 and capacitor C3 form a simple LED-flasher circuit that will operate on just over a volt. When the charge on C2 reaches the 1-volt level, U2 flashes LED1 and the charging cycle of C2 starts over. The LED continues to flash until S1 (reset) is pressed. Closing S1 deprives the SCR of holding current, thereby turning it

off. The Tel-Tale remains in that state until re-triggered by the next incoming phone call.

Construction. The prototype of the Tel-Tale was assembled on a small printed-circuit board, measuring about 1½ inches square. A template of the author's PC pattern is shown in Fig. 2. Note that in that diagram, only one set of IC pads (near the center of the board) are shown; the reason for that will become apparent in a moment.

Once you've etched your board and gathered all the parts listed in the Parts List, construction can begin. A parts-placement diagram for the Tel-Tale's printed-circuit board is shown in Fig. 3. In the author's prototype, a single 16-pin IC socket is used for both U1 and U2 (6- and 8-pin devices, respectively). You can do the same thing, or, if you happen to have 6- and 8-pin sockets on hand, you can use individual sockets. In any event, using sockets prevents damage to the IC's during soldering, and makes replacing either IC (should the need arise) simpler.

Once the IC socket (or sockets) is in place, install the rest of the components as shown in Fig. 3. Note that because of tight spacing R1, R2, and D1 were vertically mounted to the cir-

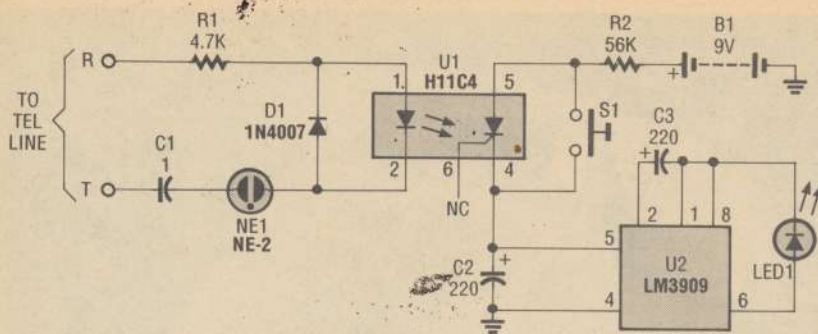


Fig. 1. The Tel-Tale is built around a couple of low-cost IC's: an H11C4 optoisolator/coupler with an SCR output (U1) and an LM3909 LED flasher (U2), and is connected to the phone line in the same manner as any extension phone.

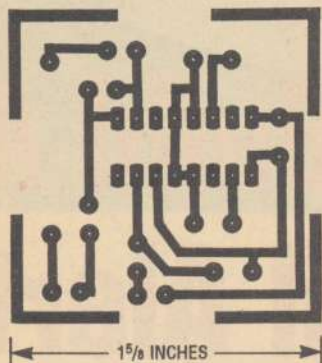


Fig. 2. The prototype of the Tel-Tale was assembled on a small printed-circuit board, measuring about 1 5/8 inches square, a full-size template of which is shown here.

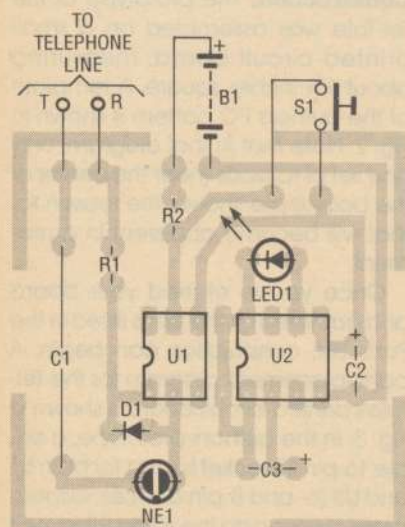


Fig. 3. Once you've etched your board and gathered all the parts listed in the Parts List, construction can begin, guided by this parts-placement diagram. In the author's prototype, a single 16-pin IC socket is used for both U1 and U2 (6- and 8-pin devices, respectively).


circuit board. When installing LED1, leave the leads long enough so that its lens will stick through a hole in the circuit's enclosure.



Here's the author's completed prototype.

The author's prototype was housed in a plastic Radio Shack enclosure (catalog number 270-293), which provides ample room for the circuit board and also has a built in battery compartment. The circuit board can be mounted using a small piece of double-sided tape. Switch S1 (either a pushbutton- or a toggle-type momentary single-pole unit) mounts to the case. Because the battery drain is low (about 0.3 mA), the author elected not to use an on/off switch in the design of this circuit.

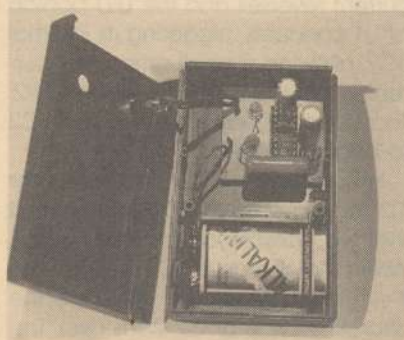If you have one of the older desk- or wall-type telephones, you may find that there is ample room to mount the



The circuit can be mounted in a plastic project box or even within some telephones.

PARTS LIST FOR THE TEL-TALE

SEMICONDUCTORS

- U1—H11C4 or NTE3046 optoisolator/coupler with SCR output, integrated circuit
- U2—LM3909 or NTE876 LED flasher, integrated circuit
- D1—1N4007 1-amp, 1000-PIV, rectifier diode
- LED1—Super-bright LED (Radio Shack 276-087)

RESISTORS

- (All resistors are 1/4-watt, 5% units.)
- R1—4700-ohm
- R2—56,000-ohm

CAPACITORS

- C1—1-μF, 200-WVDC, metallized-film
- C2, C3—220-μF, 10-WVDC, electrolytic

ADDITIONAL PARTS AND MATERIALS

- S1—SPST momentary-contact toggle or pushbutton switch
- B1—9-volt transistor-radio battery
- NE1—NE-2 neon lamp
- Printed-circuit board materials, enclosure, battery holder and connector, telephone wire, solder, hardware, etc.

circuit board and battery inside. Mount LED1 to the case of the phone and use a few inches of wire to connect it to the circuit. Most such phones also have a hook switch with unused contacts that can be used for S1. By using the hook-switch scheme, the circuit will reset itself whenever you use that phone.

Installation. With your circuit completed, connect it to the phone line using standard quad telephone wire or a modular cord. The tip and ring inputs of the unit connect to the green and red wires, respectively, inside the telephone outlet. The Tel-Tale should be mounted so that the LED can be easily seen. The LED radiates most of its light in a narrow pattern so you should be looking into the top of the LED. The next time you are called, the circuit will flash. Even if you don't have Voice Mail, you may find this device handy. It will always let you know that someone has tried to reach you. ■

Installing and Maintaining Telephone Systems

It's an easy job—if you follow these simple hints and procedures.

BY ROBERT A. YOUNG

With all the many features now offered on telephones, it is difficult to determine which model will give you the most bang for your buck! One of the more important questions that you must ask yourself is what is your greatest requirement from a phone? Is it to be your primary telephone? And, if so, will it work even when the power goes out? Will it be located in a lavishly (or even moderately) decorated room? And, if so, will it fit in with the decor of the room in which it will be located?

For many others, the question is does the phone offer all of the most modern conveniences? Is it pulse dial or touch tone? Does it include an answering machine? Is it cordless? etc. Cost and manufacturer support are also important considerations. If it is defective or fails soon after it is purchased, what is the manufacturer's replacement/repair policy?

And what about the installation—should I have it installed by a "professional," or should I attempt it myself? Or, you may want to add a modular phone to an existing two-wire system, but haven't an inkling of how to go about accomplishing that task. Depending on your situation, installation can involve a bit more than simply pushing a modular plug into a modular jack. Yes, there are many points to consider when purchasing and installing a new telephone.


In this article, we'll show you how to

install your own basic telephone network, and cover some of the tools and accessories that are available to help you to install and maintain the system. We'll also look at dialing schemes, and cover some of the features and options that are available on conventional and novel phones, cordless and non-cordless, and mobile and transportable phones.

We also cover some of the problems associated with purchasing your own phone to help you decide whether owning your own phone is in your best interests.

Basic Installation. In today's climate of deregulation, most (if not all) domestic telephones are installed by their owners. Modular telephone plugs make that task as simple as plugging in an electric lamp. Even older phones, those that do not have modular plugs, can be installed by the owner. In fact, older telephones can be adapted to modular installation, and *vice versa* (and we'll talk about that a little later in this article).

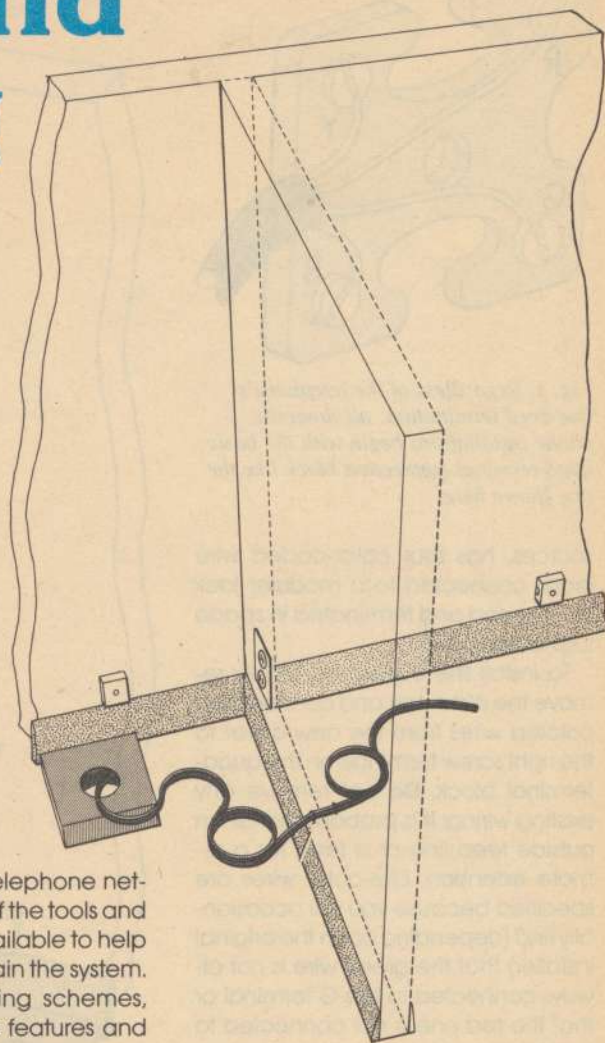Regardless of the telephone's line-cord termination, all domestic phone installations begin with the basic



quad-terminal connection block (see Fig. 1). The terminal block has four color-coded screw terminals, labeled R for red, G for green, Y for yellow, and B for black. The R and G (in telephone parlance, ring and tip, respectively) terminals are the main connection points for any telephone installation; they carry both the ring signal and verbal communications.

The Y and B terminals are used for other purposes. For instance, in older residential telephones, the Y and B terminals were connected to an external plug-in wall adapter that provided DC power to light the telephone dial.

If you are simply replacing an older existing phone with one of the newer modular units, all that you'll have to do is to replace the quad-terminal block's cover with a modular one (see Fig. 2). The cover, which is available from numerous local or mail-order

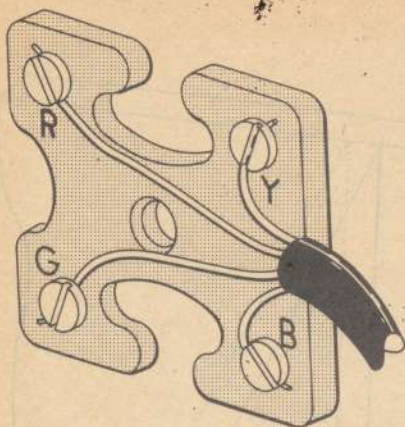


Fig. 1. Regardless of the telephone's line-cord termination, all domestic phone installations begin with the basic quad-terminal connection block like the one shown here.

sources, has four color-coded wire leads connected to a modular jack on one end and terminated in spade lugs at the other.

To install the cover, you simply remove the old cover and connect like-colored wires from the new cover to the right screw terminals on the quad-terminal block. **Do not** remove any existing wiring; It is probably either an outside feed line or a feed for a remote extension. Like-color wires are specified because you will occasionally find (depending upon the original installer) that the green wire is not always connected to the G terminal or that the red one is not connected to the R terminal—i.e., the color-code is not always followed. In fact, in some instances (where the black and yellow wires are not being used for some other purpose), you may find the black and yellow wire used in place of the red and green. That's be-

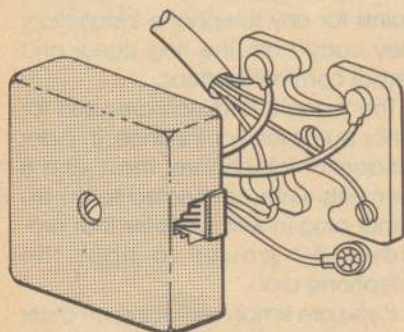


Fig. 2. To convert older installations to modular use, all you have to do is to replace the quad-terminal block's cover with a modular one, which has four color-coded wire leads that connect to the existing terminal block.

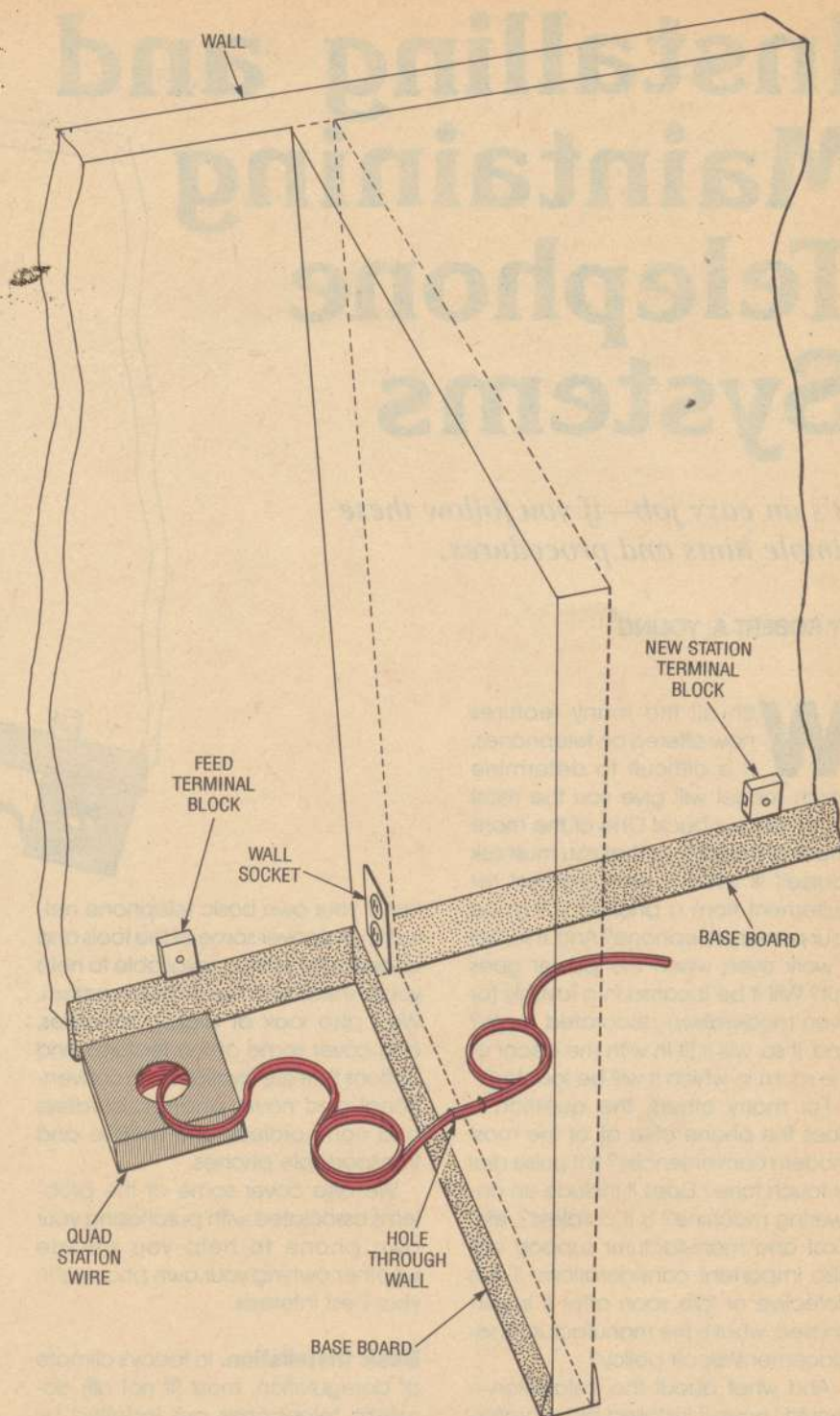


Fig. 3. When installing a new station, map out the route that the wire run is to take. If the new station is to be located in another room, which often requires that a hole be drilled through a wall, avoid (as best you can) AC receptacles.

cause, it was once common practice, when the red or green or both wires became open or shorted, to use the others as a substitute, rather than run all-new wiring.

Incidentally, although it is rare in this day and age, you may even run across twisted-pair telephone wire. In

twisted-pair telephone set-ups, the two conductors are (well, usually are) color coded as well, via a strand of either red or green thread within the insulation of each conductor. In such cases, simply connect like colored wires as before.

Once all modular jack leads have

been matched to those on the terminal block, but before you mount the cover to the terminal block, it's a good idea to check the line. That can be done in two ways: You can either connect a phone to the modular jack or you can use one of the do-it-yourself telephone line testers that are on the market. The phone method is, of course, cheap and quick, but only gives a go or no-go indication; whereas commercially available testers will diagnose any problem. (See the "Repair" section of this article for more information of the use of telephone-line testers.) Once the telephone is found to be operating properly, all you have left to do is mount the cover to the terminal block.

Adding a New Station. Adding a new station (extension phone) is nearly as easy as installing a new phone in an existing telephone outlet; the only difference is that you'll have to run wire from the closest terminal block to the new location and terminate it with a modular jack (see Fig. 3).

For the wire run, you'll need an appropriate length of quad color-coded station wire, not the flat line type. Station wire—which is designed for both inside and outside use—differs from line cord in that its conductors are solid, as opposed to the stranded stuff used for line cord (see Fig. 4). The insulation of the station wire is also thicker than that of the line cord. That's important since most wire runs are secured to the walls' base boards using a staple gun. If the gun is not properly positioned before the staple is released, it could (and often does) pierce the cable insulation. That often results in either shorting two or more wires or severing them altogether.

There are, of course, staple guns that are designed for wire installations. Such units are notched at the discharge point, so that the discharge point can easily be centered over the wire. That helps to prevent discharging the staple into the wire or its insulation. Such staple guns are available from many local and mail-order outlets that sell a range of do-it-yourself telephone accessories.

When installing a new station, first mount the new terminal block at the position that you've chosen for the new station. Then determine the most direct and convenient route from the

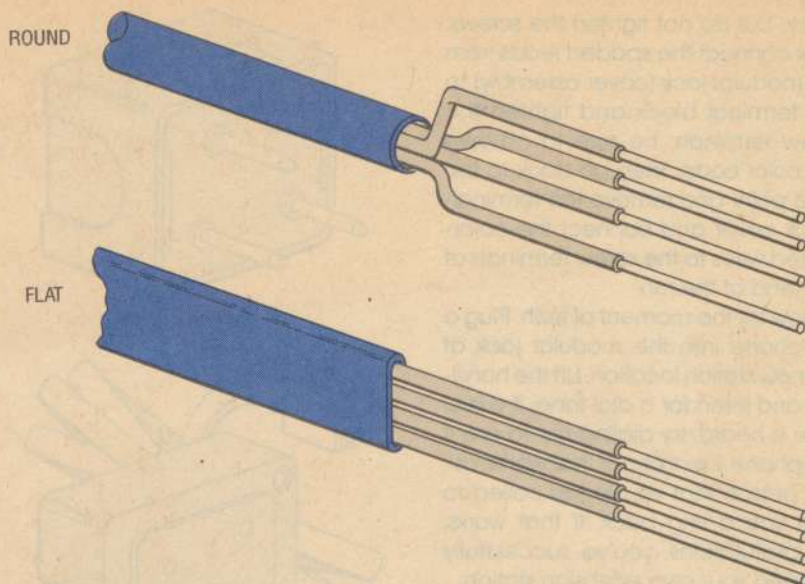


Fig. 4. Station wire—which is designed for both inside and outside use—differs from line cord in that its conductors are solid, as opposed to the stranded stuff used for line cord, and it is round rather than flat. The insulation of the station wire is also thicker than that of the line cord.

closest existing station or terminal block to the new location. If the new station is to be located in another room, it may be (and usually is) necessary to drill a hole through a wall to get to that location. When drilling through a wall, be sure that you drill at a point that's a respectable distance from any AC receptacles—the consequences of such carelessness is obvious.

Drill a hole no more than a quarter of an inch in diameter. If it needs to be enlarged, that can be done with an awl (for plaster board also known as sheet rock) or a larger drill bit. It's easier to enlarge a hole than it is to fill it in. If the hole must be drilled through cement, cinder block, or any other similarly hard substance, you'll have to use a masonry bit.

Once a hole of sufficient diameter has been drilled, feed the station wire through the hole. It may be necessary to snake the wire through the hole (particularly where sheet rock is concerned). You won't need anything fancy, in fact, an old wire hanger (the thing kind) works very well.

Form a hook in one end of the snaking wire, strip away some of the outer insulation of the station cord, and twist the four leads together at the ends only (to form a loop for the hook). If it's too thick to fit through the hole, you can either twist two wires together or make a loop in a single wire and cut

the unused leads close to the outer insulation to thin things out. But remember, fewer wires means you'll have to be more careful when pulling the wires through the hole—too much tension could snap the wire.

Hook the snake onto the wires, and feed the snake through the hole as far as you can, line up the station wire with the hole; if possible force the tip of the station wire into the hole. If necessary, flatten the hook and wire junction with a pair of pliers. From the other side of the wall, pull the snake with the station wire through to the other side. Continue to pull the wire through until you have more than enough to reach the new station site.

Starting from the new station location and leaving an extra five to ten inches or so, secure the station wire to the base board using your staple gun—keep the wire taut—working your way back to the hole in the wall. Working from the new station location back toward the feed-point location in that manner helps to cut down on wasted station wire at the end of the run.

From the other side of wall (beginning at the hole), secure the wire to the base board in the same manner, working your way to the feed-point terminal block. Go back to the new station location and connect the color-coded wires to the corresponding screw terminals on the terminal

block, but do not tighten the screws. Now connect the spaded leads from the modular jack (cover assembly) to the terminal block and tighten the screw terminals; be sure to observe the color code. Then go back to the feed point and remove the terminal-block cover and connect the color-coded wires to the screw terminals at that end of the run.

Now for the moment of truth. Plug a telephone into the modular jack at the new station location. Lift the handset, and listen for a dial tone. If a dial tone is heard, try dialing out to see if the phone is working. If that works, ask the person that you've just called to give you a ring back. If that works, congratulations, you've successfully installed your own extension station.

Phone Conversions. An older telephone can easily be adapted to a modular system and *vice versa*. Figure 5A shows an adapter that allows you to use a modular telephone in an older plug-in system. Those plug-in stations are the forerunners of today's modular system, and in their day, were considered the "ultimate" in modern convenience.

It is easy to adapt older plug-in telephones for modular installation, using the adapters shown in Figs. 5B and 5C. In both cases the adapters are nothing more than a length of four-conductor telephone wire with one end terminated in a modular plug and the other end terminated in a plug-in jack. You'd simply plug the phone into the large square block and the other end of the adapter would be plugged into a modular jack. The only real difference between the adapter in Fig. 5B and one in Fig. 5C lies in the length of wire between the plug and jack.

Now if you're really a diehard, you can also open the phone and replace the old round quad (or dual, depending on the age of the phone being adapted) line cord (the cable that connects the telephone base to the telephone line) with flat modular-type line cord. Replacing the line cord can be done in one of two ways; you can use a replacement line cord (they're available from many local electronic suppliers), which typically have modular plugs at both ends, or you can make your own modular cable.

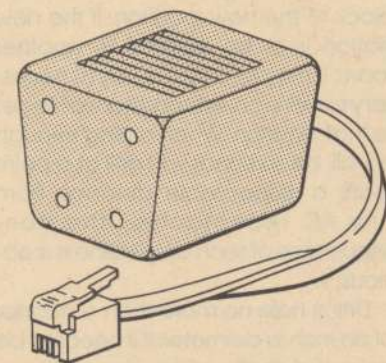
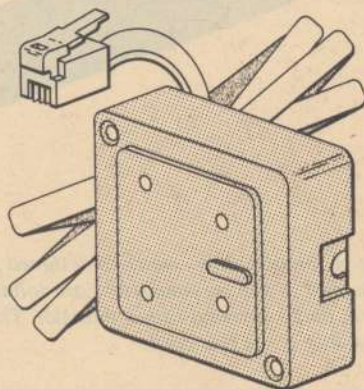
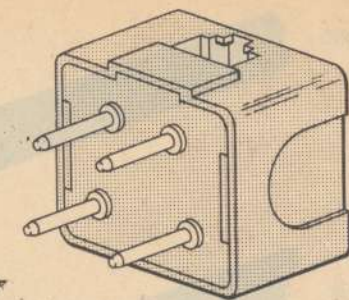


Fig. 5. The adapter in A allows you to use a modular telephone in an older plug-in system; the adapters in B and C can be used to make older plug-in telephones compatible with a modular system.

I prefer the make-your-own approach because any left-over quad cord (although it is not the best for such applications) can be used to install an additional modular jack for an extension at any location desired. In addition, making your own allows you to lengthen or shorten the line cord as you choose. (Those of my generation will recall the gouging you took when a 15-foot line cord was requested from the phone company.) The only difference between using replacement line cord and making your own is that the latter requires the additional step of connecting a modular plug to one end of the cord.

To use a replacement line cord, first remove the telephone face plate by removing the face-plate retaining screws (which are located on the underside of the phone). Then simply clip the modular connector from one end of the replacement cord, and strip back some of the outer insulation. Next strip the color-coded insulation from the conductors one at a time. Disconnect the original quad wire, one wire at a time, connecting the corresponding color from the new quad wire to the terminal previously occupied by the wire from the old line cord.

If you are making your own line cord, the next step is to connect a modular plug (see Fig. 6) to the free end of the line cord. Modular plugs, quad line cord, and the crimping tool (see Fig. 7) needed for plug installation are available from many local (Radio Shack, for one) and mail-order electronic suppliers. When purchasing modular plugs, be sure to get the four-conductor type. (There are also six-conductor units that are intended for more sophisticated units not normally found in the home.)

Once complete, the only thing left to do is replace the telephone's face plate, plug in your phone, and check its operation by placing a call.

Do-It-Yourself Line Repairs. Many residential consumers are opting to maintain their own domestic inside wiring rather than pay a monthly maintenance charge on their telephone bills. There are two reasons that one might choose that option. The most obvious reason is savings. While the cost of maintenance service is low

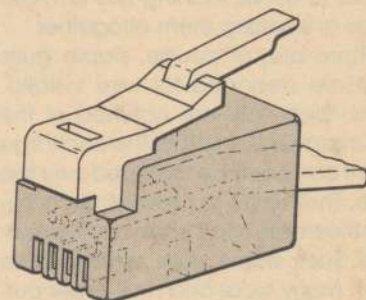


Fig. 6. Modular plugs are available from many mail-order and local, electronics and do-it-yourself home-fixings distributors. When purchasing modular plugs for domestic installations, be sure to get the four contact type, not the six conductor units.

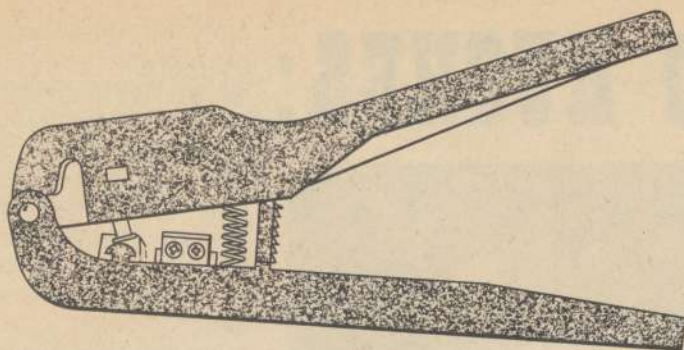


Fig. 7. This is what the crimping tool required to attach a modular plug to quad line cord looks like. To use it, simply load a plug into the tool, insert the line cord into the slot on the plug, and squeeze.

(averaging, typically, only a few bucks a month), you must be at home for those repairs, which could cost you many times its worth in lost wages. And that points to the other reason for maintaining your own inside wiring—convenience. Rather than sitting around for half a day waiting for a repairman (who may or may not show), you can repair or replace the wiring at your leisure.

There are many do-it-yourself telephone line testers on the market—such as Tele-Check Modular Line Tester from GC Electronics (GC-Thorsen, 1801 Morgan St. PO Box 1209, Rockford, IL 61105-1209; Tel., 815-968-9661; Fax, 815-968-9731) or Radio Shack's Phone Line Testers—that can be used to help maintain inside wiring.

Both units are extremely simple to use and, in fact, require no instructions to operate. You simply plug the tester's modular plug into the telephone line, and front panel labeling and annunciators on the tester give all the information that you'll need. A single LED located on the front panel lights green to indicate that the line is properly wired and functioning. The LED lights red to indicate reversed wiring, and white is used to indicate an open (or simply not operational) circuit.

Dialing Schemes. All of today's phones use one of two dialing schemes—pulse dialing or touch-tone. Pulse dialing, the oldest of the two dialing schemes, is a method by which a local loop (a circuit within the telephone) is opened and closed at a specified rate. The opening and closing of the loop produces a series of pulses (representing the number being dialed) that are transmitted to your local telephone office, which,



The Tele-Check Modular Line Tester, from GC Electronics, has no controls to fiddle with and requires no instruction manual to operate. You simply plug it in and it diagnoses telephone-line problems, and informs you through a, front-panel mounted LED.

after decoding the transmitted pulses, connects you to the specified target station.

Although most of today's pulse-dial phones are operated by pushbutton, rotary units (which are still available) also fall into this category. The difference between pushbutton and rotary type of pulse-dial phones lies in the way the series of pulses representing the numbers being dialed are produced.

The touch-tone type, on the other hand, makes sounds like musical tones. The tones are produced as a dual-tone multi-frequency signal—a system by which two frequencies are mixed together to represent the number being dialed. Pulse-dial phones can be operated on touch-tone lines, but the same cannot be said for touch tone on pulse-dial equipped lines. Obviously, touch-tone lines offer more flexibility in selecting

your phone, but touch-tone service also costs more. (Incidentally, most modern telephones offer switchable pulse-dialing or touch-tone compatibility.)

Even though most phone companies have switched to touch-tone service, it's a good idea to check with your local service provider to find out what dialing schemes are supported in your area. That's particularly important where touch tone is concerned for the reason mentioned above.

Features. Today's phones are available in a variety of styles (cartoon characters, etc.) and with many nifty features (such as cordless communication; built-in clock/radios; automatic answering machines; etc.). Some of the features, for instance clock/radios or automatic answering machines, require that the base unit (in addition to the usual telephone hook-up) be connected to an AC power source. And that brings another question into play: Will the basic phone still work if the AC power fails?

In addition, cordless phones can suffer from another (usually unforeseen) problem: the dead-battery syndrome. Because the handset of cordless phones are battery operated, it is wise to be certain that the battery or batteries used in the handset are commonly available units that will not "vanish" as the popularity of your phone fades. (I fell victim to that predicament.) Where possible, you should select a phone that uses standard batteries.

While modern features may be a strong selling point, those features can also be pitfalls; remember that the more features incorporated into the device, the greater the possibility of equipment failure.

Warranties. While few consider the possibility of telephone failure, manufacturers warranties should play a prominent role in your decision as to which unit to select. Before you buy, it's a good idea to ask to see a copy of the manufacturer's warranty that covers the unit of interest. Find out if the product is backed by a well-established customer-service record. Sturdily built models are the best defense against frequent repairs, and the inherent headaches that go along with them.

David Hughes was both dejected and angry as the three distinguished visitors from the Royal Society left his laboratory in London on February 20, 1880. Hughes had spent several hours demonstrating to them how a simple circuit, consisting of a microphone he had designed together with a telephone receiver, could detect at a distance the previously unknown "aerial electric waves" produced by a spark discharge. The distances over which Hughes could detect these waves sometimes exceeded a quarter mile.

The visitors included William Spottiswoode, President of the Royal Society, together with Professors Thomas Huxley and George Gabriel Stokes, honorary secretaries of that esteemed organization. Each was respected as an outstanding scientist.


The experiments had gone well and at first the visitors seemed astonished by the results. After a while, however, Professor Stokes began to assert that the results were not at all due to what Hughes referred to as "conduction of electric waves through the air." Rather, Stokes argued, what was being observed could be explained by known electromagnetic induction effects.

Hughes then carried out several additional experiments that pointed conclusively to the fact that the effects were not due to induction. Stokes, nonetheless, maintained his negative attitude, constantly "pooh-poohing" the results. Soon, Spottiswoode and Huxley joined Stokes in making acrimonious comments concerning Hughes' experiments.

The three men would not accept Hughes' contention that he had discovered a previously unknown type of "aerial electric wave." They did think, however, that Hughes had enough original material to write a paper for presentation to the Royal Society.

The dignitaries from the Royal So-

DAVID HUGHES:

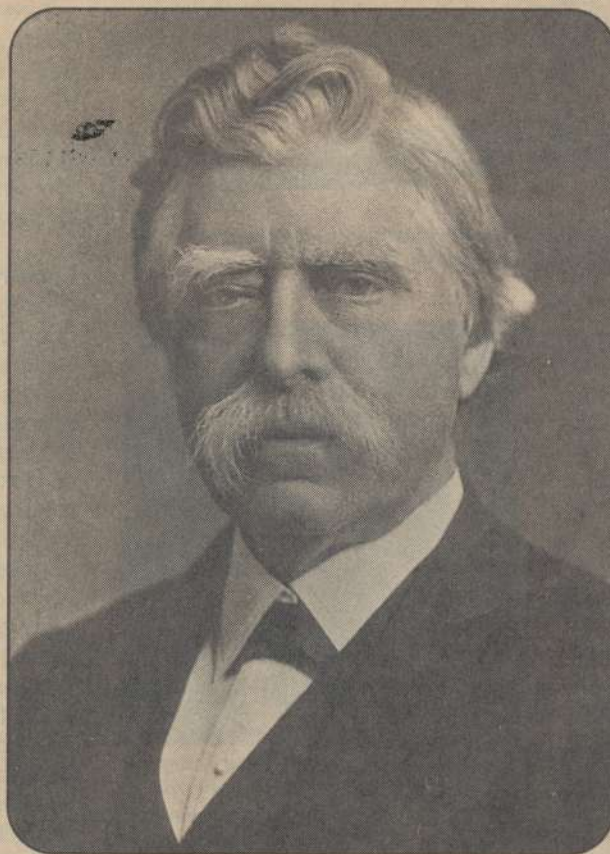

Electromagnetic Pioneer

BY JAMES P. RYBAK

Had David Hughes not been discouraged by "experts" in 1880 concerning the significance of his work, the unit of frequency today might be called the "hughes" rather than the "hertz."

ciety became very displeased when David Hughes refused their suggestion that he give his detector circuit to the Society so that others could conduct similar experiments. Hughes maintained that the instrument he had developed for his research was for him alone to use.

Unwilling to risk further embarrassment, Hughes refused to write a paper describing his experiments until he had more proof concerning the existence of the new electric waves he knew he had generated and detected. However, that conclusive proof would be published in 1888, not by Hughes but by Heinrich Hertz. Many years passed before Hughes received the recognition he deserved for this earlier work.

A Musician Turned Scientist. David Edward Hughes was born on May 16, 1831 in London, but emigrated to the United States with his family when he was seven years old. His boyhood interests and talents were in music, not science.

Hughes joined the faculty of the Roseland Academy in Bardstown, Kentucky in 1851 as a professor of music. It is both surprising and fortunate, however, that his interests soon turned toward

conducting mechanical and electrical experiments with laboratory equipment he designed and built by himself.

Hughes quickly became so accomplished in science he was appointed to the Chair of Natural Philosophy (science) at Roseland the following year. He now lectured in physics as well as in music.

Resigning his teaching position in 1853 so that he might devote more time to scientific experimentation, Hughes moved to Bowling Green, Kentucky. There he taught just enough private music lessons to be able to eat and to buy the materials needed to construct his laboratory equipment.


These existing printing telegraph systems worked reasonably well provided the telegraph lines were short. Long telegraph lines, however, exhibited considerable capacitance that tended to merge the numerous individual current pulses required for each letter into one long continuous pulse. The result was that the print wheel failed to advance the required number of steps and the wrong letter was printed.

A Successful Printing Telegraph.

By 1854, Hughes had developed an automatic printing telegraph system of his own design that worked extremely well. A sequentially operating mechanism requiring a series of current pulses was not employed by Hughes. In its place, he had developed a means for synchronizing the print wheel of the sending instrument with that of the receiving unit. Making the print wheels rotate in unison was the necessary improvement required to print the desired letters reliably.

Synchronization of the sending and receiving print wheels was achieved by having both units driven by identical clockwork mechanisms. The speed of each mechanism was governed by an adjustable, weighted vibrating spring. These speed-governing springs emitted the same musical frequency when the speeds of the two clockwork mechanisms were identical. The musical frequency generated by each spring was compared against a known frequency produced by a tuning fork. The rotations of the two print wheels were then started at the same instant through the transmission of initiating signals.

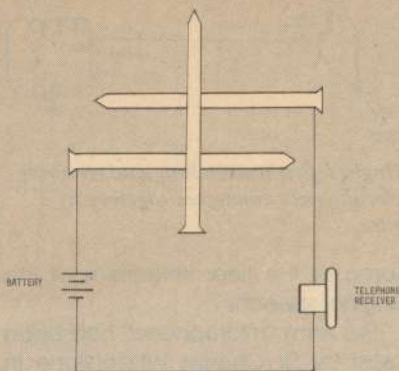The printing telegraph equipment developed by Hughes was adopted almost immediately by the American Telegraph Company. Hughes then went to England in 1857 to find additional markets for his invention. The English did not show any interest in this



The "imperfect contacts" which existed between the metal surfaces caused the "H" shaped configuration of nails to function as a microphone.

invention produced by their native son.

Ironically, when the first submarine telegraph cable was laid across the English Channel a few years later, it became mandatory that both the English and the French use the same telegraphic equipment. The French would not consider using anything other than the Hughes printing telegraph. The English, therefore, were forced to adopt the equipment that they had so cavalierly rejected just a short time earlier.

Whether motivated by stubbornness or by conviction, the only place the English installed the Hughes printing telegraph equipment was at the London end of the trans-Channel line. The messages received by telegraphers in the rest of England continued to be written by hand.

Virtually all of the other European nations, however, recognized the value of this new printing telegraph. France, Russia, Austria, and Turkey not only adopted Hughes' invention, they bestowed medals and honorary titles on him for this scientific achievement. The income Hughes received from licensing his printing telegraph made him independently wealthy by the time he reached middle age.


Despite the rejection by the English of his telegraphic printer, David Hughes returned to London in 1875 with his American-born wife to make his home. While he spent the remainder of his life in England, Hughes always retained his naturalized U.S. citizenship and maintained fond memories of Kentucky.

Experiments with Sound.

was aware that the resistance of selenium changed when light was shined on it. He also knew that the resistance of most materials was significantly affected by changes in temperature. Perhaps, Hughes reasoned, sound waves would have a similar effect on some metals.

Ordinary wire conductors showed no sensitivity to sound waves or "sonorous vibrations" as Hughes called them. He also found that wires undergoing bending or stretching similarly were unaffected by sound waves. The wires being studied by David Hughes were made part of a current-carrying circuit that contained a telephone receiver.

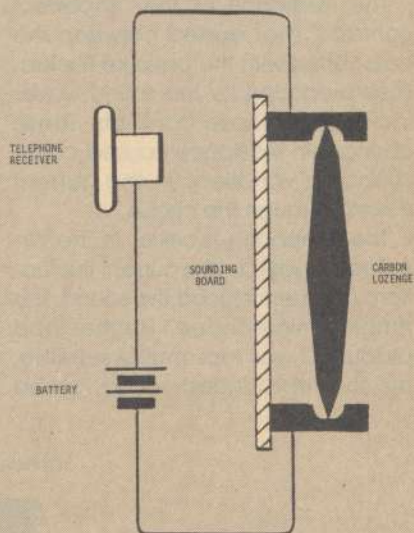The receiving unit of the telephone, first demonstrated by Alexander Graham Bell in 1876, proved to be a valuable research tool as well as an



The carbon lozenge microphone was reasonably sensitive and rugged.

important instrument for communicating. The same electromagnetic principles that made the telephone capable of receiving speech from distant points also made it capable of detecting other small fluctuations in electric currents. Hughes expected that the telephone receiver would easily detect any fluctuations in the current produced by sound waves.

Luckily, a wire broke one day while Hughes was carrying out an experiment to investigate the effects of sound waves on conductors being stretched. At the very instant the wire broke, an unusual "rushing" sound was momentarily produced by the tele-


phone receiver. The phenomenon occurred every time Hughes repeated the experiment causing the wire to break.

Hughes tried to recreate the conditions at the instant of breakage by pressing together the ends of the wire with varying degrees of force. In the course of these attempts, he found that conductors touching each other under light but constant pressure responded well to sound waves.

Further experimentation led Hughes to arrange two clean, bright iron nails parallel to each other, but separated by a space of approximately one-half inch. A circuit was formed by connecting a battery and a telephone receiver in series between the two nails. The circuit was completed by laying a third nail across the other two so that an "H" shaped arrangement of nails resulted.

The resistance of the "imperfect contacts" that existed between the nails varied with the pressure fluctuations produced by the sound waves incident on those contacts. These changes in resistance caused corresponding variations in the current flowing through the circuit.

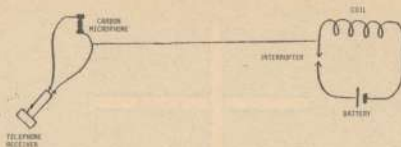The telephone receiver in the circuit responded to the current fluctuations and reproduced the sound. This simple "microphone" Hughes had produced was reasonably sensitive, but the reproduced sound lacked



Hughes' first transmitting and receiving circuits were connected together by a wire.

some of the finer inflections of the original speech.

The term "microphone" had been used by Sir Charles Wheatstone in 1827 when he discovered that musical sounds could be transmitted through both metallic and glass rods. Hughes found the term aptly descriptive and adopted it for the various forms of sound transducers he developed.

Almost immediately, Hughes said of the microphone that "we may fairly look for it to do for us, with regard to faint sounds, what the microscope does with matter too small for human vision." To demonstrate this, he placed both a housefly and a three-nail microphone mounted on an empty matchbox under an inverted drinking glass. The experiment was successful with Hughes reporting that he "could hear the fly walking with a particular tramp of its own."

David Hughes continued to conduct experiments designed to improve his microphone. Arranging from ten to twenty nails in a square

configuration that he referred to as a "log hut" resulted in both better sensitivity and somewhat improved fidelity. Still, Hughes knew, the quality of the reproduced sound needed to be improved even more.

A Much Improved Microphone.

Something inspired David Hughes to return to his original three-nail "H" microphone design. This time, however, he placed a small amount of a fine zinc and tin powder mixture between the nails at the two points where the nails were in contact. The result was that speech was reproduced clearly in the telephone receiver.


This latest discovery Hughes had made came to be known as the "multiple-contact" microphone. Clearly, however, nails and metal powder resulted in a microphone that was neither rugged nor convenient to use. Hughes now set out to find not only the best materials, but also the most practical arrangement of those materials for his microphone.

The improvement provided by the metal powder intrigued Hughes. He found that practically any metal powder would work reasonably well provided it did not become oxidized. Platinum powder did not oxidize, but was very expensive. Carbon proved to be both free from oxidation effects and inexpensive.

Hughes conducted many interesting experiments in which he tried a number of configurations and various combinations of materials. Very interesting and what initially seemed like extremely promising results were obtained when Hughes heated three small sticks of willow charcoal to white heat and plunged them into mercury. The mercury filled every pore of the carbon and remained imbedded as tiny droplets after the charcoal cooled.

The mercury-treated charcoal sticks then were arranged in the familiar "H" configuration. A more sturdy arrangement had a small lozenge shaped element of the mercury-treated charcoal loosely supported vertically between two blocks of carbon.

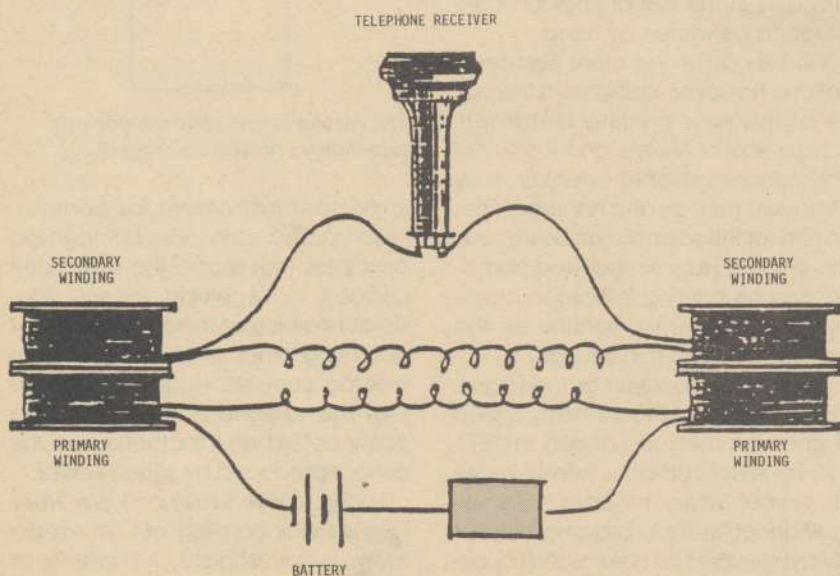The microphones constructed from mercury-treated carbon had greater sensitivity and better fidelity than those of any other combination of materials Hughes had previously tried.



The rheotome (R) used in Hughes' induction balance to produce current pulses in the circuit's primary windings initially consisted of a mechanical interrupter, but later was changed to a ticking clock and microphone.

Unfortunately, the sound transmitting ability of these arrangements was not long lasting. Within a period of only several hours after their manufacture, the performance of the mercury-treated carbon microphones deteriorated to the point where they were no longer capable of transmitting any sound. Similar microphones constructed of untreated carbon experienced no deterioration of performance.

(Those interested in constructing working models of Hughes' microphones are referred to the article "Build an 'Antique' Microphone" by Stanley A. Czarnik that appeared in the January 1991 issue of **Popular Electronics**.)

Being already quite financially secure, Hughes sought only new scientific knowledge, not monetary gain, from his development of the microphone. In 1878, he concluded the report of his microphone research to the Royal Society by saying "I do not intend to take out a patent, as the facts I have mentioned belong more to the domain of discovery than invention." Hughes felt that his reward came from being able to share his findings with the scientific community.

Edison Did Similar Work. During the early part of 1877, Thomas A. Edison developed the first of several "speaking telegraph transmitter" designs for which he would be credited. These devices actually were telephone transmitters, or microphones, and were similar in some respects to the microphones developed by Hughes.

Edison's initial design consisted of a diaphragm connected by means of a spring to three platinum points immersed in a dish of carbon granules. Sound waves acting on the diaphragm caused fluctuations in an electrical current flowing through the carbon granules and platinum points. These current fluctuations could be converted back into clearly understandable speech by Bell's telephone receiver.

Edison then designed a more practical "speaking telegraph transmitter" by using a metallic diaphragm in direct contact with a carbon disc. A patent application was filed by Edison on this telephone transmitter on April 27, 1877. Unfortunately for Edison, legal

Books and Articles of Interest.

"David Edward Hughes, F.R.S., 1831-1900," G. Burniston Brown, *Notes and Records of the Royal Society (London)*, Vol. 34, No. 2, pp. 227-239, 1980.

"The Life and Work of David Hughes," Sydney Evershed, *Journal of the Institution of Electrical Engineers (London)*, Vol. 69, pp. 1245-1250, 1931.

The Telephone, the Microphone and the Phonograph, Count Theodore A. L. Du Moncel, Harper & Brothers Publishers, 1879, Reprinted by Arno Press, New York, 1974.

A History of Wireless Telegraphy, J. J. Fahie, Dodd Mead and Co., New York, 1901, Reprinted by Arno Press, New York, 1971.

"On the Action of Sonorous Vibrations in Varying the Force of an Electric Current," David E. Hughes, *Proceedings of the Royal Society (London)*, Vol. 27, pp. 362-369, May 9, 1878.

"On an Induction-Currents Balance and Experimental Researches Made Therewith," David E. Hughes, *Proceedings of the Royal Society (London)*, Vol. 29, pp. 56-65, May 15, 1879.

Old Wires and New Waves, Alvin F. Harlow, D. Appleton Century Co., New York, 1936.

"David Edward Hughes: inventor, engineer and scientist," J. O. Marsh and R. G. Roberts, *Journal of the Institution of Electrical Engineers (London)*, Vol. 126, pp. 929-935, 1979.

"The early history of electronics: I. Electromagnetics before Hertz," Charles Susskind, *IEEE Spectrum*, pp. 90-98, August 1968.

"The Localization of the Bullet in President Garfield's Body," (unsigned under "Notes"), *The Telegraphic Journal and Electrical Review (London)*, Vol. IX, pg. 317, August 15, 1881. ■

actions by the Bell Telephone Company held up the granting of the patent for fifteen years.

Continuing his experimentation, Edison soon found that a small button of lamp-black carbon placed between two thin metal plates in series with a battery was a more efficient device for converting speech into electrical-current fluctuations. Edison applied for a patent on this telephone transmitter in 1878. The patent was awarded to him without any delays due to legal challenges.

Edison apparently had discussed his telephone transmitter designs with

W.H. Preece, chief electrical engineer for the British Post Office and a renowned electrical authority. Preece is also known to have had technical conversations with David Hughes concerning the latter's microphone experiments.

Certain similarities clearly existed between Hughes' microphones and Edison's telephone transmitters. Edison charged that Preece had committed a breach of confidence by telling Hughes of his (Edison's) invention. A "straight steal" was the phrase used by Edison to describe how he believed Hughes had gotten the idea for the microphone.

Edison found, however, that very few other persons supported him in his slanderous accusations. The personal integrities of both Hughes and Preece were highly regarded. Edison was ill-advised to have conducted these personal attacks.

The differences between Hughes' microphones and the telephone transmitters designed by Edison far outnumber the similarities. Coincidence, rather than treachery, certainly seems to be the likely cause of the similarities that do exist.

Hughes' Induction Balance. The microphone was also to play an important part in the normal operation of an "induction balance" Hughes would soon develop. More importantly from a scientific standpoint, however, the microphone would also produce some unexpected results of great scientific significance when used with that balance.

The induction balance developed by Hughes in 1879 consisted of two separate induction coils, each with a primary and a secondary winding. The secondary windings of the coils were connected together so that, at "balance," the current induced in one secondary winding cancelled the current induced in the other.

The primary windings of the induction coils were connected in series with each other as well as in series with a microphone and a battery. The microphone together with a nearby ticking clock formed a "rheotome" (literally a "current cutter") that created periodic pulses in the battery current flowing through the primary windings of the induction coils.

The current induced in the second-

ary windings exhibited the pulsating characteristic of the primary current. A telephone receiver connected in series with the secondary windings converted the current pulses into an audible signal and served as an extremely sensitive balance indicator.

The induction balance concept did not originate with Hughes. Several researchers had developed a similar circuit some twenty-five years earlier. Hughes' contribution was the use of the microphone and the telephone receiver to substantially increase the sensitivity of the circuit.

Placing a piece of metal near one of the coils caused the circuit to become unbalanced. The degree of unbalance was a function of the mass of the metal or, for pieces of metals of like weight, the type of metal used.

The sensitivity of the induction balance was sufficient to detect mass differences of less than one milligram in two samples of a pure metal. Similarly, the induction bridge could detect differences in purity as small as one part in ten-thousand in samples of equal mass.


Hughes' plan was to use the induction balance to gain information concerning the molecular structure of metals and alloys. He achieved only very limited success in this effort.

Of interest is the fact that Alexander Graham Bell used an induction bridge based on Hughes' design to locate the assassin's bullet in President Garfield. Despite success claimed in locating the bullet, physicians were unable to save the President's life.

Sparks Lead to a Discovery.

Hughes' first series of induction-bridge experiments were conducted in the fall of 1879. In those early investigations, switch contacts operated by a clockwork mechanism served as the rheotome used to produce periodic current pulses in the bridge's primary coil.

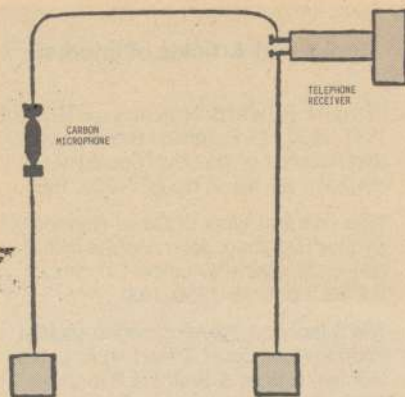With this arrangement, Hughes experienced trouble due to a clicking noise heard in the telephone receiver when he tried to balance the bridge. The clicking noise coincided with the sparks occurring across the contacts of the current interrupter mechanism. A spark, or "extra current" as Hughes called it, was produced at the contacts by the inductive voltage generated each time the current in the



Hughes improved his receiving circuit by grounding one side of both the carbon lozenge microphone and the telephone receiver.

primary coil was interrupted.

Hughes conducted numerous experiments before he convinced himself that the effects he was observing were not due to ordinary induction effects. He had studied extensively the induction effects that exist between telegraph wires and was considered an expert on the topic. Hughes knew that he was producing some new kind of "electric waves."

The sparking at the interrupter contacts actually was producing the electromagnetic waves James Clerk Maxwell had predicted mathematically some fifteen years earlier. To date, however, no one had succeeded in experimentally proving that these waves actually exist. Now, in 1879, Hughes apparently was both generating and detecting Maxwell's electromagnetic waves although he seemingly did not completely realize the true nature of the waves.

The audible response or "clicking" heard in the telephone receiver was due to the effects produced by a loose connection in the secondary circuit of the induction balance where that receiver was located. Suspecting that the loose connection was acting as what he called a "microphonic" contact, Hughes replaced it with one of his microphones, which consisted of a steel needle in light contact with a piece of carbon. The clicking in the telephone receiver persisted.

The First Coherers. Both the loose connection in the induction balance circuit and the steel-on-carbon contact of the microphone exhibited the

same behavior that would be re-discovered in 1890 by the French scientist Eduard Branly and again, independently, in 1892 by the English physicist Oliver Lodge. As Hughes had not published his findings, neither Branly nor Lodge were aware of his earlier work.

The name given the phenomenon by Lodge was the "coherer" effect. The coherer would become the most widely used and dependable detector of electromagnetic waves available until the advent of the vacuum tube.

The coherer effect is both remarkable and simple. The contact between two conductors, barely touching each other, ordinarily is not sufficient to permit an electric current to flow. However, when a nearby spark discharge occurs producing electromagnetic waves, the conductors become fused together. When that occurs, current easily flows through the junction.

Branly found that fine, unoxidized metal particles packed between metal electrodes in a glass tube normally conduct electricity very poorly. The tube of particles becomes a very good conductor, however, when a spark discharge occurs nearby. Lodge observed the same phenomenon with two small polished metal spheres barely touching each other. In both cases, tapping is required after each spark discharge to return the devices to their non-conducting state.

Following the occurrence of a spark discharge, unoxidized metal conductors ordinarily remain joined together until lightly tapped. Cohemers utilizing contacts comprised of certain other materials, however, are "self-restoring" in that they return to their non-conducting state without being tapped.

The loose contact in Hughes' original circuit together with the steel-on-carbon and carbon-on-carbon contacts in Hughes' later detector circuits formed "self-restoring" coherers. The momentary high conductivity of these contacts produced by the arrival of electromagnetic waves allowed a pulse of current to flow. That produced the clicking Hughes heard in the telephone receiver that was in series with the coherer contact.

(Continued on page 90)

ANTIQUE RADIO

By Marc Ellis

Tips and Tidbits

Well, gentle readers, I have to start off this month's column with a confession. Most of you will be picking up this issue of **Popular Electronics** on the verge of the winter season. But the publishing timetable is such that I'm writing these words back near the beginning of summer. It's a summer that has been very reluctant to arrive at the

could allow in the typical crowded "Mailbag" column. And I've been saving a few others—some for quite a while. I've also been waiting for a chance to present more of the interesting photographs that were submitted with entries to the recent "With the Collectors" contest. It looks like my opportunity to run those letters and photos has finally arrived, so let's sit back, relax, and take an unhurried look at them.

DXING ON A RADIOLA III

Dr. Dan Fielder (Professor Emeritus, School of Electrical Engineering, Georgia Institute of Technology, Atlanta, GA 30332) has owned several radio models, now considered antiques, since the days when they were new. But his fondest memories are associated with the little Radiola III that he had as a child. For those not familiar with that diminutive yet sensitive set, the Radiola III is housed in a box that measures approximately 8 x 6 x 5-inches and contains just two tubes.

Both of the tubes are type WD-11's. One serves as a regenerative detector and the other as an audio amplifier. The set provided only earphone volume, though an accessory "balanced amplifier" (using another pair of WD-11's) could be added to drive a speaker. The set used no variable capacitors; instead, adjustable coils ("variometers") were used to control tuning and regeneration.


A friend of Dan's older brother, Walter Pierce by

name, owned an identical Radiola III. Using this simple receiver, the young high-school student had set long-wave DX receiving records that attracted national attention back in the 1920's. For example, when *Radio Index* magazine ran a DX'ing contest, Walter won it with 656 verified foreign stations. Eventually, he accumulated verifications from more than 2600 stations in every country in the world.

At one point, Hugo Gernsback, founder of our publishing company and—at that time—editor of *Radio News* magazine, actually sent a writer to visit the Pierce home and document these feats. Recently, Dr. Fielder wrote to Walter and asked him to share his memories of this event and some of his DX'ing secrets, with the idea that the recollections might be printed in this column.

As evidenced by his detailed response, Mr. Pierce's memories of those eventful times are still quite sharp. When Armstrong Perry (Mr. Gernsback's representative) arrived, Walt tells us, "I was listening to LR9 in Buenos Aires, 1190 or 1200 KC, and he was amazed at the quality of the reception. Perry stayed overnight and next morning we tuned in JOAK, Tokyo; 1YA, Auckland, N.Z.; 2BL, Sydney, Australia, and many others. He was able to dispel all doubts that a farm boy in Saunderson, Rhode Island could receive stations from all over the world."

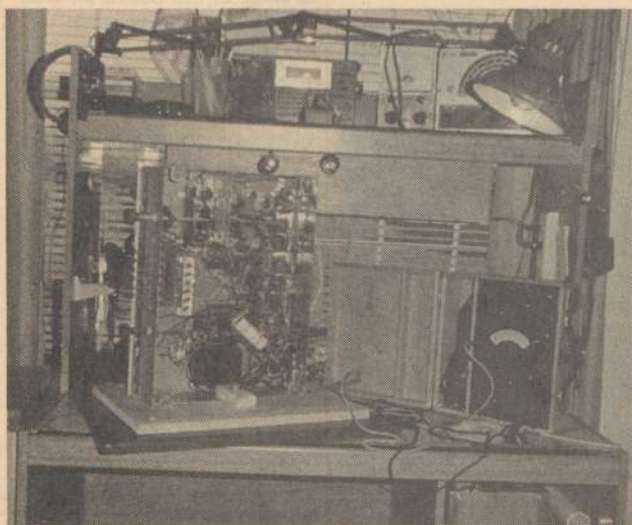Walt reports that the secret of his success was an unorthodox, and highly effi-



A heavy chassis sits atop the lazy susan installed on Hipolit Ceckowski's well-organized service bench (see text).

midwestern location where I live, but the past few weeks have finally brought some fine weather.

The weather was fine enough to make me play hooky from the Hallicrafters *Sky Buddy* restoration project I've been chronicling on these pages. So as a result (blush), I have no progress to report. However, it's an ill wind that blows no good, and I have an excellent use for the space allotted to me in this issue.

I've recently received a few letters that tell stories or share information requiring a bit more space than I



Hipolit Ceckowski's beautifully restored Grebe. He built the cabinet himself, copying it from a period photo.

cient grounding system. The ground wire was connected to a leaky old Ford radiator buried up to its filler cap in the ground. The radiator was kept full of water so that the soil around it was constantly being moistened.

Additional grounding pipes were driven all around the radiator and connected to the main ground lead with heavy copper wire. The more ground pipes he connected, the better was the reception of weak stations. There were suggestions that reception might be further improved if he would substitute some of his dad's hard cider for the water in the radiator, but that particular experiment was never tried!

Walt usually began his listening sessions by checking for station KOA in Denver. If it was coming in well, he knew conditions were favorable and settled in for some serious DX'ing. Sometimes the session lasted all night. By 2 AM, most American, Canadian, and Mexican stations were shutting down, leaving the airwaves clear for the European stations—which were just beginning their broad-



Here's Dave Booth's (Westminster, MD) workbench and listening post. Dave was one of the winners in our "With The Collectors" contest (see July, 1992 column).

cast days. Then, by 4 or 5 AM, the Japanese, Australian, and New Zealand stations would begin to come through.

Mr. Pierce's DX'ing activities ended in the late 1930's, when the American stations had become much more numerous and powerful, and had begun to stay on all night. That made it much more difficult to hear the foreign stations but, because of the difference in channel spacing (10 kHz for America, 9 kHz for Europe), it was still possible to hear DX between the stateside signals.

Many thanks to Walt and

Dan for sharing these vivid memories of DX'ing in earlier times. And if anyone knows where a Radiola III can be obtained, or has one for sale, please contact Dan at the address given above. He'd love to get his hands on one again!

THE KAISER'S CLANDESTINE STATION

About a year ago, Ron Oberholtzer (North Cape May, NJ) sent me some mini-articles on subjects that he felt had been neglected by the antique-radio press. And since his experience with radio goes

construction, all materials were brought in by ship from Germany, helping to give the project a lower profile.

The high-powered installation wasn't exactly a secret, because it boasted a 300-foot high transmitting antenna (resting, Bob tells us, on a giant insulator) and several smaller receiving ones. But the isolated, inaccessible location, and the looser security of those times, allowed the station to operate for quite a while without attracting a lot of attention. It is thought that the order for the fateful sinking of the *Lusitania* was sent through Tuckerton.

Of course, our government eventually got wind of this operation, and the facility was confiscated after our entry into the war. At war's end, RCA acquired the property and used it as the site for a multiple-frequency shortwave transmitting station. In the late 1960's, RCA built a replacement station and sold the property to a developer.

The old tower was dynamited with much public fanfare, ending decades of radio operation on the site. But the street giving access to the area is still known as "Radio Road."

Thanks to Ron for sending in this information, and I'd be glad to hear from anyone who can supply more details. For instance, I remember once reading about a ham radio operator who exposed a secret German station during the same era. The Morse transmissions were encoded by mechanically speeding them up. But the resourceful ham recorded the bursts on an Edison cylinder and was able to play them back at a slower speed. Was the Tuckerton station the one involved? It would be interesting to know.

back some 70 years, he's speaking with some authority! I've been holding Bob's letter in my "use when I have space" file and here, at last, is an opportunity to discuss one of the items.

Bob writes that back in about 1915, before the U.S. entered World War I, the German high command decided that a radio station was needed on our shores to direct U-boat activity. Without notifying our government of their intentions, they selected a sparsely-populated marshy site near Tuckerton, NJ and began building. Though local help was used for

SOME HELPFUL TIPS

Interested in replicating shortwave sets of the 1930's and 40's using coil data from vintage construction articles? Billy Pogue (Lake Havasu City, AZ) recommends that you purchase the case of 72 pharmacist's bottles offered at \$6.00 by American Science and Surplus, 601 Linden Place, Evanston, IL 60202-2610. Their dimensions and electrical characteristics are excellent for service as coil forms. If you need a plug-in unit, cement your "form" into a base taken from a broken tube.

Think the above is a good idea but don't know where to get your hands on a construction article? Billy suggests that you send for a catalogue from Lindsay Publications, Inc., P.O. Box 538, Bradley, IL 60915 (enclose a dollar with your request). Lindsay offers a rich variety of high-quality reprints, including many collections containing period shortwave hobby articles—some taken from our predecessor magazine *Short Wave Craft*.

Recently D. Derek Verner (Tuckahoe, NY) needed a 67½-volt "B" battery (Eveready 467) to power a piece of World War II surplus test equipment. Once available at a nominal cost from almost any drugstore, this battery is now available on special order for a price of about \$30.00.

Not to be daunted, Derek tried another, more inventive approach. He purchased a number of 9-volt batteries on sale from Radio Shack. He soldered seven of them together to make a 63-volt unit. Then he added a 4½-volt battery obtained by slicing open another 9-volt job and separating out 3 cells.

Though Derek wasn't really going for an authen-

tic look, he couldn't resist installing his creation in the old battery's carefully removed outer shell. It fit just fine. As a finishing touch, he filled the voids between the new battery and the old shell with some silicone caulk. Total cost: less than five dollars.

Hipolit J. Ceckowski (Vernon Hills, IL) sent me a shot of a lazy susan he made by pinning together two boards (their dimensions look like they might be approximately 10 inches by 2½ feet each) with a dowel. Even a large chassis becomes easy to work on when placed on the lazy susan, because it can be easily rotated, giving access to all sides.

In addition to that picture, I'm running another of 80-year-old Hipolit's shots showing his meticulously-restored Grebe. It's installed in a home-crafted cabinet copied from a photograph, and Hipolit also did extensive restoration work on the accompanying horn speaker. As you can see from the photograph, it was wonderful work!

WANTED: VINTAGE THEREMIN

Do you have a vintage theremin you'd be willing to donate to a good cause? Contact Joseph O'Connell, Exhibit Planner, Liberty Science Center, Liberty State Park, 251 Phillip St., Jersey City, NJ 07304-4629 (phone 201-451-0006). The Center is a newly-opening, non-profit educational institution located on the New Jersey mainland at a point very close to Liberty Island and the Statue of Liberty. They'd love to acquire an original instrument. They have the know-how to restore a defective one, and they promise to display it prominently and with the proper recognition. ■

40,083

ELECTRONIC COMPONENTS

Whether you order 1 part or all 40,083...MOUSER stocks and...can ship today!!

CALL...
(800) 992-9943

for your
FREE
CATALOG



2401 Hwy 287 N.
Mansfield, TX 76063

MOUSER ELECTRONICS

Sales & Stocking Locations Nationwide

CIRCLE 9 ON FREE INFORMATION CARD

Learn VCR repair at home!

MAKE GOOD MONEY IN YOUR OWN FULL- OR PART-TIME JOB



Professional-level home study course. You will master easy-to-learn, high-profit repairs *without* investing in high-tech instruments or a costly workshop.

Want more independence and higher income? Send or call today!

Free career kit:
800-223-4542

Name _____
Address _____
City _____ State _____ Zip _____

The School of VCR Repair

2245 Perimeter Park Drive
Dept. VM341 Atlanta, Georgia 30341

COMPUTER BITS

By Jeff Holtzman

Word BASIC

Last month, we discussed the emerging third wave in software evolution: integrated tool sets. As an example, we discussed the major features of Microsoft's Word for Windows 2.0 (WW2), which I consider to be the premier word processor for PC's. WW2 has four groups of features that make it the Mt. Everest of PC word processors: outlining, styles, templates, and the Word BASIC macro language. Last time, we talked

keystrokes, and toolbar functions to give WW2 a whole new look.

Table 1 summarizes the types of statements (that perform some task) and functions (that return information to a calling routine) available in WB. What can you do with WB that you can't do either in a word processor by itself, or in some programming language by itself?

You can use WB macros to insert arbitrary text strings (e.g., time, date, author) into a document; count and display the number of words in a document; automatically format text in specified ways; cause particular actions to occur whenever you create a new document, open a pre-existing document, or close a document; move the insertion point to various places in the document and perform an arbitrary sequence of commands when you get there; display information on the screen; create (by visually drawing) dialog boxes that look and feel more or less like "real" Windows dialogs; set up "conversations" with other Windows applications; create libraries of WB routines to share or sell; clean up ASCII text files; replace formatting with ASCII codes for typesetting; and lots more.

The nice thing is that if you have learned BASIC—any dialect on any machine—it's easy to get up to speed with WB quickly.

EXAMPLE MACROS

The following are a couple of simple macros intended to give you a

taste for what WB macros are like. The first (See Listing 1) is a macro that counts the number of words in a document and displays the value in a message box.

Note the "Sub MAIN" and "End Sub" surrounding the main body of the code. Every WB macro has a routine labeled "MAIN," and may optionally have other subroutines and functions as well. The routine works first by creating a data structure in memory corresponding to the Summary Info item of WB's File menu. The next line causes WB to update the values of that dialog box (i.e., to count the words in the document). The next line brings the updated values to accessible variables. The MsgBox line then displays a particular variable, NumWords, in a simple message box with an OK button, which the user must click before other operations can continue.


You could change that line to read:

```
Print "Number of words: " + dlg.NumWords
```

in which case the value would display in the status line until the user pressed a key or performed some action with the mouse.

The next example (See Listing 2) shows a little routine that displays the ASCII/ANSI value of a character, and then offers to delete all occurrences of it from your file. It's useful for cleaning out junk from text files downloaded by modem or imported from other word processors. The macro will not replace ASCII NUL (0), a WB limitation.

In the listing, a backslash

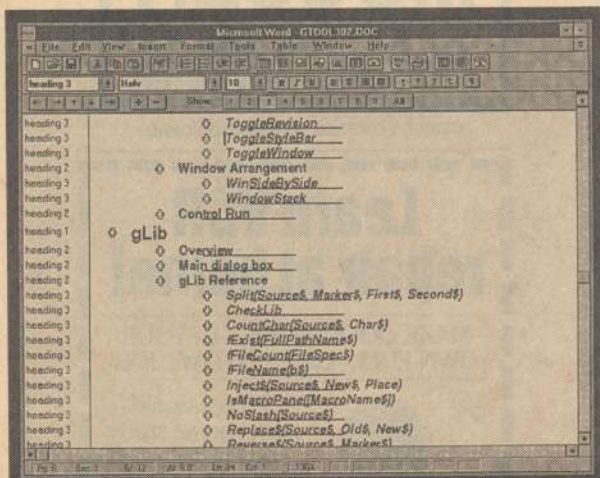

The major features of Microsoft's Word for Windows 2.0—outlining, styles, templates, and the Word BASIC macro language—make it the Mt. Everest of PC word processors.

about the first three; this time, we'll take a look at Word BASIC (WB).

WORD BASIC

You can view WB as a version of BASIC that also happens to include extensive built-in support for text-processing operations (searching, replacing, formatting, etc.), as well as support for altering the environment itself.

Conceivably, you could completely redefine menus,

Give a Friend a Year of Electronics Fun this Christmas...



Does fighting the crowds at Christmas short-circuit your holiday fun? Don't blow a fuse this year. . .for the friend who shares your love of project-oriented electronics — or a youngster who may need only a spark to ignite a life-long interest — give a gift subscription to Popular Electronics.

Popular Electronics readers get the know how they need to build exciting, educational, and useful projects like these . . .a touch light dimmer. . .a traveler's theft alarm . . .an economy NiCd battery charger. . .a voice synthesizer. . .a portable frequency counter. . .a shortwave converter. . .a stereo graphic equalizer. . .even a robot!

PLUS. . .Gizmo, our honest and straight-shooting review of the latest consumer-electronics gear. . .Market Center, featuring mail-order merchants that are ready to help you in all your hobby activities. . .articles and columns covering every aspect of the electronics hobby — including antique radio, shortwave listening, ham radio, computers, scanners, circuit design, and more!

SAVE MONEY. . .A great gift to receive, Popular Electronics is also a great gift for *you* to give! The Special Holiday Rate saves you \$23.05* off the newsstand price on each gift. You can save another \$23.05* when you start or extend your own subscription at the same time. It's our "thank-you" for sharing Popular Electronics with a friend this Christmas.

Send no money, unless you prefer. We'll be glad to bill you in January, next year. Just take a brief moment to go over your gift list and make sure you haven't forgotten anyone who might appreciate the many benefits of Popular Electronics. Then write the names on the attached Gift Certificate and mail it back in the postage-paid reply envelope. . .we'll take it from there!

Your friends will receive a handsome gift announcement card signed with your name just before Christmas. And all through the new year they'll remember and appreciate your thoughtful gift! So don't blow a fuse. . .take it easy and enjoy the holidays. Give Christmas gifts of Popular Electronics!

Popular Electronics®

*Basic sub rate—1 yr/\$21.95

GET SMART

Quick & Cheap With Books!

Order Today!



TALK!

Now you can get a ham license without a Morse code test!

All About Ham Radio by Harry

Helms tells you how. It covers what hams do... how to select equipment and antennas... using packet radio and ham satellites... operating procedures... and contacting hams in foreign countries! Also includes an introduction to radio theory and electronics. Start talking to the world today! Only \$19.95.



LISTEN!

Listen to history as it happens via shortwave radio! **Shortwave Listening Guidebook** by

Harry Helms tells you all about the shortwave bands, when and where to listen, reception patterns, and how to select the shortwave radio that's right for you. It also profiles major world broadcasters. Includes hundreds of frequencies for stations worldwide and times to hear them. Just \$16.95.



BUILD!

The Forrest Mims Engineer's Notebook by Forrest Mims (who else?) includes hundreds of

applications circuits using today's most popular linear and digital ICs! Forrest includes complete data for each IC, such as pin connections, logic tables, waveforms, & more! *If you experiment with ICs, you gotta get this book!* A steal at \$14.95.

You can get HighText books at your favorite technical bookstore, electronics parts dealer, or radio equipment dealer. Or order direct from HighText! Include \$3 per book for shipping (\$4 Canada, \$5 elsewhere). CA please add sales tax. U.S. funds only please.

HighText
publications inc.

7128 Miramar Road, Suite 15L
San Diego, CA 92121

TABLE 1

Category	Statements	Functions
Movement and selection	Move and select text	Return information about the position of the insertion point and about the text currently selected
Formatting	Format the selected text	Return information about the formatting of the selected text
Editing	Insert and delete text, insert glossary items, add and delete rows and columns in tables	Return information about the result of editing operations
Control	Establish structures for repeating tasks, testing results, and defining routines	Return information about the Word environment, such as the current time or date, and converting data from one type to another
Views and windows	Change views in a document, move windows	Return information about the size and placement of document windows
Tools	Correspond to commands on the Tools menu for checking spelling, hyphenating, checking grammar, managing the macro-editing environment, and so on	Return information about the operation of the Tools commands being used
Dialog box	Create custom dialog boxes	Return information from built-in or custom dialog boxes
File	Open, save, close, and delete files	Return information about files
DDE (dynamic data exchange)	Establish links to other applications running in Windows	Return information to a macro from another application

LISTING 1

```
Sub MAIN
Dim dlg As FileSummaryInfo
FileSummaryInfo .Update
GetCurValues dlg
MsgBox "Number of words: " + dlg.NumWords
End Sub
```

(^) at the end of a line indicates that the next line is really a continuation of the current line. The routine uses a built-in WB variable called Selection\$(), which contains the text highlighted in the document at the time the macro runs, or only the character directly to the right of the insertion point if no text is high-

lighted. The macro first assigns to A\$ the first (and possibly only) character in Selection\$(). Then the routine puts up a message box that displays the ASCII value of the character in A\$, and asks whether the user wants to delete all occurrences of it. If so, the routine then invokes the built-in replace routine, telling it to replace

LISTING 2

Sub MAIN

```
AS = Left$(Selection$( ), 1)
A = MsgBox("Value of this character = " + \
Str$(Asc(AS)) + ". Delete all occurrences?", \
"Jeff's Handy Dandy Cleaner Upper", 4)
If a = -1 Then EditReplace .Find = AS, \
.Replace = "", .WholeWord = 0, \
.MatchCase = 0, .Format = 0, .ReplaceAll = 1
```

End Sub

all occurrences of AS with a null (empty) string.

Those two examples barely scratch the surface of what WB can do. However, I hope they will inspire you to do some more research on your own. Next time, we'll discuss linking WinWord documents with files from other packages.

FOR MORE INFORMATION

The printed documentation that comes with WW2 provides almost nothing on WB. However, WW2 contains a fairly complete built-in on-line reference for all WB statements and functions; just highlight a keyword and press F1. For more in-depth coverage, you may want to refer to the following books on Word BASIC, all published by Microsoft (One Microsoft Way, Redmond, WA 98052; Tel. 206-882-8080; FAX 206-93MSFAX): *Using Word-Basic*, *WordBasic Primer*, and *Microsoft Word Technical Reference*. The latter two were originally released for version 1.x of WinWord, but still have useful information and examples. Using WordBasic documents version 2.x, and has a thorough reference section, but fewer examples than the others.

The MSAPPS section of CompuServe has a forum dedicated to WinWord; lots of good hints and samples are available there. In particular, you'll want to check

out several shareware packages of WB macros. Probably the best is the Gadfly Toolbox, which provides a useful set of macros including a version of File Open that allows you to select from a prepared list of your most-used subdirectories, as well as several macros for managing the toolbar, macro-keystroke assignments, and more. Also of interest is the Windows Office Power Pack (WOPR), which contains an editor for toolbar icons, and several ambitious, albeit buggy, fancy-print macros. By studying the macros contained in those packages, you can quickly become a WB guru. ■





Let's close the book
on forest fires.

Ad Council A Public Service of This Magazine & The Advertising Council

PCB and SCHEMATIC C.A.D.

EASY-PC

\$195

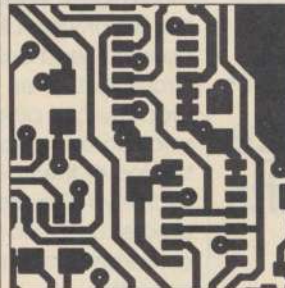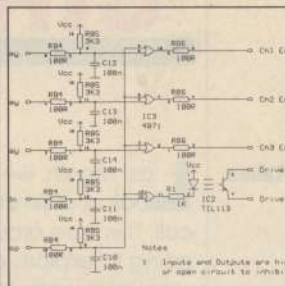

- Runs on PC/XT/AT/386/486 with Hercules, CGA, EGA or VGA display and many DOS emulations.

- Design Single sided, Double sided and Multilayer boards.

- Provides Surface Mount support.

- Exceptionally fast operation.

- Standard output includes Dot Matrix / Laser / Inkjet Printers, Pen Plotters, Photo-plotter and N.C. Drill.

- Award winning EASY-PC is in use in over 13000 installations in 70 Countries World-wide.

- Very easy to learn and use.

- Not Copy Protected.

Options - 500 Piece Surface Mount Library \$112
1000 Piece library \$75.00 Gerber Import facility \$195.00

For full details write, call, fax or use Inquiry #

Number One Systems Ltd. 1

REF: PEUSA, HARDING WAY, SOMERSHAM ROAD, ST. IVES, HUNTINGDON, CAMBS, ENGLAND, PE17 4WR

Telephone

USA: 011 44 480 61778 (7 lines)

Intl: +44 480 61778

FAX: 011 44 480 494042

BRITISH
DESIGN
AWARD
1989

AMERICAN EXPRESS,
MASTERCARD and VISA
WELCOME.

CIRCLE 5 ON FREE INFORMATION CARD



LEARN COMPUTERS!

Home study. Become an expert with personal computers for home or business use. Step-by-step instruction is easy to understand, even if you have little or no computer experience. Learn in your spare time, at your own pace. Send or call today for your free career literature.

CALL 800-223-4542

Name _____
Address _____
City _____ State _____ Zip _____

SCHOOL OF COMPUTER TRAINING

2245 Perimeter Park
Dept. KM341 Atlanta, Georgia 30341

CIRCLE 12 ON FREE INFORMATION CARD

CIRCUIT CIRCUS

By Charles D. Rakes

More High-Voltage Circuits

Last month, we took a look at a simple Tesla coil. This time around, we're going to explore a few more high-voltage circuits, the first of which is a more powerful Tesla-coil driver circuit that, when adjusted properly, can produce a small corona discharge at the top of the coil. The circuit will also produce a greater output in the energy-transmission mode of operation.

Transformer T1 (a 24-volt, 2-amp, center-tapped unit) and diodes D1–D4 (configured as a full-wave bridge rectifier) supplies about 35-volts DC to the drain of Q1 through the primary winding of T2.

A voltage plucked from the center tap of T1 is fed to a 7808 8-volt regulator (U1) and its output is used to power U2, which is configured as a tunable squarewave oscillator. With

and collapsing current in the primary of T2 that induces a current of greater magnitude in its secondary winding. The output of T2 is then applied to the Tesla coil through LED1 and LED2 (which serve as tuning indicators).

Transformer T2 was made by first winding between 12 and 20 turns of #26 enamel-coated copper wire on an Amidon Associates (2216 East Gladwick St., Dominguez Hills, CA. 90220) EA-77-250 ferrite "E" coil core for the primary, and then winding 150 to 175 turns of the same wire on top of that for the secondary winding.

Although transformer T1 is specified as a 24-volt unit, the circuit will work with units that have a lower voltage rating. If a lower voltage transformer is used in the circuit's power supply, the primary of T2 should have fewer windings—while staying within the 12- to 20-turns range—and the secondary should have more

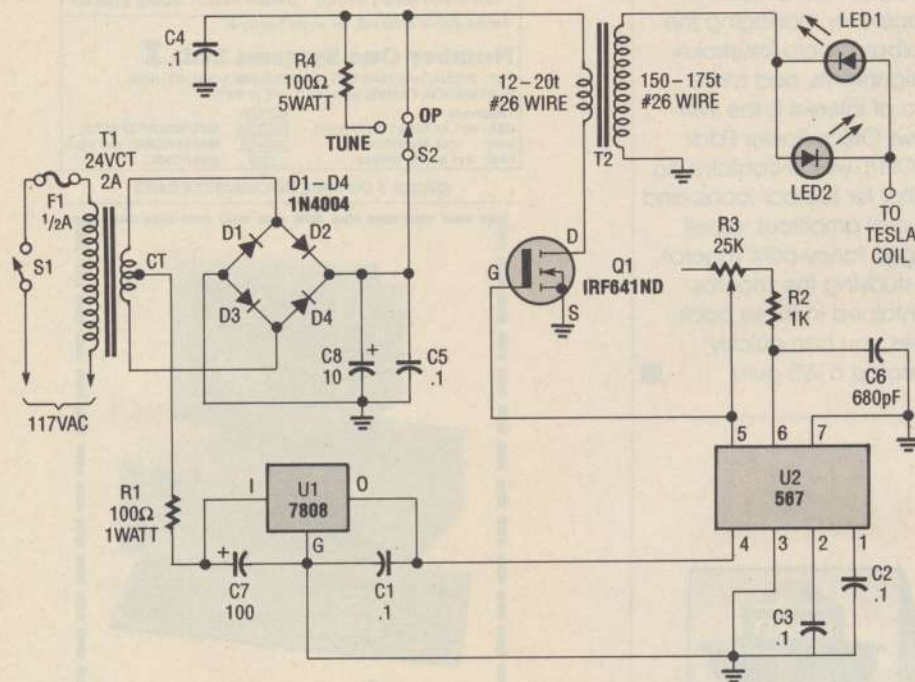


Fig. 1. The operation of this driver circuit—centered around a 567 tone decoder (U2), an IRF641-ND N-channel enhancement-mode hexFET (Q1), and a hand-wound step-up transformer (T2)—is rather straightforward.

DRIVER CIRCUIT

Figure 1 shows a schematic diagram of our first driver circuit. The operation of that circuit—centered around a 567 tone decoder (U2), an IRF641-ND N-channel enhancement-mode hexFET (Q1), and a hand-wound step-up transformer (T2)—is rather straightforward.

the component values shown, the oscillator operates at somewhere between 100 and 350 kHz, depending on the setting of R3. The output of U2 at pin 5 is applied to the gate of Q1, causing it to turn on and off in sync with the output of the oscillator. The on/off cycling of Q1 produces a continually rising

WARNING!!! This article deals with and involves subject matter and the use of materials and substances that may be hazardous to health and life. Do not attempt to implement or use the information contained herein, unless you are experienced and skilled with respect to such subject matter, materials, and substances. Neither the publisher nor the author make any representations as to the completeness or the accuracy of the information contained herein, and disclaim any liability for damages or injuries, whether caused by or arising from the lack of completeness, inaccuracies of the information, misinterpretations of the directions, misapplication of the information or otherwise.

PARTS LIST FOR THE DRIVER CIRCUIT

SEMICONDUCTORS

U1—7808, 8-volt, 1-amp, voltage-regulator, integrated circuit
 U2—567 tone decoder, integrated circuit
 Q1—IRF641-ND or similar hexFET
 D1—D4—1N4004 1-amp, 400-PIV, silicon rectifier diode
 LED1, LED2—Light-emitting diode

RESISTORS

R1—100-ohm, 1-watt, 5%
 R2—1000-ohm, 1/4-watt, 5%
 R3—25,000-ohm potentiometer
 R4—100-ohm, 5-watt, 10%

CAPACITORS

C1—C5—0.1-μF, ceramic-disc
 C6—680-pF, ceramic-disc
 C7—100-μF, 50-WVDC, electrolytic
 C8—10-μF, 50-WVDC, electrolytic

ADDITIONAL PARTS AND MATERIALS

S1—SPST toggle switch
 S2—SPDT toggle switch
 F1—1-amp fuse
 T1—24-volt, 2-amp, power transformer
 T2—See text
 Perfboard materials, enclosure, Amidon Associates, Inc., #EA-77-250 ferrite-core coil form and bobbin, heat sink, IC socket, molded AC power plug with line cord, wire, solder, hardware, etc.

turns. If the transformer has a higher output voltage rating (say 28 to 36 volts), increase the number of turns in the primary and decrease the number of secondary turns.

To obtain the best possible impedance match between your driver circuit and the Tesla coil, try experimenting with different turns ratios on T2. The time spent tweaking the driver circuit pays off in a better coil output.

To test the circuit in Fig. 1, connect its output to the bottom end of your test Tesla coil, place S2 in the TUNE position, apply power, and adjust R3 until LED1 and LED2 "burn" their brightest. Then flip S2 to op (operate) and carefully retune the circuit for maximum output.

SOLID-STATE DRIVER

Our next circuit, see Fig. 2, takes a slightly different ap-

proach to generating a high-voltage output. In this high-voltage circuit, an automotive ignition coil driven by a solid-state circuit is used to generate about 10 to 25 kV.

In that circuit, as in the previous circuit, a 567 tone decoder (U1) is configured as a low-frequency, tunable, squarewave oscillator. The oscillator's output, at pin 5, is buffered by an emitter-follower, built around Q1 (a 2N3904 general-purpose NPN silicon transistor). The collector of Q1 is tied to the positive supply rail, so that when it turns on, a positive voltage is delivered to the base of Q2 (an MJE3055 NPN silicon power transistor). As the output of U1 alternately goes high and low, Q2 follows, producing a pulsating DC voltage (12 to 15 volt) in the primary of the ignition coil (T1). That causes an even higher voltage (up to 25 kV) to be induced in

the secondary winding of transformer T1.

When assembling the circuit, the power transistor (Q2) should be mounted to at least a 2-inch square, aluminum heat sink.

Making sparks is easy with a solid-state driven coil. Simply position the ignition coil's output wire about 1/2 to 3/4 inches from circuit ground (common) and set R4 for maximum resistance. Apply power and adjust R4 for the strongest spark. Right away you should also notice an unusual smell coming from the spark discharge. That's the smell of ozone. If you intend to experiment with the circuit for long periods of time, it's a good idea to do so in a well ventilated area.

Be careful when operating the coil because the

sparks will shock you. With the Tesla coil operating at a much higher frequency, the shock hazard is lessened somewhat, but not eliminated, and it can still give you a slow-healing RF burn.

Hands off is the best advice you can get when dealing with any high-voltage circuit.

CAPACITOR-DISCHARGE DRIVER

Next is a one-shot, capacitor-discharge, high-voltage generator, consisting of two transformers (T1 and T2), a diode (D1), a fairly large value capacitor (C1), and a SPDT switch (S2), as shown in Fig. 3.

When power is applied to the circuit, T1 steps the voltage up to about 150 volts. Diode D1 rectifies the secondary's AC output,

PARTS LIST FOR THE SOLID-STATE DRIVER

SEMICONDUCTORS

U1—567 tone decoder, integrated circuit
 Q1—2N3904 general-purpose NPN silicon transistor
 Q2—MJE3055 NPN silicon power transistor
 D1—8-volt, 1/2-watt Zener diode

RESISTORS

R1, R2—100-ohm, 1/2-watt, 5%
 R3—10,000-ohm, 1/4-watt, 5%
 R4—50,000-ohm, potentiometer

CAPACITORS

C1—C4—0.1-μF, ceramic-disc
 C5—100-μF, 16-WVDC, electrolytic

ADDITIONAL PARTS AND MATERIALS

T1—Auto ignition coil
 Perfboard materials, enclosure, heat sink for Q2, IC socket, 12–15-volt DC power source, wire, solder, hardware, etc.

PARTS LIST FOR THE CAPACITOR-DISCHARGE DRIVER

D1—1N4004, 1-amp, 400-PIV, silicon rectifier diode
 C1—2–10-μF, 250-WVDC, paper
 T1—150-volt step-up transformer
 T2—Auto ignition coil
 S1—SPST switch
 S2—SPDT switch
 F1—1-amp fuse

Perfboard materials, enclosure, AC molded power plug with line cord, wire, solder, hardware, etc.

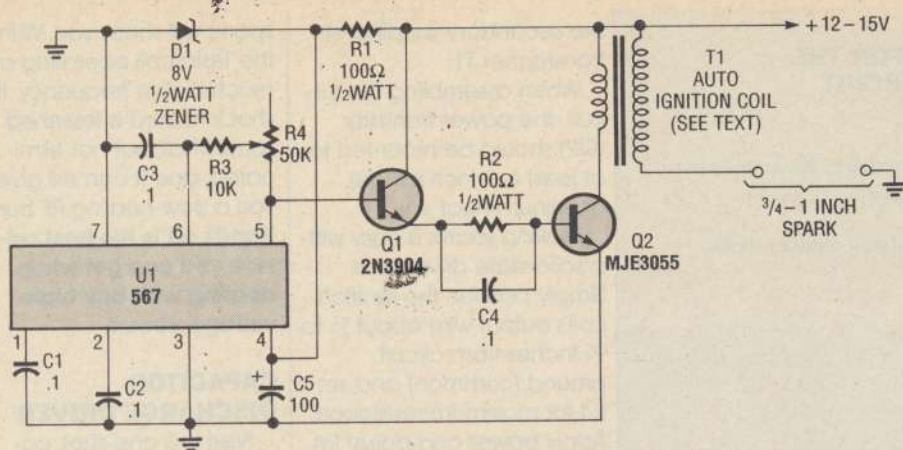


Fig. 2. The Solid-State Driver circuit takes a slightly different approach to generating a high-voltage output. In this circuit, an automotive ignition coil is used to generate from 10 to 25 kV.

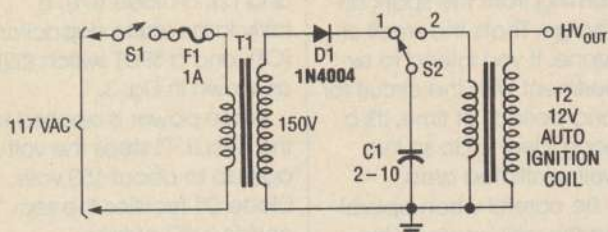


Fig. 3. The Capacitor-Discharge Driver—which is manually operated—consists of two transformers (T1 and T2), a diode (D1), a fairly large value capacitor (C1), and a SPDT switch (S2).

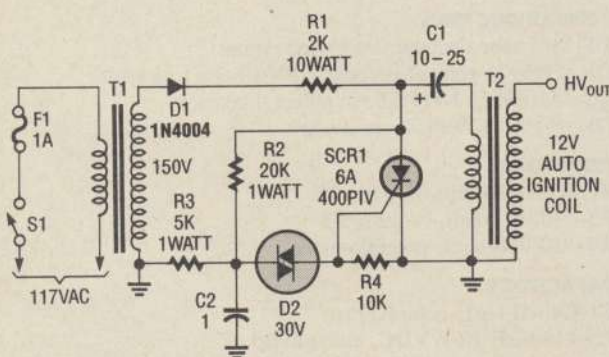


Fig. 4. The Regenerative Capacitor-Discharge Driver expands the previous circuit into a self-repeating, high-voltage generator.

producing a 200-volt peak, pulsating-DC output. With S2 in the position shown, C1 charges toward the supply voltage. Then when S2 is flipped to the other position, the charge on C1 is rapidly dumped to the low-impedance primary of an auto ignition coil (T2), resulting in a sudden burst of energy in T2's secondary.

The capacitor discharge method of generating

high-voltage has been in use for several decades delivering fire to spark plugs in high-performance passenger and race cars.

REGENERATIVE CAPACITOR-DISCHARGE DRIVER

Our next circuit, see Fig. 4, expands the previous circuit into a self-repeating, high-voltage generator. In that circuit, AC line voltage is

fed to T1 (a 150-volt step-up transformer). The output of T1 is fed to D1, which rectifies the AC voltage to provide a pulsating-DC output (of about 210 volts) that is fed through R1 to C1, causing it to begin charging toward the supply rail. At the same time, the voltage delivered to C1 is also fed through a voltage divider comprised of R2 and R3, causing C2 to begin charging.

When the charge on C2

reaches about 30 volts, diac D2 turns on supplying gate current to SCR1, causing it to fire, discharging C1 through the primary of T2 (the auto ignition coil), inducing a high-voltage output at the coil's secondary. When the charge on C1 drops below the SCR's holding level, the SCR turns off, C1 again begins to charge through R1, and the event is repeated.

The value of R1 determines the operating frequency of the circuit. The larger the resistance of R1,

PARTS LIST FOR THE REGENERATIVE CAPACITOR-DISCHARGE DRIVER

SEMICONDUCTORS

D1—1N4004, 1-amp, 400-PIV, silicon rectifier diode
SCR—6-amp, 400-PIV, (10 mA or less gate current) silicon-controlled rectifier
D2—30-volt diac, (Mouser #519-HT-32, or similar)

RESISTORS

R1—2000-ohm, 10-watt (see text)
R2—20,000-ohm, 1-watt
R3—5000-ohm, 1-watt, 5%
R4—10,000-ohm 1/4-watt, 5%

CAPACITORS

C1—10- to 25-μF, 400-WVDC, electrolytic
C2—1-μF, 100-WVDC, electrolytic

ADDITIONAL PARTS AND MATERIALS

T1—150-volt, step-up transformer
T2—Auto ignition coil
S1—SPST switch
F1—1-amp fuse
Perfboard materials, enclosure, AC molded power plug with line cord, heat sink, wire, solder, hardware, etc.

the slower the pulse rate. The smaller the resistance, the faster the pulse rate. The values of R2 and R3 can be varied to change C1's maximum charge voltage. Lowering the value of R3 increases the charge on C1, as well as the magnitude of the output voltage at the secondary of T2; increasing its value has the opposite affect.

That's all for now. Enjoy your experimenting until we meet here next month. ■

THINK TANK

By John J. Yacono

558 Finale

Last month, I continued our discussion on the 558 timer and presented some of the alarm circuits that I've received. This month, I'll continue with both themes, starting with some astable applications for the 558.

ASTABLE CONNECTIONS

Last month, I introduced the concept of connecting

low time of the output. As in almost all 558 circuits, pull-up resistors (R3 and R4) are used to assist the open-collector outputs to produce logical highs.

The circuit may seem like a bit of overkill, especially since a typical 555 astable circuit only needs two resistors and one capacitor to do the same job. However, this circuit has advantages over its 555-based competitor. For one thing, since the low-time and high-time are pretty much independent of one another, the 558 astable oscillator can produce duty-cycle values that would require additional components for the standard 555 astable circuit. The 558 circuit as shown can be designed to produce duty cycles from almost zero to 100%.

Furthermore, selecting parts values is easier. If you know the low time you want, divide it by the value of the capacitor you wish to use for C1 and the result will be the value for R1. Perform that same procedure with the high time using the value of C2 to find the value of R2 and you're done. The values of the pull-up re-

sistors (R3 and R4) are not too important since the 558 outputs can handle 100 mA of current (yes, 100). Just make sure that they limit current enough to protect the load at the circuit's output.

There is a simple variation on this circuit that really blows the doors off the 555, see Fig. 2. It functions exactly like the circuit in Fig. 1, however a variable resistor has been added. It provides a frequency-control voltage to the VCO input of the 558 timer chip. Since both sections receive the same control voltage, the timing of each section is affected to the same degree. The result is a circuit that has a duty cycle that is independent of its variable frequency (try that with a 555 or two). That method allows timing adjustment over an impressive 50 to 1 range. By the way, that same trick can be used to vary the timing of all the stages in the sequential-timing circuits presented last month.

Besides that, there is a tricky way to get a single 558 to act as an oscillator (see Fig. 3). In that circuit,

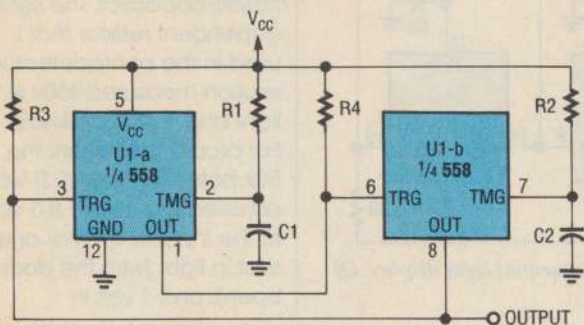


Fig. 1. Although it requires a few additional components, this astable oscillator can be designed to run rings around a 555-based version.

the sections of a 558 together to create long time delays, and to build sequential-timing circuits. That technique can also be used to design astable oscillator circuits.

A prime example of that is shown in Fig. 1. That circuit acts as an astable oscillator since each of its 558 sections triggers the other once it times out. Since the output of U1-b is used as the output of the circuit, its high time (set by the product of the values of R2 and C2) determines the high time of the circuit's output. After U1-b times out, section U1-a and its components (R1 and C1) determine how long it will be before retriggering U1-a, and thus the

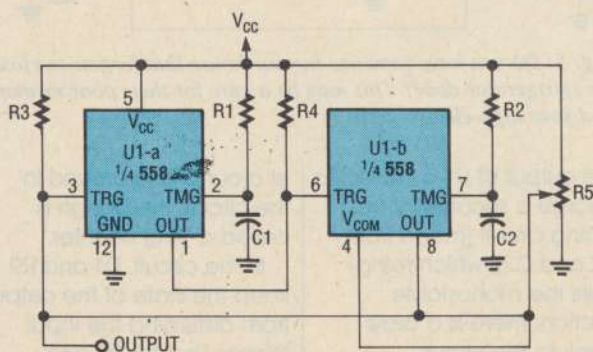


Fig. 2. By adding a potentiometer, the astable oscillator shown back in Fig. 1 can be turned into a constant duty cycle voltage-controlled oscillator with a 50-to-1 adjustment range.

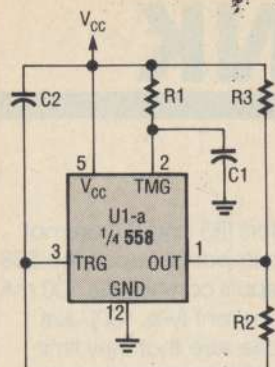


Fig. 3. A single 558 timer section can be used as an astable oscillator in a pinch. However, using this trick is only advised if the output load does not change too much.

situations where that is not a concern and you wish to use some of the 558's other sections, this is a very handy circuit.

The last 558 circuit we'll explore is shown in Fig. 4. Once a trigger pulse is sent through D1, each section will trigger the next one in line, which is reminiscent of the sequential timers presented last month. However, since the last output in the series is connected back to the primary trigger input, the circuit retriggers itself time and again. Since the trigger pulse seems to trav-

The circuit is really a good candidate for light displays. For example, with the proper interface components, the output of each section could be used to control one set of lights in a light-chaser circuit.

This is the last 558 circuit that I'll be presenting for now. However, I'd like to hear from people who use the 558 in their projects. If you have a working 558 design, or anything else applicable to this column, please send all the details to me here at *Think Tank*, **Popular Electronics**, 500-B

FRIDGE ALARM

The circuit shown in Fig. 5 could pay for itself and save you money if your refrigerator door is accidentally left open. When placed in a refrigerator (or other dark place), the circuit will sound an alarm for 30 seconds if the door is left open more than 15 seconds. That is accomplished by two monostable timer circuits—one composed of U1-a, R1, and C1, and the other made from U1-b, R2, and C2—and a light-activated trigger circuit.

The circuit is powered by a 9-volt battery placed in parallel with a 1-μF electrolytic capacitor. The light-dependent resistor that I used in the photodetector section measured 150k in light and 1.2k in darkness. For proper operation, the 50k potentiometer (R3) was adjusted to provide 8.5 volts to the input of the first one-shot in light (with the door open), and 1 volt in

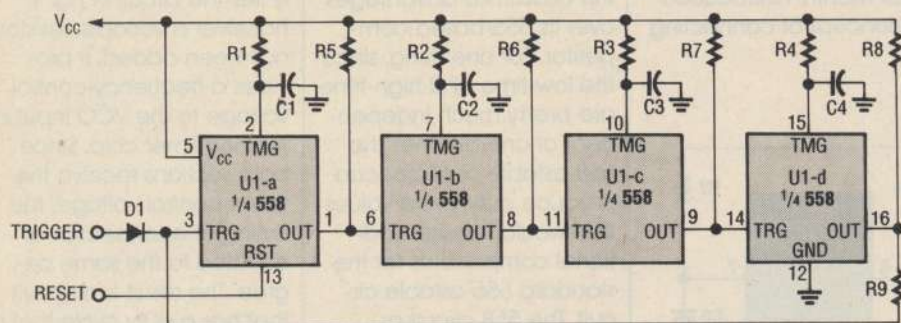


Fig. 4. This ring counter could be just the right control circuit for a sequential light display. Of course, you could add as many 558 sections to the loop as you need.

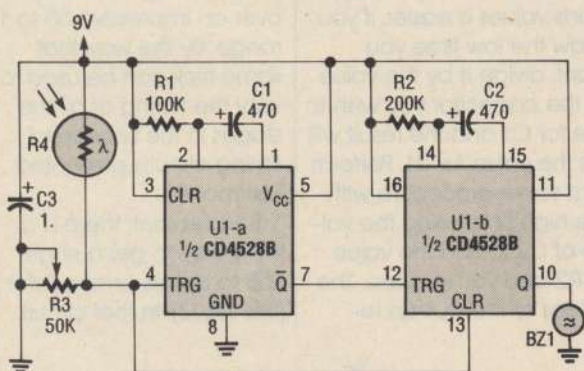


Fig. 5. Do you have someone in your house that forgets to close the refrigerator door? This may be a cure for their poor memory and your high-electric bills.

the output of U1-a is used to charge a secondary RC-timing circuit (made from R2 and C2), which retriggers the monostable section. There is a drawback to the circuit, however: changes in the load at the output can alter the low time. However, in

el around and around in the circuit, the design is called a "ring counter."

In the circuit, D1 and R9 keep the state of the output from disturbing the input trigger. Resistor R9 also keeps the reverse from happening when the unit is being externally triggered.

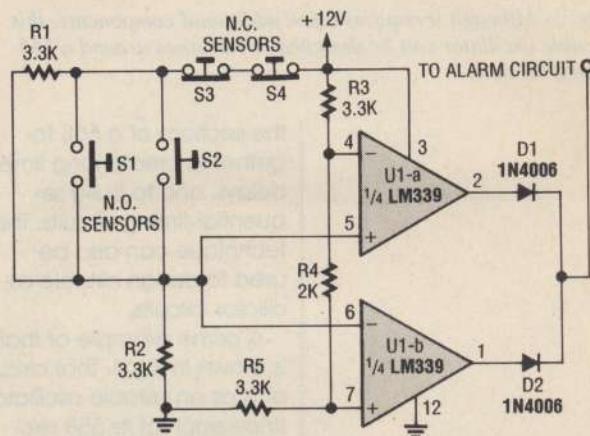


Fig. 6. This alarm actuator is a bit better than the usual alarm circuits found in this column because the wiring to the sensors is protected.

Bi-County Blvd., Farmingdale, NY 11735. If your submission is used, you'll receive a *Think Tank* II or other book as a reward. Now, let's look at what you've sent in, starting with a circuit made from two chained monostable timers.

darkness (with the door closed).

When the door opens the first one-shot fires and places a low on the second one-shot's trigger input for 15 seconds—the delay before the alarm comes on.

(Continued on page 91)

Electronics Paperback Books

GREAT PAPERBACKS AT SPECIAL PRICES

BP248—TEST EQUIPMENT CONSTRUCTION

\$5.95. Details construction of simple, inexpensive, but extremely useful test equipment. AF Gen, Test Bench Ampl, Audio Millivoltmeter, Transistor Tester and six more.

Test Equipment Construction



CMOS1—CMOS POCKET GUIDE 1

\$18.95. Works like the TTL Guides but covers all commonly used CMOS standard devices. Six major sections. The first shows the device schematic. Next is a brief description of the component and is followed by full operating details. The fourth section lists major applications, while the 5th and 6th sections present essential data for that device and a list of the relevant manufacturers. The final two sections are a valuable cross-reference.

How to Use Oscilloscopes and Other Test Equipment



BP267—HOW TO USE OSCILLOSCOPES AND OTHER TEST EQUIPMENT

\$6.95. Mastering the oscilloscope is not really too difficult. This book explains all the standard controls and functions. Other equipment is also described.

BP265—MORE ADVANCED USES OF THE MULTIMETER

\$5.95. Use these techniques to test and analyze the performance of a variety of components. Also see how to build ad-ons to extend multi-meter capabilities.

More Advanced Uses of the Multimeter



An Introduction to Loudspeakers and Enclosure Design



BP256—INTRO TO LOUDSPEAKERS AND ENCLOSURE DESIGN

\$5.95. We explore the variety of enclosure and speaker designs in use today so the reader can understand the principles involved.

Digital Audio Projects



BP245—DIGITAL AUDIO PROJECTS

\$5.95. Practical circuits to build and experiment with. Includes A/D converter, input amplifier, digital delay line, compander, echo effect and more.

BP247—MORE ADVANCED MIDI PROJECTS

\$5.95. Circuits included are a MIDI indicator, THRU box, merge unit, code generator, pedal, programmer, channelizer, and analyzer.




An Introduction to Amateur Radio



BP257—INTRO TO AMATEUR RADIO

\$6.95. Amateur is a unique and fascinating hobby. This book gives the newcomer a comprehensive and easy to understand guide to the subject.

Preamplifier and Filter Circuits

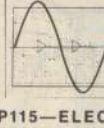

BP309—PREAMPLIFIER AND FILTER CIRCUITS

\$6.95. Provides circuits and background info for a range of pre-amplifiers, plus tone controls, filters, mixers and more. All are high-performance circuits that can be built at a reasonable cost.


BP303—UNDERSTANDING PC SOFTWARE

\$6.95. This book will help you understand the basics of various types of business software in common use. Types of software covered include word processors, spelling checkers, graphics programs, desktop publishing, databases, spreadsheets and utilities.



BP251—COMPUTER HOBBYISTS HANDBOOK

\$8.95. A wrapup of everything the computer hobbyist needs to know in one easy to use volume. Provides a range of useful reference material in a single source.

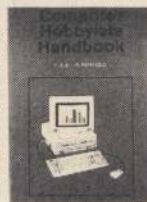

PCP115—ELECTRONIC PROJECTS FOR HOME SECURITY

\$10.00. 25 projects ranging from a single-door protection circuit that can be completed in an hour or two, to a sophisticated multi-channel security system. Each project is described in detail with circuit diagrams, explanations of how it works, instructions for building and testing, and how to adapt circuits to meet special requirements.



BP195—INTRODUCTION TO SATELLITE TV.....\$9.95. A definitive introduction to the subject written for the professional engineer, electronics enthusiast, or others who want to know more before they buy. 8 x 10 in.

BP190—ADVANCED ELECTRONIC SECURITY PROJECTS.....\$5.95. Includes a passive infra-red detector, a fiber-optic loop alarm, computer-based alarms and an unusual form of ultrasonic intruder detector.

BP235—POWER SELECTOR GUIDE.....\$10.00. Complete guide to semiconductor power devices. More than 1000 power handling devices are included. They are tabulated in alpha-numeric sequence, by technical specs. Includes power diodes, Thyristors, Triacs, Power Transistors and FET's.

BP234—TRANSISTOR SELECTOR GUIDE.....\$10.00. Companion volume to BP235. Book covers more than 1400 JEDEC, JIS, and brand-specific devices. Also contains listing by case type, and electronic parameters. Includes Darlingtons, transistors, high-voltage devices, high-current devices, high power devices.

BP99—MINI-MATRIX BOARD PROJECTS.....\$5.50. Here are 20 useful circuits that can be built on a mini-matrix board that is just 24 holes by ten copper-foil strips.

BP117—PRACTICAL ELECTRONIC BUILDING BLOCKS—Book 1.....\$5.75. Oscillators, Timers, Noise Generators, Rectifiers, Comparators, Triggers and more.

BP184—INTRO TO 68000 ASSEMBLY LANGUAGE.....\$6.95. The 68000 is a great new breed of microprocessor. Programming in assembly language increases the running speed of your programs. Here's what you need to know.

BP179—ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS.....\$7.50. Data and circuits for interfacing the computer to the robot's motors and sensors.

BP239—GETTING THE MOST FROM YOUR MULTIMETER.....\$5.95. Covers basics of analog and digital meters. Methods of component testing includes transistors, thyristors, resistors, capacitors and other active and passive devices.

BP97—IC PROJECTS FOR BEGINNERS.....\$5.50. Power supplies, radio and audio circuits, oscillators, timers, switches, and more. If you can use a soldering iron you can build these devices.

BP37—50 PROJECTS USING RELAYS, SCR'S & TRIACS.....\$5.50. Build priority indicators, light modulators, warning devices, light dimmers and more.

RADIO—100 RADIO HOOKUPS.....\$3.00. Reprint of 1924 booklet presents radio circuits of the era including regenerative, neutrodyne, reflex and more.

BP42—SIMPLE LED CIRCUITS.....\$5.50. A large selection of simple applications for this simple electronic component.

BP122—AUDIO AMPLIFIER CONSTRUCTION.....\$5.75. Construction details for preamps and power amplifiers up through a 100-watt DC-coupled FED amplifier.

BP92—CRYSTAL SET CONSTRUCTION.....\$5.50. Everything you need to know about building crystal radio receivers.

BP255—INTERNATIONAL RADIO STATIONS GUIDE.....\$7.95. Provides the casual listener, amateur radio DXer and the professional radio monitor with an essential reference work designed to guide him or her around than ever more complex radio bands.

CHECK OFF THE BOOKS YOU WANT

ELECTRONIC TECHNOLOGY TODAY INC.
P.O. Box 240, Massapequa Park, NY 11762-0240

Name _____
Address _____
City _____ State _____ Zip _____

PE1192

SHIPPING CHARGES IN USA AND CANADA

\$0.01 to \$5.00	\$1.50
\$5.01 to \$10.00	\$2.50
\$10.01 to \$20.00	\$3.50
\$20.01 to \$30.00	\$4.50
\$30.01 to \$40.00	\$5.50
\$40.01 to \$50.00	\$6.50
\$50.01 and above	\$8.00

SORRY No orders accepted outside of USA & Canada

Total price of merchandise \$ _____
Shipping (see chart) \$ _____
Subtotal \$ _____
Sales Tax (NYS only) \$ _____
Total Enclosed \$ _____

All payments must be in U.S. funds

Number of books ordered ☐

HAM RADIO

By Joseph J. Carr, K4IPV

An Antenna For DX'ing The Low Bands

Now that winter's on its way, you might want to get down to some serious DX'ing. I don't know about your DX operations, but mine tend to be better in the dead of winter than in the summer because the low bands (160, 75/80, and 40 meters) get a lot of long skip during the winter months. So this time, we'll

dipole at the optimal half wavelength. That's because even at 40 meters, the height would have to be around 65 feet. Because of the physical constraints inherent in low-frequency antennas, compensation antennas (which are a bit shorter) are sometimes used. Such antennas won't work as well as a full-sized antenna, but they work well enough to make life interesting.

LOW-FREQUENCY VERTICAL

Certain types of plumbing material have long been used in antenna construction. For example, in the days when copper tubing was inexpensive, copper verticals were popular for shortwave work. Of course, without a coating of clear lacquer or varnish, the copper soon turned an ickey green as the metal corroded.

Following World War II, aluminum tubing became popular with antenna builders. Since then, amateur-radio operators have used aluminum angle and tubing stock, along with sheet aluminum of various patterns (available from many of the larger hardware stores) for antenna construction.

Today, metal plumbing hardware has given way to plastic PVC tubing and pipe, which is also used for antenna construction (we'll explain how shortly). If the thick-wall variety (2 to 3 inches in diameter) is used, a PVC-pipe antenna can be reasonably self-supporting at heights of up to about 16 feet or so. Inciden-

tally, 16 feet happens to be one of the standard lengths of PVC pipe. If, for any given installation, the PVC lacks stability (*i.e.*, it whips around too much even at low wind velocities), it can be stabilized with guy ropes.

Putting up PVC pipe antennas can be a little tricky. Some types of PVC are too flexible for antenna work. Check the stuff before buying it. Even relatively short lengths of PVC pipe sometimes need to be guyed when used for vertical antennas in order to prevent them from blowing around in the wind. Nylon rope will serve as reasonable guys (use three or four guys about ten feet up, or where it best provides support).

Wire antennas, especially those mounted on PVC pipe, can generally handle only a limited amount of RF power. Such antennas work well with power levels up to several hundred watts, but may arc or otherwise exhibit problems at kilowatt levels.

At this point, you may be wondering just how does a plastic pipe receive and transmit radio signals? That's a fair question, and it has a reasonable answer: it doesn't. The PVC pipe is used simply as a support for a vertical wire conductor (the actual antenna). That wire conductor can be run inside or outside of the pipe, and then anchored to the pipe with machine screws and solder lugs.

Figure 1 shows a typical low-frequency antenna that can be made from either a single 16-foot length of thick-wall PVC pipe, or two

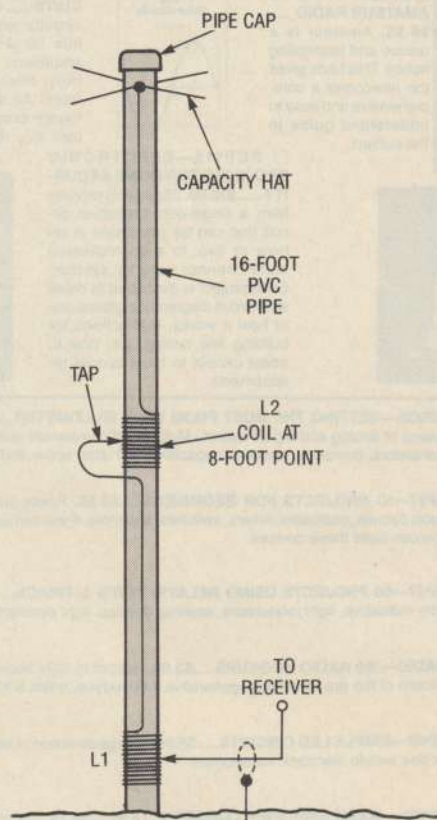


Fig. 1. A typical low-frequency antenna can be made from either a single 16-foot length or two 8-foot sections (coupled at the middle) of thick-wall PVC pipe, as shown here.

take a look at a low-frequency antenna that produces at least reasonable DX.

The old-fashioned dipole is still very popular for working the low bands. However, below 40 meters, you may be hard pressed to install a

8-foot sections coupled at the middle. That antenna, aside from the wire and PVC pipe, also has two coils, L1 and L2, incorporated into its design. Inductor L1 is used to match the antenna's feedpoint impedance to the receiver's 50-ohm input impedance. A length of 52-ohm coaxial cable is then used to connect a tap on L1 to the receiver. The coil can be from 8 to 10 turns of #12 or #14 enamel-coated wire for the 40- and 75/80-meter bands, and 15 turns for 160 meters. Of course, those are just starting points, may will be necessary to experiment to get the right number of turns.

The other coil in Fig. 1, L2, is a loading coil. It's used to increase the effective length of the antenna. All antennas that are used on frequencies lower than their natural resonant frequency exhibit capacitance. That capacitance has a capacitive reactance. The inductive reactance of the coil cancels capacitive reactance; L2 is needed to "tune" the antenna to the operating frequency.

For practical use in the 3.5- and 7-MHz bands (80 and 40 meters)—assuming a 2- to 3-inch PVC pipe and two vertical runs of #12 or #14 wire, each eight feet long—we can make L2 from 32 closely wound turns of #12 or #14 enamel-coated wire; 160 meters will require about 85 turns. The coil should be tapped every five turns or so, allowing you to increase or decrease circuit inductance (in order resonate the antenna) to accommodate different bands. A tap can be made by scraping the enamel coating from the wire at the correct point, and soldering a tap wire to it. Some hobbyists actually make little loops in

the coil wire that are used as tapping points.

A capacitance hat is then placed at the top of the antenna. The capacitance hat, which broadens the bandwidth of the antenna, can be made from four 15-inch welding or bronzing rods, stiff solid wire, or brass hobby rods. The rods should be equally spaced around the antenna, and connected to the top end of the antenna wire.

Tuning a loaded vertical can be a little tricky if you do not have the proper equipment. The best way to tune the antenna is to use an RF wattmeter, VSWR meter, dip meter, a noise bridge, or some other instrument. Another, less precise, way is to pick a distant station operating with a strong signal on the frequency that you want to hear, and then find the correct tap using the receiver's S-meter. The maximum signal strength is theoretically found when the tap is correctly set.

The reason that the second method is less precise is that the changes are going to be very subtle. Indeed, so subtle that ordinary fading (and other variations) in the signal strength may easily be mistaken for the correct setting, or may even obscure the correct setting. For that reason, I recommend using an instrumentation approach.

LOW-FREQUENCY ANTENNA GROUND SYSTEMS

A good ground is important for all antennas, especially the unbalanced types like verticals, but it is even more critical when operating in the low-frequency bands. A very good earth ground, or to at least a multiple radial counter-

poise ground, is essential.

Such a counterpoise need not have straight radials, but they should at least be resonant. Keep in mind that the efficiency of a compensation antenna is poorer than full-sized antennas at best, so we don't want to burn up any more signal in losses than is absolutely necessary.

A SAFETY NOTE

Erecting antennas can be a dangerous affair, so you are cautioned to follow **all** the rules. Don't even think about installing any antenna over a power line, or where it can fall on a power line if it gets away from you. And don't ever erect an antenna alone, always use the buddy system; I occasionally break that rule, and almost always regret it. Beside the fact that antenna work is hard

work, there's always the possibility of injury. My own injuries have been limited, thank God, to a strained back or a turned ankle. But...it's always possible to hurt something vital (your neck, for instance), so get help.

SOFTWARE

There's some new antenna software available for hams and SWL's building antennas. Called ANTLERS, the program calculates the lengths and certain other details for a wide variety of antennas. Not included in other programs is a function that calculates the inductance and resonating capacitance of radio direction-finding loops. The price of ANTLERS is \$20 postpaid. Contact me at P.O. Box 1099, Falls Church, VA 22041 if you are interested in receiving a copy. ■



NEW!
**NO-CODE
HAM
LICENSES ARE
HERE!**

All About Ham Radio by Harry Helms, AA6FW, tells how to get your *codefree* ham license and talk to the world. In over 300 pages, you'll learn about:

- packet (computer-to-computer) radio
- ham television
- using ham radio satellites
- contacting stations in foreign countries

and many other exciting topics explained in a friendly, humorous style without a lot of math and/or technical jargon. If you've been wanting a ham license, this is the book you've been waiting for!

Only \$19.95 at bookstores and radio equipment dealers. Or order direct from HighText! Add \$3 shipping (\$4 to Canada, \$5 elsewhere). CA please add sales tax. U.S. funds only please.


HighText
publications inc.

7128 Miramar Rd., Suite 15L
San Diego, CA 92121

DX LISTENING

By Don Jensen

The Shortwave Revival

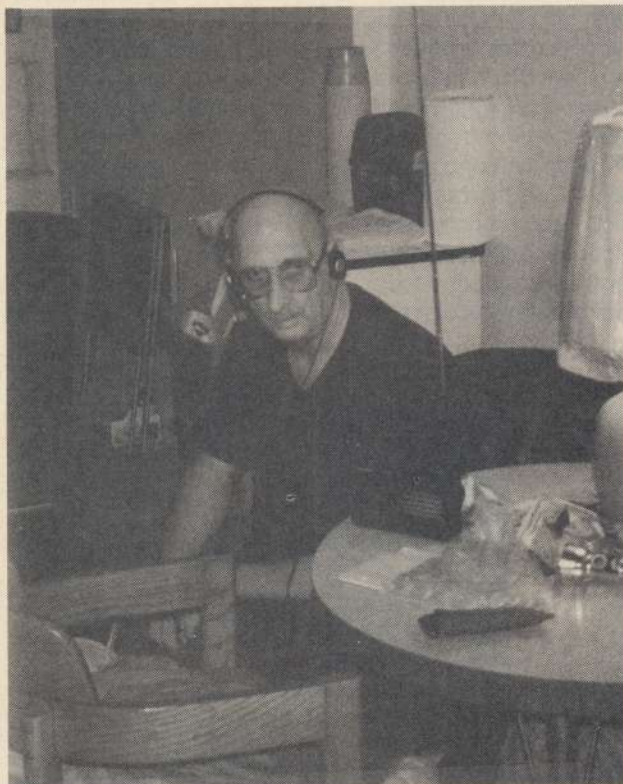

Las Vegas SWL Alan Smit says he likes to listen to the world news and music from overseas stations on his Radio Shack DX-350 receiver. Alan also notes that he is a registered monitor, WDX7DBE.

One of the more interesting developments in the world of world-band radio in the past decade has been the rebirth of private shortwave broadcasting in the United States. In the pioneer days of shortwave radio (more than 60 years ago) the first American SW

stations were privately owned and operated. Most were low-powered experimental transmitters set up by a number of AM broadcasting stations that were seeking a wider audience than their medium-wave transmissions were reaching.

For the most part, those SW'ers relayed the parent station's regular program-

ming. But as radio networks came to dominate AM radio in the U.S., stretching from coast-to-coast in the 1930's, those shortwave relays faded from the scene. With only a few exceptions, that left American SW broadcasting to the "big boys" of radio—the networks themselves, NBC and CBS, and the major electronic manufacturers, General Electric, Westinghouse, and the Crosley Corp.

Advertising revenue was the lure to private SW stations in the late 1930's and, in fact, some advertisers (Standard Oil, Firestone, Camel Cigarettes, Adams Hats) gave shortwave a try. But, by and large, commercial shortwave was a disappointment. Then came World War II, which changed things dramatically. The United States government, lacking a SW voice of its own, established the *Voice of America* in 1942, using the transmitters of the existing private stations. At war's end, the VOA was well established and has continued to grow in size and importance over the years, celebrating its 50th birthday this year.

While private SW broadcasting in the U.S. never died out completely, it did not regain the pre-war level of activity. That began to change, however, about a decade ago when interest revived. Again, as in the late 1930's, it seemed that there might be a future for commercial SW broadcasting. However, it was religious broadcasting that really sparked the revival of interest in private SW broad-

casting in the United States. Let's take a look at some of the programming currently available from those U.S. shortwave outlets.

US SHORTWAVE BROADCASTS

WYFR, Family Radio—This religion broadcaster is the successor to pioneer station WRUL, which began broadcasting in 1931 from Massachusetts. Today WYFR's headquarters is in California and its transmitters are in Florida. At the time of this writing, it could be heard on 9,505 kHz, during the 0100–0500 UTC period.

WWCR, Worldwide Christian Radio—Religion and politics can be heard from this station based in Nashville, TN. Try this one on 5,935 or 7,435 kHz during the 0100–0600 UTC time slot.

WHRI, World Harvest Radio—This station, headquartered at South Bend, IN, is primarily a religious broadcaster, but it also carries other programming, including an English service of Croatian National Radio. Look for this one on 7,315 kHz during the prime evening-listening hours in North America, 0100–0600 UTC.

WCSN/WSHB, Christian Science Monitor—The Boston-based Christian Science Church, longtime publisher of a respected newspaper, entered the shortwave-broadcasting field a few years ago. It now has two Stateside transmitting sites: WCSN at Scotts Corners, ME, and WSHB, in Cypress Creek, SC. WCSN is scheduled, at this

writing, for 0000–0200 UTC on 9,850 kHz, and at 0200–0400 UTC on 9,350 kHz. WSHB is scheduled for 7,385 and 9,455 kHz at the same time.

KVOH, High Adventures Ministries—The U.S. outlet of this religious network, which also has SW stations in Lebanon and the Pacific, broadcasts from Rancho Simi, CA. Frequencies to try are 17,775 kHz at 0000–0400 UTC and 9,785 kHz at 0400–0600 UTC.

WMLK, Assemblies of Yahweh—This persistent "Mom-and-Pop" station is operated by a small Pennsylvania religious sect. It has a limited schedule and a rebuilt shortwave transmitter operating from a former gas station; however, its small but dedicated staff has faithfully kept it on the air since 1985. Try for this one on 9,456 kHz at 0400–0900 UTC from Sunday through Friday.

WRNO Worldwide—This New Orleans-based SW'er is credited with starting the revival of private world-band radio in the U.S. Broadcaster Joseph Costello III believed that commercial SW was feasible in this country. And he seems to have proved his point since 1982. Try Saturday and Sunday nights at 0000–0300 (remember that's Sunday and Monday) UTC.

WJCR Worldwide—A relatively new SW voice is this religious station^{*} broadcasting from Upton, KY. Look for it during the North American evening hours of

0000–0600 UTC on 7,490 kHz.

Radio Miami International—This station, which has been airing Spanish programming via WRNO, says it expects to have its own station operating from Florida by year's end.

TUNING THE UTILITIES

I recently received a letter from one of our readers in Hawaii. R. Souza of Wailuku on the island of Maui, writes: "I'm a longtime scanner hobbyist but recently I tried listening to shortwave *utilities* with my DX-440 receiver. Not long afterward, I heard transmissions from the space shuttle Atlantis at 9:20 P.M. local time on 14,295 kHz.

"For about 10 minutes, I heard the astronauts talking to mission control, telling of seeing meteorites, small in size, drifting toward Atlantis. The rest of the transmission was too weak to make out and then it faded."

Reader Souza's references to "utility" stations warrants a brief explanation for those who aren't familiar with the other side of SW/DX listening. You may be most familiar with shortwave-broadcast stations, those that air regular programming for general audiences. But, outside of the SW-broadcast bands are many other types of transmissions, one- or two-way communications, some voice (usually in single-sideband mode), CW code, radioteletype, FAX, etc. They include commercial and military communications, aeronautical and maritime traffic, weather, and much more.

Usually, DX'ers lump those varied radio services under the catch-all term, utility stations. Usually this column focuses on the SW broadcasters, but I do welcome reports on interesting utility

loggings, which I will feature from time to time.

Getting back to R.S.'s letter, the logging most likely was a "real time" retransmission of a live pickup from the shuttle aired by WA3NAN at the Goddard Space Center, Greenbelt, MD. Shortwave retransmissions of space communications date back to the early moon flights and continue to provide the SWL with fascinating listening!

His letter continues "Could you give me a shortwave SSB (single-sideband) frequency for the presidential plane, Air Force 1, or any other interesting utility frequencies?"

Well, R.S., I recently noted AF-1 communicating with Andrews AFB, MD, in USB (upper sideband) on 11,229 kHz. A couple of their other favorite frequencies are 5,696 and 8,984 kHz for Coast Guard communications, particularly during North Atlantic storms or hurricanes; 8,762 kHz, a frequency used by WOO, Ocean Gate, NJ, for high seas communications; or 6,753 kHz, used by the Canadian armed forces, Trenton, Ontario, for regular weather transmissions.

MORE LETTERS

Alan Smit, Las Vegas, NV, writes to say that he's a **Popular Electronics** subscriber and a regular reader of *DX Listening*. "I hope you can use my picture in your column," says Alan. You bet! And here it is. I always welcome photos—please identify the receiving equipment pictured too—and letters with logging reports, questions or comments on SWL'ing.

Norman F. Ives Jr., Selah, WA, has returned to the listening hobby he left years ago and was pleased to see an old familiar name on the newsstand. "It looks

like the old *pop'tronics* of the late '60's and early '70's just a larger format. Is this the same magazine that used to have the DX Monitor's Club that issued me the monitor's ID, WPE1HQC? The magazine is as good as I remember. So is your column!" Today's **Popular Electronics**, Norman, is the successor to the magazine that you recall from 20 years ago, and it is still filled with the same sort of articles and columns you liked then.

As I have noted from time to time, in answer to other questions, *pop'tronics* long ago stopped issuing its monitor ID's, such as your WPE1HQC call letters. However, the program was continued by Hank Bennett's WDX Monitor Service (P.O. Box 3333, Cherry Hill, NJ 08034).

Anyone wanting details on how to get their own monitoring call (or in your case, Norm, converting your old ID to WDX1HQC) should send Hank a self-addressed stamped envelope.

DOWN THE DIAL

Here are some stations being reported recently.

ALGERIA—17,745 kHz. *Radio Algiers* has an English-language newscast at 1705 UTC, followed by identification and popular music.

BELGIUM—9,930 kHz. BRT's regular English letterbox program, "Brussels Calling" has been noted on Wednesday at 0050 UTC.

IRAN—9,022 kHz. Look for the *Voice of the Islamic Republic of Iran*, Teheran, on this out-of-the-way frequency beginning at around 0300 UTC.

SUDAN—11,710 kHz. *SNBC* in Omdurman broadcasts in Arabic at around 1345 UTC and has been noted in the eastern U.S.

*Credits: Richard Hankison, KS; Morris Sorensen, ONT; James Feeley, GA; Al Gastle, ONT; Jerry Klinck, NY; Rich D'Angelo, PA; Mike Westdal, CA; Ontario DX Association, P.O. Box 161, Station A, Willowdale, ONT M2N 5S8, Canada; North American SW Association, 45 Wildflower Road, Levittown, PA 19057

SCANNER SCENE

By Marc Saxon

Drive-Through Sermons

New from Radio Shack is the *Realistic PRO-43* handheld programmable scanner. This handful of power stores a full 200 memories (in ten banks) and covers the 30–54-, 118–174-, 220–512-, and 806–1000-MHz bands (ex-

cept for the 800-MHz cellular frequencies).

Here's a Realistic scanner that covers the exotic 225–400-MHz military UHF band that has been attracting so much interest! And, yes, both aeronautic bands are covered in AM mode, although the scanner can be switched into FM mode there if desired. There is some FM activity in the 225–400-MHz band. That band can be scanned or searched in 12.5-kHz increments.

The PRO-43 has a feature called HyperScan, which means that it scans at 25 channels-per-second but will search/scan at twice that rate. The unit's AM sensitivity is 2 μ V at 20 dB (S+N)/N at 60% modulation, while the FM sensitivity is 1 μ V at 20 dB (S+N)/N at 3-kHz deviation. The triple-conversion circuit has IF's on 610 MHz, 48.5 MHz, and 455 kHz. That provides selectivity of –6 dB at ± 10 kHz, and –50 dB at ± 20 kHz.

The scanner operates from six "AA" batteries, and can be used with NiCad batteries. An AC power supply/battery charger is available separately. A rubberized antenna with a BNC connector is supplied with the PRO-43. A large LCD readout displays frequencies as well as operating-status information (lockout, delay, priority, etc.)

This is an easy-to-use scanner, and comes in response to the many requests Radio Shack has

received to bring out a handheld that included the UHF aeronautics band along with the other bands of interest.

At \$349.95, we think that the PRO-43 is a fine addition to the Realistic line. You can see it at your local Radio Shack store.

NEWS & VIEWS

Most communications in the 225–400-MHz UHF military aeronautics band are in AM mode. As we mentioned above, sometimes you run into FM communications as well. We recently heard wideband FM (WFM) air/ground telephone calls being downlinked on 397.05 MHz. They were calls from aircraft "SAM-89671," which is the USAF plane assigned to the U.S. Secretary of State. Normally, we would have expected to hear those calls, along with Air Force One, Air Force Two, and other Special Air Mission (SAM) VIP aircraft, downlinked on 415.70 MHz (407.05-MHz uplink).

At other times, admittedly infrequently, we have monitored similar military-aircraft VIP air/ground phone-call downlink circuits in WFM mode on 336.8, 345.5, and 382.35 MHz.

We have found many interesting things to monitor in this UHF band, using regular AM mode. If your scanner covers this band, be sure to keep 239.8, 255.4, 282.8, 311.0, 319.4, 342.5, 344.6, 364.2, 372.2, 375.2, and 381.8 MHz plugged in. These frequen-



Radio Shack's Realistic PRO-43, with 200 programmable memories, covers the popular military UHF band.

cies produce interesting military aeronautic communications, ranging from the Strategic Air Command to U.S. Coast Guard Search and Rescue, as well as aeronautic weather and other information.

From Stamford, CT, comes a letter written by John Kocor. He asks if scanners that require plug-in crystals are a dead issue at this point. He also asked if we know of any sources for scanner crystals.

We wouldn't proclaim them to be totally "dead," but we feel quite comfortable in saying that they represent a technology that is rapidly fading into obscurity and disuse insofar as hobby monitoring is concerned. The development of programmable scanners saw to that. There are a couple of crystal sets for specialized uses that are still being sold, however, and many old crystal scanners probably still are used regularly. There may be some sources left for new crystals for those old Regency, Bearcat, Sonar, and other crystal scanners, but we don't know who or where they might be.

FREQUENCY SHORTAGE

Several months ago, we wrote about the strange mix of stations that use the low-power industrial frequencies such as 151.625, 154.57, and 154.60 MHz. Brian Mitchell, of Rapid City, SD, wrote recently to tell me that he has monitored undercover police officers using 154.60 MHz for surveillance operations.

Brian also sent a clipping from the *Rapid City Journal* that tells about how the local McDonald's restaurant drive-through shares one of those frequencies with the wireless microphone used by the priest at the nearby

Cathedral of Our Lady of Perpetual Help. At times the church services come in so well at McDonald's that the drive-through employees have to shut off their two-way headsets and walk out to the cars to take the orders. While this interference is unusual, everyone concerned agrees that it is certainly better than if the interference had worked in the other direction, with orders for burgers and fries drowning out the church services.

McDonald's doesn't really find the interference a bother, and usually leaves the sermons playing in their systems. People stopping by say that they like hearing them.

FROM THE MAIL SACK

K.F. Sheehan of Decatur, IL, passes along some frequencies of interest in his hometown. Those include Howard Protective Service on 464.55 MHz, Showcase Cinemas on 154.60 MHz, and both Beaver Creek and Troy High Schools on 154.60 MHz.

A letter from RM1 Thomas R. Ziko, KA5EY/4, who is with the U.S. Navy in Charleston, SC, asks if we can provide scanner frequencies relevant to NASA's space shuttle. There are zillions of frequencies used in the immediate launch and landing areas. The best bets for persons not directly in those areas would be 259.7 and 296.8 MHz, which are used when the shuttle is going to land and has reentered the atmosphere. The crew communicates with chase aircraft on those frequencies.

We want to see your frequencies, news clippings, questions, etc. Write to **Scanner Scene**, **Popular Electronics**, 500-B Bi-Country Blvd., Farmingdale, NY 11735.

DIGITAL VIDEO STABILIZER ELIMINATES ALL VIDEO COPYGUARDS



While watching rental movies, you will notice annoying periodic color darkening, color shift, unwanted lines, flashing or jagged edges. This is caused by the copy protection jamming signals embedded in the video tape, such as Macrovision copy protection. THE DIGITAL VIDEO STABILIZER: RXII COMPLETELY ELIMINATES ALL COPY PROTECTIONS AND JAMMING SIGNALS AND BRINGS YOU CRYSTAL CLEAR PICTURES.

WARNING

THE DIGITAL VIDEO STABILIZER IS INTENDED FOR PRIVATE HOME USE ONLY. IT IS NOT INTENDED TO COPY RENTAL MOVIES OR COPYRIGHTED VIDEO TAPES THAT MAY CONSTITUTE COPYRIGHT INFRINGEMENT.

FEATURES

- Easy to use and a snap to install
- State-of-the-art Microchip technology
- 100% automatic
- Compatible to all types of VCRs and TVs
- The best and most exciting Video Stabilizer in the market
- Light weight (8 ounces) and compact (1x3.5x5")
- Uses a standard 9 Volt battery (last 1-2 years)
- Fast UPS delivery
- Air shipping available
- UNCONDITIONAL 30 day money back guarantee
- 1 year warranty

(Dealers Welcome)

FREE 20P Catalog

To Order: \$59.95 ea + \$5 for p & h
Visa, M/C, COD Mon-Fri: 9-6 EST

1-800-445-9285


ZENITEK CORP. DEPT. CPE11

3670-12 WEST OCEANSIDE RD. OCEANSIDE, NY 11572

CIRCLE 16 ON FREE INFORMATION CARD

CABLE TV DESCRAMBLERS How You Can Save Money on Cable Rental Fees

Bullet Proof

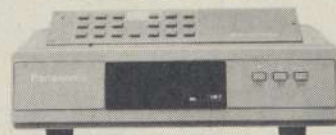

1 Unit 5+

BEST Super Tri-Bi Auto/
Var. Gain Adjustment \$119.95-\$85
Jerrold Super Tri-Bi .. \$109.95-\$79
Scientific Atlanta \$109.....\$79
Pioneer \$109.....\$79
Panasonic TZPC145.... \$99.95.....\$79
Stargate Converter..... \$95.....\$69
Digital Video Stabilizer.. \$59.95.....\$29
Wireless Video Sender.. \$59.95.....\$49.95

**US Cable'll Beat
Anyone's Price
Advertised in
this Magazine!**

30 Day Money Back Guarantee
FREE 20 page Catalog

Visa, M/C, COD or send money order to:

U.S. Cable TV Inc. Dept. KPE11

4100 N. Powerline Rd., Bldg. F-4

Pompano Beach, FL 33073

1-800-772-6244

For Our Record

I, the undersigned, do hereby declare under penalty of perjury that all products purchased, now and in the future, will only be used on Cable TV systems with proper authorization from local officials or cable company officials in accordance with all applicable federal and state laws. **FEDERAL AND VARIOUS STATE LAWS PROVIDE FOR SUBSTANTIAL CRIMINAL AND CIVIL PENALTIES FOR UNAUTHORIZED USE.**

Date: _____

Signed: _____

No Florida Sales!

CIRCLE 17 ON FREE INFORMATION CARD

ELECTRONICS LIBRARY

The Modern Amplifier Circuit Encyclopedia

by Rudolf F. Graf

A wealth of up-to-date amplifier circuits have been assembled in this one convenient source-book, which provides engineers, technicians, and students with fast, easy access to more than 250 practical, ready-to-use circuits. The book covers the whole spectrum of amplifier circuits, including audio power, high-frequency, operational, programmable, video, logarithmic-composite, wideband, audio-signal, instrumentation-logic, RF, transducer, stereo, voltage-controlled, and thermocouple circuits. The circuits appear in their original form to

cluded for readers who want additional information.

The Modern Amplifier Circuit Encyclopedia costs \$12.95 and is published by TAB Books, Division of McGraw-Hill Inc., Blue Ridge Summit, PA 17294-0850; Tel. 1-800-822-8138.

CIRCLE 98 ON FREE INFORMATION CARD

THE POWER PROFESSION: YOUR CAREER AS AN ELECTRONICS TECHNICIAN

from The Electronics Industries Association

Are you considering turning your electronics hobby into a career? This 12-page brochure provides a glimpse of the professional world of electronics, explaining what you can expect if you become a skilled electronics technician. The pamphlet includes industry overviews, charts specific growth fields with projections to

the year 2005, and outlines the training necessary to become an electronics technician, and describes various employment options. Addresses are provided for those interested in continuing their educations or obtaining more detailed information.

The Power Profession: Your Career as an Electronics Technician can be obtained by sending a legal-sized self-addressed stamped envelope to the Electronic Industries Association, Consumer Electronics Association, 2001 Pennsylvania Avenue, NW, Washington, DC 20006-1813.


CIRCLE 93 ON FREE INFORMATION CARD

WINDOWS, WORD & EXCEL OFFICE COMPANION

by Patrick J. Burns


Since its 1990 release, Windows has sold more than 13 million copies and is approaching a 10% market share among PC users. This handy, three-in-one volume provides essential support for beginning-to-intermediate PC users who are making the transition from DOS to Windows. In three well-organized sections, the book acclimates readers to the Windows environment and explains how to use two of its most popular applications: the Microsoft Word data-processing and the Excel spreadsheet programs. Each section includes valuable information on basic commands and features, instructions for performing various tasks, and helpful tutorials. Dozens of tips, tutorials, illustrations, and shortcuts that are not found in manufacturers' reference manuals round out the book.

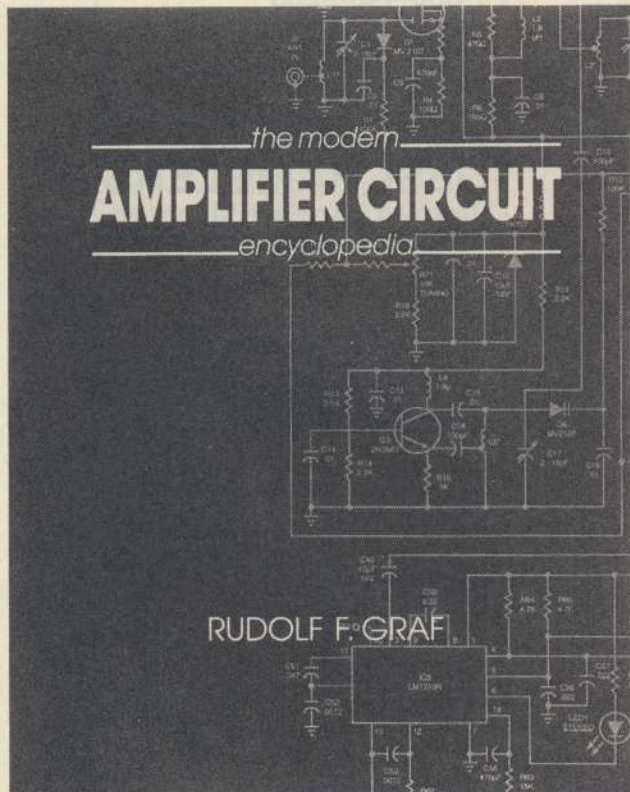The book provides an extensive introduction to Windows,



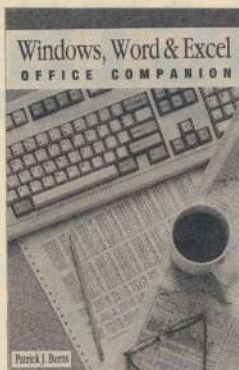eliminate transcription errors, and are organized by application for easy reference. The schematics are accompanied by a brief explanation of how each circuit works, and the original source for each circuit is in-





covering both 3.0 and 3.1, that provides a transition from keyboard pressing to mouse clicking and acknowledges, on a task-by-task basis, when one method is more efficient than the other. In addition, it explains how to exchange spreadsheet data and word-processing text within the Windows environment, determine when and how to use the Program Manager, run several applications at once, work with File Manager, activate Print Manager, format documents, manage and automate Word for Windows applications, quick-start Excel, build a database, customize the Excel Word environment, and automate spreadsheet operations.

Windows, Word & Excel Office Companion costs \$21.95 and is published by Ventana Press, P.O. Box 2468, Chapel Hill, NC 27515; Tel: 919-942-0220; Fax: 919-942-1140.

CIRCLE 92 ON FREE INFORMATION CARD

WEATHER RADIO

by Anthony R. "Tony" Curtis, K3RXK

Subtitled "A Complete Guide to Receiving NOAA, Volmet, Weather Fax, Weather Satellites, and Other Weather Information Sources," this may well be the only book to detail all the sources of weather information available via radio on longwave, medium wave, short-wave, VHF, and UHF. It explains how, when, and where to tune them, and includes details on picking up weather information from NOAA, marine weather, Volmet broadcasts, NavTex, and all the weather satellites. In addition, the book covers monitoring severe weather sit-

uations, amateur-radio weather-emergency net frequencies, land mobile-radio meteorological use frequencies, Coast Guard weather, and hurricane hunters. It even covers weather broadcasts for the Russian fishing fleet and iceberg patrols. The book also provides FAA and military weather sources, a master list of weather and weather-related frequencies, a Wind Chill Chart, and a Heat Index.

Weather Radio is available for \$14.95 plus \$2 shipping and handling from Tiare Publications, P.O. Box 493, Lake Geneva, WI 53147; Tel: 414-248-4847.

CIRCLE 91 ON FREE INFORMATION CARD

JENSEN "D" SUPPLEMENT

from Jensen Tools

This 84-page supplement to Jensen's 1992 catalog introduces new tools and test instruments for use in electronic design, assembly, and repair. It includes analyzers, monitors, meters, circuit testers, magnetic probes, static-control devices, soldering supplies, wire and cable, connectors, and other networking products. Many major manufacturers are represented in the supplementary catalog, which also features holding devices, lighting/optical aids, instrument cars, cases, and shipping containers.



The "D" Supplement is free upon request from Jensen Tools Inc., 7815 South 46th Street, Phoenix, AZ 85044; Tel: 602-968-6231.


CIRCLE 90 ON FREE INFORMATION CARD

VIDEO EDITING AND POST PRODUCTION

by James R. Caruso and Mavis E. Arthur

Written for professionals as well as home-video enthusiasts, this book describes the essentials and importance of video editing and post production. The information presented in this book can help readers to produce a finished show that will entertain, inform, and enhance the viewer's enjoyment.

The book begins with an explanation of why video editing is necessary, and then goes on to enumerate the step-by-step procedures needed to organize all the elements that make up the final production, including budgeting. Subsequent chapters cover editing equipment, investigating what various pieces do and how they work; describe different types of edit systems and equipment that can be used; explore how to use different transitions between shots; and explains how audio affects production and how to edit and mix audio. The book

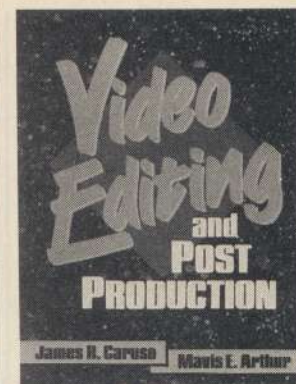

goes on to detail how to put together the final edit plan and maintain creative control and demonstrates how to actually edit the final show. Finally, the book examines how to make duplicates of the finished work for distribution.

The text is accompanied by numerous photos, illustrations, and charts. A glossary of terms is included.

Video Editing and Post Production costs \$24.95 and is published by Prentice Hall, Englewood Cliffs, NJ 07632.

CIRCLE 89 ON FREE INFORMATION CARD

Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School This proven course is easy, fast and low cost! **GUARANTEED PASS**—You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 100
P.O. Box 2824, San Francisco, CA 94126
Please rush FREE details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

NEW PRODUCTS

Laser Detector



Wars tend to escalate, and the war between law-enforcement agencies and radar-detector owners is no exception. So it's not surprising that the newest police weapon—the laser speed detector—has been counterattacked by laser-gun detectors, even though the laser gun is still limited to a few scattered places in the country. *Bel-Tronics'* first entry in that market is the

LaserAlert, which uses an adaptation of the military laser technology used in the Gulf War to detect the police laser beam and alert the driver that his speed is being detected. *LaserAlert* is programmed to receive only police laser and to discriminate against other laser or optical sources and electromagnetic interference that might trigger false alarms.

Resembling a standard micro-sized detector, the *LaserAlert* can work as a stand-alone unit or can be teamed with most three-band radar detectors to provide complete X, K, Ka, and laser coverage. It can detect both of the laser guns currently in use: the Pro-Laser from Kustom Signal and the LTI 20/20 from Laser Technology, Inc. Features include a three-LED alert meter, dim/dark modes, distinct audible alert, a windshield mount, a hook-and-

loop fastener, and a coiled power cord.

The *LaserAlert* laser-gun detector has a suggested retail price of \$129.95. For more information, contact *Bel-Tronics Limited*, 20 Centre Drive, Orchard Park, NY 14127.

CIRCLE 101 ON FREE INFORMATION CARD

INK-JET PRINTER

Royal's CJP450 ink-jet printer is one of the only compact models on the market that provides Hewlett-Packard DeskJet Plus emulation. It also provides a high level of compatibility with industry-standard software, and is fully compatible with Windows 3.0, allowing users a sophisticated level of performance from their software. With laser-quality resolution of 300 × 300 dots per inch, the *CJP450* prints at a speed of 80 characters per second (cps). Other features include the ability to print in both portrait and landscape orientations, as well as in a high-speed draft mode of 160 cps that allows users to create high-speed draft output while using only half the ink of the letter-quality mode. An optional 70-



page automatic sheet feeder provides virtually unattended printout of lengthy documents, and accommodates legal, standard, and European A-4 sized sheets. The ink-jet printer operates almost silently.

The *CJP450* ink-jet printer has a suggested retail price of \$499.95. For further information, contact *Olivetti Office USA*, Royal Consumer Business

Products, 765 U.S. Highway 202, Bridgewater, NJ 08807-0945; Tel: 908-218-5518.

CIRCLE 102 ON FREE INFORMATION CARD

RECEIVER DOWNCONVERTER

To extend the performance of test equipment and UHF communications receivers, *Ace Communications' DC 89* 800-MHz downconverter converts the frequency range of 806–900 MHz down to 406–500 MHz. The compact unit measures just 3 × 2 × 1½ inches. Frequency stability is assured by the use of a new surface-mount prescaler/synthesizer referenced to a precision quartz-crystal clock. For added versatility the *DC 89* features BNC connectors and an internal battery. The converter can even operate on handheld receivers.



The *DC 89* downconverter has a suggested retail price of \$89. For additional information, contact *Ace Communications*, Monitor Division, 10707 East 106th Street, Fishers, IN 46038; Tel: 317-842-7115; Fax: 317-849-8794.

CIRCLE 103 ON FREE INFORMATION CARD

MULTIMETER/THERMOMETER

Extech's Mini Rangemaster multimeter/thermometer com-

bines a voltmeter, ammeter, ohmmeter, frequency counter, capacitance meter, transistor tester, diode checker, and thermometer in one compact, drop-proof case. Its 41 ranges include DC voltage from 200mV to 750 volts, AC voltage to 600 volts, DC/AC current to 10 amps, resistance to 2000 megohms, and frequency from 20 Hz to 200 kHz. A Type-K thermocouple input allows the user to make temperature measurements from -50° to 1400°F and from 0° to 750°C using any standard Type-K thermocouple. Other features include 0.05% basic DC accuracy, a rotary range-selection switch, a safety-yellow case, and a built-in




stand. The handheld instrument comes with a set of test leads, a bead-wire temperature probe, and a vinyl carrying case.

The Mini Rangemaster multi-meter/thermometer has a list price of \$99. For additional information, contact Extech Instruments, 335 Bear Hill Road, Waltham, MA 02154; Tel: 617-890-7440; Fax: 617-890-7864.

CIRCLE 104 ON FREE INFORMATION CARD

BATTERY-OPERATED EPROM ERASER

Designed with hobbyists and field technicians in mind, the DE-1 EPROM eraser from UVP is battery operated, so work isn't limited to areas with wall-outlet availability. It can even be used in the car while traveling to another location. The DE-1 is small enough to fit into a tool kit, and can erase EPROM's in as little as two minutes. It features one 4-watt, 254-nm tube; a conductive foam pad to prevent electrostatic buildup; and a vertical sliding mechanism that

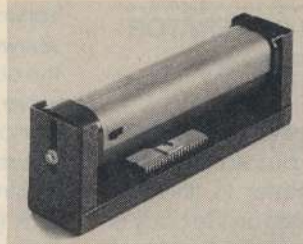

adjusts the light to the EPROM height. The DE-1 runs on four standard "AA" batteries, with an estimated battery life of more than five hours. The 1½ x 3 x 6¾-inch device holds between three and eight EPROM's depending on their size.

The DE-1 EPROM eraser has a list price of \$59.95. For further information, contact UVP, Inc., 5100 Walnut Grove Avenue, San Gabriel, CA 91778.

CIRCLE 105 ON FREE INFORMATION CARD

DIFFERENTIAL OSCILLOSCOPE PROBE

For measuring two points in a circuit without the necessity of a ground reference, *Test Probes, Inc* has introduced the ADF15 differential oscilloscope probe. The two different input signals are processed in one probe on one scope channel. That design allows the oscilloscope to be grounded for safety while the measurements are made without expensive isolation amplifiers. It also eliminates errors caused by the differences between two amplifiers and two probes. Intended for differential measurements in switching power supplies, motor controllers that use thyristors and power MOSFET's, and similar devices, the probe makes accu-



rate measurements of small signal differences even in the presence of very high common-mode voltages. It has a bandwidth of DC-15 MHz and a switchable $\times 20$ - $\times 200$ attenuation ratio. It comes with standard probes, alligator clips, and spring-tip probes with banana plug leads.

The ADF15 differential oscilloscope probe costs \$375. For more information, contact Test Probes, Inc., 9178 Brown Deer Road, San Diego, CA 92121; Tel: 619-535-9292.

CIRCLE 106 ON FREE INFORMATION CARD

PERSONAL ORGANIZER

Citizen's top-of-the-line personal calculator is the ED-9000 *Personal Digital Diary*. The ED-9000 offers a wide range of useful applications, including a checkbook planner, metric conversion, currency exchanger, expense tracking, and size conversion. With 128K of memory and "help" commands to assist the user, the handheld unit features a special F3 function key

offering a window view display with a 24-item menu. The ED-9000 also allows data link capability for downloading to an IBM-compatible PC. A comprehensive telephone directory, a personal scheduler, a world-time clock, and a business-card function complement the calculator functions.



The ED-9000 Personal Digital Diary has a suggested retail price of \$294.95. For additional information, contact CBM America Corporation, 2020 Santa Monica Blvd., Suite 410, Santa Monica, CA 90404; Tel: 213-828-8245; Fax: 213-838-0846.

CIRCLE 107 ON FREE INFORMATION CARD



Home Automation Systems

Home Automation at discount prices and unsurpassed service.

Our new catalog introduces you gently to the world of home automation. It contains a wealth of information about new and existing technology. Plus an amazing array of products at blowout prices eg: Stanley lamp modules @ \$8.95 each.

Announcing our new PLATO Home Automation System

Control by: voice, telephone, keypad, infra red and RF remote controls, time, light, motion, temperature, moisture, etc.
Control for: lights/appliances, HVAC, integrated security system, audio/visual system, telephone messaging system, interior/exterior irrigation, etc.



Mastervoice Butler in a Box, Samantha, JDS Technologies, Leviton, X10, Stanley, Heath-Zenith, Enerlogic, Aqua/Trends, our own amazing PLATO system and many, many more home automation related products. Call, fax or write for our new catalog.

- Lowest price guarantee.
- Quick start cheat sheets for most products.
- FREE system design assistance
- We can pre-program most DIY systems for you. Just plug in and you're ready to go!

Dealer inquiries invited. (714) 642-6610 ext.500

1-800-SMART-HM Orders / Catalogs
(714) 642-6610 Fax (714) 642-7190
21 Seascape Dr., Newport Beach, CA 92663

CIRCLE 18 ON FREE INFORMATION CARD



Your Ticket To SUCCESS

Over 28,000 technicians have gained admittance worldwide as certified professionals. Let your ticket start opening doors for you.

ISCET offers Journeyman certification in Consumer Electronics, Industrial, Medical, Communications, Radar, Computer and Video. For more information, contact the International Society of Certified Electronics Technicians, 2708 West Berry Street, Fort Worth, TX 76109; (817) 921-9101.

Name _____

Address _____

City _____

State _____ Zip _____

Send material about ISCET and becoming certified.

Send one "Study Guide for the Associate Level CET Test." Enclosed is \$10 (inc. postage).

THE UNCENSORED
CONTENT OF
THIS MAGAZINE IS
MADE POSSIBLE BY
THE CONSTITUTION
AND
THE BILL OF RIGHTS
OF THE
UNITED STATES.

THE CONSTITUTION. THE WORDS WE LIVE BY.

To learn more about the Constitution write: Constitution, Washington, D.C. 20006. The Commission on the Bicentennial of The U.S. Constitution.



TSM FUNCTION GENERATOR

(Continued from page 26)

one unlabeled terminal on the amplitude-scale switch. I buzzed the switch out with my multimeter to find that terminal "A" (as printed on the body of the switch) was the right one. With all the components installed, the unit was ready for calibration.

Final Adjustment. The calibration procedure proved to be the last hurdle to surmount. The process was slightly hampered by the fact that two off-board potentiometers have the same designations as two on-board pushbuttons. This is further aggravated by the fact that the amplitude-control potentiometer, which is labeled as P1 in the schematic, is called P1A in the calibration instructions. By the way, none of the control functions (frequency, amplitude scale, and amplitude) are mentioned in the documentation, only parts designations. I only learned what each control did by studying the schematic diagram.

The remainder of the calibration instructions are very difficult to sort out. They start by telling you to put one switch in an unlabeled position, and follow that up by telling you to "set" a pushbutton "for 1000 Hz," when the switch's real function is to select the sinewave output. Rather than continue to tear-apart the instructions, I'll just present my idea of how they should read to save space and help anyone wishing to build the project.

First, set all on-board trimmers to their mid position, and apply power. Turn the amplitude-control potentiometer (P1) completely clockwise, and set the amplitude-scale switch (S1) to the 1-volt position (the third position, moving clockwise). Push the 80-1000-Hz pushbutton (P3) and make sure the $\times 2$ pushbutton (P1) is disengaged (or sticking out). Select sinewave output by pressing P6. Connect an AC voltmeter and an oscilloscope between the output at point F and point D (ground) on the circuit board. Set the scope for external triggering and connect its trigger input between points K and D on the circuit board.

Regardless of the waveform that appears on the scope, adjust RA5 so the frequency of the wave is 1000 Hz.

Varying RA2 (which can be called the sinewave-shape adjustment) causes the output to transform from a triangle wave to a sinewave. Adjust that potentiometer to get the best sinewave possible. Now adjust RA1 (the symmetry trimmer) so the peaks in the wave look like the troughs. Adjust RA1 and RA2 again to get the best sinewave. Now adjust RA3 so the voltmeter reads 1-volt. If necessary, adjust RA1, RA2, and RA3 over again. Lastly, select triangle-wave output by pressing P7 and adjust RA4 till the multimeter reads 0.82 volt.

Summary of Operation. The completed circuit performed like a champ with but one exception: Unfortunately, no matter what I did, the unit refused to reach the maximum frequency of any of its ranges. I suspect that is probably due to stray inductance (as mentioned earlier) and the tolerance of the components. However, there is enough overlap between the different frequency ranges to prevent gaps in the device's overall frequency range.

One last item that bears mention is an undocumented pushbutton identified only as P10. Some examination of the circuit revealed that the pushbutton puts the unit into a frequency-shift keying (FSK for short) mode. Since there is no FSK input connection, the unit uses its output signal as the FSK input. The result is a strange signal that could be useful for ringing out cables, as the sound it would produce is probably most distinctive.

Although building the kit required some electronics sleuthing, I like the end result. To be completely honest though, my positive opinion is due in part to the fact that I didn't mind doing the extra homework myself. If you're like me in that respect, and you have some experience at electronics, then I recommend the kit. It will give you a little challenge for a couple of evenings, and a good piece of test equipment ever after once completed.

The TSM Function-Generator Kit No. 88 is available from American Design Components (815 Fairview Ave., Fairview, NJ 07022; Tel. 1-800-776-3700) as item No. 21260 for \$38.95. Contact them directly for further information or circle No. 119 on the Free Information Card.

TV/VCR SWITCH

(Continued from page 45)

the outer sheath to circuit ground and the inner wire to switch S1. Strain reliefs should be provided for the power cord and the signal cable.

Once the circuit is completely assembled, visually check for wiring errors, solder bridges, cold solder joints, etc. Clear any problems that you find. Once everything appears okay, you are ready for the smoke test.

Smoke Test. At this point, all of the components except for U3 should be mounted on or connected to the circuit board in a manner that conforms to the schematic diagram in Fig. 1. **Do not** connect the wiring from the relay to the AC line yet. Check for continuity between both of the relay's AC contacts and the circuit board's ground. There must be no continuity. If there is, find and correct the problem.

Once all is okay, plug the unit in and check for the proper voltages at pin 8 (+12 volts) and pin 4 (-12 volts) of U3's socket. If the voltages on those pins are correct, unplug the unit and install U3. Reapply power and check for proper operation of the relay with S1 in the **MANUAL** position and S2 in the **ON** position. If that checks out, unplug the unit, and assuming everything is okay so far, complete the relay's AC wiring. Close up the case and apply power again. With switch S1 in the **MANUAL** position and S2 in the **ON** position, check for 117 volts AC at SO2 (the TV outlet).

When the unit has passed all tests, it's ready for use. Plug the VCR and TV into their respective outlets. Connect the signal cable to the VCR's baseband video output (video-dubbing jack). Place the VCR in the VCR mode by operating the TV/VCR switch. Many VCR's provide no baseband output unless they are placed in the VCR mode. The TV should be set to Channel 3 or 4, since the video source selected for viewing will be delivered to the TV (which functions as a monitor) through the RF or antenna input. Now check and verify the operation of the circuit.

Once the circuit has been verified as operational, you are ready to enjoy your new video accessory, and the convenience that it provides. ■

ONE AMP CURRENT INJECTOR

(Continued from page 48)

With everything ready, push and hold the current injector's power switch. Now adjust the trimmer potentiometer (R7) until you read 1.000 amp of current on the multimeter. That's it. You're done. Once you have calibrated the unit, you can attach the box lid using four screws.

Some multimeters cannot directly measure current or don't have a 2-amp scale. If this happens to be the case, you will need to measure the current indirectly with the use of an accurate resistor of known value. A 0.1 to 1-ohm, 1% precision resistor that can handle 1 amp would be ideal. Attach the current injector clips across the calibration resistor. Then, connect the digital multimeter leads across the resistor. Set the meter to measure volts. With everything connected, press and hold the power pushbutton on the top of the unit's box. Note the voltage reading and adjust the current-control potentiometer (R7) on the circuit board for a voltage reading equal to the resistor value. If all goes well, the unit is now ready for use.

Unit Operation. With fresh batteries installed, the FET (Q1) will dissipate a maximum of 2.5 watts. The transistor dissipation will be maximum when the unit is measuring resistances below 0.1 ohms. Although you installed a small heat sink onto the transistor, it could still get very hot if the unit is operated for longer than a few minutes. I recommend that you use the system only in a momentary manner. Connect it up to the resistor to be measured, attach your digital multimeter, then take a quick measurement.

With fresh alkaline batteries, you should be able to make hundreds of measurements before the batteries have to be replaced. Also, under weak-battery conditions the power LED may turn on when the unit is not connected to a resistor but will fail to turn on when a resistor is connected. This is caused by a drop in the battery voltage under a loaded condition. The best way to make sure the unit's battery is still good is by activating the unit while the two test clips are shorted together. If the light fails to turn on, replace the batteries. ■

FREE Heathkit

Educational Systems

Electronics & Computer Software
Education Catalog

- *Fast-Track Individual Learning Programs
- *State-of-the-Art Classroom Courses
- *The Best Values in Electronics Education Today

New

Computer Aided Instruction

DC Electronics
AC Electronics
Semiconductors
Electronic Circuits

The stunning animations, hypertext glossary, and easy-to-understand text make learning the concepts of electronics a breeze...and fun!

Learn Electronics the easy and affordable way from the Masters in Electronics Training - Heathkit Educational Systems. From Basic Electricity and Electronics to Advanced Microprocessor Applications and much more, Heathkit will provide you will an unparalleled learning experience at a fraction of the cost of other programs.

For your FREE Catalog, call
Toll-Free 1-800-44-HEATH

please mention this code when calling 107-002

CIRCLE 14 ON FREE INFORMATION CARD

BIG PROFITS IN VIDEO REPAIR!

WORK FROM HOME-EARN \$85 HR!

With the tens of millions of VCRs and Camcorders in use, there currently is a **serious shortage** of trained techs to perform cleaning and repair jobs on these popular devices... Learn how you can start your own **highly profitable, Home-Based** video servicing business...

And since up to 95% of all VCR and Camcorder malfunctions are due to a simple **mechanical or electro-mechanical** failure, you need not spend months or even years of complicated study before starting **paid, professional service work!**

Let Viejo's Training Program show you how!
1-800-537-0589
or mail coupon today!

CALL TOLL-FREE

VIEJO PUBLICATIONS, INC.

4470-107 Sunset Blvd., Suite 600
Dept. VK Los Angeles, CA 90027

Yes! Rush me your **FREE OPPORTUNITY KIT** today!
(Check appropriate box)

- ☐ VCR Repair
- ☐ Camcorder Repair
- ☐ Advanced VCR Repair
- ☐ Fax Machine Repair

Name _____

Address _____

City/State _____

Zip _____

Dept. PE

CIRCLE 8 ON FREE INFORMATION CARD

DAVID HUGHES

(Continued from page 64)

New Circuits. Very quickly Hughes began to wonder whether the effects of the sparking could be detected at greater distances from their source. He now constructed a new secondary or detecting circuit consisting of a telephone receiver together with what he called his "thermopile."

This thermopile actually was nothing more than one of his carbon lozenge microphones. Perhaps Hughes used the term thermopile because he had observed earlier that heat enhanced the performance of microphonic contacts. Alternatively, he may have erroneously thought that some type of thermoelectric effects were present.

Hughes simplified his sparking circuit to include only a single cell in series with a clockwork mechanism interrupter and the primary of one of his induction coils. His transmitter and receiver were separated a distance of several feet and were connected by a wire.

By late October of 1879, Hughes found he could eliminate the induction coil from the sending circuit. Any electrical spark, no matter how it was produced, caused a sound to be heard in the telephone receiver.

The sending and receiving circuits now were located in separate rooms and were no longer connected together. Instead, the wire attached to the receiving circuit was separated from the sending circuit by a six-foot gap. In effect, Hughes had discovered the antenna and now was both sending and receiving wireless signals.

Soon, Hughes discovered that signals could be received at greater distances if both the transmitting and receiving circuits were connected to gas pipes buried in the ground. He then tried to improve reception even more by making the earth an integral part of the receiving circuit. One side of the telephone receiver was connected to a buried lead gas pipe while one side of the carbon lozenge microphone was connected to an iron water pipe.

Immediately, the clicking Hughes heard in the telephone receiver became louder. The two pipes of dif-

ferent metals, together with the moist earth, created a weak battery that increased the current flow and thus the sound heard in the telephone receiver when a spark occurred. Hughes quickly realized that putting a battery in the receiving circuit would eliminate the need for the two pipe connections.

An iron-carriage fender was connected to the transmitting circuit to see if that would improve the radiation of the waves. Soon, the iron was replaced with wire attached to pieces of wooden lath thereby creating a more effective transmitting antenna. Now signals could be heard at distances between the transmitter and receiver of up to sixty feet in the house.

Hughes now went outdoors to see if he could increase the distance between the sending and receiving circuits still further while still hearing the clicking sounds in the telephone receiver. Leaving his transmitter operating in his house, Hughes walked up and down the street with the thermopile detector and the telephone receiver. He was able to detect clicking sounds to distances in excess of a quarter of a mile.

Hughes noticed that the signals became weaker at some locations but then became stronger at others. That would seem to suggest the existence of "nodal" effects, clearly indicating that Hughes was indeed producing and detecting true electromagnetic waves.

Rejection by the "Experts." It was on February 20 in 1880 that Hughes invited the three chief officers of the Royal Society to witness his experiments. Hughes hoped that Spottiswoode, Huxley, and Stokes would confirm his conviction that an aspect of science that had never been previously observed was being demonstrated. These three leading English scientists, however, could not be convinced that David Hughes was demonstrating anything new.

David Hughes should have taken some consolation in the fact that George Stokes, the leader in downplaying the importance of these experiments, also had rejected as apparently "insignificant" several technical papers submitted to the Royal Society by such noted scientists as

Michael Faraday and James Clerk Maxwell. Even if these facts had been known by Hughes, however, the knowledge probably would have provided him with little consolation.

Badly disappointed and very discouraged, David Hughes continued his experiments in hopes of producing convincing proof that a spark discharge did indeed generate the electric waves that, he believed, were "conducted" through the air. His enthusiasm for his work, however, had been subdued as a result of Stokes' disparaging remarks. Hughes never did achieve the conclusive proof that he sought and he never presented the paper to the Royal Society as was suggested by Spottiswoode, Huxley, and Stokes.

The World Hails Hertz. In 1888, the world recognized the German physicist Heinrich Hertz as the person who first verified experimentally that Maxwell's electromagnetic waves actually exist. Hughes acknowledged the success of Hertz with true sincerity and professionalism. He in no way tried to claim any priority of achievement for himself.

It was not until 1899 that Hughes could even be persuaded to write a summary of the experiments that he had conducted in 1879 and 1880. Without this summary written shortly before his death together with the laboratory notebooks his widow later gave to the British Museum, very little would be known about these experiments.

In that summary written in 1899, Hughes publicly stated that "Hertz's experiments were far more conclusive than mine, although he used a much less effective receiver than the microphone or coherer." Hughes blamed only himself for not having publicized his own experiments at the time they were conducted and for not having pursued his own work more vigorously.

The disagreement with Spottiswoode, Huxley, and Stokes did not destroy Hughes' relationship with the Royal Society. He was elected a Fellow of the Society later in 1880 and in 1885 was awarded that organization's gold medal for scientific achievement. So greatly admired was Hughes as a scientist, an inventor, and as a person, the Royal Society chose him as its President in 1886. ■

THINK TANK

(Continued from page 76)

After the 15 seconds elapses, the first one-shot output goes high again and its low-to-high transition triggers the second one-shot's input, which in turn sounds the alarm for 30 seconds. The buzzer will shut off anytime the door is shut as the clear input (pin 13) on the second monostable will be pulled low by R3 in darkness.

—Brent Hoffman, Manchester, TN

Would anybody care to try building this circuit with a 555? If so, you know where to send the results.

ONE BETTER

I have seen a variety of very clever alarm circuits in *Think Tank* over the years (i.e., Burglar-Alarm Up-Grade and Intrusion Alarm from the April, 1991 issue). However, as an alarm technician, it seems strange that most of those circuits neglect one very important feature needed to thwart today's skilled burglar: supervised field wiring from the panel to the sensors.

In such a system, like the one in Fig. 6, the sensor loop in the field can't be defeated by opening or shorting it—either case would cause a high output to the alarm circuit. Resistors R1 and R2 form a voltage-dividing network that holds pins 5 and 6 at 6 volts. The other resistors R3, R4, and R5 form another network that holds pin 7 of U1-b at 4.6 volts and pin 4 of U1-a at 7.6 volts. So the output of both comparators (which form a window comparator) will be low as long as the proper resistance (R1) is sensed at the end of the sensor zone. Diodes D1 and D2 are needed to isolate pins 1 and 2.

In the alarm trade, R1 is known as the E.O.L. (end-of-line) device. I used a 2k resistor for R4 to give me about a 2.7-volt window; that's not too large of a window, but wide enough to allow for any long runs of wire. As you can see by the diagram, the circuit will support both normally open and normally closed sensors so you can use whatever type of magnetic switches or other devices you have on hand.

—Stephen Hughes, Irving, TX

Definitely an improvement, although a thief could still defeat the sensors individually without ill effect. Also, I don't think the diodes are needed as the sections of the LM339 have open-collector outputs. By the way, to produce active highs, the circuit will require a pull-up resistor at its output.

Since there are no more letters on alarm circuits, let me take the time to answer a query about a very common practice in electronics—using wire nuts over solder joints.

HOT ISSUE

Fairly frequently in **Popular Electronics**, I see references in the articles to the fact that wire nuts should be used on AC connections as solder melts when passing high current. I don't understand this. Assume the connection has a resistance of between 0.001 ohm and 0.1 ohm. With a current of 10 amps, the heat dissipated would be $I^2R = 100R$, which would be between 0.1 watt and 10 watts. That is certainly not very much. Where's my error?

—Fred S. Parmentia

Your math is just fine, but your solder-joint resistance measurement is a little conservative. Solder joints for

large connections, such as the ones necessary to connect heavy-gauge Romex, tend to have greater resistance (0.1 to 0.5 ohms is pretty typical). That's because during soldering the wire dissipates heat quickly, forming a colder joint. Anything above 0.15 ohms at ten amps starts generating heat dangerously close to that of a low-wattage soldering iron.

Also many AC devices pull very high amounts of current (called "in-rush current") when first turned on, raising the current ante as well. Each application of in-rush current will erode the junction, raising the resistance and the heat developed by the joint; not good.


And consider what would happen if the AC load shorts. For a brief period of time (before your house-

hold circuit breaker kicks in) a very large current will flow through the joint. That could be disastrous.

Further still, since the wires and solder are made of different alloys, the solder joint forms a two-junction thermocouple. So if you pass current through the junction, it will generate heat. That heat will be produced in the region where the wire and solder meet, thermally stressing that area. In other words, the greatest amount of heat will be produced in the most undesirable place. Over the years, that thermal stress will undo the solder joint.

Last, wire nuts are practical. Since you're going to have to insulate the solder joint anyway, why not use a wire nut? It will attach easier and stay on better than electrical tape. ■

It opens wide. You'll say Ahhh!

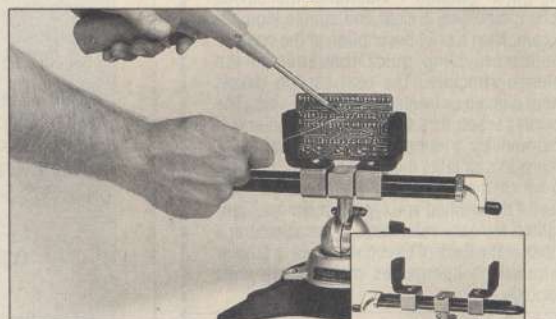

The newly improved 334 Portable PanaVise now has a self-centering head big enough to easily hold objects up to 9 inches across! Double action jaws make quick work of clamping. Reversible jaw pads are ribbed on one side and grooved on the other for plenty of gripping power. And, weight is centered over the vise, so you'll be able to hold heavier objects. Plus, our newly patented 305 low profile base provides full tilt, turn and rotation control, and now holds twice as much weight as its predecessor. The new 334 Portable PanaVise. It cuts even the biggest jobs down to size.

PANA VISE

1485 Southern Way • Sparks, NV 89431 • (702) 353-2900 • FAX (800) 395-8002

CIRCLE 7 ON FREE INFORMATION CARD

SPECIAL FROM ETT

☐ TTL1 —
TTL POCKET GUIDE,
Volume 1,
7400 — 74200
..... \$18.95.



☐ TTL2 —
TTL POCKET GUIDE,
Volume 2,
74201 — 74640
..... \$18.95.



☐ TTL3 —
TTL POCKET GUIDE,
Volume 3,
74641 — 7430640
..... \$18.95.



☐ TTLX —
ALL THREE GUIDES,
Vols 1, 2, & 3
(save \$6.00)
..... \$50.85.

Each volume provides a comprehensive listing of all commonly used TTL integrated circuits within the range of types noted. The combination of three volumes covers 7400 through 7430640 TTL products from all major manufacturers. All current families are covered: standard, low power, Schottky, low power Schottky, advanced Schottky, advanced low powered Schottky, high speed and fast Schottky. There are eight sections to the book. Section 1 illustrates the device schematic using a clear and simple logic diagram. Next a brief description of the components, providing quick reference to the internal structure. The next section details input signals or levels at individual pins. The fourth section lists major applications and is followed by a summary of essential data. Below this, a table indicates the TTL families in which the device is available, and finally, device description and type number are highlighted for easy reference. A manufacturer's index at the back of the book shows in tabular form which companies manufacture each package.

MAIL TO: Electronic Technology Today, Inc.
P.O. Box 240
Massapequa Park, NY 11762-0240

SHIPPING CHARGES IN USA AND CANADA

\$0.01 to \$5.00 ..	\$1.50	\$30.01 to \$40.00 ..	\$5.50
\$5.01 to \$10.00 ..	\$2.50	\$40.01 to \$50.00 ..	\$6.50
\$10.01 to \$20.00 ..	\$3.50	\$50.01 and above ..	\$8.00
\$20.01 to \$30.00 ..	\$4.50		

SORRY, No orders accepted outside of USA and Canada

Total price of merchandise	\$ _____
Shipping (see chart)	\$ _____
Subtotal	\$ _____
Sales Tax (NYS only)	\$ _____
Total Enclosed	\$ _____

Name _____
Address _____
City _____ State _____ Zip _____

49-MHZ FM TRANSMITTER

(Continued from page 42)

whip antennas are chrome plated and therefore do not readily accept solder. The mounting hardware makes it a lot easier to attach a lead wire to the antenna. Once all of the components have been installed or connected to the circuit board, check your work for accuracy. If all appears okay, move on to the test and adjustment phase of the construction.

Test and Adjustment. Before using the 49-MHz FM Transmitter, you must adjust R10, L1, T1, and T2. The tuning-core setting for L2 as supplied by the

factory is satisfactory and should not require adjustment. When adjusting any of the Toko coils (L1, T1, and T2), use a $\frac{3}{64}$ -inch blade, non-metallic alignment tool or, as a last resort, a jeweler's screwdriver. The cores are very brittle and fit snugly. Because of that, it is wise to avoid any unnecessary adjustments.

Initially, set R10 to about the 2-o'clock position. Fully extend the telescoping antenna, connect a 9-volt battery to the circuit, and press S1. Then, using a DC voltmeter, check for 3 volts at the R12/R13 junction; if the voltage is otherwise, the oscillator may not tune to the crystal's frequency. The core of inductor L1 may be adjusted to fine tune the oscillator's frequency. Generally, however, that is not required.

The cores of RF transformers T1 and T2 should be adjusted for maximum RF-output power. That is indicated by a dip in the DC emitter voltage, or a peak in reception range. As an alternative, you can lightly couple the probe of a 50- or 100-MHz oscilloscope to the antenna, and then tune T1 and T2 for maximum signal strength. Once the adjustments are completed, your transmitter is ready for operation.

Conclusion. The 49-MHz FM Transmitter offers many advantages over other 49-MHz transmitters and wireless microphones. Its highly stable VCXO keeps its signal locked on frequency. It's easy construction and low cost allow you to build as many transmitters you need to operate on the frequencies that are of interest to you. And the 9-volt power requirement allows you to use a battery or a 9-volt wall adapter. In addition, the 49-MHz FM Transmitter is just plain fun to build and use, offering insight into the world of RF circuits. ■

SPECIAL COMPONENT SOURCES

Toko Inductors
Digi-Key Corporation
701 Brooks Ave. South
Thief River Falls, MN 56701-0677
Tel. 800-344-5439

Varactor Tuning Diode (Motorola)
Circuit Specialists
P.O. Box 3047
Scottsdale, AZ 85271-3047
Tel. 800-528-1417

49.890 MHz Crystal (may be used at 16.630 MHz)
Jameco Electronics
1355 Shoreway Rd.
Belmont, CA 94002
Tel. 800-831-4242

2SC1687 NPN RF Transistor
MCM Electronics
858 E. Congress Park Dr.
Centerville, OH 45459-4072
Tel. 800-543-4330

CRYSTAL SOURCES

International Crystal Manufacturing Co. Inc.
P.O. Box 26330
729 W. Sheridan
Oklahoma City, OK 73126-0330
Tel: 800-426-9825
Fax: 800-322-9426

Jan Crystals
2341 Crystal Dr.
P.O. Box 06017
Fort Myers, FL 33906-6017
Tel: 800-526-9825
Fax: 813-936-3750

Crystek Crystals Corp.
1000 Crystal Dr.
FT. Myers, FL 33907
Tel: 813-936-2109
Fax: 813-939-4226



ELECTRONICS MARKET PLACE

FOR SALE save

CABLE descrambler liquidation. Major makes and models available. Industry pricing! (Example: Hamlin Combo's, \$44 each... Minimum 10 orders). Call **WEST COAST ELECTRONICS**, 1 (800) 628-9656.

JERROLD, Tocom and Zenith "test" chips. Fully activates unit. \$50.00. Cable descramblers from \$40.00. Orders 1 (800) 452-7090. Information (310) 867-0081.

OSCILLOSCOPE 50 MHz, dual channel, solid state calibrated, manual \$250.00. 1 (800) 835-8335 X-123.

PRINTED circuit boards — etched, drilled, tin plated. Single sided \$1.25/sq. inch. No setup charge. **CHELCO ELECTRONICS**, 61 Water Street, Mayville, NY 14757. 1 (800) 388-8521.

LASER & solar energy products Lasers from \$15.00. We specialize in laser and solar energy products for commercial, and hobbyist applications. Free catalog: **DESIGN IMAGES**, Dept. P7, Box 292125, Lewisville, TX 75029. (214) 221-9711.

CABLE Descramblers! Build your own descrambler for less than \$12.00 in seven easy steps. Complete instructions \$10.00. Radio Shack parts list and **FREE** descrambling methods that cost nothing to try included. **HARRYWHITE**, PO Box 1790, Baytown, TX 77520.

CLASSIFIED AD ORDER FORM

To run your own classified ad, put one word on each of the lines below and send this form along with your check to:

Popular Electronics Classified Ads, 500-B Bi-County Boulevard, Farmingdale, N.Y. 11735

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$11.00.

() Plans/Kits () Business Opportunities () For Sale
() Education/Instruction () Wanted () Satellite Television

Special Category: \$11.00

PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

(No refunds or credits for typesetting errors can be made unless you clearly print or type your copy.) Rates indicated are for standard style classified ads only. See below for additional charges for special ads. **Minimum: 15 words.**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15 (\$23.25)
16 (\$24.80)	17 (\$26.35)	18 (\$27.90)	19 (\$29.45)	20 (\$31.00)
21 (\$32.55)	22 (\$34.10)	23 (\$35.65)	24 (\$37.20)	25 (\$38.75)
26 (\$40.30)	27 (\$41.85)	28 (\$43.40)	29 (\$44.95)	30 (\$46.50)
31 (\$48.05)	32 (\$49.60)	33 (\$51.15)	34 (\$52.70)	35 (\$54.25)

We accept MasterCard and Visa for payment of orders. If you wish to use your credit card to pay for your ad fill in the following additional information (Sorry, no telephone orders can be accepted.):

Card Number

Expiration Date

PRINT NAME

SIGNATURE

IF YOU USE A BOX NUMBER YOU MUST INCLUDE YOUR PERMANENT ADDRESS AND PHONE NUMBER FOR OUR FILES. ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.

CLASSIFIED COMMERCIAL RATE: (for firms or individuals offering commercial products or services) \$1.55 per word prepaid (no charge for ZIP code)...**MINIMUM 15 WORDS.** 5% discount for same ad in 6 issues within one year; 10% discount for 12 issues within one year if prepaid. **NON-COMMERCIAL RATE:** (for individuals who want to buy or sell a personal item) \$1.25 per word, prepaid...no minimum. **ONLY FIRST WORD AND NAME** set in bold caps at no extra charge. Additional bold face (not available as all caps) **30¢ per word additional.** Entire ad in boldface, \$1.85 per word. **TINT SCREEN BEHIND ENTIRE AD:** \$1.90 per word. **TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD:** \$2.25 per word. **EXPANDED TYPE AD:** \$2.05 per word prepaid. Entire ad in boldface, \$2.45 per word. **TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD:** \$2.55 per word. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD PLUS ALL BOLD FACE AD:** \$2.95 per word. **DISPLAY ADS:** 1" x 2 1/4"—\$205.00; 2" x 2 1/4"—\$410.00; 3" x 2 1/4"—\$615.00. **General Information:** Frequency rates and prepayment discounts are available. **ALL COPY SUBJECT TO PUBLISHERS APPROVAL. ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 18th of the fourth month preceding the date of issue (i.e.; Sept. issue copy must be received by May 18th). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding work day. Send for the classified brochure. Circle Number 49 on the Free Information Card.

CABLE TV DESCRAMBLERS ★ CONVERTERS ★ and ACCESSORIES.

**SAVE MONEY.
DON'T RENT!**

PANASONIC,
PIONEER, JERROLD, OAK,
SCIENTIFIC ATLANTA
AND MORE. LOWEST PRICES.
FREE CATALOG.

(800) 234-1006
CABLE READY COMPANY

FREE electronics catalog. Transistors, IC's, electronic components, etc. Call **INTERNATIONAL MICROELECTRONICS** (817) 561-2244. PO Box 170415, Dept. PE, Arlington, TX 76003.

SITELINE LASERS, INC. is offering its 5 — 8 milliwatt He-Ne lasers and power supplies for sale at manufacturers pricing. Supplies can be purchased in Do-It-Yourself kits. Send SASE and phone number for free catalog, or call (206) 481-9490.

CB RADIO OWNERS!

We specialize in a wide variety of technical information, parts and services for CB radios, 10-Meter and FM conversion kits, repair books, plans, high-performance accessories. Thousands of satisfied customers since 1976! Catalog \$2.

CBC INTERNATIONAL
P.O. BOX 31500PE, PHOENIX, AZ 85046

LASERS Uniphase model 1107P 632.8nm .8mW helium neon with laser power supply. Slightly used. Power supply requires 48VDC input power. \$55.00 each + \$5.00S/H or SASE for info. **P.E.P. ENTERPRISES**, PO Box 92, Northville, MI 48167.

SOLDERLESS breadboards with versatile magnetic mounting. Modules have 840 tie-points and are color coded and numbered. \$6.50 each. Add \$2.00 S&H. **OMEGATRONICS**, PO Box 911, Bloomingdale, IL 60018.

FREE CATALOG

FAMOUS "FIRESIK" BRAND CB ANTENNAS AND ACCESSORIES. QUALITY PRODUCTS FOR THE SERIOUS CB'er. SINCE 1962
FIRESIK ANTENNA COMPANY
 2614 EAST ADAMS
 PHOENIX, ARIZONA 85034

MORSE Code music? Powerful-breakthrough! 43 Morse Code characters sent with a rhythmic beat. Easy way to learn or retain Morse Code skills. Now the secret is yours! Order "The Rhythm of the Code" cassette today! Send \$9.95 to: **KAWA RECORDS**, PO Box 319-PE, Weymouth, MA 02188.

SURPLUS solar panels, 105 watt set, \$469.99 unfurnished \$300.00. 35 watt \$189.99. All panels 5 year warranty. Visa, Mastercard. (602) 276-5083.

HUGE 100 page communications catalog of shortwave, amateur and scanner equipment. Antennas, books, and accessories too. Send \$1.00 to: **UNIVERSAL RADIO**, 6830 Americana Pkwy., Dept. PE, Reynoldsburg, OH 43068.



Quality Microwave TV Antennas

WIRELESS CABLE - IFTS - MMDS - Amateur TV
 Ultra High Gain 50db(+) • Tuneable 1.9 to 2.7 GHz.
 • 55-Channel Dish System \$199.95
 • 36-Channel Dish System \$149.95
 • 20-Channel Dish System \$124.95
 • Optional Commercial Grid Antenna (not shown) Add \$50.00
 • Yagi Antennas, Components, Custom Tuning Available
 • Call or write (SASE) for "FREE" Catalog
PHILIPS-TECH ELECTRONICS
 P.O. Box 8533 • Scottsdale, AZ 85252
 (602) 947-7700 (\$3.00 Credit all phone orders)
 MasterCard • Visa • American Express • COD's • Quantity Pricing

300 Experimenters Circuits — Complete in 6 practical books using diodes, relays, FET's, LED's, IC 555's, and IC CA3130's for building blocks. Only \$33.00 plus \$5.50 for shipping. USA and Canada only. US funds. **ETT, INC.**, PO Box 240, Massapequa Park, NY 11762-0240.

GENERAL Instrument DPV-7's \$250.00. Tocom, Zenith, Scientific Atlanta, \$150.00 to \$250.00. Call **CABLE WORLD**, 1 (800) 234-7193.

ELECTRONIC components! Dependable name brands. Huge selection. No minimum order required. Rapid order processing with low prices. Satisfaction guaranteed. Send for free catalog to: **BUSSEY DEBARR**, PO Box 902, Webster Station, Alameda, CA 94501.

SAVE 50-75% + on all electronic products: computers, stereo, TVs, parts, More. Self or profit. Info \$1.00 **SASE. EMPIRE**, PO Box 1414, Bristol, VA 24201. (615) 764-0186.

REMOVE LEAD VOCALS

From
 Records & CD's
 513-444-2276

Build this kit which removes lead vocals from standard stereo records, CD's, tapes or FM broadcasts. Sing along with the background music. Use with any home component stereo. Additional kit adds reverb to your voice, then mixes it with music. **Pre-assembled** boards also available. Call or write for **free info.** **Weeder Technologies**, 14773 Lindsey Rd., Mt. Orab, Ohio 45154.

PLANS & KITS

HOBBY/broadcasting/ham/CB/surveillance transmitters, amplifiers, cable TV, science, bugs, other great projects! Catalog \$1.00 **PANAXIS**, Box 130-H11, Paradise, CA 95967.

BUILD — five-digit, ohms, capacitance, frequency, pulse, multimeter. Board, and instructions \$9.95. **BAGNALL ELECTRONICS**, 179 May, Fairfield, CT 06430.

BUILD 0-50 volt regulated dual tracking power supply. Schematics and instructions. \$5.95. **SMS ENGINEERING** 5932 West Bell Road, Suite D106, Glendale, AZ 85308.

FASCINATING Electronic Devices! Dazers! Lasers! Transmitters! Detectors! Free energy! Tesla! Kits/assembled! Catalog \$4.00. (refundable) **QUANTUM RESEARCH**, 17919-77 Avenue, Edmonton, Alberta T5T 2S1.

DESCRAMBLER kits. Complete cable kit \$44.95. Complete satellite kit \$49.95. Add \$5.00 shipping. Free brochure. No New York sales. **SUMMIT PE**, Box 489, Bronx, NY 10465.

FREE! Catalog of fun and easy-to-build electronic kits. **LNS TECHNOLOGIES**, 20993 Foothill Blvd., Suite 307P, Hayward, CA 94541-1511.

SURVEILLANCE transmitter kits tune from 65 to 305 MHz. Mains powered duplex, telephone, room, combination telephone/room. Catalog with **Popular Communications**, **Popular Electronics** and **Radio-Electronics** book reviews of "Electronic Eavesdropping Equipment Design," \$2.00. **SHEFFIELD ELECTRONICS**, PO Box 377785-A, Chicago, IL 60637-7785.

CABLE descramblers, build your own, SSAVI, gated sync, sinewave. \$14.95. **CABLETRONICS**, box 30502PE, Bethesda, MD 20824.

RADIO controlled car starter. Build and assemble a remote control car starter. Start your car from inside the house. For plans and instructions send \$10.00 to **JEFF COX**, 1418-B Forestdale Blvd., #201, Birmingham, AL 35214-3016.

AUTOMOTIVE electrical monitor. Complete kit \$6.95. Assembled \$9.95. \$3.00 S/H. NY residents add tax. **VR ELECTRONICS CORPORATION**, 47-30 196 St., Flushing, NY 11358.

ETCH PCB's yourself, new technique, no chemicals, easy, cheap, full instructions, sharefare, \$1.00. **SASE. NICKNAP PRODUCTS**, Suite 297, CN 1907, Wall, NJ 07719.

TEST-aids for testing units in full service mode. Starcom VII, \$40.00; Starcom VI, \$30.00; Starcom DPBB, \$50.00; Pioneer, clears error codes E2 E3 E4 E5, \$75.00; Pioneer cubes, will not alter internal serial number, \$175.00; Tocom VIP 5503/5507, \$25.00; S.A. 8500, \$25.00; 8550, \$30.00; 8580, \$40.00, 8570/90, \$50.00; Zenith Ztac, \$25.00; security tools and remotes. **N.E. ENGINEERING** (617) 770-3830.

60 SOLDERLESS Breadboard Projects in two easy-to-read pocket books. Complete with circuit descriptions, schematics, parts layouts, component listings, etc. Both books (BP107 & BP113) only \$11.90 plus \$3.50 for shipping. USA and Canada only. US funds. **ETT, INC.**, PO Box 240, Massapequa Park, NY 11762-0240.

ANTIQUE RADIO CLASSIFIED

Free Sample!

Antique Radio's
 Largest Circulation Monthly.
 Articles, Ads & Classifieds.

6-Month Trial: \$15. 1-Yr: \$27(\$40-1st Class).
 A.R.C., P.O. Box 802-L8, Carlisle, MA 01741

BUSINESS OPPORTUNITIES

YOUR own radio station! Licensed/unlicensed. AM, FM, TV, cable. Information \$1.00 **BROADCASTING**, Box 130-H11, Paradise, CA 95967.

EASY work! Excellent pay! Assemble products at home. Call toll free 1 (800) 467-5566 Ext. 5730.

MAKE \$75,000.00 to \$250,000.00 yearly or more fixing IBM color monitors. No investment, start doing it from your home (a telephone required). Information, USA, Canada \$2.00 cash for brochure, other countries \$10.00 US funds. **RANDALL DISPLAY**, Box 2168-H, Van Nuys, CA 91404, USA. Fax (818) 990-7803.

HOME assembly work available! Guaranteed easy money! Free details! **HOMEWORK-P**, Box 520, Danville, NH 03819.

FREE information! Research engineer earns living with stocks safely. **HILL**, PO Box 48194, Niles, IL 60648.

FEDERAL loans for small businesses now available. 1 (800) 777-6342 for free details.

ELECTRONICS dealers: Expand your product line. **Make \$\$\$!** Become an American Electronics Dealer! Profit opportunities since 1965. Call **WAYNE MARKS**, 1 (800) 872-1373.

DISTRIBUTORS needed — High profits, untapped markets. Mini satellite antennas for homes, RV's & business use. As low as \$361.00. 24 hrs. (913) 599-8286.

EARN \$1000.00 weekly in multi-level marketing! Guaranteed!! Free information. Send **SASE** to **VENTURE ENTERPRISES**, Box 2084-P, Provo, Utah 84603.

ELECTRONICS business in beautiful Salida Colorado includes inventory and real estate. \$65,000.00. Contact **SOUTHWEST CENTENNIAL**, 245 E. Hwy. 50, Salida, CO 81201.

BEST BY MAIL

Rates: Write National, Box 5, Sarasota, FL 34230

BOOKS—CATALOGS—MAGAZINES

ELECTRONIC ENGINEERING. 8 volumes complete. \$109.95. No prior knowledge required. Free brochure. **BANNER TECHNICAL BOOKS**, 1203 Grant Ave., Rockford, IL 61103.

OF INTEREST TO ALL

YOU TOO CAN import from Taiwan and Hong Kong. Free information. Box 661, Dallas, GA 30132.

JOB SEEKERS! GET jobs you want. Guide shows insider secrets, details: Pacificwest, Box 245-(PE), Simi Valley, CA 93062.

MONITOR CORDLESS TELEPHONE Conversations from your home or car. For details send \$10.00 to: Bennett Distributors, 824 EA. Rand Road, Suite 186, Arlington Heights, IL 60004.

HERBS, SPICES, SASE: Herb Sense, 1032 Irving St., Box 446-(PE), San Francisco, CA 94122.

BALDING: 30 DAY MONEY BACK GUARANTEE - PAUL ROBERTS' Hair Loss treatment. Send just \$9.95 to: **PAUL ROBERTS**, Dept. A12, P. O. Box 1758, Media, PA 19063. **ASK FOR FREE GIFT WITH PURCHASE.**

MONEYMAKING OPPORTUNITIES

\$1500.00 A WEEK At Home. For Free Information Send A Stamped Envelope To: American Dream, PO Box 1533-1, North Wales, PA 19454.

WANTED

PROTECT and market your new product ideas! Call **THE IDEA EXCHANGE** — Fast, professional, confidential: 1 (800) 272-6875.

SATELLITE TV

FREE Catalog — Do-it-Yourself. Save 40%-60%. Lowest prices worldwide, systems, upgrades, parts. All major brands factory fresh and warranted. **SKYVISION**, 1048 Frontier, Fergus Falls, MN 56537. 1 (800) 334-6455.

SATELLITE TV — Do It Yourself, major brands discounted, We'll beat everyone's price. Discount **LARRY**, (609) 596-0656.

VIDEOCIPHER II descrambling manual. Schematics, video and audio, \$18.95. Videocipher II 032, \$15.00. Videocipher II plus, \$20.00. Software, \$25.00. **CABLETRONICS**, Box 30502PE, Bethesda, MD 20824.

T.V. FILTERS

T.V. notch filters, phone recording equipment, brochure \$1.00. **MICRO THinc.**, Box 63/6025, Margate, FL 33063. (305) 752-9202.

HOME EXTERMINATION

NEW book: "Become Roach-Free" Exterminator explains: in detail. \$20.00 EPE, POB 74C, Calhoun, LA 71225-0074.

COMPUTERS

DEAL directly and save with the number one manufacturer of computers and peripherals in the world Taiwan over 290 addresses \$12.50 +\$2.50 S/H. **G.R. STRINGER**, PO Box 30563, Houston, TX 77249-0563.

TELECOMMUNICATIONS

CORDLESS phone scandal! Long-range eavesdropping secrets exposed. Millions unaware! Protect your privacy. \$12.00. **AIRWAVES**, 5319 University, Suite 300PE1, Irvine, CA 92715. (Hurry! Limited offer.)

EDUCATION/INSTRUCTION

LEARN IBM PC assembly language. Disk \$5.00. Book \$18.00. **ZIPFAST**, Box 12238, Lexington, KY 40581-2238.

VCR repair. Save money — make big profits! Learn how from *How to Keep Your VCR Alive*. "This detailed, step-by-step manual enables anyone with no previous knowledge or experience to fix most VCR problems easily, quickly, and inexpensively with a few simple tools." — *Small Press Review*. Highly recommended by *Electronic Servicing and Technology*, *Modern Electronics*, *Popular Electronics*, *Popular Communications*, *Videomaker*, *Video*, *Nuts and Volts*, and many other electronics and video magazines "Far better than Viejo at 1/7 the cost." 403 page book, with 704 illustrations, plus professional head-cleaning tool. Obtain from B. Dalton or send \$24.95 to **WORTHINGTON PUBLISHING**, 6907-202H Halifax River Drive, Tampa, FL 33617. Publisher pays S&H. Money-back satisfaction guarantee!

ELECTRONICS tutorial software. Nine diskettes. Over 1000 screens of information and help on DC, AC, analog and digital. Q&A format. IBM \$25.00. **TUTOR-TECH**, 5591 Kimberly St., San Jose, CA 95129. (408) 252-3223.

LEARN computers. Tutorials and software. Programs sampler \$11. Catalog \$1.00. Complete IBM software line — education, business, scientific, games, Windows. State disk size. **VISTA-PE SOFTWARE**, 95106 Huaala Place, Mililani, HI 96789.

LEARN electronics, math, computer programming simultaneously. Book \$28.95 (includes shipping). **HI-TEK PUBLISHING CO.**, 325 Aleut Court, Fremont, CA 94539.

TEACH yourself electronics and digital basics. Programmed courses. \$17.00 each, both \$29.00. Satisfaction guaranteed. **TEKNOLEDGY SOURCES**, 6050 NW 68th St., Parkland, FL 33067.

PATENT it yourself. Eliminate huge fees. Complete practical instructions \$9.95: **PATENT GUIDE**, PO Box 654, Gurnee, IL 60031.

MASTERCARD AND VISA are now accepted for payment of your advertising. Simply complete the Classified Ad order form and we will bill you.

THIS IS A BOLDFACE EXPANDED-TYPE AD WITH A TINT SCREEN. See how it jumps out on the page. To order your ad in this format calculate the cost at \$2.70 per word.

BUY BONDS

FREE CATALOG!
1-800-648-7938
JERROLD HAMLIN OAK ETC
CABLE TV
DESCRAMBLERS

- Special Dealer Prices!
- Compare our Low Retail Prices!
- Guaranteed Prices & Warranties!
- Orders Shipped Immediately!

REPUBLIC CABLE PRODUCTS, INC.
4080 Paradise Rd. #15, Dept. PE1192
Las Vegas, NV 89109
For all other information (702) 362-9026

*****PRESENTING*****
CABLE TV
DESCRAMBLERS
*****STARRING*****
JERROLD, HAMLIN, OAK
AND OTHER FAMOUS MANUFACTURERS

- FINEST WARRANTY PROGRAM AVAILABLE
- LOWEST RETAIL / WHOLESALE PRICES IN U.S.
- ORDERS SHIPPED FROM STOCK WITHIN 24 HRS.
- ALL MAJOR CREDIT CARDS ACCEPTED

FOR FREE CATALOG ONLY **1-800-345-8927**
FOR ALL INFORMATION **1-818-709-9937**

PACIFIC CABLE CO., INC.
7325 1/2 Reseda Blvd., Dept. 2020
Reseda, CA 91335

WE'RE THE #1 HOPE FOR THE #3 KILLER: LUNG DISEASE

AMERICAN LUNG ASSOCIATION®
The Christmas Seal People®

Space contributed by the publisher as a public service.

FUN WITH ELECTRONICS

Coil Design and Construction Manual



□ **160—COIL DESIGN & CONSTRUCTION MANUAL** \$5.95. How to make RF, IF, audio and power coils; chokes and transformers. Practically every possible type is discussed.

□ **PCP113—THE PC MUSIC HANDBOOK** \$13.95. Learn the basics of computer music systems. For the professional musician, gifted amateur or just plain curious.



□ **BP297—LOUDSPEAKERS FOR MUSICIANS** \$6.25. Loudspeaker design from the musician's point of view! All you need to know, and you should be able to design your own after reading this.

□ **BP277—HIGH POWER AUDIO AMPLIFIER CONSTRUCTION** \$6.25. Here's background and practical design information on high power audio amplifiers capable of 300 ± 400 watts r.m.s. You'll find MOSFET and bipolar output transistors in inverting and non-inverting circuits.



□ **BP302—A CONCISE USER'S GUIDE TO LOTUS 1-2-3 RELEASE 3.1** \$6.25. If you are a PC user and want to upgrade to Lotus 1-2-3 release 3.1, this book can teach you how to do that in the shortest and most effective way.

□ **BP298—A CONCISE INTRODUCTION TO THE MACINTOSH SYSTEM AND FINDER** \$6.25. This introduction for those new to the Mac, this book also serves as a quick refresher for experienced owners that have not used the machine in some time.

MAIL TO: **Electronic Technology Today, Inc.**
P.O. Box 240
Massapequa Park, NY 11762-0240

SHIPPING CHARGES IN USA AND CANADA

\$0.01 to \$5.00	\$.15	\$30.01 to \$40.00	\$5.50
\$5.01 to \$10.00	\$.25	\$40.01 to \$50.00	\$6.50
\$10.01 to \$20.00	\$.35	\$50.01 and above	\$8.00
\$20.01 to \$30.00	\$.45		

SORRY, No orders accepted outside of USA and Canada

Total price of merchandise \$
Shipping (see chart) \$
Subtotal \$
Sales Tax (NYS only) \$
Total Enclosed \$

Name
Address
City State Zip

ADVERTISING INDEX

POPULAR ELECTRONICS magazine does not assume any responsibility for errors that may appear in the index below.

Free Information No.	Page		
—	47th Street Photo	15	11
6	AMC Sales	26	9
—	Antique Radio Classified	94	—
—	CBC International	93	5
—	CIE	11	—
—	CLAGGK, Inc.	4	7
—	Cable Ready Company	93	15
—	Command Productions	85	—
—	Electronic Tech. Today	77, 92, 95	—
—	Electronics Book Club	19, CV3	—
—	Firestik II	94	12, 13
—	Grantham College	28	17
14	Heathkit	89	8
—	HighText Publications, Inc.	70, 79	—
18	Home Automation Systems	87	—
—	ISCET	88	16
			Kepeco Inc.
			MD Electronics
			Mouser
			NRI Schools
			Number One Systems Ltd.
			Pacific Cable
			Panavise
			People's College
			Phillips Tech
			R.E. Video Offer
			Republic Cable
			The School of VCR Repair
			U.S. Cable
			Viejo Publications
			WJMK
			Weeder Technologies
			Zentek Corp.

ADVERTISING SALES OFFICE

Gernsback Publications, Inc.
500-B Bi-County Blvd.
Farmingdale, NY 11735
1-(516) 293-3000

Larry Steckler
President

Christina Estrada
Assistant to the President

For Advertising ONLY
516-293-3000
Fax 1-516-293-3115

Larry Steckler
publisher

Arline Fishman
advertising director

Denise Mullen
advertising assistant

Kelly McQuade
credit manager

Customer Service/Order Entry
1-800-435-0715
1-800-892-0753
7:30 AM - 8:30 PM EST

SALES OFFICES

EAST/SOUTHEAST

Stanley Levitan
Eastern Sales Manager
1 Overlook Ave.
Great Neck, NY 11021
1-516-487-9357, 1-516-293-3000
Fax 1-516-487-8402

MIDWEST/Texas/Arkansas/ Oklahoma, Colorado, Arizona

Ralph Bergen
Midwest Sales Manager
One Northfield Plaza, Suite 300
Northfield, IL 60093-1214
1-708-446-1444
Fax 1-708-559-0562

PACIFIC COAST/Mountain States

Mike Brooks
Pattis/3M
1800 North Highland Avenue
Suite 717
Hollywood, CA 90028
1-213-462-2700
Fax 1-213-463-0544

PE Market Center
Nicki Van Suydam
Pattis/3M
1800 North Highland Avenue
Suite 717
Hollywood, CA 90028
1-213-462-2700
Fax 1-213-463-0544

GET THE LATEST ADVANCES IN ELECTRONICS

WITH A SUBSCRIPTION TO

Electronics
Radio Combined with
Electronics
NOW



ENJOY THE WORLD OF ELECTRONICS EACH MONTH!
Electronics Now looks to the future and shows you what new video, audio and computer products are on the horizon. What's more you'll find helpful, monthly departments such as Video News, Equipment Reports, Hardware Hacker, Audio Update, Drawing Board, Computer Connections, New Products, and more. All designed to give you instruction, tips, and fun.

SUBSCRIBE TODAY

Just fill out the order card
in this magazine and mail it in today.

FOR FASTER SERVICE CALL TODAY
1-800-999-7139

5PGL7



One tree can make
3,000,000 matches.



One match can burn
3,000,000 trees.




A Public Service of This Magazine
& The Advertising Council




1367P \$29.95
Softcover



3804P \$19.95
Softcover

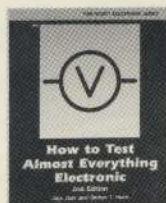


2925P \$10.95
Softcover

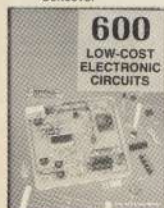


3219P \$18.95
Softcover




2613P \$17.95
Softcover

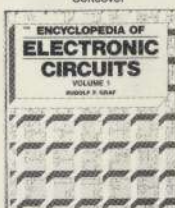

1938-XXX \$60.00
Counts as 3

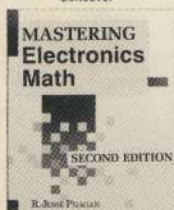

3589 \$27.95

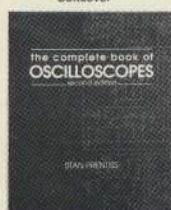

3825 \$26.95



3610 \$28.95

Select any 5 books


for only \$4⁹⁵

(values up to \$146.75)

when you join the Electronics Book ClubSM



4000P \$9.95
Softcover

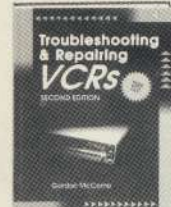

3777-XX \$32.95
Counts as 2



2867P \$18.95
Softcover



3540 \$26.95




2883P \$18.95
Softcover




3374P \$16.95
Softcover




3671 \$29.95

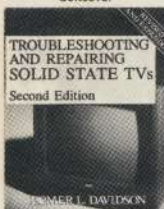


3700-XX \$36.95
Counts as 2

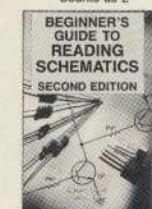

3632P \$10.95
Softcover

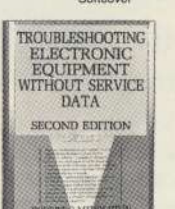

9290-XX \$36.00
Counts as 2

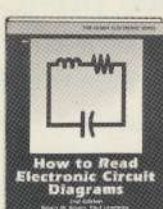


2880P \$14.95
Softcover



3627P \$19.95
Softcover



3765 \$29.95

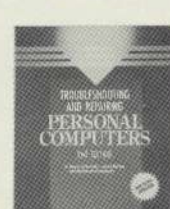

3677-XX \$34.95
Counts as 2

As a member of the Electronics Book Club...

... you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off of regular publishers' prices. If you want the Main Selection do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. And you'll be eligible for **FREE** books through our **NEW Bonus Book Program**. Your only obligation is to purchase 3 more books during the next 12 months, after which you may cancel your membership at any time. ©1992 EBC All books are hardcover unless otherwise noted. (Publishers' prices shown) A shipping/handling charge and sales tax will be added to all orders.

If coupon is missing, write to:
Electronics Book Club, Blue Ridge Summit, PA 17294-0810

Your most complete and comprehensive source for the finest electronics books.

ELECTRONICS BOOK CLUBSM

Blue Ridge Summit, PA 17294-0810

YES! Please rush me the books indicated below, billing me just \$4.95 plus shipping/handling & tax. Enroll me as a member of the **Electronics Book Club** according to the terms outlined in this ad. If not satisfied, I may return the books within ten days and have my membership cancelled. A shipping/handling charge and sales tax will be added to all orders.

--	--	--	--	--

If you select a book that counts as 2 choices, write the book number in one box and XX in the next.
If you select a Counts as 3 book, write the book number in one box and XXX in the next 2 boxes.

Name

Address

City State

Zip Phone

Valid for new members only, subject to acceptance by EBC. Canada must remit in U.S. funds. Applicants outside the U.S. and Canada will receive special ordering instructions. PE1192

The Amazing Maze.



**YOUR HOME . . .
the television series,
will help guide you through it.**

For most families . . . our homes are the biggest purchase we'll ever make. From time to time we've all thought about making changes to our homes. By watching the YOUR HOME television series, you can catch all of the latest ideas and trends designed to get you through the maze of products that will enhance the beauty, functionality, and quality of the time that you spend at home. Whether you're building a dream kitchen or attempting to create the home theater experience, from the simple to the exotic, YOUR HOME has a wealth of great ideas. It's like going to the world's biggest home and garden store each and every week.

Tune into upcoming shows to check out the best and brightest in home products and services:

ACTION INDUSTRIES

The most comfortable recliners from one of America's oldest names in quality furniture. . . Lane.

ALCOA BUILDING PROD.

Quality Aluminum, Vinyl, and Steel Building products featuring Lake Forest Exteriors.

EMSON

The Ultimate Squeeze, Juice Extractor for healthy great tasting juices made at home.

GARLAND

Garland Ranges, started as a range for professionals and it's stayed that way.

HARTCO

Pattern Plus—Acrylic Impregnated Hardwood Flooring.

INFINITY SYSTEMS, INC.

Infinity. . . We get you back to what it's all about. . . Entertainment.

Check your local cable listing for the time and channel number in your area.

A presentation of

WJMK • 2424 N. Federal Highway • Boca Raton, FL 33431 • (407) 367-0703


229

Popular
Electronics


FactCard

Transistor Applications

LOW-LEVEL AUDIO AMPLIFIER

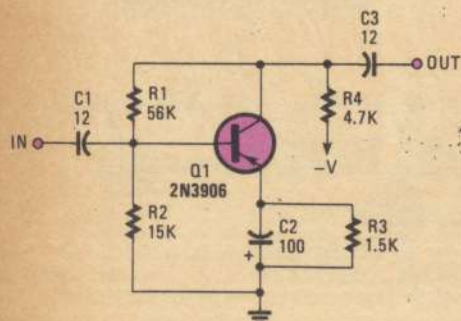

AUDIO OSCILLATOR

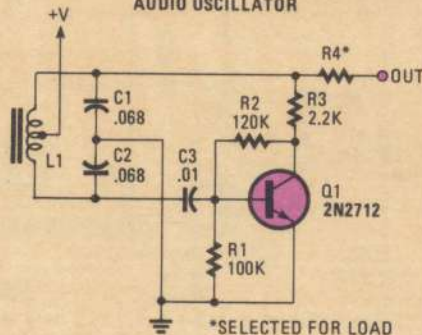

For the best
in hobby
electronics
read
Popular
Electronics

During
the next
12
months

Popular Electronics will feature timely and informative articles that help you get the most from your hobby. Each issue will include:

- Exciting construction projects for the beginning and advanced builder
- News and reviews on the hottest new consumer and hobby gear
- Helpful hints and circuits that are an experimenter's delight
- Technology articles that entertain while they teach
- Stories and columns that cover every important part of our hobby from antique radio to computers
- and much more!

Don't take a
chance on missing
even one
exciting issue.
Subscribe now
and save!


230

Popular
Electronics


FactCard

Transistor Applications

SCHMITT TRIGGER

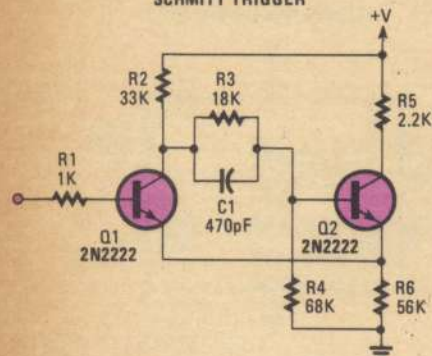

PHASE-SHIFT OSCILLATOR

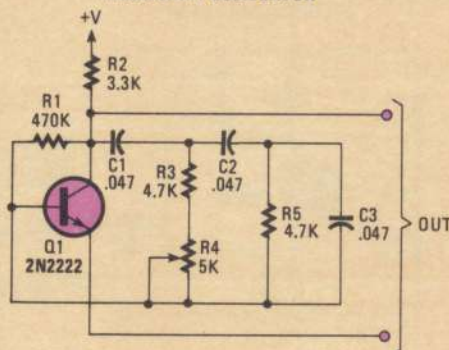


231

Popular
Electronics


FactCard

Passive Filter Configurations

L FILTERS

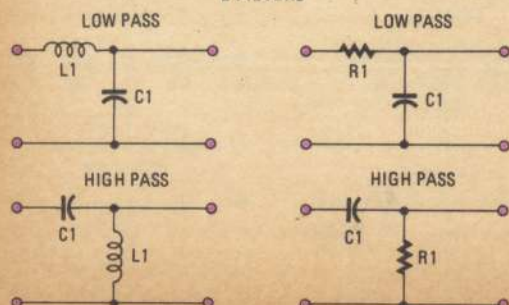

PI FILTERS

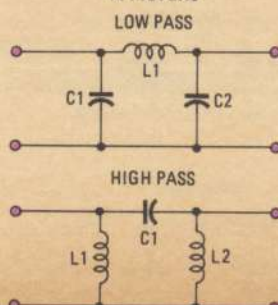

The magazine for the
electronics activist and the
consumer electronics
enthusiast!

The best in hobby electronics
appears each and every month
in Popular Electronics!

Subscribe Today!

229

Popular
Electronics

FactCard

Transistor Applications


Here are
your free
FactCards!

Introducing Popular Electronics *FactCards*.


Each issue, **Popular Electronics** will present 3 new *FactCards*, each dealing with one of a variety of electronics topics. Some will deal with electronics basics, some will deal with discrete components, some will deal with IC's, and some will deal with circuits and applications.

All will contain the type of information electronics hobbyists need, but sometimes must search to find. With *FactCards*, you can find that information in a hurry.

CRYSTAL-CONTROLLED HARTLEY OSCILLATOR

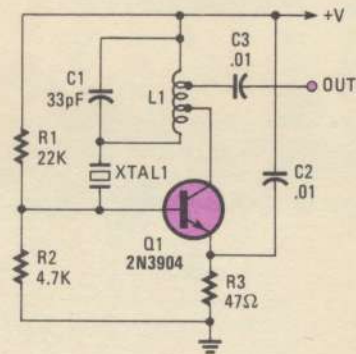

MONOSTABLE MULTIVIBRATOR

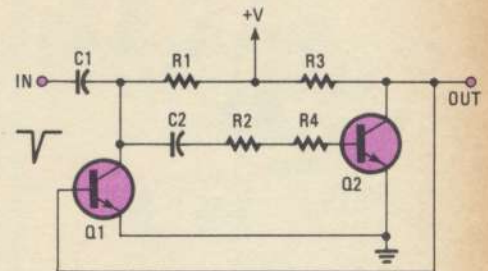


230

Popular
Electronics


FactCard

Transistor Applications

COLPITTS OSCILLATOR

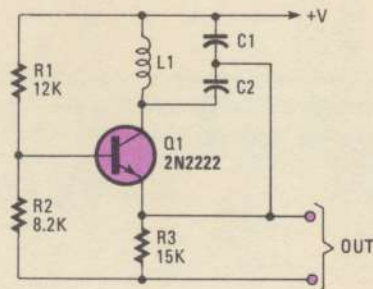

ASTABLE MULTIVIBRATOR

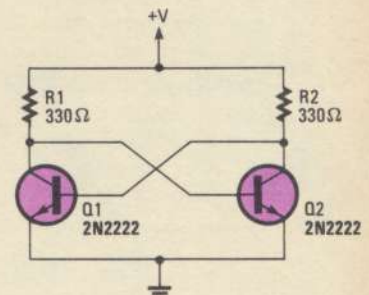

231


Popular
Electronics

FactCard


Passive Filter Configurations

PI FILTERS

LOW PASS

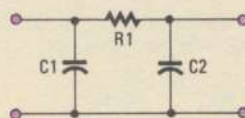


HIGH PASS

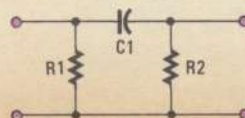


T FILTERS


LOW PASS

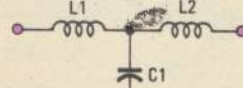


HIGH PASS

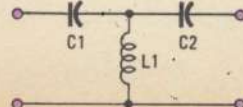

LOW PASS

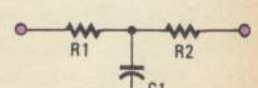

HIGH PASS

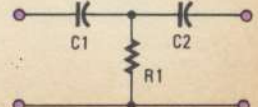

Clip your
cards,
save them,
and start
building
your
FactCards
library
today!

Popular
Electronics